

# RADAR JAMMER

NOTES:

X BAND = -114 DBM/CM<sup>2</sup>  
IT IS 10.490-10.560GHZ

K BAND = -104 DBM/CM<sup>2</sup>  
IT IS 24.040-24.260GHZ

Ka BAND = -100 DBM/CM<sup>2</sup>  
IT IS 34.590-34.810GHZ

---

LASER IS 800-1100NM

---

YOU WILL NEED TO BUILD A CONTINUOUS IR LIGHT SOURCE TO JAM LASER.

POLICE USE MAINLY K AND KA BAND TO CATCH YOU. PICK A DIVERSE RANGE WHEN DESIGNING YOUR CIRCUIT.

---

THIS IS A PASSIVE JAMMER. SO IT IS LEGAL IN ALL MOST ALL STATES. IF YOU EXPOSE THE JAMMER TO A K BAND FREQUENCY AT ALL TIMES IT MAKES THE JAMMER AN ACTIVE JAMMER.

THAT'S IT.

---

YOU CAN USE A RADAR DETECTOR MICROWAVE WAVEGUIDE TO ACT AS THE RADAR JAMMER'S uWave OUTPUT, OR MAKE YOUR OWN BY RECONSTRUCTING THE DETECTORS WAVEGUIDE.

YOU CAN ALSO USE THE uWave DIODE FROM THE DETECTOR TO ACT AS THE JAMMER'S DIODE.

---

I'M SURE YOU'VE ALL HEARD THE RUMORS ABOUT PUTTING ALUMINUM FLAKES UNDER YOUR HUBCAPS OR PAINTING SPECIAL PAINT ON YOUR CAR BUT THOSE EITHER DO NOT WORK OR COST TOO MUCH. THERE

ACTUALLY IS A SPECIAL TYPE OF PAINT THAT IS ANTI-RADAR BUT IT COSTS WAY TOO MUCH FOR A TYPICAL JOE.

THERE ARE EASIER WAYS TO JAM RADAR BUT THEY ARE SUPER ILLEGAL AND INCORPORATE BREAKING MANY FCC RULES AND REGS. SOME OF THOSE WAYS ARE TO SIMPLY BUILD AN OSCILLATOR THAT OPERATES SYNCHRONOUSLY AT ALL THREE BANDWIDTHS AND TRANSMIT THOSE FREQUENCIES AT 360 DEGREES FROM EITHER THE TOP OR BOTTOM OF YOUR VEHICLE. YOU CAN ALSO USE THE BODY OF YOUR VEHICLE TO ACT AS A MIRROR LIKE WAVEGUIDE TO BOUNCE 40-50 PERCENT OF THE SIGNAL FROM YOUR TRANSMITTER DIODE OUTWARD ULTIMATELY JAMMING THE POLICE RADAR BEFORE IT EVEN REACHES YOU. BUT THAT IS ILLEGAL. IF YOU CANNOT BUILD AN OSCILLATOR WE CAN SUGGEST USING 3 MICROWAVE DIODES, EACH FOR EACH BAND OF RADAR, ALL THREE IN CONTINUOUS OPERATION AND MODULATED USING A MMIC HF MIXER IC, FEED WHITE NOISE INTO THE SIGNAL AND TRANSMIT. THAT'S IT. DO YOU NEED HELP? CONTACT UUE.



C1 = 1H103KT

Q1 = M78L05A

R1 = ORG BLK GLD GLD

C2 = C1

C3 = 101 Disc

XT = 4.0MG Ceramic Resonator

C4 = 201J

R2 = BRN GRN BLK GLD

R3 = RD RD BRN GLD

Q2 = CENPN 2222A

C5 = C1 C6 = 10nF @ 16V

R4 = YW ORG BRN GLD

R5 = GRN BRN BLK GLD

R6 = ORG BLK GLD GLD

R7 = ORG BLK GLD GLD

D1 = Silicon Diode

LED1,2 = LASER  $\alpha$  90xnm

LED3,4 = LED visible.


SW1 = Push Button Sw.

R8 = BRN BLK RD GLD


R9 = RD RD BRN GLD

BZ1 = Piezo Buzzer


IC1 = THAILAND  74HC02N  
A85800PS  
Hnn9709B

IC2 =  M74HC74BI  
F994B9635  
MALAYSIA

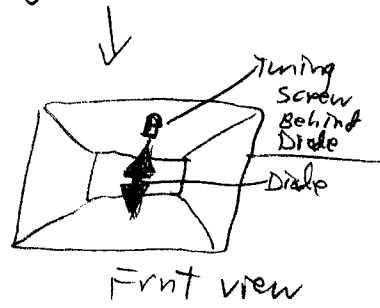TXD = MICROWAVE Diode (max Ka)  
w/ waveguide



Top view

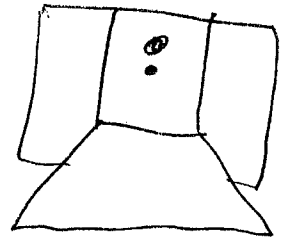

IC3 = CSC-001  
9703  
615B-1168