

AMATEUR ROBOTICS • MICROCONTROLLERS • COMPUTER CONTROL • ELECTRONICS Q&A

# Nuts & Volts

August 2000  
Vol. 21 No. 8

Exploring Electronics And Technology For A New Millennium



[www.nutsvolts.com](http://www.nutsvolts.com)

*A Tethered  
Backyard Explorer-Bot*

*Build A Party Strobe Light*

*FET Principles And Circuits*

*The Hidden Sounds  
On Your Telephone Line*

**AND MORE!**

U.S. \$4.50 CANADA \$6.50





# PROFESSIONAL DISK DUPLICATION

## CLONE, TEST OR REPAIR ANY HARD DRIVE

**\$995!**



- SUPPORTS IDE, SCSI, SCA & NOTEBOOK DRIVES
- COPIES AND SERVICES HARD DRIVES
- PRINTS TEST REPORTS ON YOUR PRINTER
- DATA RECOVERY MODE BUILT-IN

Copy entire hard drives with this pro service station. Set up any SCSI or IDE drive with your original software. Attach a blank drive and press start. Make copies quickly and easily.

Use the built-in drive service system to make used drives run like new! Eliminate defective sectors, and restore hard drives to error-free condition with the factory re-mapping system. Test hard drives for top reliability using the built-in test feature. Print analysis reports on any standard parallel printer. Get the technology used by drive repair services. Call today!

## 25GB MP3 PLAYER

**\$395!**

after mail-in rebate



- PLAYS OVER 10,000 SONGS FROM HARD DISK!
- PLAYS STANDARD AUDIO AND MP3 CDs AND CD-R
- DOWNLOADS MP3 FROM CD-R TO HARD DRIVE
- POWER AMPLIFIER DRIVES SPEAKERS DIRECTLY

MP3 is here! Get high performance digital sound and store over 15,000 songs on hard disk. Download over 300 songs from a single CD!

Grab new music from the net. Use your PC to create custom MP3 CDs with just the songs you like. Load them to the internal hard drive for realistic, 3-D theater sound. Patented digital signal processing gives you crystal clear sound. No PC connection is required. Connect any stereo system, or directly power external speakers. Get digital sound and room-filling bass.

The hard drive organizes your music in folders. ID-3 tags display the title, album, and artist on a large LCD. Use the jukebox feature for an entire evening of great music. Play songs randomly or in sequence from the internal hard drive. Unlike CD changers, the A/V certified 25 GB hard drive won't wear out, even under continuous use. Call now and try your MP3 player tomorrow!



### CORPORATE SYSTEMS CENTER

3310 WOODWARD AVE. • SANTA CLARA, CA 95054

WWW.DUPEIT.COM

**408 330-5524**

Over 80% of the Fortune 500 depend on CSC products. Shouldn't you? Call today. Most orders ship within 24 hours! Call now for more information and a free price comparison guide. Quantity discounts are available for dealers and system builders. Copyright laws must be observed when duplicating CDs and hard drives. © 2000 CSC.

## COPY ANY CD NOW NO PC REQUIRED

**from \$995!**



- MULTI-FORMAT DUPLICATION - FAST AND EASY!
- DUAL 8X DRIVES MAKE TWO COPIES AT ONCE
- INTERNAL 25GB HARD DRIVE STORES IMAGES
- PRO AUDIO MODEL HAS SP/DIFF AND ANALOG I/O

Instantly copy music and CD-ROM compact discs. Make backup copies of your favorite music and software on rugged, permanent CDs. Produce discs quickly and economically. Make custom audio CDs with just the songs you like.

Use our dual drive units to copy two CDs simultaneously, or choose the Pro Audio model to make crystal clear music CDs from any analog or digital source. Dupe-It copiers are totally self-contained. No additional software or hardware is required. Call today for more information!

## MULTI DRIVE IDE DUPLICATORS

**from \$495!**



- COPIES EVERYTHING, PARTITIONS, O/S, THE WORKS!
- BOTH STANDARD AND ULTRA, FOUR AND SEVEN DRIVE MODELS ARE AVAILABLE NOW!
- THE ULTIMATE HIGH SPEED PRODUCTION TOOL FOR SYSTEM BUILDERS AND CORPORATE MIS

Copy entire hard drives with ease. Multi-drive duplicators are an essential tool for dealers and system builders. Why spend hours installing and formatting drives when you can dupe them instantly? Work like the pros. Get your own multi-drive, stand-alone duplicators today. CSC offers a complete line of four and seven drive copiers in both standard and ultra versions. Ultra models transfer data faster than any hard drive! Rates of over 1GB per minute are supported.

Set up any IDE drive with all your original software. Attach blank target drives, and press "start". It's that easy! You can duplicate four drives in less time than it takes to copy one on a fast PC! Your duplicate drives will be identical, bit-for-bit perfect copies, with all the files, partitions, and information on the original drive. Building systems is tough enough. Why spend hours installing software? Save time. Save money. Call today and let us Fed-X your duplicator for a risk-free evaluation!



# HSC Electronic Supply

Serving  
Silicon Valley  
since 1964!

...brings you a potpourri of high-tech goodies for the techno-tinkerer!  
For thirty years we have been your source for Silicon Valley exotica!

## License-Free Two-Way Radio!

- ◆ Fanon "Courier KF-310, factory-new in box!
- ◆ Stay in touch at the park, in the mall or on the road!
- ◆ Transmits up to two-mile range without a license
- ◆ Full-power (5W) with extras not found on others!
- ◆ LCD backlit display for use day or night
- ◆ Uses new "Family Radio Service band -- all 14 channels, plus 38-channel CTCSS encode-decode
- ◆ VOX or Push-to-talk, w/3-type call tone
- ◆ Auto "power save" mode, auto-squelch
- ◆ Monitor button, speaker/mic jack, wrist strap
- ◆ Uses four "AAA" batteries (not included)
- ◆ Perfect for camping, sports, road trips, work... more!



Now...Special  
Bulk Purchase  
allows us to offer  
a reduced price!

Extra Special!  
Pack of 16 AAA  
Heavy Duty batteries,  
only \$2.95!

HSC#18198 \$39.95/ea  
...or Get TWO for \$74.95

## Seagate 1 GB Hard Drive!


- ◆ Seagate ST31012A 1 GB 3.5" hard drive
- ◆ Great for back-up, add-on or small dedicated systems
- ◆ IDE 40-pin connector
- ◆ Refurbished, 90-day HSC warranty



HSC# 18275 \$39.50
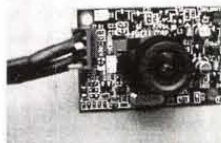
## Tiny Color CCD Camera!

- ◆ Camera-on-a-board measures 1.87" x 1.3", 1" thick!
- ◆ Has glass micro-lens element, not pinhole lens!
- ◆ DSP on board for auto white-balance, shutter
- ◆ Standard NTSC composite video output
- ◆ 350 lines horiz. resolution, good low-light sensitivity
- ◆ Uses 4 - 5 VDC, only 150 mA! Three AA batteries would power it for over six hours!
- ◆ New in OEM pkg. (no box), 90-day HSC warranty



HSC#18209 \$69.95

## 32X CD-ROM Drive!

- ◆ Acer Peripherals Model 632a
- ◆ Perfect for back-up, add-on or home-built systems
- ◆ Standard IDE 40-pin interface
- ◆ Refurbished, 90-day HSC warranty



HSC# 80537 \$39.50

## Multimeter Specials!

- ◆ Model #AEC-1890 3 1/2 Digit LCD DMM
- ◆ Adjustable large flip-up display for the easy viewing
- ◆ 0.5% basic accuracy, dual-slope integration A/D
- ◆ Measures AC/DC volts, ohms, current, capacitance, hFE & temperature (temp. probe included)
- ◆ Ranges: 1000VDC, 700VrmsAC, 200 ohm - 200 Megohm, 20 mA - 20A, 2nF - 20 uF, NPN/PNP hFE
- ◆ Separate jacks for capacitors and transistors
- ◆ "HOLD" function to capture measured peaks
- ◆ Soft rubber cradle protects meter, prevents skids
- ◆ Brand new! - With test leads
- ◆ Compare at prices of \$70, \$80 and up!



HSC# 80504 \$39.95

- ◆ Some people just don't like digital meters...
- ◆ Soltec HM102S 20 KOhm per Volt Multimeter
- ◆ Ranges: 0-1000VDC, 0-1000VAC, 0-50uA, 0.5, 5, 50 & 500 mA, 0-20 MOhm with X1, X10, X1K & X10K ranges
- ◆ Standard banana-plug test leads, manual included
- ◆ Carrying handle/stand, measures 3.5" x 5.25" x 1.5", mirrored dial for parallax-corrected readings
- ◆ New... 90-day warranty



HSC# 18260 \$9.95

## Keypad Mouse!



- ◆ "Unia" mouse with multi-function keypad!
- ◆ Numeric & special function keys, including SHIFT, ALT, RETURN
- ◆ Unique all-in-one ergo design for easy data entries
- ◆ Ideal for CAD, spreadsheet, games... etc
- ◆ LED indicators, 400/1200dpi switchable
- ◆ PC/AT compatible, w 9-pin D conn.
- ◆ New, 90-day warranty

HSC# 80539 \$9.95

## Quality Surge Suppression!

- ◆ Tripp Lite "Isobar"
- ◆ Multi-outlet surge suppressor / line filter
- ◆ Four outlets, two isolated filter banks
- ◆ Clean pulls, 30 day HSC warranty
- ◆ Compare at \$49.95!



HSC# 18315 \$19.50

- ◆ Tripp Lite "Isobar6"
- ◆ Premium surge suppressor / line filter
- ◆ Six outlets, three isolated filter banks
- ◆ Clean pulls, 30 day HSC warranty
- ◆ Compare at \$65.00!



HSC# 18314 \$25.00

## ATX Computer Power Supply

- ◆ Power Computing TCX-200
- ◆ Perfect for upgrading! Put modern motherboards into older cases
- ◆ 200W fan-cooled power supply
- ◆ Standard Mini-tower form-factor, ATX connector
- ◆ Units are brand new w/90-day warranty



HSC#18304 \$17.50

## SCSI Drive Cases

Just in...two new styles of SCSI drive case. Perfect for those RAID systems, server backup, or other mass storage systems! Both feature: Power and drive status LEDs, front panel off/on switch, RCA audio jacks & connecting cables, SCSI ID switch, fan-cooled switching power supply. Attractive beige color, curved front panels. Rear panel is punched for SCSI-1 (ICN-50) daisy-chain connectors, internal SCSI cable not included. Brand new in box, 90-day warranty

- ◆ Two-bay case
- ◆ Measures 6.3" x 7.0" x 11.25"
- ◆ 80-watt power supply



HSC# 18267 \$39.95



- ◆ Four-bay case
- ◆ Measures 10.3" x 7.125" x 14.3"
- ◆ 200-watt power supply

HSC#18268 \$49.95

## CAT-5e Cable Special!

- ◆ 350+ Enhanced CAT5e 100MHz horizontal cable
- ◆ 4-Pair, 24 AWG solid conductor
- ◆ Meets UL/CSA TIA/EIA 56B standards
- ◆ Exceeds proposed 1 GHz Standards
- ◆ Available in White, Blue or Grey - Your choice
- ◆ Price is for 1000' spool -- wire your house!

HSC#5E8XX1001 \$69.00

## LED Rainbow!

- ◆ A variety of LED's for just about any project!

◆ T1 (3mm dia.)		
Red	L34HD	10
Green	L34GD	12
Yellow	L34YD	12
Blue	80535	1.50
◆ T1 3/4 (5mm dia.)		
Red	L53HD	10
Red Hi-Inten. (1000mcd)	L5014	49
Red Blinking	L56BHD	60
Green	L53GD	12
Green Blinking	L56BGD	65
Yellow	L53YD	12
Yellow Blinking	L56BYD	75
Blue	80534	1.75
White	L54PNC	2.49
Bi-Color (R-G, 2 leads)	L57EGV	35
Bi-Color (R-G, 3 leads)	18220	25
Tri-color (RGB, 6 leads)	80538	6.50
Infrared	80536	1.5
◆ Jumbo (10mm dia.)		
Red	L813ID	40
Green	L813GD	40
Red Blinking	L816BID	1.25

## Unique Project Base for Video Hackers!

- ◆ Perfect for experimenters, tinkers and the just curious... Logitech Videoman videoconference camera system!
- ◆ These were sold with Hewlett Packard S-700 UNIX workstations for videoconference capability
- ◆ The camera's brightness, contrast and shutter speed can be PC bus controllable
- ◆ We have technical data sheets for the camera. A condensed information sheet is included with camera pinouts and basic specs. Full specification document (camera only) available for \$2.00 (cost of printing)
- ◆ The camera is on a weighted stand that extends from 13" tall to over 20" tall
- ◆ Color camera is digital output only (not NTSC as was previously believed)
- ◆ Note: HP and Logitech will provide no information on these items!
- ◆ Interface box has two SCSI-II ports on back, and a DC power input (we do not have the adapter), and on the front it has a mic. out jack, composite video input (BNC), and the connector for the camera cable
- ◆ Units are new!

Now! Some technical data is available (Camera only)!

HSC#17503 Lower Price for set! \$19.95  
HSC#17503a Camera Only \$12.50  
HSC#17503b Interface Only \$12.50



## SCSI Adapters for PC's

- ◆ Initio INI-9100AS high-performance PCI host adapter
- ◆ Supports 32-bit data transfers up to 133MB/sec, 10MB/sec. sync transfers
- ◆ PNP compatible, includes manual & driver disk
- ◆ PCI 2.1 compliant, auto-termination on board
- ◆ Compatible with CD & CD-Rs, optical & tape drives, scanners, 'Zip' & 'Jaz' drives, NON-bootable



HSC#18218 \$29.50

- ◆ Adaptech model AVA-1505A1 -- Brand Name Quality!
- ◆ Single, complete PC connection
- ◆ For single non-bootable SCSI2 peripheral
- ◆ New, OEM pack, with install diskette & manual



HSC#17995 \$17.50

Special! ...w/DB25 adapter & cable \$19.95

**Halted**  
specialties co.

**HSC**

**Electronic Supply**

Toll Free (Orders Only) 1-800-4 HALTED  
Internet World Wide Web:  
3500 Ryder St., Santa Clara, CA 95051  
4837 Amber Ln., Sacramento, CA 95841  
5681 Redwood Dr., Rohnert Park, CA 94928

(1-800-442-5833)  
<http://www.halted.com>

(408) 732-1573

(916) 338-2545

(707) 585-7344

FAX your orders to:

(408) 732-6428



## Visit HSC's Website!


- ◆ Pay us a virtual visit on the World Wide Web!
- ◆ Simply point your browser to <http://www.halted.com>
- ◆ Site is constantly being revised, please visit often!
- ◆ Or, you can email your order to [hscmail@halted.com](mailto:hscmail@halted.com)
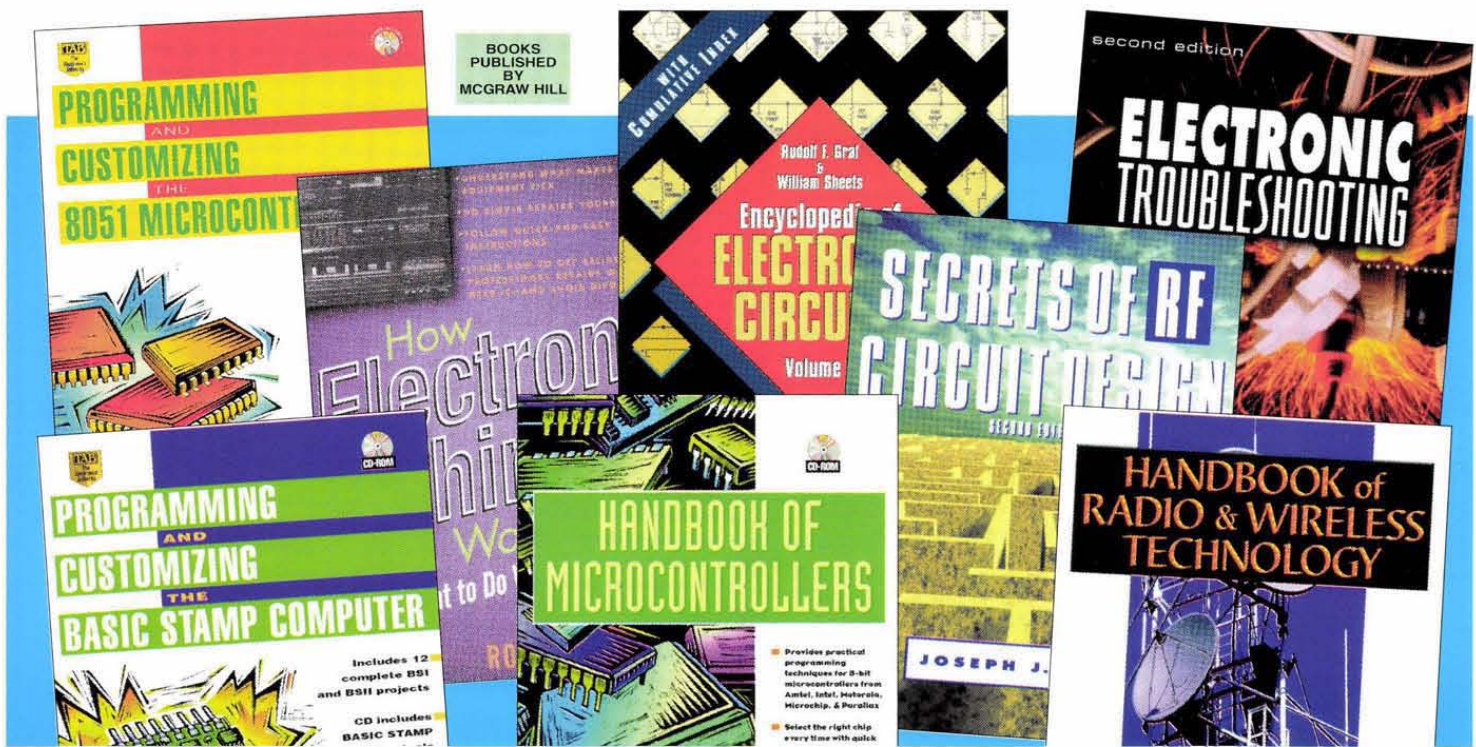
## Weekly Web Specials!

- ◆ A new section has been added to our web page!
- ◆ Simply go to [www.halted.com](http://www.halted.com) and click the top button!
- ◆ Items from our ads, as well as non-advertised items
- ◆ Also, you can download our catalog as Adobe PDF files

Terms: Some quantities limited, all items subject to prior sale. Minimum order: \$10.00 plus shipping. Orders under \$20.00 subject to \$2.00 handling fee, in addition to shipping. All orders shipped FOB Santa Clara, CA (this means you pay freight) by UPS Surface (no P.O. Boxes) unless otherwise specified, in which case prevailing carrier rate plus \$5.00 handling fee applies. Prepaid orders that don't include shipping charges will be shipped freight COD. There is a \$5.00 UPS charge added to shipping charges for COD shipments. If you have questions about your order, please call Customer Service at (408) 732-1854 M-F 9AM to 5PM PST.





# Nuts & Volts Book Store

**Call 1-800-783-4624 today!**  
WE ACCEPT VISA AND MASTERCARD

AUTHOR/TITLE	REG PRICE	SUB PRICE
Axelsson, JL — Making Printed Circuit Boards	\$22.95	\$20.65
Brown, RM & Lawrence — How to Read Electronic Circuit Diagrams	\$19.95	\$17.95
Carr, J — Practical Antenna Handbook	\$39.95	\$35.95
Carr, J — Secrets of RF Circuit Design	\$29.95	\$26.95
Davidson, HL — Build Your Own Test Equipment	\$22.95	\$20.65
Davidson, HL — Radio Receiver Projects You Can Build	\$21.95	\$19.75
Davidson, HL — Troubleshooting and Repairing Consumer Electronics Without a Schematic	\$24.95	\$22.45
Edwards, S — Programming and Customizing the BASIC Stamp Computers	\$34.95	\$31.45
Gibilisco, S — Amateur Radio Encyclopedia	\$29.95	\$26.95
Gibilisco, S — Handbook of Radio and Wireless Technology	\$44.95	\$40.45
Gibilisco, S — TAB Encyclopedia of Electronics for Technicians and Hobbyists (hard cover)	\$69.50	\$62.55
Gibilisco, S — The Illustrated Dictionary of Electronics	\$39.95	\$35.95
Goodman, R — How Electronic Things Work ... and What to Do When They Don't	\$24.95	\$22.45
Graff, R — Encyclopedia of Electronic Circuits	\$39.95	\$35.95
Horn, DT — Basic Electronics Theory	\$26.95	\$24.25
Horn, DT — Ready-to-Build Telephone Enhancements	\$17.95	\$16.15
Lenk, J — Circuit Troubleshooting Handbook	\$39.95	\$35.95
McComb, G — The Robot Builder's Bonanza	\$18.95	\$17.05
Predko, M — Handbook of Microcontrollers	\$54.95	\$49.45
Predko, M — Programming and Customizing the PIC Microcontroller	\$39.95	\$35.95
Predko, M — Programming and Customizing the 8051 Microcontroller	\$39.95	\$35.45
Sinclair, J — How Radio Signals Work	\$24.95	\$22.45
Tomal, D/Widmer, N — Electronic Troubleshooting	\$34.95	\$31.45
Veley, V — The Benchtop Electronics Handbook: 260 Most Common Popular Electronics (cloth cover)	\$65.00	\$58.50

Send check or money order to Nuts & Volts, 430 Princeland Court, Corona, CA 92879. Include a complete shipping address (no P.O. Boxes, please). Shipping & handling \$4.50. CA residents add 7.75% sales tax. Or, call our toll-free order-only line at 1-800-783-4624 and use your MasterCard or Visa. ALL ORDERS MUST BE PREPAID.

**10%  
OFF**

**FOR PAID SUBSCRIBERS**



# Contents

VOLUME 21 • NO. 8 • AUGUST 2000

Call our  
subscription  
order only  
line at  
1-800-783-4624

## articles ...



## columns ...

### AMATEUR ROBOTICS NOTEBOOK 6 Robert Nansel

This month, we finish the wiring and electronics for Jiffy, take a look at an unusual three-wheeled robot controlled by a Palm Pilot, dabble into some historical and philosophical musings on the nature of hacking and the nurture of innovation, then wind things up with some suggested summer reading.

### ELECTRONICS Q & A 26 TJ Byers

### OPEN CHANNEL 14 Joe Carr

VLF Radio.

Take a more extensive look at ELF, VLF, and LF.

### STAMP APPLICATIONS 64 Jon Williams

Stamps in the Lab continued ...

Last month, we kept our PC connected to the Stamp and used it as an "information provider," pumping out data. This month, we want to ask our Stamp for specific information and also give it information to affect its behavior.

10. Ham Gear for Sale .....	38	120. Components .....	60
20. Ham Gear Wanted .....	0	125. Microcontrollers .....	60
30. CB/Scanners .....	38	130. Antique Electronics .....	60
40. Music & Accessories .....	0	135. Aviation Electronics .....	60
50. Computer Hardware .....	39	140. Publications .....	60
60. Computer Software .....	39	145. Robotics .....	61
70. Computer Equip. Wanted .....	40	150. Plans/Kits/Schematics .....	61
80. Test Equipment .....	40	155. Manuals/Schem. Wanted .....	61
85. Security .....	40	160. Misc. Electronics For Sale .....	61
90. Satellite Equipment .....	42	170. Misc. Electronics Wanted .....	62
95. Military Surplus Electronics .....	58	175. BBS & Online Services .....	62
100. Audio/Video/Laser .....	58	180. Education .....	62
110. Cable TV .....	58	190. Business Opportunities .....	63
115. Telephone/Fax .....	59	200. Repairs/Services .....	63

Classified Ad Index

Advertiser's Index ...	83	News Bytes .....	12
Classified Ad Info ...	82	NV AdMart .....	76-78
Dealer Directory ...	18	NV Bookstore .....	4
Events Calendar ...	35	Prize Drawing .....	47
New Product News ...	93	Reader Feedback ...	2
		Tech Forum .....	79

Departments

### POWER SUPPLY DESIGN

#### SOFTWARE 20

Ken Coffman

Meet Power456 plus: A software tool that can help you keep track of all the details of a switched-mode power supply design, and help you design the compensation.

### THE HIDDEN SOUNDS ON YOUR TELEPHONE LINE 31

ML Shannon

"Listen-Down-The-Line" with this simple amplifier that lets you hear exactly what's happening on your phone line.

### HANDHELD SATELLITE/CELL PHONE FROM GLOBALSTAR 43

Gordon West

With the failure of the Iridium satellite/terrestrial portable phone system, many people have their doubts about this type of communication system. However, Globalstar can alleviate these concerns since their "satellite" system is just like using cellular.

### A TETHERED BACKYARD

#### EXPLORER-BOT 48

Karl Lunt

Adding a simple tether to an easily-constructed robot frame can give you a powerful, fun-to-run machine with little cost or work.

### TAKING THINGS APART: THE JOY OF MICROCONTROLLER DISASSEMBLY — PART I 54

Tim Deagan

This article will describe the basic concepts you need to understand how a disassembler works.

### FET PRINCIPLES AND CIRCUITS (PART 4) 70

Ray Marston

In this final installment, you'll take a look at practical VMOS power FET circuits.

### BUILD A PARTY STROBE LIGHT 84

Fred Blechman  
and David McDonald

Flash back to the disco scene with this "like totally kewl" sound-sensitive strobe with built-in microphone. However, its applications aren't limited to pounding music, dazzling lights, and mirrored balls.

### IOKIT AND BRIDGE SOFTWARE 87

Don L. Powrie

Construct this cost-effective power supply which includes a two-channel voltmeter, an SPT relay, an optically isolated digital input, and some expandability.



# AMATEUR ROBOTICS

by Robert Nansel

## NOTEBOOK

This month, I finish the wiring and electronics for Jiffy, take a look at an unusual three-wheeled robot controlled by a Palm Pilot, and admire its wheels (even though they aren't made from peanut butter lids). I also have some historical and philosophical musings on the nature of hacking and the nurture of innovation, and I'll wind things up with some suggested summer reading.

### Jiffy Gets Wired

The first job is to mount the four AA-cell battery holders inside the front and rear chassis. The reason for two battery holders is to more uniformly distribute the weight between the front and rear chassis. This helps the skid-steer system work more predictably. Also, one pack powers the servos and the other powers the electronics.

I used double sticky foam tape to mount the holders. Clean the bottom surface of each battery holder (RadioShack #270-391) with alcohol, then roughen the surface with sandpaper or a file so the foam tape will adhere better.

Position and orient the battery holders with the ends of the holders pressed up against the inside wall of each chassis compartment and the wires facing inboard (i.e., toward the swivel; see Photo 3). Press firmly into place.

The second job is to drill the mounting holes for the power

switch and the LED power-on indicator. The power switch is a DPDT submini center-off toggle switch (RadioShack #275-620A), and it requires a 1/4" hole for the threaded mount and an optional 1/8" hole 1/4" to the side for the regis-

tration tab. For the registration hole I drilled a 1/8" dimple, just deep enough to take the tab. The LED (RadioShack #276-018) comes with its own snap-in holder, and it requires a 5/16" hole.

I placed the power switch hole in the rear chassis by eye, on the centerline of Jiffy. I put it a little back from the tilt sense potentiometer so that the solder lugs of the switch would be accessible inside the box — about 3/4" from the front outside edge of the box. The hole for the indicator LED goes

another 1/2" back from the center of the switch hole, but be sure the body of the LED holder will clear the front edge of the battery holder (Photos 1 through 3).

Instead of the nut provided with the switch, I used one of the

able on a picnic table without AC power), I had intended to place most of Jiffy's electronics on a RadioShack project board.

Accordingly, I wanted to do all the soldering with a butane soldering iron. However, I had never used a butane soldering iron before, and my first few attempts to solder with it proved disastrous.

No, I didn't set the table on fire or scorch my pants (though these are distinct risks with this sort of iron), but I did ruin a few project boards. It's hard to get the tip temperature low enough to prevent delaminating the copper pads. The particular style of board I used — RadioShack #276-158, one pad per hole — compounded the problem.

Soldering the pins of an IC socket was not hard, but the heavier pins of header connectors proved to be a different story. Even though I pre-cleaned the copper pads with a scrubbing pad and liberally applied flux

paste, I never managed to get good solder joints before too much heat built up and the pads delaminated. The iron — a RadioShack #64-2182 — is rated for 10-60 watts, and the tip that comes with it is a little larger than I would ordinarily use for PCB work. A smaller 1mm tip is available, and perhaps that would have solved the problem (that and a bit more practice).

Whatever the ultimate solution may have been, I decided to obviate the problematic PCB soldering by falling back on a solderless bread-

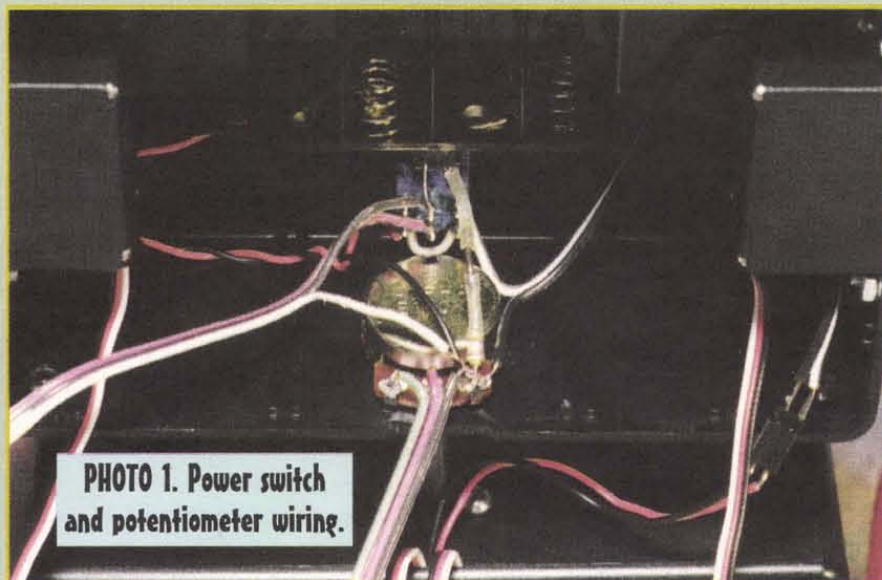


PHOTO 1. Power switch and potentiometer wiring.

new rubber caps to secure the switch. These caps (RadioShack #275-1596) fit over the toggle lever of submini switches and have threaded brass inserts that match the thread size. They also have a rubber O-ring seal, so between that and the rubber sheath over the toggle, the whole assembly comes out reasonably water tight.

### Sacramental Solder Smoke

In the spirit of keeping the robot simple and cheap (and build-


**Motron Electronics**

PO Box 2748  
Eugene OR 97402-0280  
(541) 687-2118

**DTMF Controller**

**Only \$149.00** Plus SH

<http://www.motron.com/>

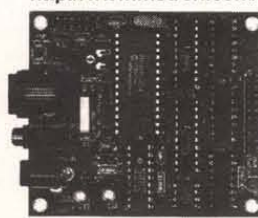

Auto-Kall® AK-16  
DTMF Controller Board

The **Auto-Kall® AK-16** DTMF Controller Board features 16 relay driver outputs and DTMF to X-10 house control capability! Control the relay driver outputs, X-10 modules, or both with your radio keypad! X-10 operation requires the PL-513 Power Line Interface (\$20). The **AK-16** mates readily with our **RB-8/10** (\$99) or **RB-16/10** (\$149) relay boards. The 0-12 digit security code is user programmable using your DTMF keypad. Additional features include re-programmable CW ID and several modes of operation, including two with CW response. The **AK-16** is a fully assembled and tested printed circuit board.

Price and Specifications are subject to change without notice.



Visa, MasterCard, American Express, Discover  
And Government Purchase Orders accepted.  
SH: \$8 USA; \$11 Canada; \$16 Foreign  
Se Habla Español. Pida Por Don Moser.



Info: (541) 687-2118

Orders: (800) 338-9058

Fax: (541) 687-2492

## PROGRAMMABLE SOLENOID

- Low cost motion control
- Wide operating voltage (12 - 28)
- Onboard programming and parameter storage
- Self-contained electronics

### Rotary (PPS-1)



\$95.00 + \$5 s/h

### Linear (PPS-2)



\$145.00 + \$5 s/h

- Simple connection only 3 wires: Power, Ground, and CMD signal
- Long Life: Brushless ball bearing stepper
- Constant current Torque/Force

The Picard Programmable Solenoid (PPS) delivers the motion capability of a sophisticated stepper motor system with the simplicity of a solenoid. This eliminates the non-linear and erratic banging motion of a traditional solenoid. The electronics of the PPS allows the user to program and store the desired motion profile using the simple user interface. The innovative PPS gives programmability to the motion of a solenoid without the expense of a costly motion control system.

## PICARD INDUSTRIES

Specializing in Miniature Smart Motors and Sensors

4960 Quaker Hill Road  
Albion, New York 14411

Phone/Fax 716-589-0358

Email: [jcamdep4@iinc.com](mailto:jcamdep4@iinc.com)  
[www.picard-industries.com](http://www.picard-industries.com)



CAL4SERV.BAS

Calibrate 4 servos

## LISTING 1

\* Set up I/O bits

```
DIRS = %1111111111111111
```

\* Make all I/O bits outputs  
\* Only bits 0, 1, 2, and 3 are connected.  
\* The rest are left as unconnected outputs to save power & prevent possible erratic operation

\* Send 1.5 msec pulse trains to all four servos to calibrate STOP settings

main:

```
PULSOUT 0, 750
PULSOUT 1, 750
PULSOUT 2, 750
PULSOUT 3, 750
```

```
PAUSE 10
```

```
GOTO main
```

```
END
```

board (RadioShack #276-175, Photo 4). This proves to be much more compatible with building on a picnic bench, anyhow — and quicker. Some soldering is still required for the power switch, power-on LED, and various cables, but it's easy to make these joints since they aren't as delicate.

### Point-to-Point

Photos 1, 3, and 5 show the general layout of wiring. I used one end-tap lug of the potentiometer as a convenient point to make all of the ground connections, and the solder lugs of the switch itself for the B+ connections. The rest of the wiring is accomplished with jumpers on the solderless breadboard as seen in Photo 4. The BS2 is on the left, in the middle are four three-pin header connectors for the Futaba servos, and on the right are two

more three-pin headers, one for power (bottom) and one for the relative tilt sensor (top). The solderless breadboard is mounted to the bottom lid of the rear compartment (what I call the "brain pan").

Everything is connectorized so the two chassis boxes and the brain pan can be separated (see Photo 5). Three cables run from the front compartment to the rear: two ribbon cables for the servos and one for the battery holder.

Photos 2 and 6 show a fourth cable emerging from the rear chassis. This cable is the four-wire BS2 programming cable. It connects straight through to pins 1 through 4 of the BS2-IC. I added this cable because I got tired of opening the box every time I wanted to reprogram the BS2.

To accommodate the cable, you'll need to widen the slot the other cables run through. I used

solid-wire ribbon cable, so the cable is just bent out of the way when not being used. If you are satisfied with your program, you can also tuck the cable away inside the box.

### A Different Servo Hack

Listing 1 is a brief bit of PBASIC code to allow you to calibrate your servos' STOP range. Most people modify servos for continuous rotation by replacing the

servo potentiometer with a fixed resistor voltage divider. This works fine, but for Futaba servos, there is an easier way that's less intrusive and much more convenient.

Dismantle the servo as normal, but leave the bottom plate and circuit board undisturbed. The output gear/shaft of the servo has a silver-gray bearing ring in its hollow underside, and beneath that ring is a slotted nylon coupler that the potentiometer shaft rides in. With a

little bit of levering, you can easily pop the bearing ring and slip the nylon coupler out. Set aside the nylon coupler (save it if you ever want to convert the servo back to ordinary operation), and press the bearing ring back into place. Shave off the mechanical stop lobes on the upper side of the output gear as usual. Repeat this process for the other three servos.

Now, instead of putting the output gears back and reassembling the servos, leave the tops off so the feedback pot shafts are visible. Connect the servos to Jiffy's brain, download CAL4SERV.BAS, and run the program. All the program does is send 1.5-msec pulsetrains to each of the servos. The motors for all four servos will probably start running.

Tweak the feedback pots of each until the motor stops. Reassemble the servos without disturbing the pot settings (the pots have a fair amount of friction, but you can put a drop of hotglue on the pot shafts to hold them more securely, if you like). That's it.

(Next month, I'll get into software to really give Jiffy a workout.)

### Omnidirectional Drive

One of the bonuses of being a member of the Seattle Robotics

# Go Wireless With Our Modules

## SILRX/TXM

SILRX — \$26.00 ea.

TXM — \$15.50 ea.

The TXM and SILRX modules are a transmitter and receiver pair which can achieve a one-way radio data link-up to a distance of 200m over open ground.

Both units are supplied in space-saving single-in-line packages and offer SAW controlled, wide band FM transmission/reception.

The modules are particularly suited to battery-powered, portable applications where low power and small size are critical design criteria.



## TX2/RX2

TX2 — \$19.50 ea.

RX2 — \$38.50 ea.

The TX2 and RX2 radio transmitter and receiver pair enable the simple implementation of a data link at up to 40kbit/s at distances up to 75m in-building and 300m open ground. Both modules combine full screening with extensive internal filtering to ensure EMC compliance by minimizing spurious radiations and susceptibilities. The TX2 and RX2 modules will suit one-to-one and multinode wireless links in applications including car and building security, EPOS and inventory tracking, remote industrial process monitoring, and computer networking.

Because of their small size and low power requirements, both modules are ideal for use in portable, battery-powered applications such as hand-held terminals.



900 MHz

AVAILABLE NOW

## RPC

RPC — \$99.00 ea.

The RPC module is an intelligent transceiver which enables a radio network link to be simply implemented between a number of digital devices. The module combines an RF circuit with processor-intensive low-level packet formatting and recovery functionality, requiring only a simple antenna and 5V supply to operate with a microcontroller or a PC.



## BiM

BiM — \$69.00 ea.

The BiM module integrates a low-power UHF FM transmitter and matching superhet receiver together with data recovery and TX/RX change over circuits to provide a low-cost solution to implementing a bi-directional short-range radio data link.



## Lemos International Co., Inc.

65 Southbridge Street, Auburn, MA 01501

Phone (508) 798-5004 ♦ Fax (508) 798-4782

www.lemosint.com ♦ sales@lemosint.com

All products available in either 418 or 433 MHz

Write in 187 on Reader Service Card.


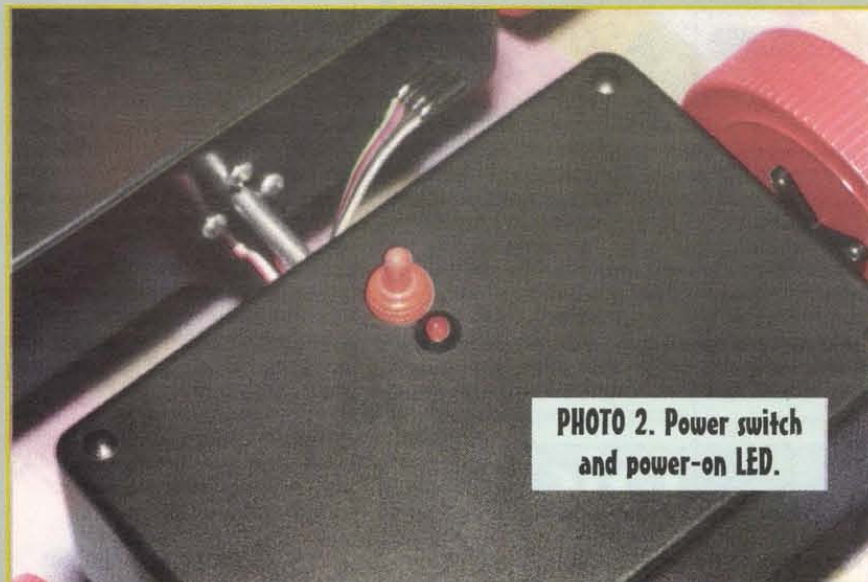


PHOTO 2. Power switch and power-on LED.

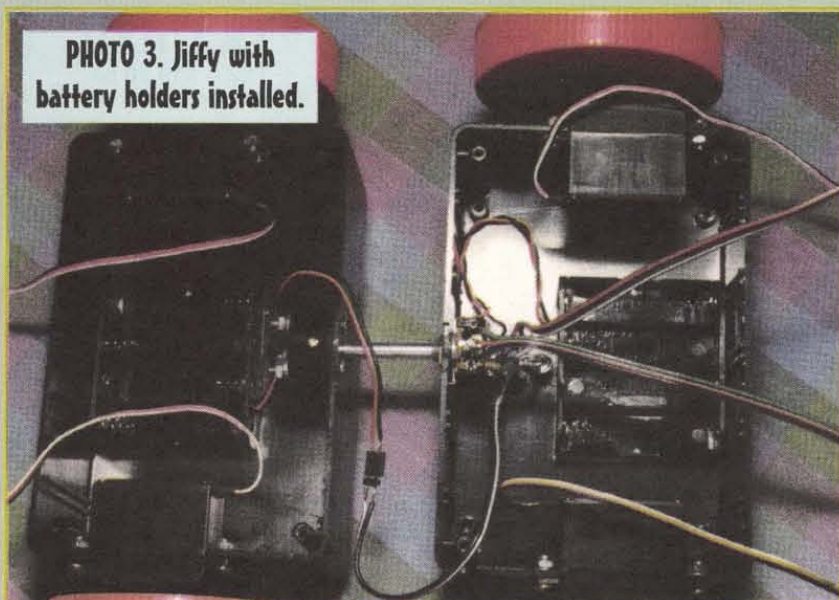

**PHOTO 3. Jiffy with battery holders installed.**



uses wheels that roll in the normal way, but they also roll from side to side — roller wheels which permit 360-degree multidirectional movement. To see what I mean, take a look at [www.cs.cmu.edu/~reshko/PILOT/](http://www.cs.cmu.edu/~reshko/PILOT/)

The nifty thing about these wheels is they cost only \$5.00 each. You can also use these wheels to replace standard swiveling caster wheels. You can find information on these wheels — called Trapo-brand All-Side Rollers — at North American Roller Products, Inc., P.O. Box 2142, Glen Ellyn, IL 60138-2142. You can also call them

at (630) 858-9161. The contact I spoke to was Jerry Miller, and he can be reached at [jhmnap@aol.com](mailto:jhmnap@aol.com). Now, Jerry told me his company's wheels aren't really intended to be used as drive wheels; they are really only meant to be used on product conveyers. But they sure look worth a try. (Sorry, no website for this company.)

But back to the Palm Pilot Robot. As it turns out, the people who designed the robot are local to me at Carnegie Mellon. Though they are just 20 miles up the Ohio river from the Robot Ranch, I would have likely never stumbled across

Anyway, because of the SRS list, I heard about a particularly interesting robot: the Palm Pilot Robot which uses a *holonomic* drive system. A *holonomic* drive is drive where the robot's translation and rotation on a plane surface are independent of each other. The vector sum of the rotational vectors of all the wheels determines the direction and speed of the robot's translation and rotation. In other words, the robot can position itself anywhere on a plane in any orientation. The robot accomplishes this using three servo-driven omnidirectional wheels. Omnidirectional? That's right, it

Society list server is that I find out about cool robot links that other people come across, many more links than I even have time to investigate each month. If you aren't a member of the SRS list, you should be. It's free, and it's one of the best sources of ideas and how-to information on amateur robotics on the web.

To join, go to the new SRS list site at [www.egroups.com/invite/SeattleRobotics](http://www.egroups.com/invite/SeattleRobotics) and click the "JOIN" button. You may also visit the eGroups web site to modify your subscription: [www.egroups.com/mygroups](http://www.egroups.com/mygroups).

their website on my own if it hadn't been for the person who posted the URL to the SRS list. This points out how important the new virtual gathering places — such as the SRS list — can be.

## Invention and Place

Histories of innovation usually concentrate on the end product — the successful invention or the brilliant inventor. But this approach to history tends to obscure the process of innovation itself. No innovation occurs in a vacuum; all great innovations have as background the places, institutions, and times that drive the process. Some of these places were extraordinary, but too often, little is known of them.

Boston in the 60s and 70s was such a place, the fulcrum of a technological revolution that we are reaping the fruits of. The institution was the workshop of Charles Williams, Jr.

Williams, a successful independent engineering consultant, employed 25 talented technicians and specialists at 109 Court Street, where his R&D facility occupied the entire third floor. The building was shabby, but the rent was cheap. What he saved on rent he used to equip his lab with the best equipment and materials he could buy. Williams often took on "White Knight" consulting contracts.

In the consulting business, a "White Knight" is a consultant brought in by a company to troubleshoot a hopelessly mired engineering project. It's risky work, but Williams enjoyed pushing the envelope; when successfully concluded, these projects almost always meant more business for his shop, either in new referrals or in short-run manufacturing of finished products. If his success could be summed up in three principles, they would be: 1) Stay small; 2) Hire the best; and 3) Stay current.


But sometimes the story of a man can better be told by the stories of the people around him. In the midst of the turbulence of the war and the civil rights struggles of the 60s, many businessmen of his generation scorned the rebellious

## Use your PC as a scope and datalogger!

PC-based Instruments!
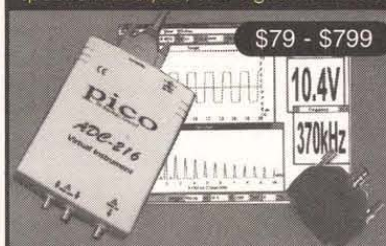
### Parallel Port Scope

spectrum analyzer, and digital multimeter



\$79 - \$799

**ADC Virtual Instruments** turn your PC or laptop into a sophisticated storage scope AND spectrum analyzer AND multimeter. Display simultaneously on large screen! 100MS/s 8-bit or 1.2MS/s 12-bit or 333kS/s versions. Great for schools, test depts, etc. Input to Excell LabView/NT drivers included.

### Environmental Logging

record temperature, humidity, etc.



\$129 - \$645

**ENVIROMON** - temperature (thermistor), humidity & light sensors, door position, etc. Record for 365/24 without a PC even if power fails. Monitor 30 sensors 400 yds away. With cables and easy software. Remote audio alarm. Use TC-08 for most thermocouples.

### osziFOX

20MS/s handheld scope



\$129

**osziFOX** - handheld storage scope and DVM - stand-alone or plugs into your PC for display, store-to-disk, printing in color. Inputs to 100V, trigger, backlit LCD.

Download FREE demo software. Sales only: 1-888-7SAELIG  
[www.saelig.com](http://www.saelig.com) 716-425-3753 • -3835 (fax) [saelig@aol.com](mailto:saelig@aol.com)

**pico**  
Technology Limited®


Stocked in NY by Saelig Company: Virtual Instruments, I2C and embedded controllers, BITlink 2-wire networks, RS232/422/485, frame grabbers, etc. See [www.saelig.com](http://www.saelig.com) for Product of the Month!

If you have suggestions, questions, or comments about amateur robotics topics or, if you want to come to High GEAR, you can reach me at:

Robert Nansel  
Box 228  
Ambridge, PA 15003

E-Mail:  
[bnansel@nauticom.net](mailto:bnansel@nauticom.net)



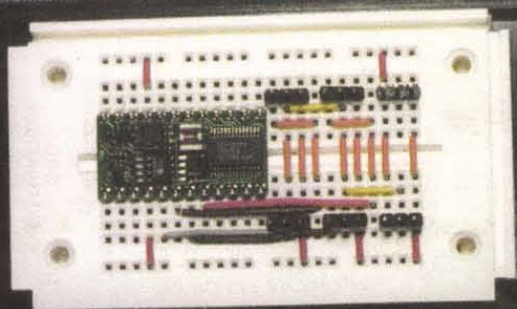

**PHOTO 4. Jiffy's brain mounted on chassis lid**

youth of America, but Williams actively embraced them. Williams especially had a soft spot for young hackers, and his workshop became a haven for them.

They came to his workshop to talk, to listen, and to dream, and some of them eventually even went to work for him. Students and dropouts, drifters and dreamers, they came and shared their visions of a better tomorrow, their hunger for change.

## A Hacker Named Al

One hacker, known by his friends as "Al" was an oddball by any definition. He'd dropped out of school and had subsequently lost or quit every job he ever had, too lazy — to his parent's dismay — to make it in corporate America. In Boston, Al worked just hard enough at his day job to keep from getting fired. He lived on junkfood (pie was his favorite), kept late hours, and it showed. In his early 20s, he was rough, spoke poorly, and lacked most basic people skills. He was, in a word, a nerd.

Al found in Charles Williams and the people surrounding him the technical and emotional nourishment that he needed to transform himself. He rubbed elbows with techies with far more education than he, but at 109 Court Street, what mattered was the quality and workability of your ideas, not the level of your education.

Al was inspired by everything he saw and heard at 109 Court Street. In the nutrient medium that Williams provided, Al's native genius overcame his laziness and lack of education. Though he never understood people, he understood the technology. He began his own consulting company in the late 60s, a

time when the idea of the information appliance and digital networks were just being born. He concentrated first on data communication equipment, earning the admiration and dollars of business people who increasingly came to depend on the new "boxes" on their desktops — and on Al's guru-like ability to debug them. From there he branched out to recording, multimedia, and lighting systems. His story has become the classic of the garage-hacker-to-billionaire-entrepreneur genre.

## A Hacker Named Alec

Another hacker, a foreign student from Scotland, came to 109 Court Street a few years later in the 70s. His name was also Al, though he preferred to be called Alec. Where Al was unkempt and rough, Alec dressed well and was anything but a nerd in appearance. He was a well-educated, polished man who spoke eloquently on many topics. He was about Al's age, but looked older. Alec mixed easily with the liberal elite of Boston.

But Alec — like Al — was a night owl. He was a radical, exploring the fringes of perception and expression. He taught in an experimental school during the day and at night tinkered with exotic telecommunications hardware, filling his apartment with various "blue boxes," "red boxes," and "black boxes." He was the original phreaker, and his goal was nothing less

than the overthrow of America's telecommunications megacorporation.

For all his education and polish, Alec was not as technically able as Al. He depended on the Court Street scene not only for his raw materials and equipment, but for technicians to build what he visualized. His first assistant was George Hamilton, a man "loaned" to him by Moses Farmer, a sometime military contractor who frequented Williams' workshop.

Farmer, an establishment engineer (but a hacker in spirit), depended on Charles Williams' firm for quick-turn engineering prototypes and advanced materials. Among other things, Farmer was working on improving torpedos for the Navy. Two years after the economy soured in '73, Farmer decided to close his Boston operations to concentrate on his torpedo contracts in Newport, RI. He took George Hamilton with him, so Alec had to find someone else to help him build his increasingly


starting a Fortune 500 company.

For both Al and Alec, the influence, encouragement, and technical support of Charles Williams was crucial; 109 Court Street in Boston was the nexus of change. Throughout history, certain places and people have been central to change — places like Detroit for the automobile, Silicon Valley for semiconductors, Coalbrookdale for steam engines.

The technologies that germinated at Charles Williams' 109 Court Street shop are no less momentous in their effects on our lives, but the place and the man aren't well known. We remember the people he encouraged, people like Al and Alec.

If we understand fully what happened at 109 Court Street, if we can feel the atmosphere of that place, we have a chance to make it happen today for amateur robotics. With the World Wide Web, physical places aren't quite as crucial as they once were, but robot builders still need hacker-friendly places — real and virtual — to exchange information, to buy leading-edge supplies, and to share the energy of like-minded gearheads. Most of all, we need the spirit that drove Al and Alec to create.

Al and Alec? You most likely know them as Thomas Alva Edison and Alexander Graham Bell; their times were the 1860's and '70s.

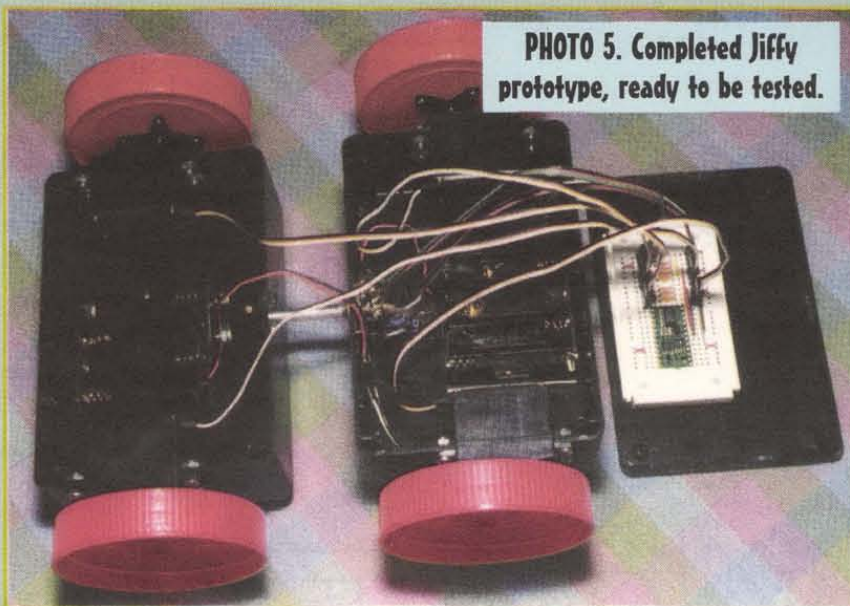

**PHOTO 5. Completed Jiffy prototype, ready to be tested.**

sophisticated gear.


He went to Charles Williams for help. Williams assigned Tom, his best technician, to Alec, and thus Hamilton lost his chance for fame and fortune. With Tom's help, Alec's ideas finally bore fruit a year later. Along with Alec's venture capitalist, their's was to become yet another story about two guys in a garage

And, as Paul Harvey would say, now you know the rest of the story.

## Summer Reading

I have several books I want to mention, but only room for one. The one will be a great little book, *Personal Robotics: Real robots to construct, program, and explore the*



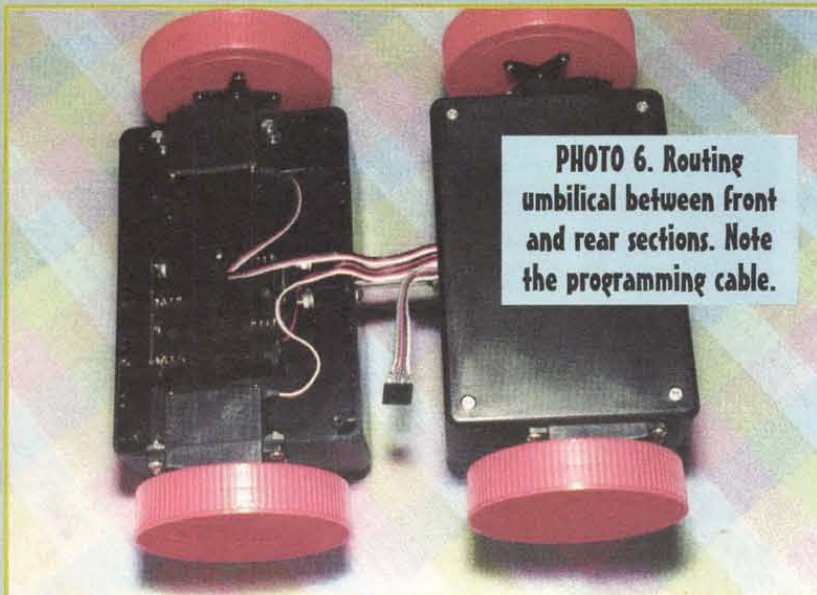

**PHOTO 6. Routing umbilical between front and rear sections. Note the programming cable.**

he gives reviews of beginner, intermediate, and advanced robotic kits available on the market.

Raucci talks about Capsela, LEGO MindStorms, Learning Curve's Robotix, among others in the beginner's realm, the offerings of BEAM Robotics, OWI Elekits, Robix, FisherTechnik, and Rug Warrior Pro in the intermediate range, and the Pioneer series of robots marketed by ActivMedia for the advanced range.

I was prepared not to like this book because I have a low opinion of a couple of the kits Raucci discusses, but I came away favorably impressed.

Raucci is quite up front with the capabilities and limitations of the various kits he covers. I

would have liked to see a few more advanced robot systems, and there was no coverage at all of legged robot systems. Still, Raucci won me over.

A nice touch is his thought-provoking introduction to robotics in Chapter One. This pointed me toward the short story "The Artist of the Beautiful" (also known as "The Mechanical Butterfly") written in 1844 by Nathaniel Hawthorne. For all the flowery 19th century prose, this story is well worth downloading. In it, you'll meet Owen Warland, who is a watchmaker — and builder of robot butterflies!

The dream has indeed been around a long, long time. You can find the story in the Hawthorne anthology *Mosses From an Old Manse* as a free e-text at the Project Gutenberg website ([www.gutenberg.org](http://www.gutenberg.org)). Enjoy.


Next time: more Jiffy & coverage of High GEAR (wherein Jiffy goes camping & gets muddy). **NV**

world by Richard Raucci (AK Peters, Natick, MA, 1999, ISBN 1-56881-

089-X). The author of this book doesn't tell you how to build robots,

with the capabilities and limitations of the various kits he covers. I

**FIGURE 1: JIFFY SCHEMATIC**

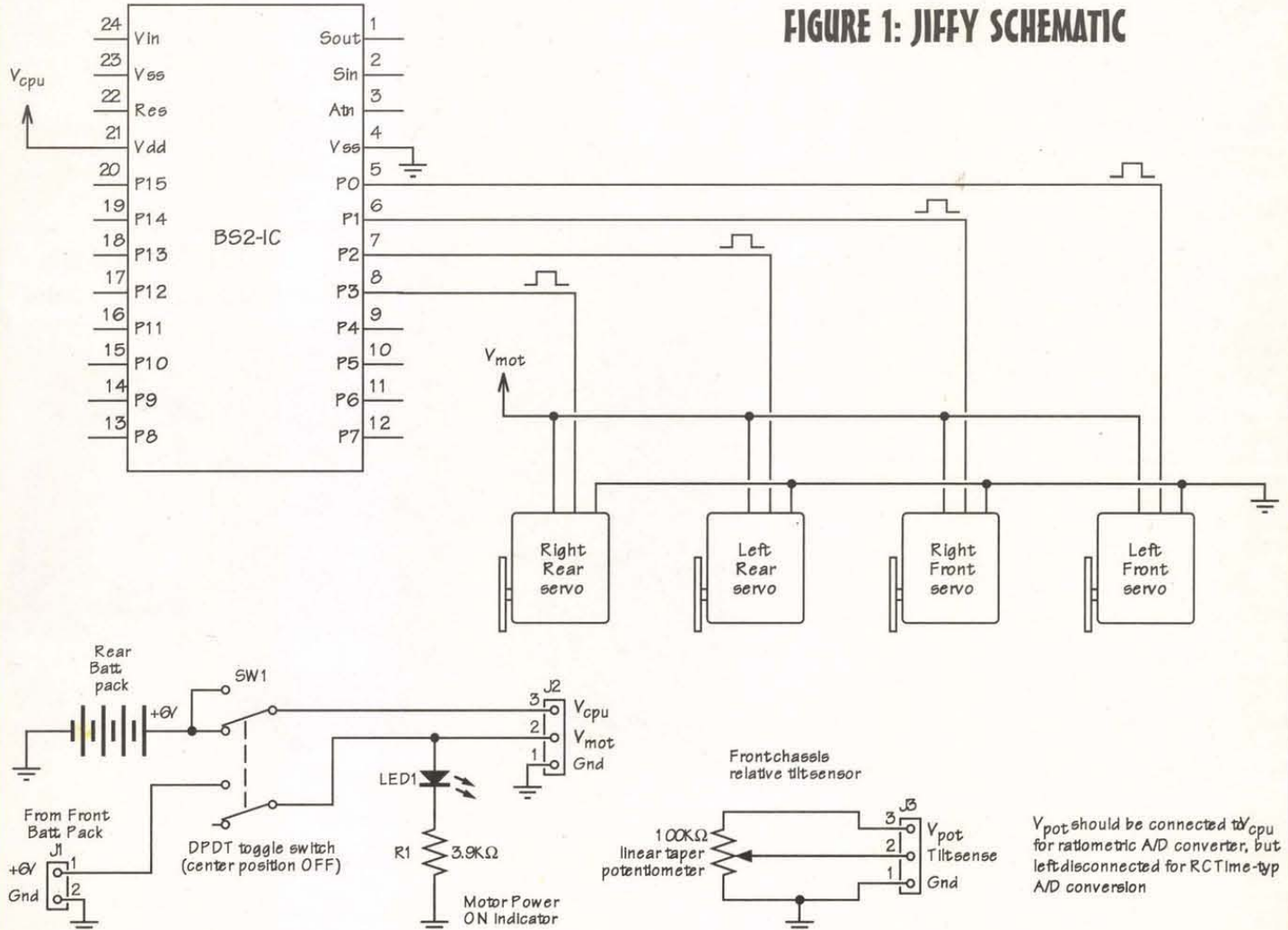



We accept Visa,  
Mastercard, AmEx,  
and Discover

# Attention: Nerds-Geeks

Fax: 318-424-9771

To Order Call 1-800-227-3971 [www.shrevesystems.com](http://www.shrevesystems.com)

## Parts for your Vintage Mac!



**Peltier Junction**  
with heat sink, works on 5V & 12V  
1 3/16" x 1 3/16"

**\$10 each or 3 for \$25**



**Global Village Gold**  
Internal Modem  
14.4 Com Slot **ONLY \$1**



**Global Village Bronze**  
External Modem  
2400 Bps/9600 Fax **ONLY \$1**

## MONITOR BLOWOUT!

19"-21" fixed res 1024 X 768  
**ONLY....\$49** as is



H.P. 17" fixed res 832 X 724  
**ONLY....\$99** 30 Day  
Warranty



13"-14" fixed res 640 X 480  
**ONLY....\$25** as is



H.P. 17" fixed res 640 X 480  
**ONLY....\$99** 30 Day  
Warranty



15" Radius Pivot  
**ONLY....\$25** as is



16" Rasterops fixed 832 X 624  
**ONLY....\$99** 30 Day  
Warranty



**\$5**

**LC Power Supply**  
+5V, -5V, +12V Output

**MacAlly ADB Keyboard**



**\$19**



**Apple IIE Logic  
Board  
\$19**




**Apple Color  
Composite Display**  
Great for Surveillance  
Refurbished **\$69**



**PAS16 Audio CMS Tower SCSI Case**  
**Spectrum** Holds 4 5.25 full height drives  
16 Bit Sound Editing Card **ONLY \$19**



**\$79**

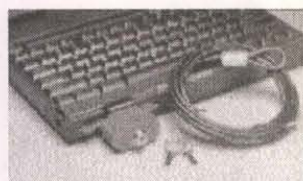

**Drive Lock Security System** for  
Portable Computers-protects your  
data if lost or stolen!

**ONLY.....\$5**



**\$19**

**Curtis ADB Track Ball**



**Apple  
Remote  
Control  
\$5 EACH**



**PDA Genuine  
Leather Carry  
Case**  
Let your palm  
pilot lead the life  
of luxury!

**\$5**



**Membrane  
Track Pad for  
laptop \$2**

### RAM

1 MB 30 Pin 4 For \$1  
4 MB 72 Pin 2 For \$5

**Apple II 256K Memory  
Expansion Kit**  
HM51256P-10 **ONLY \$1**

### Miscellaneous

Apple 8 bit Video Card	\$19
LaserWriter IINT	\$199
Apple ADB Keyboard	\$19
1.44 Super Drive	\$49
Clone ADB MouseII	\$19
Quicktake 100 Camera	\$99
Bernoulli 90 MB EXT	\$10
44MB SyQuest Ext	\$10
88MB SyQuest Ext	\$19

**Be sure to check us out on the web at  
<http://www.shrevesystems.com> for the best  
prices on Vintage Mac gear!**

**\$25 minimum  
order**

**Shreve Systems**  
1200 Marshall st  
Shreveport, La 71101

Returns subject to a 15% restocking fee.  
Prices are subject to change without notice. We accept Visa,  
Mastercard, AmEx, Discover



# Newsbytes

## TDK BRINGS NEW VELOCITY TO CD BURNERS WITH THE NEWEST VELOCD REWRITER

**R**ip, Rock and Roll performance helped make TDK's first veloCD™ burner a runaway success with music-passionate PC users. Now, TDK takes performance to the next level with a new veloCD burner that boasts the world's fastest writing (12X), rewriting (10X), and audio ripping (24X) speeds. TDK adds to this the power of fail-safe write assurance technology, which eliminates buffer underrun errors to create the world's first multitasking-compatible CD burner.

The new veloCD burner offers bit-perfect 24X digital audio ripping. Ripping or digital audio extraction is the necessary first step in all CD recording operations. Ripping with a typical CD-ROM or DVD-ROM drive is often slow and inaccurate, sometimes yielding audible clicks and pops in the CD copy. With 24X ripping and 12X writing, the new TDK veloCD burner offers a one-drive alternative for CD-to-CD-R recording that's better sounding and takes less than half the time of most two-drive setups.

### No More CD Coasters

Also key to the superior reliability of the new veloCD burner is the inclusion of BURN-Proof™ write assurance technology, which eliminates buffer underrun errors. These errors — which are fatal to the writing process — result from momentary interruptions in the data flowing to the write laser. They typically occur when the user tries to perform another task during the writing process or when the source cannot supply data fast enough to the writer.

To prevent buffer underrun errors, the veloCD continuously monitors the status of its built-in buffer memory. When a buffer underrun error is about to occur, the veloCD suspends recording until the buffer is re-filled. To continue recording at the appropriate place, the veloCD drive compares the recorded data with the data in its buffer and synchronizes adjacent frames. With this technique, the drive restarts recording at exactly the precise position where recording was originally suspended ... no more failed sessions ... no more CD coasters.

### The Fastest CD ReWriting

CD rewriting is becoming an important tool for day-to-day data backups. A dramatic advance over conventional CD rewriters, which typically max out at 4X, the new veloCD burner is capable of 10X rewriting with the convenience of drag-and-drop recording.

To achieve full 10X rewriting speed, it's necessary to use a new generation of TDK CD-RW discs. Easily identified by their high-speed logo, the new TDK CD-RW discs use a specially formulated phase-change material to achieve the ideal combination of high sensitivity and long-term data stability. Like conventional CD-RW media, the new high-speed discs can be recorded and rewritten more than a thousand times with no loss in data accuracy and reliability.

The new veloCD burner is about 40% faster and has more than three times the storage capacity of a ZIP disc and is the ideal medium for larger multimedia file backups.

### Ultimate Music Management and Recording Software

Designed as an all-in-one solution for CD music and multimedia recording, the new veloCD burner comes complete with music management and recording software.

**Digital Mixmaster** gives users a convenient jukebox interface, easily customizable with a broad range of colorful graphic "skins." It handles day-to-day music management

and recording functions including CD playback, ripping, MP3 playback, Internet-accessed track labeling, and CD recording (including on-the-fly conversion of MP3 music files and playlists into play-anywhere CDs).

Also included with the new veloCD internal ATAPI/EIDE burner is **Nero 5.0** multimedia recording software. Nero makes it easy to copy virtually every type of CD-ROM and CD-Audio disc, including multisession discs and several new hybrid formats. Nero can even control two veloCD burners simultaneously, making it easy for corporate users to convert their desktop PCs into a flexible duplication station.

TDK's 12X/10X/32X internal ATAPI/EIDE veloCD burner will be available this August at a suggested retail price of \$349.00.

*BURN-Proof is a registered trademark of Sanyo Electric Co., Ltd. (Japan).*

\*\*\*\*\*

## RECORD RADIO SHOWS ON YOUR PC ... WITH CYBERCORDER 2000

**S**kyhawk Technologies announces the availability of Cybercorder 2000, a program that lets users record radio shows or any sound input on the PC hard disk drive.

Cybercorder 2000 allows you to use your PC like a VCR to schedule audio recordings. Simply connect the output jack(s) of the audio source to the input jack of your sound card, adjust the Windows mixer, and you are all set to record. Cybercorder 2000 lets you record with any of the audio compression formats, sampling rates, and frequencies available on your system to save disk space. Recordings are saved on disk as standard .wav files.

You can play back a recording by selecting one from the list of completed recordings. You can easily advance a recording forward and reverse by various step sizes using the customizable playback window. You no longer have to miss your favorite radio shows with Cybercorder 2000.

Cybercorder 2000 costs \$19.95 for a single-user license. Site licenses are available. For more information, visit the Skyhawk Technologies web site at:

[skyhawktech.com](http://skyhawktech.com) or write to:

**Skyhawk Technologies**

3166 Neptune Drive, Riverside, CA 92503

Voice: (909) 688-8923 Fax: (909) 637-0296

Email: [info@skyhawktech.com](mailto:info@skyhawktech.com)

\*\*\*\*\*

## iTestApps.com UNITES SOFTWARE DEVELOPERS AND BETA TESTERS

**F**ineware Systems announces the launch of iTestApps.com, a web site and newsletter that bring together companies looking for beta testers for their software, and individuals interested in participating in beta testing projects.

Beta testing is a crucial phase of the software development cycle that allows a pre-release version of a new program to be tested under real-life conditions by potential users. Until now, it has been a challenge for software developers to find a team of qualified testers with the proper mix of computer skills, hardware, and operating systems to ensure that their new programs have been tested in a wide variety of environments.

For a \$300.00 listing fee, iTestApps.com helps companies locate qualified beta testing volunteers. iTestApps will include a description of the company's beta testing needs in six issues of the twice-monthly iTestApps newsletter which

Published Monthly By  
**T & L Publications, Inc.**  
430 Princland Court  
Corona, CA 92879-1300  
(909) 371-8497  
FAX (909) 371-3052

E-Mail — [editor@nutsvolts.com](mailto:editor@nutsvolts.com)  
URL — <http://www.nutsvolts.com>

Subscription  
Order ONLY Line  
1-800-783-4624

PUBLISHER  
Jack Lemieux N6ZTD

EDITOR  
Larry Lemieux KD6UWV  
MANAGING EDITOR  
Robin Lemieux KD6UWS

CONTRIBUTORS  
Robert Nansel  
Joe Carr  
Jon Williams  
Ray Marston  
TJ Byers  
Gordon West  
Fred Blechman  
David McDonald  
Don Powrie  
Karl Lunt  
Tim Deagan  
Ken Coffman  
ML Shannon

ON-THE-ROAD EXHIBIT  
COORDINATOR  
Audrey Lemieux N6VXW

SUBSCRIPTIONS  
Abby Madain

CLASSIFIED ADS  
Natalie Sigafus

DISPLAY ADS  
Mary Gamar

Copyright 2000 by  
**T & L Publications, Inc.**  
All Rights Reserved

All advertising is subject to publisher's approval. We are not responsible for mistakes, misprints, or typographical errors. Nuts & Volts Magazine assumes no responsibility for the availability or condition of advertised items or for the honesty of the advertiser. The publisher makes no claims for the legality of any item advertised in Nuts & Volts. This is the sole responsibility of the advertiser. Advertisers and their agencies agree to indemnify and protect the publisher from any and all claims, action, or expense arising from advertising placed in Nuts & Volts. Please send all subscription orders, correspondence, UPS, overnight mail, and artwork to: 430 Princland Court, Corona, CA 92879.



is sent to end-users seeking beta testing opportunities. In addition, the company receives four insertions of its New Product Announcement in the newsletter, once the beta testing has been completed, and the new software released.

iTestApps gives beta testers a chance to look at new software, with leading-edge programming interfaces and techniques, months before it will be available to the general public. The iTestApps newsletter is free for anybody who would like to consider becoming a beta tester. Beta testers are invariably rewarded with free copies of the final programs when they are released.

The iTestApps newsletter listing costs \$300.00 for commercial software developers, less for shareware and freeware developers, and multi-use discounts are available. For more information, including online FAQs for both companies looking for testers and individuals who want to become testers, visit [www.iTestApps.com](http://www.iTestApps.com), or contact iTestApps' parent company:

#### Fineware Systems

P.O. Box 75776, Oklahoma City, OK 73147

Phone: (405) 943-4533

Fax: (405) 942-7819

Email: [fineware@fineware.com](mailto:fineware@fineware.com)

\*\*\*\*\*

## RECORD YOUR PHONECALLS TO HARD DISK ... FREE ... WITH VERITAPE

**B**lue Starfish Ltd. has released Veritape 1.3, a Windows 98/95 program that lets you record your telephone calls straight to your hard disk — all you need is a PC, a voice modem, and Veritape, and it's free!

Once Veritape is installed, you just click Record and talk as normal. No special telephone or other equipment is required. Store your important business negotiations, create a permanent record of your voicemail messages, tape family news so you can play it to others. You no longer need to make notes while trying to pay attention to the call, and you'll avoid the embarrassment of forgetting what you were told (or even what you said!). Veritape stores your calls digitally, with a description to allow you to find them again easily. You can play back your calls at any time, or email them to a friend or colleague.

Veritape is free for personal use, but organizations are required to buy Veritape if they install two or more copies. Veritape can be downloaded from [www.veritape.com](http://www.veritape.com).

Organizations or individuals who buy Veritape (it costs US \$30.00), can remove the advertising within the program, and use two bonus features: Veritape will compress calls into your choice of format, and can automatically email them. In addition, registered users receive priority support and free upgrades for a year.

For further information, see the Veritape website [www.veritape.com](http://www.veritape.com), or email [info@veritape.com](mailto:info@veritape.com). (The site also covers the legal implications of recording calls.) For information on multi-copy licences contact [sales@veritape.com](mailto:sales@veritape.com) or mail:

#### Blue Starfish Ltd.

Alkington Hall West, Alkington, Manchester,  
M24 1WD, UK

# reader FeedBack

## Superbot 2.1

In your April 2000 (Vol. 21 No. 4) issue you advertise Superbot 2.1 software for Website downloads (Page 21). I downloaded the software to give it a try (URL has changed to <http://www.sparkleware.com/index.html>). The software is a "mole." It appears to grab personal data from your PC and upload it to (?). As soon as the software sees an open internet connection, your PC's hard drive and modem go to town ... without advising the user what it is doing.

This is unethical development in the least and you should consider action against the company that posted the article, before it reflects poorly on N & V.

**Anonymous  
via Internet**

#### Response:

*This accusation has absolutely no basis in fact. SuperBot version 2.1 does not, and never did, upload any personal data from your computer to any location.*

*The current version of SuperBot, v2.3 beta, incorporates third-party technology to display advertisements in the program. This tool prompts users of SuperBot for some basic information, such as age and gender, and this information is used to determine which types of advertisements are shown. Although we did not design this technology, we are familiar with its mode of operation, and we have absolutely no reason to suspect that any covert transmission of any personal information is taking place.*

*I cannot even guess why anyone would spread such a rumor, except perhaps to damage SuperBot's reputation as the world's best offline browser.*

*(I believe a similar smear campaign was recently conducted against a product named GoZilla.) If you would like more information on the SuperBot v2.3 advertising module, please see the Cydoor Technologies website at <http://www.cydoor.com>.*

*Again, SuperBot v2.1 NEVER uploaded ANY DATA of ANY KIND to ANY LOCATION.*

**Chris Marshall  
EliteSys**

## Telephone Busy Light

I am happy to see all the feedback on the Telephone Busy Light and its subsequent letters, and I must own up to the errors pointed out by Mr. Stiles. My letter quoted a minimum 10 megohm DC resistance, a figure I retrieved from my 1977 photocopy of the Part 68 regulations (47 CFR 68). Ten megohms is the old value; the FCC has relaxed the requirement to 5 megohms. This DC resistance must be met for all potentials less than 100 volts. The 1977 FCC rules also included the DC resistance in the definition of REN, but the modern rules do not, so Mr. Stiles is again correct. I should have used the current regulations. The old specification was the basis for my large RENs.

CFR stands for the Code of Federal Regulations, and title 47 is the FCC rules. Your local library should have a copy in its reference section, or you can view it on the web at many sites. The FCC has a quick search at [www.fcc.gov/mmb/asd/bickel/47CFRrule.html](http://www.fcc.gov/mmb/asd/bickel/47CFRrule.html); the GPO maintains [www.access.gpo.gov/nara/cfr/index.html](http://www.access.gpo.gov/nara/cfr/index.html). I encourage everyone to go to the source.

Mr. Harkey's circuit presents a 4.7M DC resistance (if the diodes have no leakage current), so it fails the 5M requirement. The resistors should be larger. From an engineering standpoint, we must include the diode leakage current and make sure the total current at 100V is less than 20 microamps, but a single 1N400x rectifier may leak 10 microamps. It may be better (and cheaper) to move the series resistors to the other side of the rectifiers and use signal diodes. In any event, tip and ring should have series limiting resistors with 400V ratings to withstand line surges.

Maybe a line surge shorted out Mr. Stiles' RadioShack 43-443, but his comments raise another issue about that unit. Mr. Stiles said that it draws 1.9 to 3mA from the phone line when it is off hook. If several units are on one phone line, do they refuse to release the line after a call? Do they get dim? One of my phones has a self-powered busy light, but it flashes at a very low duty cycle, and its current draw should be much less than 1mA.

**Gerald Roylance  
Mountain View, CA**

*Continued on page 81*

**www.nutsvolts.com**

### Professional 10 HOUR RECORDER

"BUILT LIKE A BATTLESHIP"

- Heavy duty commercial recorder - NOT improvised from consumer models
- 12, 14, and 16 hour models also available
- BUILT-IN voice activation (add \$30)
- Applications information included
- Dimensions: 11.5 x 7.0 x 2.75"

**SPECIAL Nutsvolts Price..**

**\$159**

**FREE 40-PAGE SPECIAL EQUIPMENT CATALOG!**

COD's OK. Sorry, no credit cards. Free catalog USA only; other countries \$5. Price includes UPS to 48 States on Pre-Paid Orders

**Viking Systems International** 100 North Hill Drive #42, Brisbane, CA 94005  
Phone (415) 467-1220 • Fax: (415) 467-1221 • Web: [vikingsysintl@aol.com](mailto:vikingsysintl@aol.com)

Write in 120 on Reader Service Card.

Nuts & Volts Magazine/AUGUST 2000 13



# Open Channel

## VLF Radio

In past editions of this column, I have written about ELF, VLF, and LF radio in conjunction with RadioScience Observing. That is, the observation of radio phenomena in the ELF, VLF, and LF portion of the radio spectrum (5 KHz to 500 KHz). This month, I want to spend a little more time on the topic.

### What Are ELF, VLF, and LF?

The ELF, VLF, and LF portion of the radio spectrum are those frequencies between 5 KHz and 500 KHz. In general, about 5 to 20 KHz are considered ELF ("extremely low frequency"), 20 to 100 KHz are considered VLF ("very low frequency"), and the rest of the spectrum (100 to 500 KHz) are considered LF ("low frequency").

The Europeans have been using LF bands for AM broadcasting for years. These stations are found on 145 to 285 KHz. A notable station, often audible in the USA, is Radio 252 on 252 KHz. It runs about a 1,000,000 watts. In the middle of winter, especially, these stations are often audible in the USA and Canada. The Europeans call these frequencies "long wave."

The VLF and LF portions of the spectrum are also home to US Navy communications, WWVB (the National Institute of Standards and Technology radio station at Fort Collins, CO) on 60 KHz, and between 160 and 190 KHz a group of people called LowFers. These stations operate under Part-15 of the FCC Rules and Regulations, and are limited to 1 watt of RF power and an antenna length of 15 meters. They have demonstrated some amazing ranges given the limitations they work under.

Beginning at about 200 KHz, and continuing up to 420 KHz, are a number of Non-Directional Beacons (NDB). They are located near airports to aid navigation using airborne direction-finding equipment. NDBs tend to run about 200 watts of RF power into a simple Marconi antenna, with some coastal stations running 2.5 kW to reach further out to sea.

The frequencies in the ELF and VLF region are peculiar, especially the lower frequencies (5 to 30 KHz). These frequencies are often used for detecting solar flares and sudden

ionospheric disturbances (SIDs). It seems that the level of distant stations goes up, not down, during a SID event. The same SID event that will wipe out the short-wave spectrum will enhance the ELF/VLF signal.

It does this neat trick by ionizing the ionosphere down through the D-layer. Because these frequencies have very long wavelengths,

the distance between the bottom of the D-layer and the earth's surface form a waveguide. This is the reason why the ELF/VLF signal strengths increase ... waveguides are very good conveyers of electromagnetic energy!

The wavelengths of ELF, VLF, and LF stations are amazingly long. For example, at 10 KHz, the wavelength is about 18 miles long. At 76 KHz, it is about 2.46 miles, and at 137 KHz (the site of a future amateur radio allocation), it is 1.3 miles. A quarter wavelength vertical on 137 KHz would be 1,800 feet long!


The Longwave Wireless Club of America (<http://www.lwca.org>) is active in ELF, VLF, and LF Dxing and their magazine - *The Lowfer* - is obligatory for anyone doing any

firmed two-way LF transatlantic QSO on the 136 KHz amateur radio frequency allocation. The contact must be between a station on the North American continent (Canada or USA), and Europe (defined as continental Europe, Great Britain, Northern Ireland, and the Republic of Ireland). Here are the details:

1. An award will be granted to the first USA station and the first Canadian station (two awards) to receive a European 136 KHz station.
2. An award will be granted to the first European amateur station to receive either a USA or Canadian 136 KHz station.
3. The Challenge involves a pair of trophies for the first two-way Europe-USA 136-KHz contact (once the band is allocated to amateurs by the FCC).
4. A pair of trophies will be awarded for the first Europe-Canadian 136 KHz contact.
5. Prior to the award of the trophies, certificates will be awarded to the pair of amateur radio stations who currently hold the distance record for two-way QSOs on 136 KHz.

The certificates will be awarded for the distance record will be presented at the Friedrichshafen Ham Radio event and at the RSGB International HF & IOTA

Figure 2

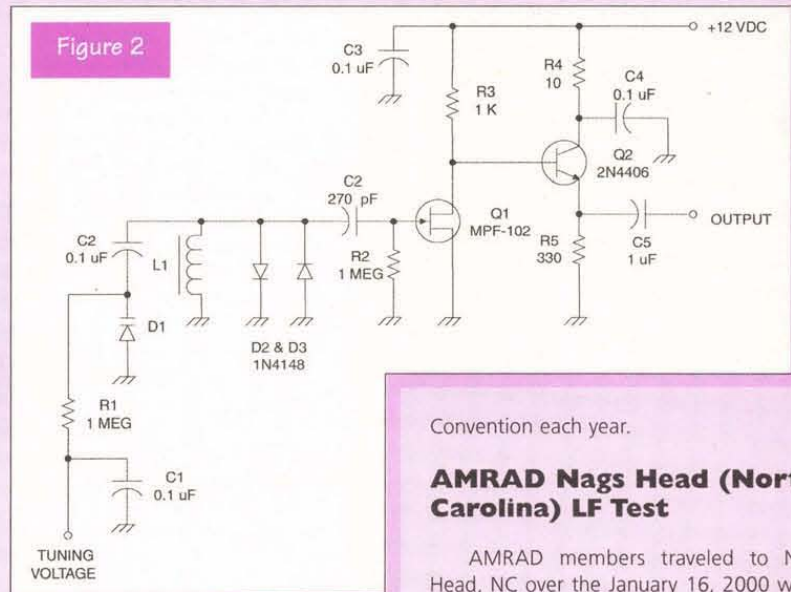

Convention each year.


### AMRAD Nags Head (North Carolina) LF Test

AMRAD members traveled to Nags Head, NC over the January 16, 2000 weekend to try some new and improved equipment on LF bands. The Nags Head site was chosen for a number of reasons. For one thing, it is almost free of the power line noise that afflicts these wavelengths at other locations in the country. Second, European signals arrive across the Atlantic Ocean. Even a short distance over land severely attenuates such signals, so they tend to be down in the mud.

### ELF, VLF, and LF Preamplifiers

There are a number of shortwave receivers on the market that go down to 100 KHz, 50 KHz, or even 25 KHz in one case. The rub is that they tend to be less sensitive on these lower frequencies than they are on

Figure 1

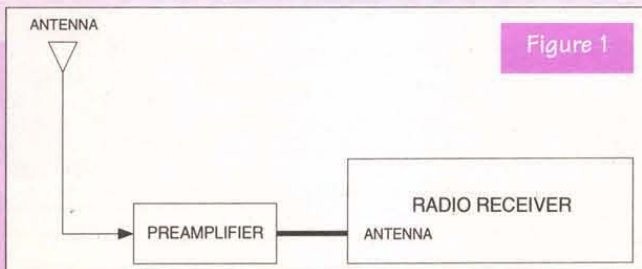

work in the region.

### LF Transatlantic Challenge

The LF Transatlantic Challenge is provided by the Amateur Radio Research and Development club (AMRAD, <http://www.amrad.org>), and is in honor of the late Peter Bobek (DJ8WL/DAOLF) in honor of his work on 160 meters and 137 KHz. The challenge is actually collectively sponsored by Deutsche Amateur Radio Club (DARC), AMRAD, and the Radio Society of Great Britain.

Two pairs of trophies will be awarded, one for each pair of amateur radio stations who make the first con-



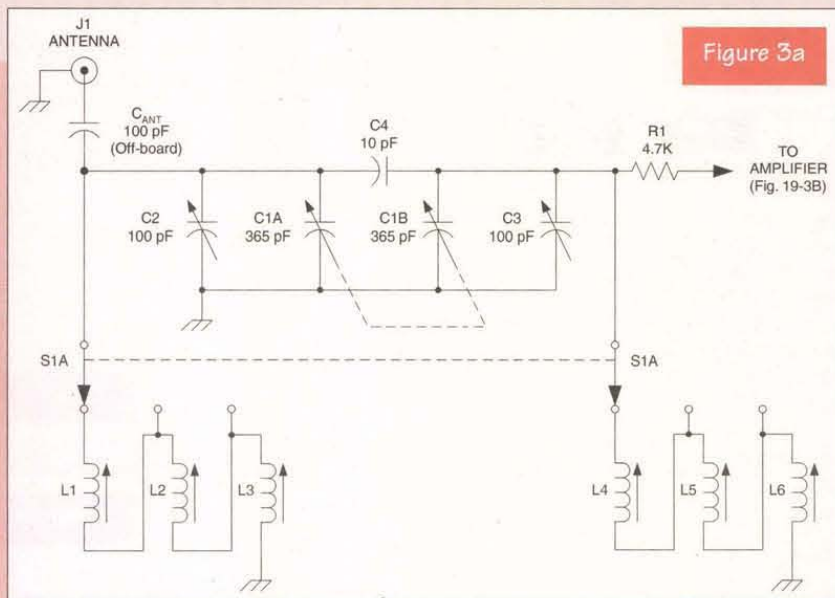


Figure 3a

## Preamplifiers

Figure 2 shows the circuit for a simple cascade preamplifier consisting of an MPF-102 JFET and a 2N4406 bipolar NPN transistor. The voltage gain is about 3.3 at frequencies of 136 KHz to 250 KHz (the power gain is much larger). For this frequency range, use a 4.7 mH iron core coil for L1, and an NTE-618 varactor for D1 (the NTE-618 is available through replacement parts dealers, and has a capacitance of 440 pF at one volt, and 90 pF at eight volts DC).

Figure 3 shows a three-band VLF preselector and preamplifier for use ahead of a receiver (i.e., between the antenna and the receiver antenna terminals).

The circuit of Figure 3 has two major sections: preselector (Figure 3A) tuning and amplification (Figure 3B). The preselector tuning consists of a dual-section, reactance-coupled parallel L-C tuning network. The main tuning capacitor (C1A, C1B) is a two-section ("dual") AM broadcast variable.

Most of those capacitors are 365 pF per section (be careful, some models have an oscillator section that is less than 365 pF per section ... you want a dual 365 pF unit). Also useful are dual 380 pF, 400 pF, 440 pF, or 500 pF capacitors, all of which I've seen in recent catalogs.

The main tuning capacitor sections are trimmed by small variable capacitors (C2 and C3). For this particular project, I selected the Sprague-Goodman 10-mm type. These capacitors are designed for top adjustment, so are good for cases where the printed circuit board is mounted inside of a cabinet (the recommended approach).

The three inductors in each side of the tuning network (L1/L2/L3 and L4/L5/L6) are switch selected. The switch is a 2P3T rotary switch, i.e., it has two poles and three positions. These are a little hard to find in some stores, but the 3P3T are much easier, and will work well (just ignore the third set of contacts). The inductors are arranged so that in position "A," all three are connected in series; in position "B," two are connected in series; and in position "C," only one coil on each side (L3 and L6) is connected into the circuit. The values for these coils are:

COIL	VALUE	NUMBER
L1/L4	56 mH	TK-1721
L2/L5	56 mH	TK-1721
L3/L6	33 mH	TK-1724

The two halves of the L-C tuned circuit are coupled by a small mutual reactance. Although either capacitive or inductive reactance can be used for this purpose (although in different ways), the method used in Figure 3 is the capacitive version. Capacitor C4 is used to couple energy from one side of the L-C tank circuit to the other. A 10-pF disk ceramic or silvered mica unit will suffice. The idea is to get as small a value that will couple the two sides without allowing too much interaction. Some people prefer to use a small (<12 pF) variable capacitor in place of C4.

The tuning ranges with the coils shown were measured for the various positions of S1 as follows:

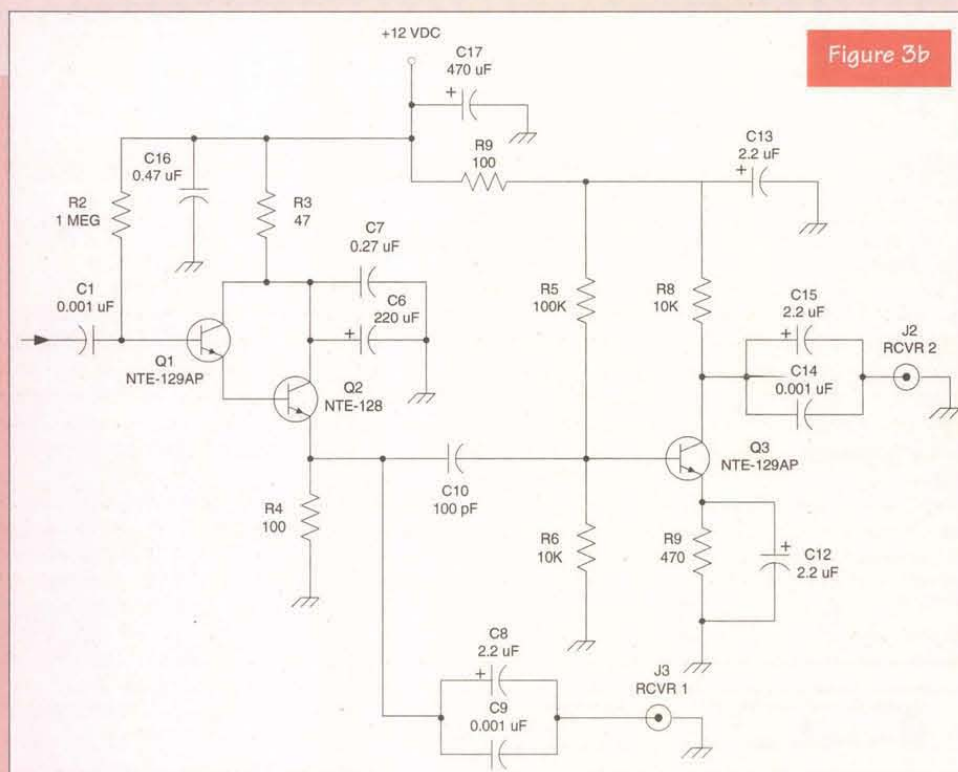


Figure 3b

the shortwave bands. In fact, they are considerably less sensitive in the VLF/LF portion of the spectrum than they are on the shortwave bands. Thus, it behooves the radioscientist observer to plug in a preamplifier before the circuit to try and get that sensitivity up.

But before we tackle the subject of VLF preamplifiers, let's consider a little bit about preamplifiers in general. Figure 1 shows the placement of a preamplifier or preselector ahead of a radio receiver. The preamplifier is connected in the line between the antenna and the antenna input of the receiver. But it is not as simple as all that ... there

are tigers in them thar woods!

The simple fact is that the preamplifier should not deteriorate the receiver's third-order intercept point (TOIP) and dynamic range in order to achieve its benefits. In addition, the Friis noise equation tells us that the preamplifier should have a lower noise figure than the radio receiver. This is because the noise figure of the first stage absolutely dominates the noise performance of the entire system, and the preamplifier becomes the first stage. If the criteria of no deterioration of either TOIP or dynamic range, and low noise, are met, then you are ready for a preamplifier.



## 2 Great Books by Joseph Carr



### SECRETS OF RF CIRCUIT DESIGN

From one of today's most respected electronics authors comes this pragmatic,

intermediate-level guide to designing, building, and testing all types of radio frequency circuits. Filled with functional projects that demonstrate the principles of RF circuits, this revision of a bestseller also provides a handy parts list and sources of components.

### PRACTICAL ANTENNA HANDBOOK



The most popular book on antennas ever written, widely known as "the antenna builder's bible."

This Third Edition is a work for anyone with an interest in antennas, from the newest of novices to the most experienced engineer. This empowering book gives you all kinds of projects and material that explains why what you did works.

As a paid subscriber to  
**Nuts & Volts**, you'll receive  
**10% off the list price!!**

(See ad on page 4 for ordering details and other titles currently available.)

## Open Channel VLF Radio

A	20.8-36 KHz
B	25.2-44.4 KHz
C	39.1-70.8 KHz

You can alter the frequency range by selecting different coils from the same series in the Digi-Key catalog, or from some other source (including winding your own, if you are so inclined). Keep in mind that the frequencies are approximate and will differ from the frequencies found from the equation (on your calculator) because of two reasons: First, the inductances have a tolerance associated with them; and second, the inductors have significant capaci-

tance. The values will be within 15 percent or less, but if the frequency that you desire is close to the margin for some particular coil, then be prepared to use a different coil. If you choose to build the circuit for a different set of frequencies, then follow this rule of thumb: the frequency change is proportional to the square root of the inductance change.

The signal from the tuned circuit is coupled into a two-stage amplifier (Figure 3B) consisting of three transistors (Q1, Q2, and Q3). Transistors Q1 and Q2 are connected into the Darlington amplifier configuration, so offer a very high input impedance. This stage produces some power gain, but little voltage gain.

If it were a common emitter circuit, rather than a common collector circuit, the gain would be huge (i.e., the product of the betas of Q1 and Q2). Because Q1/Q2 is an emitter follower (common collector) ampli-

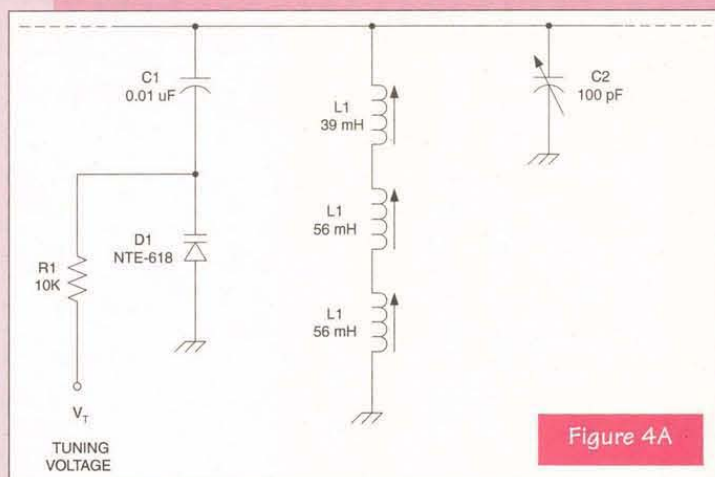


Figure 4A

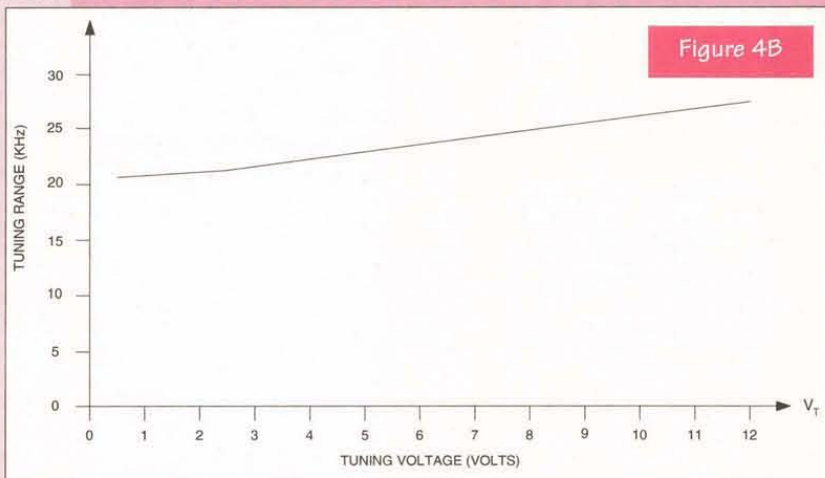


Figure 4B

er, the signal is taken from the emitter of Q2 and fed to two destinations: a low gain output (OUT1) and the input of the final amplifier stage (Q1).


The circuit of Q1 is a common emitter amplifier. It uses the standard voltage divider form of biasing, with an emitter resistor to stabilize the circuit. The output of this amplifier is taken from the collector, and fed to the high gain output (OUT2).

The transistors selected for this project are the NTE-128 and NTE-129AP (also, the ECG-128 and ECG-129AP will work, as well). These parts are available from many parts distributors. Neither transistor is particularly critical, however. Q1 and Q2 were replaced with 2N4401 in one version, and worked the same as the selected transistors. Transistor Q2 can be any "audio output/video driver" NPN silicon device with a gain-bandwidth product of 100 MHz, and a beta gain around 90.

The power distribution network takes the +12 VDC power supply, and sends it to the two stages. In both stages, there is a small value resistor (R3 and R9) used to improve decoupling between stages. The actual decoupling is performed by capacitor pairs C6/C7, C11/C13, and C16/C17. In each case, a pair of capacitors — one low value and one a high value electrolytic — is used.

The high value capacitors are used to smooth power supply variations and reduce any power supply noise, as well as decoupling low frequency feedback through the DC

## Order Today!

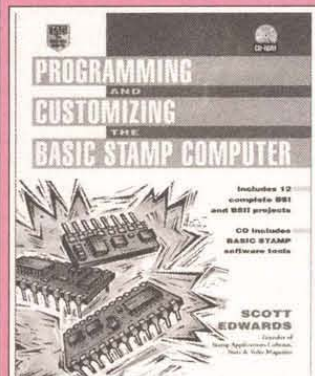

### "PROGRAMMING AND CUSTOMIZING THE BASIC STAMP COMPUTER" by Scott Edwards

Build smart electronics projects with the inexpensive, simple-to-use, surprisingly powerful BASIC Stamp.

**ONLY \$34.95**

As a paid subscriber to  
**Nuts & Volts**, you'll receive  
**10% off the list price!!**

(See ad on page 4 for ordering details and other titles currently available.)

### Mr. NiCd

### AUGUST 2000 SUPER SPECIALS!

### THE BEST BATTERIES IN AMERICA!

Packs & Charger for YAESU FT-50R / 40R / 10R:

FNB-40xh (5w NiMH)	7.2v	650mAh	\$41.95
FNB-47xh (5w NiMH)	7.2v	1800mAh	\$49.95
FNB-41xh (5w NiMH)	9.6v	1000mAh	\$49.95

For YAESU FT-51R / 41R / 11R:

FNB-38 pack (5w)	9.6v	700mAh	\$39.95
------------------	------	--------	---------

For YAESU FT-530 / 416 / 816 / 76 / 26:

FNB-26 pack (NiMH)	7.2v	1500mAh	\$32.95
FNB-27s (5w NiMH)	12.0v	1000mAh	\$45.95

For YAESU FT-411 / 470 / 73 / 33 / 23:

FNB-11 pack (5w)	12.0v	600mAh	\$24.95
FBA-10 6-Cell AA case			\$14.95

Packs for ALINCO DJ-580 / 582 / 180 radios:

EBP-20ns pack	7.2v	1500mAh	\$29.95
EBP-22nh pk (5w)	12.0v	1000mAh	\$36.95
EDH-11 6-Cell AA case			\$14.95

For ICOM IC-21A / T22-42A / W31-32A / T7A:

BP-180xh pk (NiMH)	7.2v	1000mAh	\$39.95
BP-173 pack (5w)	9.6v	700mAh	\$49.95

For ICOM IC-W21A / 2GXA / V21AT (Black or Grey):

BP-132s (5w NiMH)	12.0v	1500mAh	\$49.95
-------------------	-------	---------	---------

For ICOM IC-2SAT / W2A / 3SAT / 4SAT etc:

BP-83 pack	7.2v	600mAh	\$23.95
For ICOM 02AT etc & Radio Shack HTX-202 / 404:			

BP-8h pack 8.4v 1400mAh \$32.95

BP-202S pack (HTX-202) 7.2v 1400mAh \$29.95

For KENWOOD TH-79A / 42A / 22A:

PB-32xh pack (NiMH) 6.0v 1000mAh \$29.95

PB-34xh pack (5w NiMH) 9.6v 1000mAh \$39.95

For KENWOOD TH-78 / 48 / 28 / 27:

PB-13 (original size) 7.2v 700mAh \$26.95

For KENWOOD TH-77, 75, 55, 46, 45, 26, 25:

PB-6x (NiMH, with plug) 7.2v 1200mAh \$34.95

Mail, phone, & Fax orders welcome! Pay with

Mastercard / VISA / DISCOVER / American Express

Call 608-831-3443 / Fax 608-831-1082

Mr. NiCd - E. H. Yost & Company

2211-D Parview Road, Middleton, WI 53562

CALL OR WRITE FOR OUR FREE CATALOG!

Cellular / Laptop / Videocam / Commercial & Aviation packs too!

E-mail: ehyst@midplains.net



power supply. The low value capacitors are used for high frequency decoupling.

Alignment of the circuit is relatively straightforward, although it requires a signal generator. The signal generator could be an RF generator that goes down to 10 KHz (a few exist), or an audio generator, or function generator that has a low impedance sine wave output (50 ohms or 600 ohms) ... which is about all of them.

Alignment begins with the tuning capacitor (C1) fully meshed, the bandswitch set to position "D," and either an AC voltmeter or oscilloscope monitoring the amplified output (OUT2). Alternatively, connect the preselector to the receiver and find the minimum frequency point on its dial.

Adjust the signal generator frequency until a peak is found. In all likelihood, the first cut will show a "double humped" tuning characteristic because the two halves of the L-C network are not adjusted to the same frequency. Adjust L3 and L6 for a peak response. Next, adjust C2 and C3 for a peak response. These adjustments are interactive, so do it two or three additional times to make sure that the actual peaks are reached.

Next, set the tuning capacitor fully open (all the way unmeshed). Find the peak frequency by adjusting the signal generator. For this adjustment, leave the inductors alone and just peak C2 and C3.

Next, align band "B" in the same manner, except that the capacitors are not trimmed. That means you adjust L2/L5 only. Finally, adjust band "A" by following the same procedure for L1/L4.

## Variation on the Theme

There are two variations on the circuit that may interest some readers. First, is varactor tuning for those who can't find the dual tuning capacitors, or don't want to use the capacitor. In this circuit (Figure 4A), an AM BCB varactor (voltage variable capacitance) diode is used to replace

the capacitor.

The varactor selected is the NTE-618, which has a capacitance of a few pF up to 440 pF, as the applied reverse bias tuning voltage VT is changed from 12 VDC down to 1.00 VDC. Capacitor C1 is used to provide DC blocking that keeps the tuning voltage (VT) from affecting (or being affected by) the inductors and following circuitry.

The tuning characteristic for the VLF preamplifier, found during a bench test, is shown graphed in Figure 4B. With this combination, the tuning ranged from 20.5 to 28.5 KHz when the trimmer was set to 45 pF and the inductances were set to 116.5 mH.

## Reducing AM BCB Interference on VLF

The AM broadcast band covers 540 to 1,700 KHz, while the LF and VLF frequencies are those frequencies below 540 KHz. Therefore, one should not expect interference from local AM broadcast stations while noodling around in the "down unda" bands, right? No, not by a long shot. There are two basic reasons.

First, the AM stations may tend to be very local. Second, radio stations tend to be high powered. One location where I lived was known locally as "Intermod Hill" because there were a large number of radio transmitters up there, including two FM BCB (50 kw each) stations and

A way to solve the problem is to use a low-pass filter (LPF) ahead of the receiver that has a cut-off frequency somewhere below 540 KHz. Figure 5 shows a seven-element LPF with a 0.1 dB ripple factor, designed for 50-ohm input and output impedances. The LPF consists of four inductances (L1-L4) and three capacitors (C1-C3). Each capacitor is made up of two parallel capacitances in order to obtain the correct capacitance.

Those capacitors should be a relatively stable, five percent tolerance, type such as the Panasonic B-Series polyester or V-Series metallized film capacitors. For receive-only applications, the voltage rating is not an issue, so 50-WVDC capacitors in those series will work nicely.

The inductance values shown in Figure 5 are for the VLF version of the tuner, for which a 120 KHz -3 dB cut-off frequency is specified. The 75-mH inductors are Toko TK-4256, while the 130-mH inductors are Toko TK-4262. If you want to make the LPF work for a different cut-off frequency, then consult Table 1 for component values:

The layout of the LPF circuit should follow "good low frequency RF practices," which means that you want at least a small separation between the inductors. Construction on perforated board is quite satisfactory. My initial version was built "rat's nest" style on printed circuit perf-board. That form has printed circuit connection points on a 0.1 X 0.1

TABLE 1

BAND	L1/L4	L2/L3	C1	C2	C3
<300 KHz	33 mH	56 mH	0.015 mF	0.0167 mF	0.015 mF
<500 KHz	18 mH	33 mH	0.009 mF	0.01 mF	0.009 mF

one 5,000 watt AM BCB station. Living just a few blocks from that 5,000-watt gigablaster tore a hole in every receiver I owned. With such strong field strengths, almost all receivers overloaded.

Incidentally, the way I graded receivers in those days was how free they were from such interference. And it wasn't always the most expensive model that was the most free of problems.

inch pattern, so is easy to solder to and use.

By the way, the same circuit can be used for any frequency. This LPF is somewhat universal. To find the values of the components, use the following formulas:  $L1 = L4 = 9.4/\text{FMHz}$ ;  $L2 = L3 = 16.68/\text{FMHz}$ ;  $C1 = C3 = 4538.9/\text{FMHz}$ ; and  $C2 = 5008.3/\text{FMHz}$ , where FMHz is the frequency in MegaHertz. The coils can be made from T-37-xx toroidal cores, or selected from the Toko coils. Select fixed coils with a 5 mm (0.2 inch) pin spacing ... which is nearly all of them in that catalog.

## Connections ...

I can be reached by snail mail at P.O. Box 1099, Falls Church, VA 22041, or via E-Mail at CARRJ@AOL.COM.

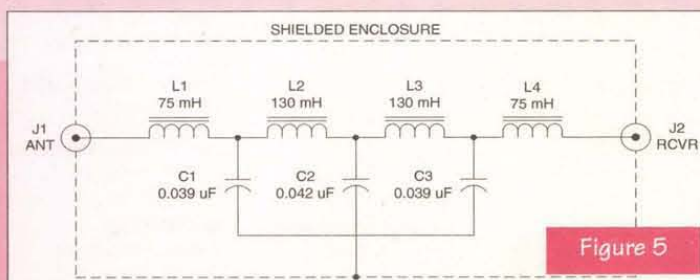


Figure 5

# JFETS

ULTRA LOW NOISE  
LS843 - 3nV/Hz typ

TIGHT MATCHING  
LS843 - 1 mV max

- ◆ N & P Channel
- ◆ Duals & Singles
- ◆ Custom Screening
- ◆ Die, SMT, Thru-Hole
- ◆ No Order Minimum
- ◆ COD's Accepted

Second Source for Domestic & Foreign JFETs & Bipolars

Full Service U.S. Manufacturer of Specialty Linear Products

## LINEAR SYSTEMS

4042 Clipper Court  
Fremont, CA 94538  
510-490-9160/510-353-0261 (Fax)  
E-mail: 3623671@MCI.MAIL.COM

Write in 35 on Reader Service Card.

## Question: Who Uses .45 Shells

- The Lone Ranger
- GI Joe
- Metrologic

Answer: All the Above

Metrologic manufactures and sells low voltage (3Vdc), stable output (3mW)

DIODE LASERS  
housed in rugged  
"Bullet Packs"

For information on our laser diodes, laser and optics kits as well as a FREE catalog including over 100 laser experiments contact us at:

1-800-667-8400

www.metrologic.com

"Innovative Leaders in Laser Technology for over 30 Years"

**Metrologic**



NJ Phone: 856.228.5544  
90 Coles Road  
Blackwood, NJ 08012

laser@metrologic.com

Write in 31 on Reader Service Card. 17







# GPS Mapping?

We've got you covered

**IBM ROAD WARRIOR**  
Professional Road Equipment

**USE IN DIRECT SUNLIGHT**

**Takes MAXIMUM**

**ABUSE**

strictly for professionals

**Waterproof!**

The ONLY Waterproof computer under \$5,000

Silicone Rubberized & Diecast Case! Shock Mounted 1GIG Drive!  
ESD/EMF & RF Resistant, Works from -4 to 120 Deg F & Vacuum to 15,000 ft  
> 1-PCMCIA (type 1, 2 or 3), Serial & Parallel Ports in rear  
> 16m Ram / 1m Video / 32 Bit Local Bus 486-50 Mhz & Math Co-processor,  
> 28.8k Modem (Internet Ready) > Hydrate Battery (\$150 Value) > W95  
> Sound & Mic > 8.25" Display-64 Shade Monochrome REFLECTIVE

**OPTIONS**

> GPS Receiver & s/w Preinstalled \$159 > Floppy Drive \$89  
> 12V Car cord \$29 > Desktop 48X Cd Rom \$159 > Touch Screen \$89  
> 33k Baud PCMCIA Fax-Modem Upgrade \$35 > Carry Strap \$6  
> 2gig Drive \$129 / 3 gig \$189

This was a unique (one shot) purchasing opportunity  
IT'S NOT OPEN STOCK

WHEN THEY'RE GONE, THEY'RE GONE FOR GOOD  
Sold till recently by IBM through their Local Area Network Div  
at \$4,699 & \$6,912 as shown here. (they were never discounted)

**EveryTown USA**  
**GPS**  
Preloaded option



**CD Rom Works with ANY Computer**

Desktop Parallel Port CD Drive  
Built-in Printer Port  
Power Supply & Audio output  
for DOS, W3.1, W95, W98

48X!  
cheapest anywhere

**\$159**

Our Customers Call back with

**96Meg!**

only \$96!

**64Meg**

only \$64!

GPS Fully Installed \$159

**Rave Reviews!**

Low Price / High performance

Compare at  
**\$1,500**

**Sale**

**\$888** -or-

4 Easy payments of  
**\$229**

**5070 "Traveler" Includes:**  
233Mhz MMX, 3Gig, 32M Ram  
56k Modem, 24X CD, Floppy,  
MP3 Stereo, W95SE, Mic, Touch Pad Mouse,  
3hr Bat, 2 USB ports, IR Port, 2 PCMCIA ports,  
Serial & Parallel Ports, Super Lightweight 3.3 lb  
9.5" x 7" x 1.5", 8.5" 16million Color SVGA Display,  
Supports High Resolutions up to 1024 x 768  
FREE Lifetime NetcomTech support (our customers say our tech support is the best in the world)

5070 is the leading maker of Computer Motherboards for FAMOUS BRAND NAME computers. The  
"Traveler" has every "State of the Art" feature you want at a Spectacular price.  
Runs ANY program with ease. Light weight & Ultra portable

**Why will this Small Laptop Become your Pal?**

You bring a big machine with you less & less often because it's a pain to  
drag around. Millions of PDA owners already know this. Unlike PDA's this is  
desktop power with a fraction of the BIG machine Bulk & Weight.

**Razor Sharp, BRIGHT & Easy Viewing**  
**Comfortable Typing with Wrist Rests**

1 Year Warranty - Satisfaction Guaranteed - The Friendliest People - The Best Customer Service

PAYMENT PLAN with Credit Card -or- Layaway ONLY

COD's SINGLE PAYMENT ONLY

ORDERSONLY 800-733-3733 ORDERSONLY

FAX 843 650 5777 10-8 EST Mon - Fri

Email for Detailed Information

843-650-5700 For Questions-or-

email: netcomd@aol.com

Looks so nice  
in person,  
it'll give ya  
Goose Bumps

**CUSTOM Carry Case**  
**\$24**

**EveryTown USA**  
**GPS**  
Preloaded option

**IBM Thinkpad**  
**Pentium**

Huge 10.5" TFT Active Matrix SVGA Color Display  
Includes Docking station, Lets you add an ISA board  
75 Mhz Pentium Processor  
33k FAX MODEM - 2 PCMCIA Expansion Slots  
Dual Infrared Ports (Front & Rear)  
Track Point Eraser Head Mouse (Very Responsive)  
All Standard Ports (15, 1P, VGA, 1Kbd)  
Pop out - Hard Drive, Ram, Battery & Floppy.  
Ram & Hard Drive Easily Expandable & Upgradable.  
Includes Power Supply & Hydrate Battery  
Free Lifetime Tech Support Web Site Creator Software  
Internet Ready, America On Line (Full install)  
Fax Modem Software, Searchable Owners Manual s/w, W95  
2 Gig Hard Drive Standard -or- 3 Gig \$149 Option  
24M Ram Optional Carry case \$35 Auto Power Converter \$49  
**PRELOADED GPS OPTION \$159**

Orig  
**\$3,499**  
**\$3,949** Dock

**IBM**

4 Easy payments of  
**\$175!**

**DOCK INCLUDES:**  
LAN Card, Speakers,  
Built-in Power Supply &  
Fan, SCSI Port, Parallel,  
Serial, Keyboard, Mouse,  
Monitor, Stereo in & out,  
Headphone Jack, Carry  
handle, LED Status,

**HIDDEN ISA CARD  
PORT IN DOCK**  
You can install any  
ISA card!



**Sale**

**IBM Docking Station INCLUDED**



# Power Supply Design Software

**P**ower supplies are not that difficult to design, but keeping track of all the details can be a real chore. At least the elementals are constant: power, voltage, current, magnetics, capacitors, etc. Devices may change, but the physics of power design do not. Once you've mastered the basics, you have some skills that won't be obsolete next year like a lot of other engineering skills.

## Buck Regulator Design

The most common power supply topology is the buck converter. Basically, an input voltage is chopped by a switch and filtered. Right away we sense the advantage of the switched-mode power supply; the switches are either on or off and therefore dissipating little energy (we'll ignore switching losses for now). Energy is stored in a series inductor; it charges and discharges around an operating point that supports a regulated load voltage.


Taking a look at Figure 1, a couple of things jump out. First of all, there is no isolation, the input ground is connected to the output ground. Second of all, if the switch (Q1) is always on, the output will be equal to the input, this is the absolute maximum output voltage that could be achieved. Practically, the output must be less than the input. The circuit operates in two modes:

- With Q1 on, D1 is off, and L1 is charging.
- With Q1 off, D1 is conducting, and L1 is discharging.

The best way to visualize circuit operation is to remember that an inductor resists a changing current; with a current flowing through L1 and into the load, when Q1 turns off, the current will continue to flow and the only possible path for current to be sourced is through D1. The output is proportional to the input voltage and the duty cycle of Q1's conduction.

The trickiest part of a buck regu-

**Figure 2**  
Power Input and Output Specification

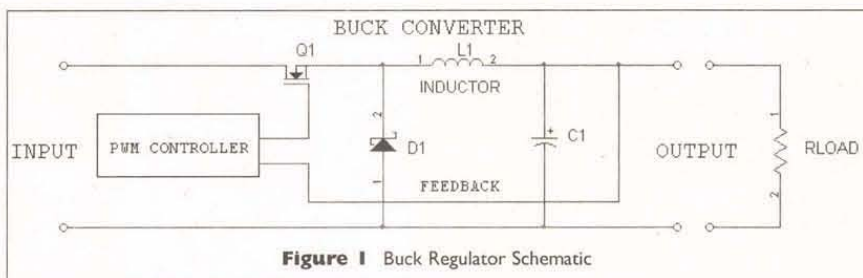

**Figure 1** Buck Regulator Schematic

lator design is transfer function; we need to assure that the output is stable for all input and load conditions. If the load or input voltage changes, we prefer the output move smoothly to the new operating point without overshoot.

We also want the output to change fast enough to avoid significant voltage droop. If it appears these requirements are contradictory, that's because they are.

## Power Supply Design Software: Power456 plus


Fortunately, a software tool exists which can help us keep track of all the details of a switched-mode power supply design and help us design the compensation to keep our power supply stable. This software is called Power456 plus and is available from

Ridley Engineering (see contact information elsewhere in this article). Power456 is a group of applications based on the Microsoft Excel spreadsheet.

To get started, we invoke Power456 and press the START button. Then we select the Enter Power Specifications button and we see the screen shown in Figure 2.

For this example, I defined a 3.3V 6.6W power supply with an 18V  $\pm 20\%$  input. Press OK and a menu with a complete selection of power supply topologies appears (see Figure 3). We're studying the buck topology, so we'll click on the Buck selection. A top-level view of the design pops up, (see Figure 4).

All of a sudden our simple buck converter looks more intimidating, but don't panic yet. All the elements of Figure 1 are in this block diagram with

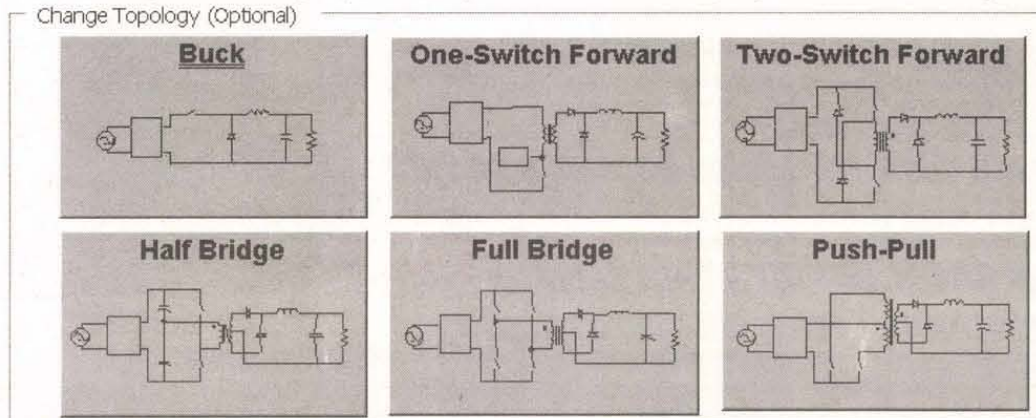

**Figure 3** Power Supply Topology Selection



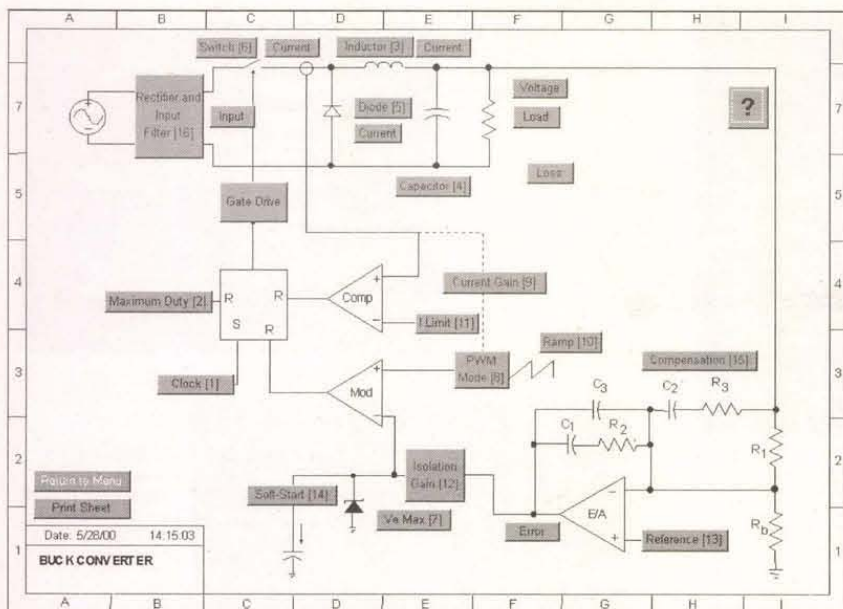


Figure 4 Buck Regulator Block Diagram

Ken Coffman is a Field Applications Engineer in the Pacific Northwest for Nu Horizons, the fifth largest semiconductor distributor in the United States. Ken is the author of *Real World FPGA Design with Verilog* (available from [www.bytechservices.com](http://www.bytechservices.com) or [www.amazon.com](http://www.amazon.com)) and the forthcoming *Practical FPGA Designer's Guide to VHDL and Verilog* (available in 2001).

#### Contact Information

Contact Ridley Engineering:  
Voice: (770) 642-1918  
FAX (770) 642-6133  
E-mail: [www.ridleyengineering.com](mailto:www.ridleyengineering.com)

Contact Ken Coffman:  
E-mail: [kcoffman@nuhorizons.com](mailto:kcoffman@nuhorizons.com)  
[www.bytechservices.com](http://www.bytechservices.com)  
[www.nuhorizons.com](http://www.nuhorizons.com)

Thanks to Craig Ranta who made some constructive suggestions for this article.

References and recommended reading:  
Ridley Engineering Power456 Help files  
*Feedback Loop Stability Analysis*, Walter S. Friauf, published by McGraw-Hill, 1998

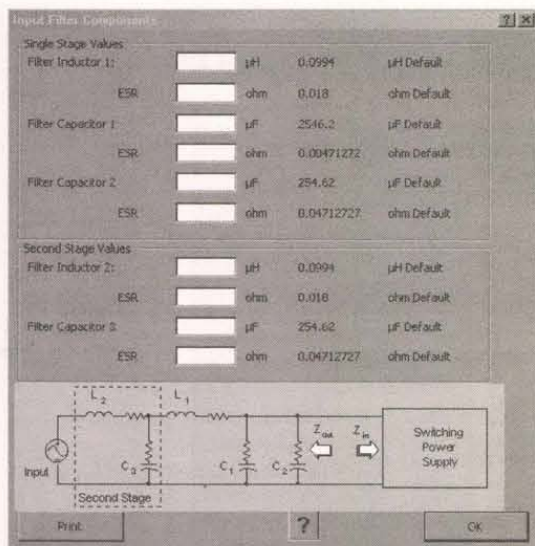


Figure 5 Input Filter Components

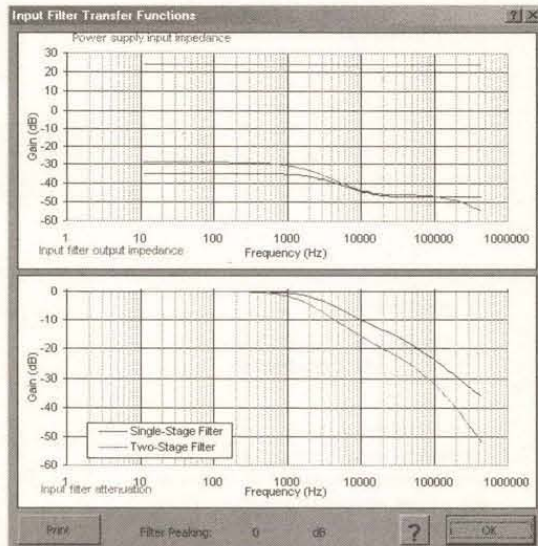


Figure 6 Input Filter Impedance/Attenuation Plots

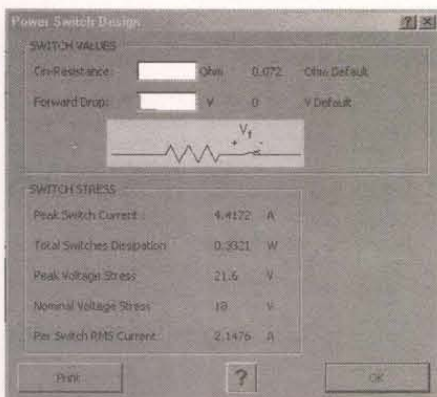


Figure 7 Transistor Switch Stresses

details of the input filter, the PWM controller and the compensation circuit expanded.

Don't you hate it when an application note leaves out essential parts of a real-world design? Power456 will keep you out of trouble by including all the sections of a complete design.

The characteristics of these devices will not affect the circuit analysis.

Figure 6 shows the transfer function (filter output impedance vs. frequency and attenuation vs. frequency plots) of the input filter. Figure 7 summarizes the transistor switch stresses.

This is a good thing! If you click on the input filter block, the Input Filter Component screen is displayed (see Figure 5).

You will note that Power456 has filled in default (nominal) values for capacitor and inductor characteristics; enter in the real values for the components you choose and the analysis will reflect these parameters. The only things missing are the transient voltage suppressors and fuses necessary for operating in offline applications.

MOSFETs are modeled with on-resistance only (as shown with forward drop set to zero); bipolar transistors are modeled with both on resistance (to reflect bulk resistance of the device) and forward drop (to reflect  $V_{ce(sat)}$ ).

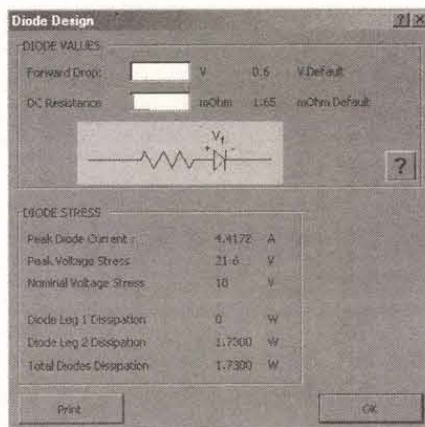
It may not seem natural to think of the diode as a switch, but that's the way it acts in the buck converter circuit. Like the bipolar transistor, as shown in Figure 8, the diode is modeled as a forward drop and bulk resistance (the forward resistance is small for a power diode, so the default value is 0; fill in the more correct value from the diode data sheet, as necessary).

Figure 9 shows the current plots for the diode and transistor switch. When the switch turns on, it quickly sources current to charge the inductor flux. When the transistor is off, the inductor begins discharging with the diode closing the loop.


The power supply designer must choose the desired control mode. There are two traditional modes of
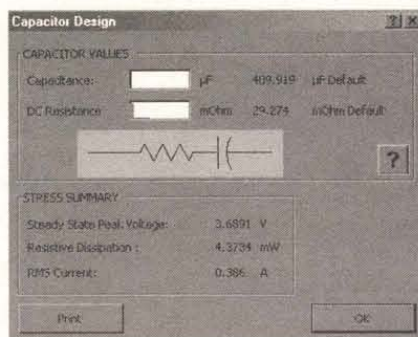
# Power Supply Design Software

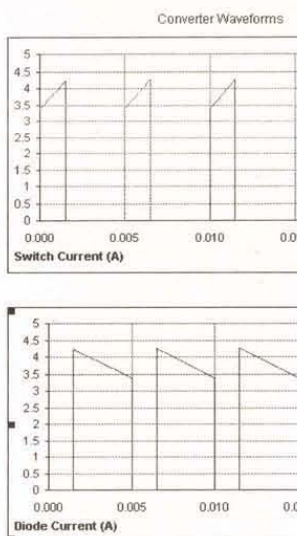





**Figure 8**  
Diode  
Stress  
Summary




**Figure 10**  
Output  
Capacitor  
Characteristics



**Figure 9** Diode/Transistor  
Current Waveforms

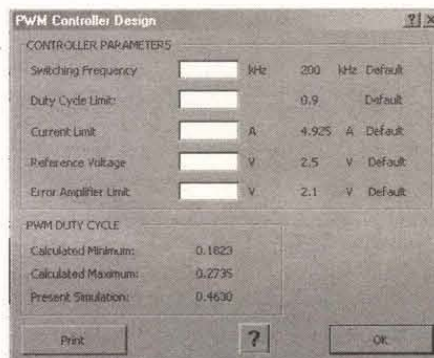

**Figure 11**  
Pulse Width  
Modulator (PWM)  
Controller  
Characteristics

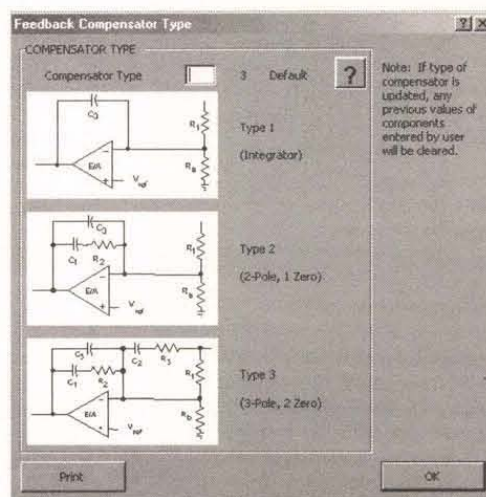

**Figure 12**  
Feedback  
Compensation Types

control: voltage mode and current mode. A voltage-mode controller samples the output voltage and compares the voltage sample to the PWM ramp voltage. When the output is less than the ramp, Q1 is turned on and vice versa. This gives proportional control; the greater the difference between the ramp and the output, the longer period that the power switch is turned on.


Current-mode control sums the switch current with a compensating ramp signal and compares this to an error voltage (proportional to the difference between the output voltage and the reference voltage). A built-in advantage of this control mode is the inherent cycle-by-cycle current limit which protects the transistor.

Ridley Engineering recommends current mode control for all switched-mode power supply topologies, except the half bridge. Figure 10 summarizes the characteristics of the output filter capacitor (C1). Figure 11 shows the controller parameters including the reference voltage; these values can be filled in to reflect the characteristics of the selected power supply controller.

## Feedback Compensation Design

Power456 supports three types of

**Figure 13**  
Feedback  
Compensation Types  
Help Screen

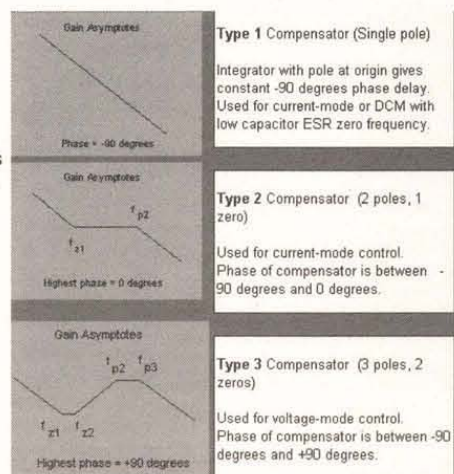

compensation networks as shown in Figure 12. The simplest is called Type 1 (one pole), an integrator circuit which allows the output to slew to operating points at a fixed rate. Type 2 compensation adds a pole/zero network

to speed up the slew rate at lower frequencies with rapid attenuation at higher frequencies to assure stability. Type 3 adds yet another pole/zero pair. Each screen has a handy help button (?) which brings up background



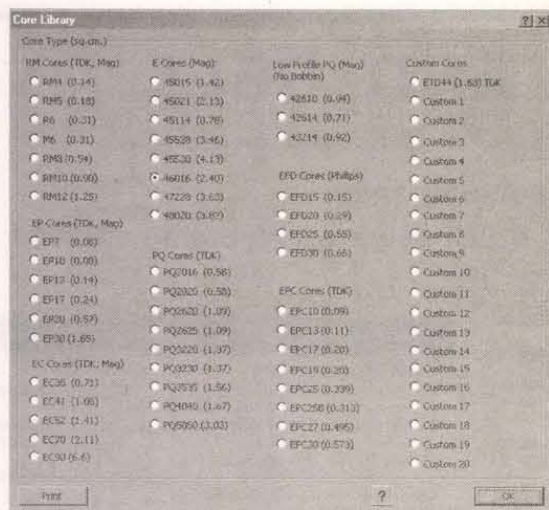


Figure 18 Core Library

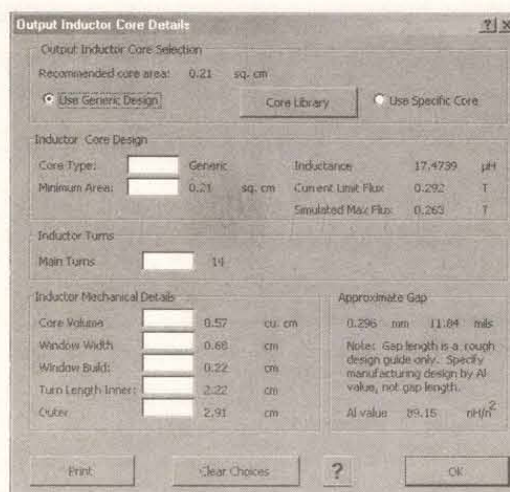


Figure 16 Output Inductor Core Details

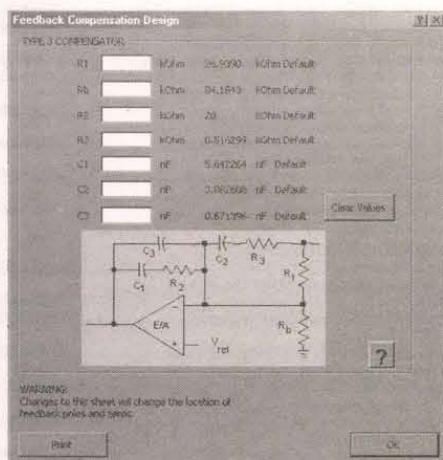


Figure 14 Feedback Compensation Design

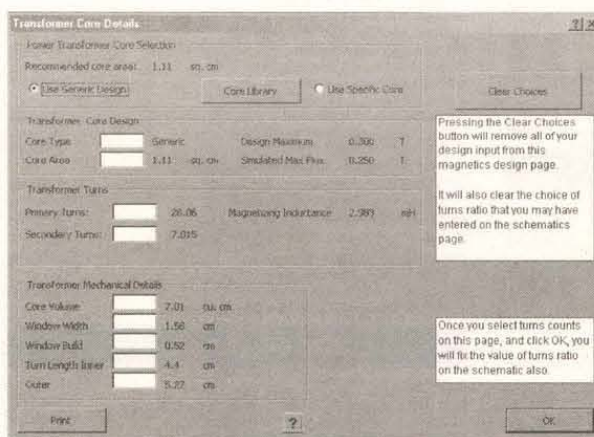


Figure 17 Transformer Core Details

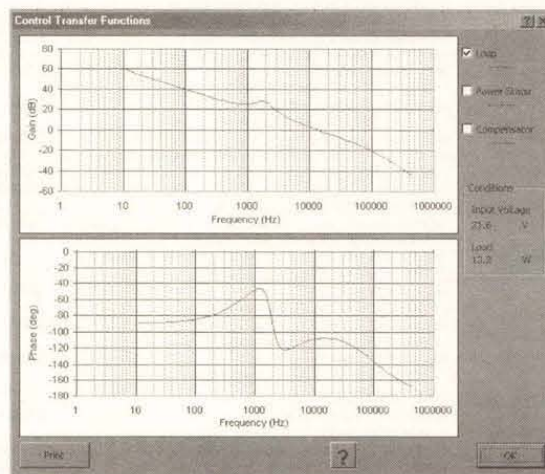


Figure 15  
Feedback  
Network Bode  
(Gain/Phase)  
Plots

information. The help screen for the Feedback Compensation Type is shown in Figure 13.

The compensation network component values are entered in the Feedback Compensation Design sheet as shown in Figure 14. The resulting Bode (gain/phase) plots for Type 3 feedback networks are shown in Figure 15.

The basic rule for network stability is to assure that phase margin exists at all frequencies. Phase margin means that negative feedback (-180 degrees) is assured.

To achieve this, when the network phase reaches somewhere around -90 (for a total of about -270 degrees when 180 degrees for the inverting amplifier is included), the gain should be zero or negative.

What you absolutely do not want is positive gain when the total phase approaches 360 degrees; this is positive feedback and is the very definition of instability. Remember that the inverting op amp circuit in the feedback circuit contributes -180 of phase and the RC feedback network contributes additional negative phase depending on the feedback component values and the frequency in question.

Usually, for a typical buck regulator design, the inductor is purchased off-the-shelf. However, to support the design of the inductor (and the design of magnetics for more specialized designs), an inductor core design sheet is provided. Figure 16 shows an example. The physical and electrical properties of the inductor are entered and the inductor values are used in the analysis of circuit operation (losses, etc.).

Power456 can also be used to design transformers for other power supply topologies (including an isolat-

ed buck topology). Figure 17 illustrates the transformer design sheet. Power456 includes a core library with common commercially-available core styles and materials; other cores can be entered to customize this library.

As far as I know, the Ridley Engineering power supply design tool is unique in its completeness, low cost, and ease of use. The list price of \$995.00 will more than pay for itself when the first reliable and well-documented power supply design is achieved with its help. **NV**



# WESTERN TEST SYSTEMS

# WE BUY AND SELL

Inquiries 307-635-2269 • Fax 307-635-2291

Orders 800-538-1493

2701 Westland Court, Unit B, Cheyenne, Wyoming 82001

## OSCILLOSCOPES & ACCESSORIES

### OSCILLOSCOPES

HP 54100D Dual Channel 1 GHz / 40 MS/s Digitizing Oscilloscope	\$875.00
TEK 7104 1 GHz 2-Channel Oscilloscope, w/7A29,7A29-04,7B10,7B15	\$2,000.00

### PROBES

HP 1122A Probe Power Supply	\$150.00
TEK 1101 Accessory Power Supply, for FET probes	\$175.00
TEK A6902B Voltage Isolator, DC-20 MHz, 20 mV-500 V/div.	\$500.00
TEK P6046 100 MHz Differential Probe	\$400.00
TEK P6101A pair 1X 34 MHz Probe pair, 10 Megohm/32pF, new in plastic	\$50.00
TEK P6201 900 MHz 1X/10X/100X FET Probe	\$400.00
TEK P6202 500 MHz 10X FET Probe	\$150.00
TEK P6205 750 MHz 10X FET Probe, for TDS series	\$325.00
TEK P6701-opt.02 O/E Converter, 450-1050 nm/0-1 mW, DC-700 MHz, ST conn.	\$175.00

### CALIBRATION

TEK 067-0587-02 Signal Standardizer Calibration Fixture	\$750.00
---	----------

## WAVEFORM GENERATORS

### FUNCTION

HP 3310A 5 MHz Function Generator	\$250.00
HP 3314A-001 Function Generator, 0.001 Hz-19.99 MHz, 30 Vp-p, HP1B	\$1,200.00
HP 3325A 21 MHz Synthesized Function Generator, HP1B	\$900.00
HP 3325A-002 21 MHz Synthesized Function Generator, HV output option	\$1,200.00
TEK AWG5102 Arb. Waveform Gen., 20 MS/s, 12 bits, 50ppm synthesis <1MHz	\$650.00
TEK AWG5105-opt.02 Arbitrary Waveform Generator, dual channel option	\$800.00
TEK D0501 Digital Delay & Burst Gen., for function & pulse gen's	\$200.00
TEK FG5010 Programmable 20 MHz Function Generator, TM5000 series	\$800.00
TEK FG501A 2 MHz Function Generator, TM500 series	\$275.00
TEK FG502 11 MHz Function Generator, TM500 series	\$275.00
TEK FG503 3 MHz Function Generator, TM500 series	\$250.00
TEK RG501 Ramp Generator, TM500 series	\$175.00
WAVETEK 288 20 MHz Synthesized Function Generator, GPIB	\$650.00

### PULSE

BERKELEY NUCLEONICS 7085B Digital Delay Generator, 0-100 mS, 1 nS res., 5 Hz-5 MHz	\$550.00
HP 8007B 100 MHz Pulse Generator	\$450.00
HP 8012B 50 MHz Pulse Generator, variable transition time	\$500.00
HP 8082A 250 MHz Pulse Generator	\$1,250.00
TEK PG502 250 MHz Pulse Generator, Tr<1nS, TM500 series	\$500.00
TEK PG508 50 MHz Pulse Generator, TM500 series	\$350.00
WAVETEK 802 50 MHz Pulse Generator	\$250.00

## VOLTAGE & CURRENT

### VOLTMETERS

FLUKE 845AR High Impedance Voltmeter / Null Detector	\$400.00
HP 3456A 6-1/2 Digit Voltmeter, HP1B	\$450.00
HP 3478A 5-1/2 digit Multimeter, HP1B	\$450.00
KEITHLEY 181 6-1/2 digit Nanovoltmeter, 10 nV sensitivity, GPIB	\$800.00
SOLARTRON 7081 8-1/2 digit Voltmeter	\$3,000.00
TEK DM5010 4-1/2 digit Multimeter, TM5000 series plug-in	\$300.00
TEK DM501A 4-1/2 digit Multimeter, TM500 series plug-in	\$225.00

### CALIBRATION

FLUKE 510A AC Reference Standard, 10 VRMS, 0-10 mA	\$450.00
FLUKE 515A Portable Calibrator, DC/AC/Ohms, line & battery power	\$900.00
FLUKE 520A Transconductance Amplifier, DC-5 kHz, 0-20 A	\$1,900.00

### VOLTAGE SOURCES

HP 6115A Precision Dual Range Power Supply, 50V 0.8A / 100V 0.4A	\$750.00
KEITHLEY 228 Programmable Voltage/Current Source	\$1,900.00

### CURRENT METERS & SOURCES

HP 6181C DC Current Source, to 100 V, 250 mA	\$500.00
HP 6186C DC Current Source, to 300 V, 100 mA	\$750.00
TEK CT-5 High Current Transformer for P6021/A6302, to 1000A	\$750.00
TEK P6022 AC Current Probe w/termination, 935 Hz-120 MHz, 6 A pk	\$250.00

## IMPEDANCE & COMPONENT TEST

### L.C.R.

BOONTON 62AD 1 MHz Inductance Meter, 2-2000 uH	\$550.00
--	----------

BOONTON 72BD 1 MHz Capacitance Meter, 3-1/2 digit display	\$650.00
BOONTON 72C 1 MHz Capacitance Meter, 1-3000 pF full scale	\$800.00
GR 1658 RLC Digibridge, 120 Hz / 1 kHz	\$1,000.00
GR 1659 RLC Digibridge, 120 Hz / 1 kHz / 10 kHz	\$1,100.00

### STANDARDS

E.S.I. SR-1 Standard Resistor, various values	\$125.00
E.S.I. SR1010 Resistance Transfer Standards, 1 Ohm-100 K/step	\$550.00
E.S.I. SR1050-1M Resistance T ransfer Standard, 1 Megohm/step	\$2,000.00
GENERAL RADIO 1409-SERIES Standard Capacitors	\$150.00
GR 1406 Standard Air Capacitors, GR900 connector, 0.1% acc.	\$275.00
GR 1432-U 4-Decade Resistor, 0-111.1 Ohms, 0.01 Ohm resolution	\$100.00
GR 1433-J 4-Decade Resistor, 0-11.11 Ohms, 0.1 Ohm resolution	\$150.00
GR 1433-K 4-Decade Resistor, 0-1.110 Ohms, 0.1 Ohm resolution	\$150.00
GR 1433-L 4-Decade Resistor, 0-111.100 Ohms, 10 Ohms resolution	\$150.00
GR 1433-P 5-Decade Resistor, 0-1.1111 Megohm, 10 Ohm resolution	\$500.00
GR 1433-X 6-Decade Resistor, to 111,111.0 Ohms, 0.1 Ohm res.	\$250.00
HP 4440B 4-Decade Capacitor, 40 pF-1.2 uF	\$750.00

### T.D.R.

TEK 1503B-03.04 T.D.R., 0-50,000 ft., chart recorder & battery power	\$3,000.00
TEK 1503-opt.04 Time Domain Reflectometer, 0-50,000 feet, chart recorder	\$1,400.00

## POWER SUPPLIES

### SINGLE OUTPUT

HP 6110A 0-3000 V 0-6 mA CV/CL Power Supply	\$250.00
HP 6207B 0-160 V 0-200 mA CV/CC Power Supply	\$200.00
HP 6263B 0-20 V 0-10 A CV/CC Power Supply	\$375.00
HP 6268B 0-40 V 0-5 A CV/CC Power Supply	\$375.00
HP 6267B 0-40 V 0-10 A CV/CC Power Supply	\$550.00
HP 6271B 0-60 V 0-3 A CV/CC Power Supply	\$375.00
HP 6274B 0-60 V 0-15 A CV/CC Power Supply	\$650.00
HP 6299A 0-100 V 0-750 mA CV/CC Power Supply	\$200.00
HP 6384A 0-4-5.5 V at 8 A CV/CL Power Supply	\$125.00
HP 6443B 0-120 V 0-2.5 A CV/CC Power Supply	\$450.00
HP 6632A System DC Power Supply, 0-20 V, 0-5 A, 100 Watts, HP1B	\$750.00
HP 6652A 0-20 V 0-25 A 500 Watt Programmable Power Supply, HP1B	\$1,875.00
KEPCO ATE 36-30M 0-36 V 0-30 A CV/CC Power Supply	\$900.00
KEPCO ATE 36-8M 0-36 V 0-8 A CV/CC Power Supply	\$375.00
LAMBDA LK-352-FM 0-60 V 0-15 A CV/CC Power Supply	\$600.00
SOERENSON DCR 150-3B 0-150 V 0-3 A CV/CC Power Supply	\$500.00
SOERENSON DCR 600-0.75B 0-600 V 0-750 mA CV/CC Power Supply	\$550.00
SOERENSON DCS 40-25 0-40 V 0-25 A CV/CC Power Supply	\$650.00
SOERENSON SRL 20-12 0-20 V 0-12 A CV/CC Power Supply	\$350.00
SOERENSON SRL 60-8 0-60 V 0-8 A CV/CC Power Supply	\$500.00
TEK PS501-1 Power Supply, 0-20 V, 2 mV res., 400 mA, TM500 series	\$175.00

### MULTIPLE OUTPUT

HP 6205C Dual Power Supply, 0-40 V 300 mA & 0-20 V 600 mA, CV/CL	\$300.00
HP 6228B Dual 0-50 V 0-1 A CV/CC Power Supply	\$375.00
HP 6236B Triple Output Power Supply, +/- 0-20V 0.5A & 0-6V 2.5A	\$375.00
HP 6253A Dual 0-20 V 0-3 A CV/CC Power Supply	\$375.00
HP 6255A Dual 0-40 V 0-1.5 A CV/CC Power Supply	\$375.00
KEPCO MPS-620M Triple Output Supply, dual 0-20V 1A tracking & 0-6V 5A	\$200.00
TEK PS5010 Programmable Triple Power Supply, TM5000 series	\$450.00
TEK PS503A Dual Power Supply, TM500 series	\$200.00

### MISCELLANEOUS

ACME PS2L-500 Programmable Load, 0-75 V / 0-75 A / 500 Watts max.	\$350.00
BEHLMAN 25-C/D/OSCD-1 AC Power Source, 250 VA, 0-130 VAC, 45-2000 Hz	\$850.00
HP 59501B HP1B Isolated DAC/Power Supply Programmer	\$175.00
HP 6060A 300 Watt Programmable Load, 0-60 A / 3-60 V, HP1B	\$950.00
KEPCO BOP 20-20M Bipolar Op Amp/Power Supply, to 20 V 20 A	\$675.00
KEPCO BOP 50-2M Bipolar Op Amp/Power Supply, to 50 V 2 A	\$400.00

## TIME & FREQUENCY

### UNIVERSAL COUNTERS

TRANSISTOR DEVICES DAL-50-150 Programmable Load, 0-50 V, 0-15 A, 100 Watts max.	\$200.00
HP 5315A 100 MHz/100 nS Universal Counter	\$350.00
HP 5315A-001 100 MHz / 100 nS Universal Counter, TCXO reference	\$400.00
HP 5315A-002,003 100 MHz/100 nS Univ. Counter; batt. power & 1 GHz C-ch.	\$550.00
HP 5315A-003 100 MHz/100 nS Univ. Counter, 1 GHz C-channel option	\$450.00
HP 5316A 100 MHz/100 nS Universal Counter, HP1B	\$450.00
HP 5316B 100 MHz / 100 nS Universal Counter, HP1B	\$550.00
HP 5335A-10,30,40 200 MHz/2 nS Universal Counter, OCXO ref., 1.3 GHz C-ch	\$950.00
HP 5370B 100 MHz/20 pS Universal Counter, 11 digits	\$1,200.00
PHILIPS PM6672/411 120 MHz/100 nS Universal Counter, C-channel 70-1000 MHz	\$375.00
TEK DC500A Programmable 100 MHz/100nS Counter/Timer, TM5000 series	\$200.00
TEK DC5009 Programmable 135 MHz Univ. Counter/Timer, TM5000 series	\$350.00
TEK DC503A 125 MHz/100 nS Universal Counter, TM500 series	\$275.00
TEK DC509 135 MHz / 10 nS Universal Counter, TM500 series	\$275.00

### FREQUENCY COUNTERS

FLUKE 7220A-010,131,351 1.3 GHz Counter; battery power, OCXO, and res. mult.	\$500.00
HP 5342A 18 GHz Frequency Counter	\$900.00
HP 5343A-001 26.5 GHz Frequency Counter, OCXO reference	\$3,000.00
HP 5343A-001,011 26.5 GHz Frequency Counter, OCXO reference, HP1B	\$3,500.00
HP 5345A/5355A/5356B 26.5 GHz CW/Pulse Frequency Counter	\$3,500.00
HP 5364A Microwave Mixer / Detector, for modulation domain an.	\$2,000.00
HP 5368A-004 3 GHz Frequency Counter, HP1B; OCXO reference option	\$1,000.00

### MISCELLANEOUS

HP 105B Quartz Oscillator, 0.1 / 1.0 / 5.0 MHz, battery power	\$1,100.00
HP 5087A-opt 032 Distribution Amplifier, 12 outputs at 5 MHz	\$1,750.00

## AUDIO & BASEBAND

### SPECTRUM ANALYSIS

HP 3586C Selective Level Meter, 50 Hz-32.5 MHz, 50 & 75 ohms	\$1,200.00
---	------------

### DISTORTION ANALYZERS

HP 8903A Audio Analyzer, 20 Hz-100 kHz	\$1,200.00
--	------------

### RMS VOLTMETERS

FLUKE 8922A True RMS Voltmeter, 180 uV-700 V, 2 Hz-11 MHz	\$450.00
--	----------

### OSCILLATORS

HP 3336C-004,005 21 MHz Synthesizer/ Level Gen., OCXO & hi accuracy att.	\$1,400.00
TEK SG502 Sine/Square Osc., 5 Hz-500 kHz, 70 dB step atten., TM500	\$200.00

### MISCELLANEOUS

HP 3575A Phase-Gain Meter, 1 Hz-13 MHz, single display	\$600.00
HP 3575A-001 Phase-Gain Meter, 1 Hz-13 MHz, dual display	\$850.00
HP 461A Amplifier, 20 dB or 40 dB gain, 1 kHz-150 MHz	\$125.00
HP 467A Power Amplifier, X1/X2/X5/X10, DC-1 MHz, 10 W output	\$375.00
KROHN-HITE 3103 High/Low Pass Filter, 10 Hz-3 MHz, 24 dB/octave	\$350.00
KROHN-HITE 3200 High Pass / Low Pass Filter, 20 Hz-2 MHz, 24 dB/octave	\$275.00
KROHN-HITE 3202 Dual HP/LP/BP/ BR Filter, 20 Hz-2 MHz, 24 dB/octave	\$450.00
KROHN-HITE 3342R Dual HP/LP Filter, 0.001 Hz-99.9 kHz, 48 dB/octave	\$900.00
ROCKLAND 852 Dual Highpass/ Lowpass Filter, 0.1 Hz-111 kHz	\$650.00
WAVETEK 716 Brickwall Filter	\$1,500.00

## RF & MICROWAVE

### SPECTRUM ANALYZERS

HP 11517A/18A/19A/20A Mixer Set, 12.4-40.0 GHz, for HP 8555A/8569A	\$500.00
HP 11970A WR28 Harmonic Mixer, 26.5-40 GHz	\$1,100.00
HP 11970K WR42 Harmonic Mixer, 18.0-26.5 GHz	\$1,100.00
HP 11970Q WR22 Harmonic Mixer, 33-50 GHz	\$1,400.00
HP 11971A WR28 Harmonic Mixer, for HP 8569B	\$800.00





# 90 DAY WARRANTY PARTS AND LABOR • 10 DAY INSPECTION TEST EQUIPMENT WANTED CALL OR FAX LIST • OPEN ACCOUNTS



HP 11971K WR42 Harmonic Mixer, for HP 8569B	\$800.00
HP 70620B Preamplifier, 1.0-26.5 GHz, for 70000 series	\$3,900.00
HP 8559A/853A-001 Spectrum An., 0.01-21 GHz, 1 kHz res., w/rackmount frame	\$3,500.00
HP 85640A Tracking Generator, 300 kHz-2.9 GHz, for HP 8560 series	\$5,000.00
HP 8568B Spectrum Analyzer, 1, 00 Hz-1.5 GHz, 10 Hz min. res.	\$8,500.00
HP 8569B Spectrum Analyzer, 10, 10 Hz-22 GHz, 100 Hz min. res. bw.	\$5,500.00
TEK 492-opt.02 Spectrum Analyzer, 50 kHz-18 GHz, 1 kHz res.	\$4,250.00
TEK WM782V WR15 Harmonic Mixer, 50-75 GHz	\$1,500.00

## NETWORK ANALYZERS

HP 11650A Network Analyzer Accessory Kit, APC7	\$600.00
HP 11665B Modulator, 0.15-18 GHz, for HP 8755/6/7	\$250.00
HP 85054A Type N Calibration Kit, for HP 8510 series	\$1,800.00

## SIGNAL GENERATORS

HP R85026A WR28 Detector, 26.5-40 GHz, for HP 8757 series	\$1,200.00
---	------------

## SIGNAL GENERATORS

FLUKE 6060A Synthesized Signal Gen., 0.1-1050 MHz, 10 Hz res., GPIB	\$1,650.00
FLUKE 6060A/AN Synthesized Signal Generator, 10 kHz-520 MHz, 10 Hz	\$950.00
FLUKE 6060B/AN Synthesized Signal Gen., 0.1-1050 MHz, 10 Hz res.	\$1,900.00
GIGATRONICS 600/6-12 Synthesized Source, 6-12 GHz, 1 kHz res., GPIB	\$2,500.00
GIGATRONICS 875/50 Levelled Multiplier, x4, 50.0-75.0 GHz output, -3 dBm	\$2,500.00
GIGATRONICS 990/2-8 Synthesized Signal/Sweep Gen., 2-8 GHz, 1 MHz res., GPIB	\$2,500.00
GIGATRONICS 9T900-opt.26A Synthesized Signal Gen., 0.01-20 GHz, 1 kHz res.	\$6,000.00
HP 11707A Test Plug-in for HP 8660 series	\$500.00
HP 11720A Pulse Modulator, 2-18 GHz, 80 dB on/off ratio	\$450.00
HP 3335A-001 Synthesizer/Level Gen., 200 Hz-81 MHz, -87 to +13 dBm	\$3,500.00
HP 8656A-001 Signal Generator, 0.1-990 MHz, 100 Hz res., HP1B, OCXO	\$1,600.00
HP 8657A-002 Signal Generator, 0.1-1040 MHz, 10 Hz res., HP1B	\$2,750.00
HP 8660C/8660A/8663B Synth. Sig. Gen., 1-1300 MHz, AM / FM	\$2,500.00
HP 8660C/8660A/8663B Synthesizer, 1-2600 MHz, 1 Hz res., AM / FM	\$3,250.00
HP 8672A Synthesized Signal Generator, 2-18 GHz, +3 dBm output	\$4,500.00
HP 8684B Signal Generator, 5.4-12.5 GHz, AM/ WBFM/ Pulse	\$3,000.00

## SWEEP GENERATORS

HP 8350B/83522A Sweep Oscillator, 10-2400 MHz, +13 dBm levelled	\$3,900.00
HP 8350B/83540A-002,004 Sweep Oscillator, 2.0-8.4 GHz, 70 dB step attenuator	\$3,900.00
HP 8350B/83545A-002 Sweep Oscillator, 5.9-12.4 GHz, 70 dB step attenuator	\$3,900.00
HP 83570A RF Plug-in, 18.0-26.5 GHz, +10 dBm levelled	\$6,000.00
HP 83592B RF Plug-in, 10 MHz-20 GHz, +13 dBm levelled	\$8,000.00
HP 8601A Generator/Sweeper, 0.1-110 MHz, +20 dBm levelled	\$400.00
HP 8620C Sweep Oscillator Frame	\$550.00
HP 86222A RF Plug-in, 10-2400 MHz, +13 dBm levelled	\$1,000.00
HP 86222B RF Plug-in, 10-2400 MHz, +13 dBm lvd., crystal markers	\$1,200.00
HP 86222B-002 RF Plug-in, 10-2400 MHz, +13 dBm lvd., 70 dB step att.	\$1,350.00
HP 86222B-E69/8620C Sweep Oscillator, 0.01-2 GHz & 2-4 GHz, +10 dBm, w/frame	\$1,500.00
HP 86230B RF Plug-in, 1.8-4.2 GHz, +10 dBm unlevelled	\$375.00
HP 86241A-001 RF Plug-in, 3.2-6.5 GHz, +8 dBm levelled	\$300.00
HP 86260A-H04 RF Plug-in, 10.0-15.0 GHz, +10 dBm unlevelled	\$500.00
HP 86290C RF Plug-in, 2.0-18.6 GHz, +13 dBm levelled output	\$1,850.00
WAVETEK 962 Sweep Generator, 1.0-4.0 GHz, markers, +12 dBm unlvld.	\$950.00

## POWER METERS

BOONTON 428/41-4E Analog Power Meter, with 1 MHz-18 GHz sensor	\$450.00
HP 432A/478A Power Meter, -30 to +10 dBm, 10 MHz-10 GHz	\$300.00
HP 435B/8481A Power Meter, -30 to +20 dBm, 10 MHz-18 GHz	\$900.00
HP 435B/8482B Power Meter, 0 to +43 dBm, 100 kHz-4.2 GHz	\$1,500.00
HP 435B/8482H Power Meter, -10 to +34 dBm, 100 kHz-4.2 GHz	\$900.00
HP 436A-022/8481A Power Meter, -30 to +20 dBm, 10 MHz-18 GHz, HP1B	\$1,200.00
HP 436A-022/8484A Power Meter, -70 to -20 dBm, 10 MHz-18 GHz, HP1B	\$1,200.00
HP 437B/8481D Power Meter, -70 to -20 dBm, 10 MHz-18 GHz, HP1B	\$2,200.00
HP Q8486A Power Sensor, 33.0-50.0 GHz, WR22, for 435/6/7/8	\$1,200.00
HP R8486A WR28 Power Sensor, 26.5-40 GHz, for HP 435/6/7/8	\$1,500.00

## RF MILLIVOLTMETERS

BOONTON 92C RF Millivoltmeter, 3 mV-3 V i.s., 10 kHz-1.2 GHz	\$500.00
RACAL-DANA 9303 RF Millivoltmeter, 10 kHz-2 GHz, -70 to +20 dBm	\$750.00

## AMPLIFIERS, MISCELLANEOUS

AMPLIFIER RESEARCH 4W1000 Amplifier, 40 dB gain, 4 Watts, 1-1000 MHz	\$950.00
HP 11729B-003 Carrier Noise Test Set, 5 MHz-3.2 GHz	\$2,250.00
HP 415E SWR Meter	\$200.00
HP 8406A Comb Generator, 1/10/100 MHz increments, to 5 GHz	\$500.00
HP 8447A Amplifier, 20 dB, 0.1-400 MHz, 5 dB NF, +6 dBm output	\$375.00
HP 8447E Amplifier, 22 dB, 0.1-1300 MHz, +13 dBm output	\$750.00
HP 8901A Modulation Analyzer, 150 kHz-1300 MHz	\$1,500.00
HP 8901B-1,2,3 Modulation An., 0.15-1300 MHz, rear input, OCXO, ext.LO	\$2,000.00
HUGHES 1177H01F000 TWT Amplifier, >30 dB gain, 2-4 GHz, 10 Watts output	\$1,750.00
HUGHES 1177H10F000 TWT Amplifier, >30 dB gain, 1.4-2.4 GHz, 20 Watts	\$2,500.00
HUGHES 8010H13F000 TWT Amplifier, >30 dB gain, 3-8 GHz, 10 Watts	\$2,500.00
RF POWER LABS ML50 Amplifier, 2-30 MHz, 47 dB gain, 50 Watts, metered, 28V	\$275.00
ROHDE & SCHWARTZ ESH2 Test Receiver, 9 kHz-30 MHz	\$3,750.00

## COAXIAL & WAVEGUIDE

AEROWAVE 28-300/10 WR28 Directional Coupler, 10 dB, 26.5-40 GHz	\$300.00
AMERICAN NUCLEONICS AM-432 Cavity Backed Spiral Antenna, LHC, 2-18 GHz, TNC(f) *NEW*	\$95.00
AVANTEK AMT-400X2 WR28 Active Doubler, +10 dBm in/ +10 dBm out 26-40 GHz	\$450.00
BIRD 6735-300 1 kW Load, 25-1000 MHz, LC(f), with wattmeter	\$650.00
BIRD 8201 500 Watt Oil Dielectric Load, DC-2.5 GHz, N(f)	\$350.00
FXR/MICROLAB S3-02N Triple Stub Tuner, 200-1000 MHz, 100 Watts max., N(m/f)	\$125.00
FXR/MICROLAB SL-03N Stub Stretcher, 0.3-6.0 GHz, 100 Watts max., N(m/f)	\$75.00
GR 874-LTL Constant Impedance Trombone Line, 0-44 cm, DC-2 GHz	\$400.00
HP 11590A-001 Bias Network, 1.0-18.0 GHz, APC7	\$450.00
HP 11636A 2-Way Power Divider, DC-18 GHz, N(m/f)	\$300.00
HP 11691D-001 Directional Coupler, 22 dB, 2-18 GHz, N(f)-all ports	\$450.00
HP 11692D Dual Directional Coupler, 22 dB, 2-18 GHz	\$800.00
HP 33321K Programmable Step Atten., 0-70 dB, DC-26.5 GHz, 3.5mm	\$475.00
HP 33327L-006 Programmable Step Attenuator, 0-70 dB, DC-40 GHz, 2.9mm	\$1,000.00
HP 7740 Dual Directional Coupler, 20 dB, 215-450 MHz	\$275.00
HP 7760 Dual Directional Coupler, 20 dB, 940-1900 MHz	\$275.00
HP 7770 Dual Directional Coupler, 20 dB, 1.9-4.1 GHz	\$275.00
HP 7780-011 Dual Dir. Coupler, 20 dB, 100-2000 MHz, APC7 test port	\$450.00
HP 8431A 2-4 GHz Band Pass Filter, N(m/f)	\$150.00
HP 8494G-002 Programmable Step Attenuator, 0-11 dB, DC-4 GHz, SMA	\$350.00
HP 8496A-002 Step Attenuator, 0-110 dB, DC-4 GHz, SMA	\$375.00
HP 8497K-004 Programmable Step Attenuator, 0-90 dB, DC-26.5 GHz	\$750.00
HP K42A WR42 Flat Broadband Detector, 18.0-26.5 GHz	\$350.00
HP K532A WR42 Frequency Meter, 18.0-26.5 GHz	\$450.00
HP K752D WR42 Directional Coupler, 20 dB, 18.0-26.5 GHz	\$450.00
HP K870A WR42 Slide Screw Tuner, 18.0-26.5 GHz	\$275.00
HP K914B WR42 Moving Load, 18.0-26.5 GHz	\$300.00
HP Q752D WR22 Directional Coupler, 20 dB, 33-50 GHz	\$650.00
HP R382A WR28 Direct Reading Attenuator, 0-50 dB, 26.5-40 GHz	\$2,250.00
HP R422A WR28 Crystal Detector, 26.5-40 GHz	\$400.00
HP R752D WR28 Directional Coupler, 20 dB, 26.5-40 GHz	\$450.00
HP R914B WR28 Moving Load, 26.5-40 GHz	\$250.00
HP V365A WR15 Isolator, 25 dB, 50-75 GHz	\$750.00
HP V752D WR15 Directional Coupler, 20 dB, 50-75 GHz	\$650.00
HP X870A WR90 Slide Screw Tuner	\$150.00
HUGHES 45322H-1110/1120 WR22 Directional Couplers, 10 or 20 dB, 33-50 GHz	\$350.00
HUGHES 45712H-1000 WR22 Frequency Meter, 33-50 GHz	\$750.00
HUGHES 45714H-1000 WR15 Frequency Meter, 50-75 GHz	\$900.00
HUGHES 45721H-2000 WR28 Direct Reading Attenuator, 0-50 dB, 26.5-40 GHz	\$1,000.00
HUGHES 45722H-1000 WR22 Direct Reading Attenuator, 0-50 dB, 33-50 GHz	\$1,000.00
HUGHES 45724H-1000 WR15 Direct Reading Attenuator, 0-50 dB, 50-75 GHz	\$250.00
HUGHES 45732H-1200 WR22 Level Set Attenuator, 0-25 dB, 33-50 GHz	\$1,400.00
HUGHES 45752H-1000 WR22 Direct Reading Phase Shifter, 0-360 deg, 33-50 GHz	\$400.00
HUGHES 45772H-1100 WR22 Thermistor Mount, -20 to +10 dBm, 33-50 GHz	\$650.00
HUGHES 45773H-1100 WR19 Thermistor Mount, -20 to +10 dBm, 40-60 GHz	\$750.00
HUGHES 45774H-1100 WR15 Thermistor Mount, -20 to +10 dBm, 50-75 GHz	\$600.00
HUGHES 47316H-1111 WR10 Tuneable Detector, 75-110 GHz, positive polarity	

HUGHES 4771H-2310 WR28 Phase Locked Gunn Osc., 32.000 GHz, +18 dBm	\$2,000.00
HUGHES 47742H-1210 WR22 Phase Locked Gunn Osc., 42.000 GHz, +18 dBm	\$2,750.00
KRYTAR 201020010 Directional Detector, 1-20 GHz, SMA(f)/SMC	\$200.00
KRYTAR 2616S Directional Detector, 1.7-26.5 GHz, K(f)/m/SMC	\$200.00
M/A-COM 3-19-300/10 WR19 Directional Coupler, 19.5 dB, 40-60 GHz	\$450.00
MICA C-121506 Circulator, 17.5-24.5 GHz, SMA(f)/m/m	\$75.00
MINI-CIRCUITS ZFDC-20-4 Directional Coupler, 19.5 dB, 1-1000 MHz, SMA(f)	\$25.00
NARDA 3000-SERIES Directional Couplers	\$150.00
NARDA 3020A Bi-Directional Coupler, 50-1000 MHz, N	\$475.00
NARDA 3024 Bi-Directional Coupler, 20 dB, 4-8 GHz	\$375.00
NARDA 3090-SERIES Precision High Directivity Couplers	\$225.00
NARDA 368BNM Coaxial High Power Load, 500 Watts, 2.0-18 GHz, N(m)	\$500.00
NARDA 3752 Coaxial Phase Shifter, 0-180 deg./GHz, 1-5 GHz	\$1,000.00
NARDA 3753B Coaxial Phase Shifter, 0-55 deg./GHz, 3.5-12.4 GHz	\$1,000.00
NARDA 4000-SERIES SMA Miniature Directional Couplers	\$75.00
NARDA 4226-10 Directional Coupler, 10 dB, 0.5-18.0 GHz, SMA(f)	\$275.00
NARDA 4227-16 Directional Coupler, 16 dB, 1.7-26.5 GHz, 3.5mm(f)	\$325.00
NARDA 4242-20 Directional Coupler, 20 dB, 0.5-2.0 GHz, SMA(f)	\$100.00
NARDA 4247-20 Directional Coupler, 20 dB, 6.0-26.5 GHz, 3.5mm(f)	\$200.00
NARDA 4247B-10 Directional Coupler, 10 dB, 6.0-26.5 GHz, 3.5mm(f)	\$200.00
NARDA 5070-SERIES Precision Reflectometer Couplers	\$300.00
NARDA 562 DC Block, 10 MHz-12.4 GHz, 100 V max., N(m/f)	\$65.00
NARDA 765-10 10 dB Attenuator, 50 Watts, DC-5 GHz, N(m/f)	\$165.00
NARDA 791FM Variable Attenuator, 0-37 dB, 2.0-12.4 GHz	\$600.00
NARDA 792FF Variable Attenuator, 0-20 dB, 2.0-12.4 GHz	\$375.00
NARDA 794FM Direct Reading Variable Attenuator, 0-40 dB, 4-8 GHz	\$375.00
OMNI-SPECTRA 2085-6010-00 Crystal Detector, 1-18 GHz, negative polarity, SMA(m/f)	\$50.00
PAMTECH KYG1014 WR42 Junction Circulator, 18.0-26.5 GHz	\$250.00
SONOMA SCIENTIFIC 21A3 WR42 Circulator, 20 dB, 20.6-24.8 GHz	\$75.00
TEKTRONIX 2701 Step Attenuator, 0-79 dB, DC-1 GHz, AC or DC coupled	\$175.00
TRG B510 WR22 Direct Reading Attenuator, 0-50 dB, 33-50 GHz	\$900.00
TRG V510 WR15 Direct Reading Attenuator, 0-50 dB, 50-75 GHz	\$900.00
TRG V551 WR15 Frequency Meter, 50-75 GHz	\$600.00
TRG W510 WR10 Direct Reading Attenuator, 0-50 dB, 75-110 GHz	\$1,000.00
TRG W551 WR10 Frequency Meter, 75-110 GHz	\$750.00
WAVELINE 100080 WR28 Terminated Crossguide Coupler, 30 dB	\$200.00
WEINSCHIEL 150-110 Programmable Step Attenuator, 0-110 dB, DC-18 GHz, SMA	\$450.00
WEINSCHIEL DS109 Double Stub Tuner, 1-13 GHz, N(m/f)	\$150.00
WEINSCHIEL DS109LL Double Stub Tuner, 0.2-2.0 GHz, N(m/f)	\$150.00

## COMMUNICATIONS

HP 3780A Pattern Generator / Error Detector, 1 kb/s - 50 Mb/s	\$850.00
HP 4935A Transmission Impairment Measuring Set	\$600.00
HP 59401A HP1B Bus Analyzer	\$375.00
MICRODYNE 1200MR 215-320 MHz Telemetry Receiver, PSK modulation	\$450.00
TEK 1410R NTSC Gen. w/SPG2 sync. generator, TSG7 color bars	\$800.00
TEK 1411R PAL Gen. w/SPG12 sync. TSG11 color bars; TSG13 linearity	\$750.00
TEK 1411R PAL Test Gen. w/SPG12, TSG11, TSG13, TSG15, TSG16	\$1,000.00
TEK 1411R PAL Test Gen. w/SPG12, TSG11, TSG12, TSG13, TSG15, TSG16	\$1,100.00
TEK 1411R-opt.04 PAL Test Gen. w/SPG12, TSG11, TSG13, TSG15, TSG16	\$1,400.00
TEK 147A NTSC Test Signal Generator, with noise test signal	\$800.00
TEK 148 PAL Insertion Test Signal Generator	\$700.00
TEK 520A NTSC Vectorscope	\$750.00
TEK 521A PAL Vectorscope	\$750.00

## MISCELLANEOUS

EG&G / P.A.R. 5302 / 5316 Lock-in Amplifier, 100 mHz-1 MHz, GPIB / RS232C	\$2,250.00
FLUKE 2180A RTD Digital Thermometer	\$500.00
P.A.R. 5206-95, 98 Two-Phase Lock-in Amp., 2 Hz-100 kHz, GPIB	\$1,500.00
TEK TM5006 5000-series 6-slot Programmable Power Module	\$500.00
TEK TM504 500-series 4-slot Power Module	\$175.00
TEK TM506 500-series 6-slot Power Module	\$250.00
TEK TM515 500-series 5-slot Traveller Power Module	\$250.00



# ELECTRONICS *Q & A*

With TJ Byers

In this column, I answer questions about all aspects of electronics, including computer hardware, software, circuits, electronic theory, troubleshooting, and anything else of interest to the hobbyist.

Feel free to participate with your questions, as well as comments and suggestions.

You can reach me at:  
**TJBYERS@aol.com**  
 or by snail mail at  
 Nuts & Volts Magazine,  
 430 Princeland Ct.,  
 Corona, CA 92879.

## What's Up:

Need to fix a bunch of monitors or power supplies? Not a problem, it's probably a common component.

Capacitive ESR revisited, and a nudge about vacume tubes. More to come on valves next month. Finally, Mars as art — 25,000 photos on the web as eye candy.

### Shrinking PC Monitor

**Q** - I have acquired several late model 15-inch super VGA monitors recently, and many of them exhibit a common problem. The picture is usually pulled in at the sides, and sometimes at the top and bottom as well. These monitors use software pots for adjustments, but I believe the problem is deeper than that. Usually a capacitor in the horizontal or vertical circuitry is the culprit, but without a schematic, I have little to go by. Do you know of a source of published information that is available without having to be a retailer or dealer?

**Dave Frechette**  
via Internet

**A** - Schematics for PC monitors are available from Sams Photofact (1-800-428-7267; [www.hwsams.com](http://www.hwsams.com)). If your particular model isn't listed in their catalog, use a schematic from a model of the same screen size and same manufacturer. While the PCB layout may not be the same, the electronics should be nearly identical (e.g., similar schematics).

From the symptoms you describe, I can make a good guess as to what the problem is. You're right, it's a capacitor — but not in the horizontal or vertical circuits. The culprit is an open capacitor in the low-voltage power supply. You see, there are several capacitors in the main power supply section, so if one goes open it doesn't shut down the monitor. Instead, it lowers the output voltage which results in lower HV and a smaller image all around. For this fix, you don't need a schematic. Simply locate the low-voltage filter caps (probably a few hundred uF rated at 180 volts) and bridge a good capacitor of similar value across each in succession until the screen expands to full size. That will be the defective cap. After a few monitors, you'll probably notice a pattern, in that the same capacitor will be the defective one. Be careful! Even though it's called a low-voltage power supply, the voltages are lethal and not isolated from the AC line.

### Shrinking AT Power Supply


**Q** - I'm an electronic technician who has acquired several defective AT switching power supplies rated at 230 watts. The only problem is that the +12 volts is low. Where could I find a representative schematic for one of these power supplies?

**John Najvar**  
via Internet

**A** - Chances are you can't. This was one of the best-kept secrets of the PC industry, where it was nearly treasonous to even acknowledge you had possession of such a document. Nonetheless, most were pretty straightforward with a few innovations here and there. In the Sept. '96 issue, I did an in-depth article on "PC Power Supply Repair." You can still order that issue through our website at [www.nutsvolts.com](http://www.nutsvolts.com).

But from the information you've given me, I can tell you where to start looking. First of all, only the +5V line is regulated. None of the other output voltages are regulated, for good reason. This is a consumer (not military) switching power supply, and costs have to be kept down. As it turns out, the only output that's critical is the +5V line, which has to be maintained in a narrow range of 4.75 to 5.25 volts —  $\pm 5\%$ , or better. Although the other voltage outputs are unregulated, most PC AT

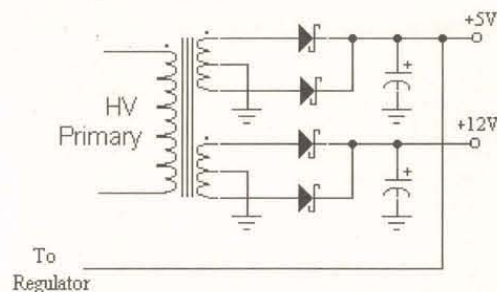switching supplies have their other output currents balanced so that these output voltages seldom veer more than 10% from normal. So, if the +5V line is within tolerance, it means the problem is exclusively in the 12-volt circuit, shown below.



My first thought is that if you have a bunch of these 230W power supplies, they are probably from the same vendor — and it's a good bet that the vendor bought a batch of cheap filter caps from one source. Suspect #1: One or more bad filter caps. Jumper the caps with a good capacitor of equal value and see if the voltage increases or not. A significant increase is a bad cap. Suspect #2: A leaky diode. These come as a pair in one package, and need to be replaced as such. Suspect #3: The power supply can't provide the current your load is putting on it — it may be dragging it down to the point where it can't deliver the goods. If this is the case, you can try increasing the value of the output caps and lower the current demands on one of the other supplies. Just because it's labeled as 230 watts, it's not really. Add up all the output currents and voltages listed, and you'll see it exceeds the "claimed" 230W. Power supply manufacturers rate the 230 watts on "typical" usage. If it still doesn't work, toss it.


### Lights-On Reminder

**Q** - I live in Florida, which has more than its fair share of rain, and drive a Toyota pick-up truck. My problem is that I way too often forget to turn off the headlights after driving in the rain. So far I have completely depleted two batteries and it's becoming very expensive.

If I could impose upon you, I would like a circuit that would audibly warn me when the lights are on and the engine is off.

**Ted Mylenbusch**  
Keystone Heights, FL

**A** - Sure, and here it is:

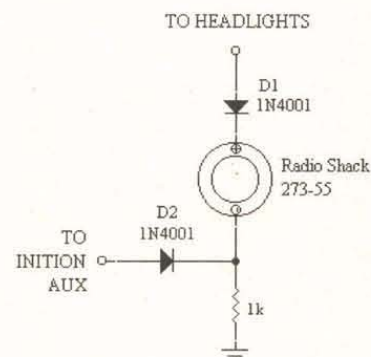

Back in the days of old, this would be called a logic circuit, as in the diodes are steering the beeper's current. When both the ignition and the headlight inputs are high, the beeper is essentially shorted out by D2. The alternator is charging the battery, and you have lights up front. Both diodes are forward biased. Turn the ignition off, though, and it's another story. Now, the 1k resistor has no place to go but to ground, which activates the beeper. Translated, if both HEADLIGHTS and IGNITION AUX are high, you have an AND gate. Both




inputs have to be high for the output to be high, and no buzzer. When the lights are on and the key is off, the siren starts screaming its head off.

## Hit The Ground Running


**Q** I've been studying electronics as a hobby for the last few years, and something has always bugged me. In the battery-operated circuits, I noticed that only the positive voltage is shown as the input voltage. What should I do with the negative half of the voltage from the battery? Should the negative voltage be sent to ground?

Wayne C. Green, Jr.  
via Internet


**A** Let me see if I can put this in a context that covers both battery and line-operated power sources. Electronics operates on the principle of current flow, which means electrons flows from the negative terminal of a power source to the positive terminal. (I know the flow seems backwards, but blame it on Ben Franklin, who guessed wrong when lightning knocked him down instead of up). So here's how it looks schematic-wise.

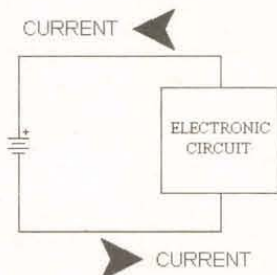

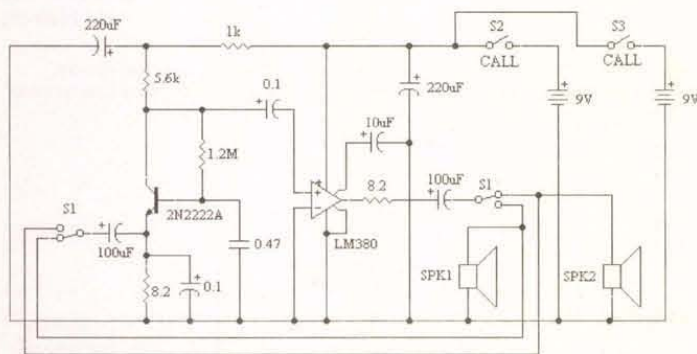Now let's expand the electronic circuit part to be ... how about a "Two-Way Intercom?" Here's the original circuit.



And this is how it looks after cleaning up the negative half of the circuit into the GND symbol. Same circuit, same results, but cleaner-looking. Why does the negative go to ground? Because of lightning! Just kidding — it's because it makes sense. If one wire is grounded — planted into earth — that means the risk of electrical shock is reduced by 50%. So in answer to your question, wire your negative battery terminal to ground, which is a common line.

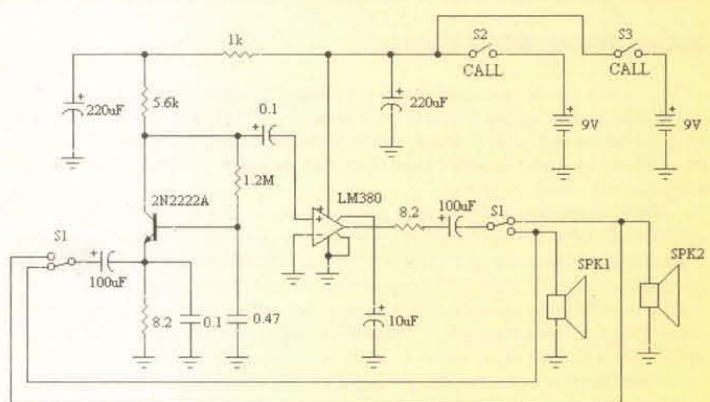

Before I go, I have to stress an important point — ground loops. One of the reasons grounds are shown as a symbol and not a wire is because a wire can generate what's commonly called a ground loop. That is, ALL the current sinks to this point, and like all resistive devices, a ground wire has voltage drop across it, which can lead to instability in a circuit. To avoid this situation, it's recommended that you pick a spot — any spot — on the finished project that you call GND, to which all ground wires terminate. Period, literally. A single point, and you'll never have a ground loop.

## Can a 5881 Turbocharge a 6L6 Amp?

**Q** I was recently told by a friend that I could turbocharge my guitar amp by replacing the 6L6's with 5881 or KT88 vacuum tubes. I checked a tube chart at [www.nostalgiaair.org](http://www.nostalgiaair.org) and found the pin layouts were the same. However, I couldn't compare their electrical characteristics because none were given for the 6L6 tube. I'd appreciate any guidance you could provide on this topic.

Al Lovecky  
via Internet

**A** You're right, there are no specs for the 6L6 at this site, but simply plugging in a new tube won't turbocharge your amplifier. Why? Because the circuit parameters are the same, so the output wattage will be the same. To gain more performance from a tube upgrade you have to:

- Increase plate voltage.
- Normalize grid bias for the new operating curve.
- Make sure your output transformer can handle the extra power.

Unless you can make *all* these changes, nothing will improve. And unless you know how to shift the bias properly, you can easily end up with less performance than you have now. My suggestion: buy a bigger amp or seek the help of a professional tube guy, not the advice of a fellow musician. BTW, the 5881 is identical to the 6L6GC. Here's a chart showing the difference between them.

Parameter	6L6	6L6GC	5881	KT88
Plate voltage	360	500	500	560
Screen voltage	19	30	30	50
Heater current	270	450	450	450
	0.9	0.9	0.9	1.6

## PRINTED CIRCUIT BOARDS

QUALITY PRODUCT

FAST DELIVERY

COMPETITIVE PRICING

We will beat any competitor's prices!!!

- \* UL approved
- \* Single & Double sided
- \* Multilayers to 8 layer
- \* SMOBC, LPI mask
- \* Reverse Engineering
- \* Through hole or SMT
- \* Nickel & Gold Plating
- \* Routing or scoring
- \* Electrical Testing
- \* Artwork or CAD data
- \* Fast quotes

10 pcs (3 days) 1 or 2 layers \$249

10 pcs (5 days) 4 layers \$695

(up to 30 sq. in. ea.) includes tooling, artwork, LPI mask & legend

PROTOTYPE THROUGH PRODUCTION

**PULSAR, INC**

9901 W. Pacific Ave.  
Franklin Park, IL 60131

Phone 847.233.0012

Fax 847.233.0013

Modem 847.233.0014

yogii@flash.net · flash.net/~yogii

Write in 36 on Reader Service Card.

## SATELLITE TV — HACKERS 'BIBLE'!

### The SECRETS are REVEALED!

- The principles of security
- Descrambler building blocks
- Smart cards, information wars & stupid mistakes
- Cracking codes (includes DirecTV source code)
- Installing and hooking up descramblers
- Video manipulative systems...and much more...


**www.baylin.com**  
or... call 800-483-2423

ORDER via Internet or Send \$60 plus \$5 s/h to:

Baylin Publications, 1905 Mariposa, Boulder, CO 80302

MASTER, VISA & AMEX / COD orders accepted

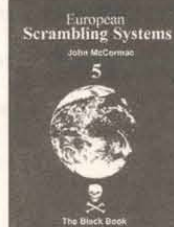**FREE CATALOG — Satellite TV books, videos and software**



576 pages, 6" x 8-1/2"

**NEW!**  
5th Edition

Telephone: 303-449-4551  
FAX: 303-939-8720

Write in 37 on Reader Service Card.

Nuts & Volts Magazine/AUGUST 2000 27



## Mmm, Mmm Good Power

**Q** I made a power supply to run an AT-style motherboard inside my car. The power supply converts +12 volts to +5, +12, and -12. But when I plug my homemade power supply into the motherboard and turn on the power, nothing happens until I close and then open the reset pins. The motherboard then boots properly.


When I connect a desktop AT power supply to the motherboard, it boots up normally without requiring the reset pins to be closed and then opened. If I remove the Power Good (orange) wire from the AT power supply, the motherboard won't boot until I close/open the reset pins. It appears that the problem with my homemade power supply lies with the Power Good signal. I tried tying this line to the +5-volt lead from my power supply, but the motherboard still doesn't boot without the reset maneuver.

What exactly does the motherboard expect from the Power Good line and how do I simulate that in a homemade power supply?

**Tom Paciorkowski**  
via Internet

**A** When the power supply is first turned on, it takes time for the electronics to settle down. It takes a finite time for the filter caps to charge up, the semiconductors to kick in, and the output voltages to settle down. Typically, it takes between 100 mS and 500 mS before the power supply outputs are within tolerance, depending on the particular unit, and the Power Good line goes high — the cue for the motherboard to power up.

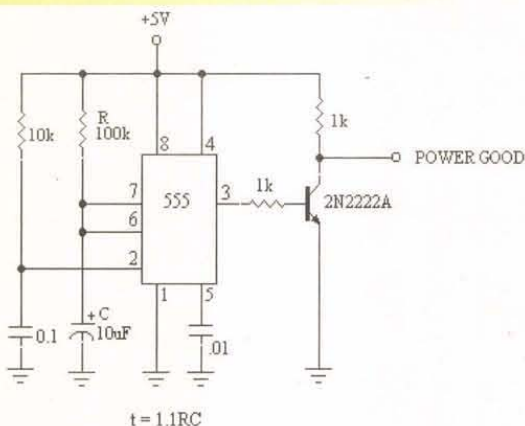In the AT power supply, this is accomplished using comparator circuitry that guarantees the +5-volt output is within tolerance before applying the Power Good signal. You can do the same thing with your home-built power supply, but this circuit is simpler.



It's basically a one-second delay timer built around a 555 chip. When 5 volts is applied to the chip, the output (pin 3) goes low. After a time determined by C and R, the output goes high and stays high until you shut off the power supply. This output drives a 2N2222A transistor that connects to the Power Good input of the motherboard, which will now boot up properly. The values shown are for a delay of one second, which should be plenty of time for your power supply to settle in. However, you can adjust that period up or down by increasing or decreasing the value of R, respectively; the formula is shown on the schematic.

For you musicians and audiophiles, here's another good source for select-tube types: [hereford.ampr.org/cgi-bin/tube](http://hereford.ampr.org/cgi-bin/tube).

I'm presently looking at a software application that may satisfy all tube lovers' needs. Stay tuned, most likely next month.

## Correspondence Studies

**Q** I am interested in taking a correspondence course in computer servicing. I've been looking for ads for these schools without success. There used to be many, such as NW, Coyne, NRI, etc. Are they all out of business?

**Arden Ebert**  
via Internet

**A** Without real hands-on experience and video feedback, it's difficult to effectively learn computer repair from afar using just textbooks. Consequently, most electrical/radio correspondence schools have been replaced with on-line courses and self-study video tapes. Some of the on-line courses send you a PC to play with, but most rely on visuals and diagnostic tools that are either mailed to you or downloaded from their web site. Prices

and course contents vary widely, so it pays to shop around. Here's a short list of places to get you started.

## Correspondence Schools

**NRI**

<http://www.mhcec.com/courses.htm>

**ICS Learning Systems**

<http://www.icslearn.com/ICS/courses.htm>

**Foley-Belsaw Institute**

<http://www.computerrepairschool.com/>

## Online Courses

**Professional Career Development Institute**

<http://www.pcdi-homestudy.com/courses/jj/>

**INTEC College — Distant Education**

[http://www.intec.edu.za/educ/dist\\_edu.htm](http://www.intec.edu.za/educ/dist_edu.htm)

**Oliver Worldclass Labs**

[http://www.oliverlabs.com/comp/pc\\_repair.htm](http://www.oliverlabs.com/comp/pc_repair.htm)

## Self-Study

**Specialized Solutions**

<http://www.quickcert.com/a-plus.htm>

**Marcraft**


<http://www.mic-inc.com/mc.htm>

## Simpler ESR Meter


**Q** I read with interest your response in the June 2000 column to the question of measuring ESR in an electrolytic capacitor. For me, this is overkill. I don't need to measure the electrolytic in circuit — in fact, most are in my junkbox. The capacitance meter says they are within tolerance, but I wonder about their ESR because the last two I tried as replacements didn't fix the ripple problem. Do you have anything in the way of a simpler ESR meter?

**Carl Peterson**  
via Internet

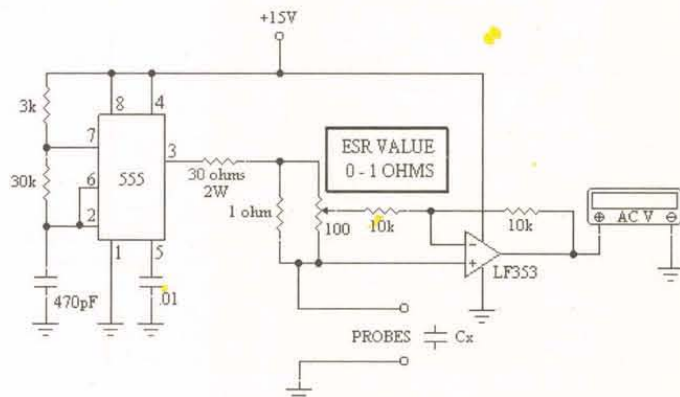**A** Just so happens that I have one in the hopper — one that almost made it to the June issue except for limited space. So thank you for asking, and here you are.



This instrument uses a low-cost DMM or analog multimeter display. As mentioned in the last column, the ESR (Equivalent Series Resistance) of a capacitor can be measured using an AC voltmeter. This AC voltmeter consists of a balanced bridge-like circuit, where the ESR of the capacitor under test is compared to the resistance of a potentiometer. The 555 chip functions as a 50-kHz squarewave generator. A current of about 180 mA is forced through the capacitor under test. When the ESR VALUE pot is adjusted to the same resistance value as the capacitor's ESR, the output voltage drops to a null. The dial is calibrated in ohms — 0 to 1.00 — and the ESR value can be directly displayed by looking at the position of the knob.

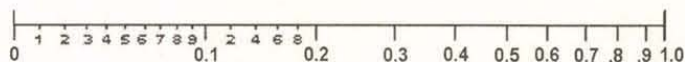

To make a measurement, adjust ESR VALUE until  $V_{out}$  nulls out — it doesn't have to dip to zero, just the lowest point. Read the setting and that's the ESR of the cap under test. This tester is designed for use with capacitors of 100 µF or greater, where the ESR value is less than 1 ohm. Here's a handy reference guide. Just remember the values are typical for computer grade capacitors, and may not be the values found in standard aluminum types. In



other words, a RadioShack 1,000 uF cap with an ESR of 0.9 ohms isn't defective.

Capacitance Value	ESR Value (ohms)
100 uF	1.0
500 uF	0.5
1000 uF	0.1
5000 uF	0.05
10,000 uF	0.01

Because most values fall under 0.1 ohm, I've used a log taper (also called audio taper) potentiometer for more precise measurements. Just make sure that you use a good quality slider pot, and insert it into the circuit with the tapered end above ground (pointing up on the schematic).

## MAILBAG

Dear TJ:

In my experience, the quickest way to diagnose a dried-out electrolytic is to bridge it with a known-good capacitor of at least half its marked capacitance and at least the same working voltage. In practice, a 100 uF, 50V capacitor and a 40 uF, 450V capacitor were all I needed to diagnose almost all my ills.

Dear TJ:

The impedance of the headphone amp, page 62 Apr. '00 issue, is not 600 ohms as implied in the emitter follower. Unlike a tube whose plate impedance is high, the impedance of an emitter follower is the base resistance divided by the transistor gain in parallel with the load resistor (guessing <50ohms). The circuit will still work as intended, but it might mislead readers into thinking that the emitter resistor is matching the impedance.

Paul Futscher  
Willits, CA

Dear TJ:

Just received my Apr. '00 issue and stopped at the answer to G. Lehmann about connecting an eight-ohm headset to his Drake receiver. Although the circuit you suggest is admirably biased in the linear region, I can only see

## Cool Web Sites

Portrait of a planet; art from mars.  
mars.jpl.nasa.gov/mgs/msss/camera/images/may\_2000/index.html  
mars.jpl.nasa.gov/mgs/msss/camera/images/index.html

about 1 mA peak-to-peak into an eight-ohm load before serious distortion occurs. This works out to be about 1 microwatt RMS. I didn't catch where he wanted the ear-phones to be used by his dog. Notwithstanding the folklore of the cathode follower having some similarity, don't forget there was a great deal more Class-A power going on in the tube circuit than your "equivalent" circuit is showing. A matching transformer is really the most practical solution, albeit mundane. Audio power is what we are listening to, not voltage similarity across the terminals.

W. Chou  
via Internet

Response:

It's a typo. The value should be 60 ohms, not 600. I wrote this column while in Trinidad using Paint Shop Pro on a small notebook PC (didn't have my CircuitMaker schematic capture software), and viewing conditions weren't always the best. Fortunately, 600 ohms will work kinda, so it's not a total loss. Sorry for the mistake, and thanks for pointing it out.

TJ Byers  
Q & A Editor

## Order Today!



### "PROGRAMMING AND CUSTOMIZING BASIC STAMP COMPUTERS" by Scott Edwards

Build smart electronics projects with the inexpensive, simple-to-use, surprisingly powerful BASIC Stamp.

**ONLY \$34.95**

As a paid subscriber to *Nuts & Volts*, you'll receive **10% off the list price!!**

(See ad on page 4 for ordering details and other titles currently available.)

## Polaris can supply you with all of today's Hottest Video Technology, Micro Cameras to Professional Security Supplies

Color video camera  
Power/Video cable  
330 TV Lines  
3.6mm Lens  
LP-850c  
\$179.95

Color & weatherproof  
Power/Video cable  
4.3mm Lens  
WP-300c \$229.95

1" (Dia.) x 2.4" (L) w/o stand

Weather Proof

LP-850w  
\$169.95

Weather Proof

Built-In Infrared  
Illuminator, Camera  
can See in the Dark  
without Additional  
Light Source!

Color 400 TV Lines  
Power/Video cable  
Lens: C-mount  
Auto Iris  
TC-300ux  
\$229.95

Length: 1.3" Diameter: .8"



LP-850p \$179.95

Length: 1.9" Diameter: .9"

LP-850l \$109.95
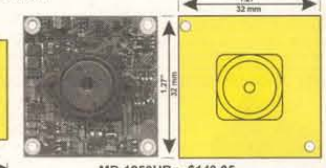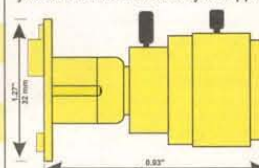
### 470 TV Lines Color "Micro-Zoom" Video Board Camera

470 TV Line Color Board Cameras. Technology has added high resolution to its smallest cameras. We've added a Vari-Focal lens to an already powerful board camera. The 4-8mm Vari-focal lens is a tool you won't be able to live without once you added this camera to your application.



MB-1250HRP \$149.95

- MB-1250HRVF \$199.95  
470 Hi-Res Vari-Focal Color Camera
  - MB-1250HRP \$149.95  
470 Hi-Res Pinhole Color Camera
  - MB-1250p \$99.95  
350 Low-Res Pinhole Color Camera (not pictured)
- MB-1250HRP & MB-1250p  
Same physical look two resolution options to choose from: 470 or 350 TV lines.

MB-1250HRVF \$199.95

### Flat Screen TFT-LCD Monitors

TFT-4 \$209.95  
Color 4" Screen.  
(Size: 6" (W) x 4.5" (H) x 2" (D))  
An excellent 4" monitor for one camera monitoring or for setting up cameras during installation or maintenance.



COLOR  
5.6" TFT  
and  
6.4" TFT  
Monitors

TFT-5.6 \$429.95  
TFT-6.4 \$479.95  
(includes: patch cable & power supply)

### Wireless Video

GW-2400S - \$449.95  
Includes: 2.4 Ghz  
Color Wireless  
Camera.  
Receiver with  
Built-In Monitor.

GW-2400 \$229.95

- 1 - 4 Transmitting Channels.
  - Can be integrated with other wireless applications.
  - Up to 985 ft. Operating Distance.
  - Dimensions: 2.5" (W) x 2.18" (H) x 3.28" (D)
- Video/Stereo Audio

GM-2400  
\$269.95  
(Monitor/Receiver)

Transmitter

Receiver




Free  
Polaris  
Video  
Catalog

CM-500CBC, A tough aluminum  
cased Color CMOS camera with  
mounting bracket. BNC video &  
barrel power connection for Plug &  
Play hook-up. View through  
standard VCR or Monitor!

- 1/3" Color CMOS
- 380 - TV Line
- 1 LUX
- Lens 3.6 mm
- Auto Iris

CM-500CBC  
\$129.95

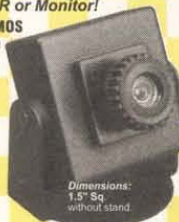

Dimensions:  
1.5" Sq.  
without stand.

### CMOS C-Mount B/W & Color Cameras



(Comes with a 3.6mm lens. Shown)



(Comes with a 3.6mm lens B/W model comes with stand)

(C-Mount option w/o 3.6mm lens)

B/W Camera: CM-220 \$69.95  
Color Camera: CM-220c \$139.95

The CM-220 & CM-220c are truly  
outstanding performance cameras with  
380 Line Resolution & C-Mount options.

Polaris Industries  
<http://www.polarisusa.com>

**1-800-752-3571**

470 Armour Drive NE • Atlanta GA 30324-3943 • Tech Info 404.872.0722 • FAX 404.872.1038

Write in 33 on Reader Service Card.

Nuts & Volts Magazine/AUGUST 2000 29



**ULTRA MINI AND WEATHERPROOF, "LIPSTICK"**  
Sleek black anodized, alum. housing. O-Ring sealed & RAINPROOF. Adj. tilting mount. 1/3" CCD, 380 Lines, 0.3 Lux, AGC, Auto Shutter. 9-12VDC @100mA, 4mm, f1.8, 78° FOV real glass lens, NTSC video. <100µm IR SENSITIVE. 23mmx50mm, 36" cable with BNC video & DC barrel jack. GM-200K, PINHOLE Model. So tiny you can install it directly into a door. Only a 0.9" diameter hole! Specs as above. 90° FOV Pinhole lens. 1/2 ounce! Size only 23mm x 35mm long. Think of the places you could put this little jewel.  
**LOOK! SPECIAL MAY PRICE, GM-200KSTD...\$69**  
**LOOK! SPECIAL MAY PRICE, GM-200KPH...\$69**

**SALE ON ALL TYPES OF COVERT CAMERAS, all available with audio.**  
Specification for all models include: 1/3" CCD, 410 Lines Res., 0.3 Lux sensitivity, Power from 9 to 12VDC @100mA, 90° FOV lens except dome and PIR which are 80°, All focus from 2 ft. to infinity. Standard NTSC video out. SENSITIVE to IR. note: Smoke & Motion detectors not functional. Clock & Exit operate normally. Dome is 3.5"H x 5.5"Diam. Don't see what you want? We can put a camera in anything you desire.



Smoke Det., Motion Det., Clock or Dome Camera, Special...\$69ea.  
Exit Sign, Special...\$79ea. Please add \$10 for audio. (any model)

**WORLD'S SMALLEST**  
...100mW...  
**VIDEO TRANSMITTER, ON SALE**  
Incredibly only 0.9" x 0.8" x 0.37" Transmits crystal controlled hi-res. images with 100mW output! The transmitter you've been waiting for. Shown actual size. Much smaller than the 9V battery which powers it. Draws only 35mA! Factory tuned. Receive on cable channel 59. Will work with color or B&W cameras. UHF Bow tie antenna with balun and 3' cable for TV included. Perfect with our GM1000A. **SPECIAL TVX-100...\$159 with GM1000A CAMERA...\$209**

**NEW, 9" SECURITY MONITORS**  
We were fortunate to obtain these Hi-res 700 Line. B&W units. Original manufacturers boxes, 90 day warranty. BNC video in and loop through. Rugged steel case. Current production model. Limited qty. They will make your video look super!  
**SPECIAL...\$119.00ea. 2 for \$229.00**

**TEKTRONIX 2465, 4 Chan., 300MHz, O'Scope,**  
With on screen waveform stats  
One of the most popular & powerful scopes available at a reasonable cost. Features: 500ps/Div sweep, 2mV/Div vertical sensitivity, 1Mohm / 50-ohm input, 500MHz trigger bandwidth, four channels. On-screen waveform cursors provide vert. & horiz. scale factors, trigger level, voltage, time, freq., phase, ratio values and mode indication. Complete with 2 probes, and manual. Excellent condition. 90 day warranty. **Very Ltd. Qty...\$1295.**

**TEKTRONIX 2445, 4 Chan., 150MHz, O'Scope,**  
With on screen waveform stats  
One of the most popular & powerful scopes available at a reasonable cost. Features: 500ps/Div sweep, 2mV/Div vertical sensitivity, 1Mohm / 50-ohm input, 500MHz trigger bandwidth, four channels. On-screen waveform cursors provide vert. & horiz. scale factors, trigger level, voltage, time, freq., phase, ratio values and mode indication. Complete with 2 probes, and manual. Excellent condition. 90 day warranty. **Very Ltd. Qty...\$1295.**

**NEW, "COLOR STEALTH CAM", MICRO SIZE, with AUDIO!**  
That's right! COLOR! In the same size package too! Sleek aluminum housing fits like a glove! Removable mtg. bracket & a 1.3M cable with BNC vid., RCA aud., internal mic & DC pwr. jack for, no sweat hook up. Why fool around with an open P.C. board? Now you can have the "COLOR STEALTH CAM".  
• 1/3" • 350 Lines  
• Auto Shutter  
• 270k pixels  
• Focus 10mm to inf.  
• 1 ounce!  
• 0.7 Lux • AGC  
• Pwr 6-12V @30mA  
• Std. 7 mm, 56° FOV lens  
• NTSC video  
• Size: 31mm sq. x 28mm d.  
**GM-4000S-STD w/audio SPECIAL \$89ea.**

**B & W "STEALTH CAM", MICRO SIZE, with AUDIO!**  
The sleek aluminum housing fits like a glove! Removable mtg. bracket & a 1.3M cable with BNC vid., RCA aud., internal mic & DC pwr. jack for, no sweat hook up. Why fool around with an open P.C. board? Now you can have the "STEALTH CAM".  
• 1/3" • 350 Lines  
• Auto Shutter  
• 270k pixels  
• Focus 10mm to inf.  
• 1 ounce!  
• 0.7 Lux • AGC  
• Pwr 6-12V @30mA  
• Std. 7 mm, 56° FOV lens  
• NTSC video  
• Size: 31mm sq. x 28mm d.  
**GM-4000S-STD w/audio SPECIAL \$89ea.**

**NOW YOU CAN SEE WHAT THE "FISHES ARE DOIN' (down 60 ft.) UNDERWATER B&W CAMERA with INTERNAL, INFRARED ILLUMINATOR!**  
Sleek black anodized, BRASS, housing. O-Ring sealed & WATERPROOF. Adjustable mount incl. Specs: 1/3" CCD, 400 Lines res., 0.05 Lux sensitivity, AGC, Auto Shutter. 12VDC @225mA, 4mm, 78° FOV lens, A real glass lens. NTSC video out. Superior construction. SENSITIVE to IR.  
Ultra small Size only: 1.25" diam. X 2" long. With 60 ft. cable. Perfect as a remote area inspection camera. Great for general outdoor use as well. **GM-300KIR...\$179**

**NEW! NOW YOU HAVE COLOR (down to 60 ft.) UNDERWATER.**  
Built-in WHITE LIGHT LED'S, Sleek black anodized, BRASS, housing. O-Ring sealed & WATERPROOF. Adjustable mount incl. Specs: 1/4" CCD, 350 Lines res., 0.5 Lux sensitivity, AGC, Auto Shutter. 12VDC @120mA, 4mm, 78° FOV lens, A real glass lens. NTSC video out. Superior construction. Ultra small Size only: 1.25" diam. X 2" long. With 60 ft. cable. Perfect as a remote area inspection camera. Now with six super bright, white LED'S! BRAND NEW.  
**GM-400KW-LED...\$219ea.**

**PORTABLE MINI PRINTER, 40 COLUMN, with INTERNAL NI-CAD POWER!**  
The model S0222-1000 is a NEW and very cool, self contained, alphanumeric, impact type printer. It features a standard parallel port and an internal Ni-Cad power supply. Can also be powered via the 9VDC power adapter supplied. Uses standard 2" wide paper rolls available everywhere. Has self test function and diagnostic mode. Can emulate Epson and Citizen 560. It will print from the LPT port of your PC. Very rugged and well made. Perfect for any remote printing or data logging application.  
Size: 8" L x 4" W x 3.5" H. **OUR PRICE...\$49ea. or 2 for \$75**

**Robotic Sample Processor, from Cavo Scientific**  
Bring your automated system up to speed with this Robotic Sample Processor. It is an XYZ module that is fast and flexible with user friendly software available. (NOT SUPPLIED) Install the RSP XYZ as the nucleus for your new system. Of course the system can be configured for many other motion automation applications as well. Your imagination is the key. Overall size: 31"W x 22"D x 7"H. X travel (dual long axis) is 22", the Y travel (dual short axis) is 12", the Z axis is limited only by the length of the rod inserted into the linear bearing unit. (user supplied). The module is supplied with dual arms as pictured, variable sensitivity liquid level sensing and encoders. The electronics support a number of auxiliary devices including diluters, valves, peristaltic pumps, sample racks and single, multichannel or cap piercing probes. Mix and match from different Cavo modules and build the system that fits your needs. The RSP can be controlled using a simple user interface. (We do not have the info). Software controls the arm movements and its accessories as well as performing diagnostics and data handling functions. For more information please see [www.cavo.com](http://www.cavo.com)  
**Robotic Sample Processor, RSP-XYZ...\$695ea.**

**END FIELD OF VIEW GUESSWORK! 3.5 to 8mm VARI-FOCAL LENS**  
Brand New, super f1.8 lens allows you to smoothly adjust from a 97° FOV @ 3.5mm to a 44° FOV @ 8mm. Now you can frame your area of interest just the way you want it! Standard CS-Mount with adjustable focus and iris. **SPECIAL...\$79ea. or 2 for \$149**

**SUPER, MINI C-MOUNT CAMERAS, Super sensitive, GM410 or the general purpose GM412, The GM-412 specs: B&W, size 1.5" sq. X 2.4", 250,000 Pixels, 380 Lines Resolution, Sensitivity 0.3 Lux, The GM410 specs: size only 1.5" sq. X 1.6" L, >270,000 Pixels, 410 Lines Res., Sens. 0.05 LUX, Both cameras are 1/3" CCD with AGC & Electronic shutter. 12V @100mA power. NTSC out. IR SENSITIVE, BNC video out. Both use std. DC pwr. jack. Aluminum housings with dual threaded top and bottom mounting. True performance not hype! These cameras will outperform ANY camera in this magazine. Multi-lens options are available to exploit their superior performance. GM412 shown bottom. GM410 shown top. Prices are less - c'mount lenses.  
**GM412...\$99, GM410...\$169****

**C-MOUNT LENS OPTIONS:**  
**LOW LIGHT:** 16mm, f1.6, 15° FOV .....\$39ea.  
8mm, f1.3, 40° FOV .....\$49ea.  
4mm, f1.4, 78° FOV .....\$49ea.  
**STANDARD:** 4mm, f2.0, 80° FOV .....\$24ea.  
6mm, f2.0, 60° FOV .....\$24ea.  
8mm, f2.0, 40° FOV .....\$24ea.  
12mm, f2.0, 28° FOV .....\$24ea.

**NEW! Low Cost MICRO CAMERAS,**  
1/3" CCD, 410 Lines Res., 0.3 Lux sens., AGC, Auto Shutter. Pwr. from 9 to 12VDC @100mA, 250k PIXELS, Std. model, 4mm, 78° FOV lens, Pinhole, 90° FOV. A real glass lens. Both focus from 10mm to infinity. Std. NTSC video out. 1/2 ounce! SENSITIVE to IR. Size: 1.25" sq. x 1" d. PH is 0.6" d. 1.6M long wiring harness with connectors included. WARNING: Don't confuse these models with LOW RESOLUTION, HIGH LUX C-MOS CAMERAS  
**GM-1000A-STD...\$59ea.**  
**GM-1000A-PH...\$59ea.**  
**GM-1000A-CMNT...\$59ea.**  
**Micro Lenses for GM1000 series**  
2.5mm, 150°, FOV, f2.0 .....\$22ea.  
8.0mm, 40°, FOV, f2.0 .....\$22ea.  
4.3mm, 78°, FOV, f1.8 .....\$22ea.  
6.0mm, 60°, FOV, f2.0 .....\$22ea.  
5.0mm, 70°, FOV, PH .....\$22ea.

**6V@12AH SEALED, RECHARGEABLE,**  
New Panasonic, LCR6V12PI. Tough to get at a discount. Very compact. Two top mounted 1/4" faston connectors. Perfect for high drain projects.  
Size: 5.9" L x 3.7" H x 1.9" D  
**2 for \$20, or 10 for \$89**

**IT WILL MOVE YOU! PRECISION, XY TABLE.**  
Long travel. Really nice and like new. (removed from a \$100K film scanner) Super X-Y table offers approximately 24" x 24" of travel. The system is shock mounted to a rugged tubular steel, wheeled base with a creme colored powder coat finish. Dual, heavy duty, Berger RDM-566-50, 1.3A, 1.40m stepper motors are attached. Heidenhain 500ppr encoder on one axis. Perfect for laser system. Overall size is 55" x 44" x 39" Ships via truck.  
**Sorry Last One...\$1295**

**WOW! COMPUMOTOR, 4000 MOTION CONTROLLER PLUS, TWO, SERIES LE, STEPPER MOTOR DRIVERS.**  
Motion, 1 to 4 axes of step & direction control. Accepts encoder position feedback. I/O. Optically isolated programmable inputs (24) and outputs (24) compatible with industry standard signal conditioning products.  
Features: 4000 Programmer/Operator Panel. Detachable can be mounted remotely. Dedicated jog function for each axis. Four-line, backlit, Liquid Crystal Display (LCD). Six soft-function keys labeled by the LCD change definition as needed. Sealed membrane keypad. Language, Simple BASIC-like motion control program language. No software supplied. Multiple programs may be entered and saved. Feedrate override allows operator interaction. Insert, edit, copy & delete functions. User-defined operator prompts. Linear interpolation on up to four axes. Teach mode uses analog joystick (not supplied) inputs or operator panel jog keys. Interface Capability. Remote programming capability over RS-232C and IEEE-488, remote program downloading and uploading. Second RS-232C port for operator messages or control of other devices. **Special System...COMP4000/LE...\$1495 Ltd.Qty.**

**DOVER AIR BEARING X/Y TABLE, is ULTRA PRECISE.** Like New. The ultimate in precision motion control. Leadscrew operated air bearing tables with 1-20 Microns typical repeatability. Straightness, <1 micron each axis, angular error, <1 arc/sec. Squareness, <5 arc/sec. Unit has 4"x5" travel with two Compumotor LE57-SI-MTR steppers attached. Ready to play with our Compumotor 4000 series system above. **DOVER-B45...\$949 with COMP4000/LE & cables \$2250**

**CO2, 120Watt CW, SEALED GLASS LASER HEADS**  
Integral Hard Sealed Mirrors, NEW!

High quality water cooled heads. Were originally designed for medical application. All models are similar in construction. Size of the model 103: 60" x 3.2" diam. Model 160: 44" x 3.2" diam. Model 135: 35" x 3.2" diam. Power requirement, model 103, 40KV trigger with 25KV @ 10 to 30ma operating current. Model 160 and 135, 30KV trigger with 15-20KV @ 7 to 20ma operating current. These are not toys. They must conform to Class IV CDRH regulations when assembled into a functioning system. Perfect for engraving, cutting and drilling most materials. Only three available. Only one 200W system. We don't expect any more.  
**Special 200W dual tube head with metal housing & dual power supply...\$4395.**  
**Limited Quantity...100+ Watts...\$1475., 35Watts...\$895.**

**SUPER SPECIAL OFFER, ACCESSORIES TO COMPLETE YOUR CO2 SYSTEM!**

**CO2 Power Supplies:** for 100Watt+ Tube...\$495ea. Supply for 35Watt Tube...\$399ea. 100W, power supplies are used, tested and guaranteed. 35Watt, power supplies are NEW! Supplies are not sold without laser tube purchase. Articulated beam delivery arm with focusing hand piece. Brand new. A fantastic item. Regular price - \$3500.00! With purchase of tube...\$895ea. Arm without laser tube...\$1295ea.

**A NICE ASSORTMENT OF CO2, and YAG OPTICS TO MAKE YOUR LIFE EASIER!**  
All NEW and factory boxed first quality, BK-7 glass or ZnSe.  
ITEM # NAME DESCRIPTION MISC.  
RPI0-02 RISLEY PRISM 1deg. AR @1064 & 540 to 650nm Alignment/multi wavelength path.  
RPI0-03 RISLEY PRISM 1deg. AR @450 to 650nm Alignment/multi wavelength path.  
BS10-01 BEAM SPLITTER AR @45deg for 1064nm YAG or CO2, High Power  
BS01-02 BEAM SPLITTER AR @45deg for 1064nm YAG or CO2, High Power  
DUAL-01 MIRROR/HT-HR HT @45deg for 532nm, HR for 1064nm High Power  
PLCV-01 DUAL FREQ LENS HT for 1064 and 632nm >98.5%, 113mm Focus CO2 & HeNe ZnSe.  
**Order by Item Number. All models priced at \$25ea. or 2 for \$39**

**10V @ 2.5 AH SEALED, LEAD ACID, PACK.** Each pack has 5 cells are arranged as 1X5 cells. Enclosed in an ABS outer shell. Removed for photo! Perfect for high drain applications. Make custom packs of any rating. Size: 7.5" L x 2.8" H x 1.5" D  
**SALE! 6-five packs for \$20, 40 for \$99**

**SECURE ON-LINE ORDERING**  
**WWW.RESUNLTD4U.COM**  
**RESOURCES UN-LTD.**  
VISA, MC, AMEX, DISCOVER, COD, ON-LINE  
ORDER: 800-810-4070 TECH:LINE 603-668-2499  
FAX: 603-644-7825 EMAIL [sales@resunltd4u.com](mailto:sales@resunltd4u.com)  
300 BEDFORD STREET, MANCHESTER, NH 03101



# The Hidden Sounds on Your Telephone Line

by ML Shannon

Have you ever thought about what might be happening on your telephone line while you are not using it? Probably not. After all, what could happen? Unless ... you start to wonder ... am I suggesting that someone might have tapped your phone?

No. At least not in the normal meaning of 'tap' where someone is monitoring your calls. If someone were, you probably wouldn't hear anything.

I refer here to the use of your line to make calls. And for testing purposes. Voices, sometimes, and exotic sounds like tones, chirps, rotary dialing clicks, analog data, and other noises are some of the sounds you will hear using the simple device described in this article. You can build it yourself for about \$10.00.

More on this coming up, but first a look at telephone systems and wiring. It may be in any of several configurations, so I will use my neighborhood in San Francisco as an example.

When you first have telephone service installed, a computer system called COSMOS, or Computer System for Mainframe OperationS will check your address to determine if there has previously been service there, and if so, the cable and pair numbers that were used. You are then assigned a number with a prefix in your area; a test is run to determine that the line is in working order, and the mainframe computer is programmed to turn on the Dial Tone. This may be at the Central Office (CO) or a technician may check the wiring at the other end, and from there request Dial Tone from the CO.

Now, your pair of wires begins its path to your phone from the

Central Office. Your line is ported from the 'switch' — the mainframe computer — to a distribution frame. The frame, at least with the more modern systems, holds a large number of small printed circuit boards — 'cards' — each of which controls about eight individual lines. The computer and the frame, are called OE — Originating Equipment.

Then your pair — along with many others — goes from the distribution frame into the cable vault, frequently located below ground level, and then into the outside world. Your pair may be within any of various different types and sizes of cable, but typically, it will be an F1 Feeder Cable with 1,200 pairs. This wiring, once it leaves the CO is called the Outside Cable Plant.

## Appearances

From the cable vault, there may be any number of appearances on your line, an appearance being a place where the line can be physically accessed. This includes:

### Junction Points

A Junction Point (JP) is an underground maintenance area located beneath the street and accessed through a manhole where you sometimes see several Telco trucks parked. The large 'accordion' tube you see provides fresh air as methane gas is sometimes present.

### Bridging Boxes

A 'B' or 'Bridging' Box — sometimes called Service Area Interface, which is usually located on a street corner or in an alley — is about three by five feet across and two feet deep.

### Splicing Boots


In some areas, phone wires are overhead on telephone poles called 'aerials' so the pairs will go to an Aerial Service Terminal also known as a 'splicing boot' at the top of the pole.

Eventually, your pair of wires

PHOTO 1



PHOTO 2

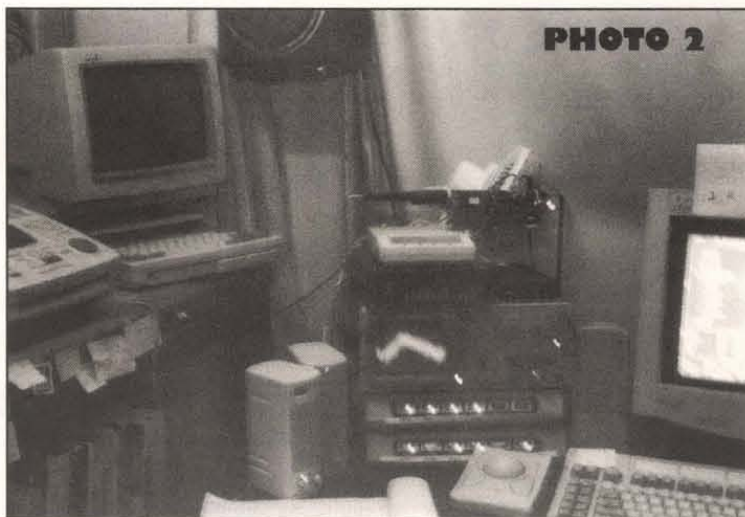

enters your home or apartment building one of two ways. Aerial wiring uses a Drop Wire that goes from the telephone pole to a small connection box on the outside of the building. Older types were an aluminum can about the size of a brick called a Single Pair Station Protector (SPSP) and newer types are plastic, called a Telephone Network Interface.

Underground wiring enters through a conduit and terminates at a panel often called a 66 block. The term '66' is, apparently, an old Bell System part number for a connection block with a 25 pair capacity.

Both of these are known as the

Point of Demarcation or usually just 'demarc.' Beyond that, the (inside) wiring is the responsibility of the building owner.

This wiring — your pair from the CO to your telephone — is called a Loop or Local Loop — a loop of wire from the CO and back.

## Multiples

What is significant about all this is that the pair of wires used for your line probably has been used for someone else's phone sometime in the past and it might still lead to a different location called a Multiple.

In the Junction Points — or if



above ground, the Splicing Boot — a certain number of pairs separate from the distribution cable and lead into your building. These pairs then terminate in that building — that is, they end there and don't double back.

So, when your pair separates, it is disconnected from continuing on to the next appearance by removing a jumper. But once in a while, this jumper is not removed, which means that your pair does continue on to another Junction Point and possibly into another house or apartment building. This is one way an illegal wiretap can be set up, if the tapper knows the right cable and pair numbers and can get into the JP.

Now, in a situation where this is true, your line will go into the 66 block at this other location and then might go to an unused modular block or may be connected with the heavy wire with thick black insulation used in older buildings and to a

connection block that uses spade clips and screw terminals. It may have been there for years without anyone using it, especially the older type of wiring, and the block might be behind some piece of heavy furniture that hasn't been moved in years, such as a bookcase.

On the other hand, the block might be accessible, perhaps in an apartment that has been vacant for some time.

### Sleepers

Now, one day, someone moves in, and they happen to plug a phone in to the modular jack and it works — there is dial tone. It becomes an extension phone on your line! Now, they may not realize this, they may assume that their new service has already been turned on since this can be done overnight. So, they would be able to make calls on your line. This is called a "Sleeper On The Line."

Incidentally, it is also possible that you might be a multiple on someone else's line. You can use the amplifier in this article to find out by checking any unused connection blocks you may have. And should you find dial tone, you will want to know whether or not it is your own line. You can do this by calling yourself which, of course, will get you a busy signal. But if your phone does ring, then you know you are calling from another number. Or you can use ANI, a number you call that has a computerized voice that reads back the number you have called from. Like other test numbers, ANI is proprietary but if you dig around on the web, you will eventually find one for your area.

### The Hidden Sounds

It is not all that rare that there

is a sleeper on your line; it does happen. So, you will, of course, hear the ordinary conversations that people make, unless there is something unusual happening at the other appearance. Or something unlawful, in which case you might want to immediately call 611, report 'unknown trouble,' and hope like heck the telco technician finds the sleeper!

### Telco Technicians

Here is what happened to me while researching one of my books.

When telco technicians are making routine tests on the lines, or installing a new line, they go to an appearance, typically a B-Box. There, they need to call the Central Office and arrange to 'get dial tone' on a particular pair. And to do this, they need an available pair to use to connect their test or 'butt' sets. In some places — cities — there is a 'floater,' a line set aside for telco people for this purpose. But in others, there is no floater, so the technician just picks a pair that is 'handy.' I will explain.

Next time you see a technician working at an open B-Box, go over and have a look. On the inside of the door is a pair of terminals. It is these that the test set is connected to. From these terminals is connected a short pair of wires with clips on the end. These are used to connect to one of the punch down connectors in the B-Box. And since these wires are only so long (about 18 inches), they will reach to only so many of the terminals. So the technician picks one at random that is within reach, sets their test set to 'listen only' to see if the line is in use

**W**hat does the law — local and Federal — say about using this simple device? You would be well-advised to consult an attorney, which I am not. But I do have an opinion. If you use it to listen in on a conversation that is taking place on an extension phone of your own line and the people talking are not made aware that you are listening, then this is unlawful.

As to crosstalk, you probably won't be able to make out much of what is being said, but you are not 'tapping' the other lines. You are simply monitoring your own line and someone else is "using" it without your permission.

Now with Telco technicians using your line, well, this is problematic. I suspect that they aren't really supposed to use a person's line without their permission, but the Communications Act of 1934 may apply here — accessing any line for maintenance purposes — another question best answered by an attorney.

(at least most of the time they do!), and then uses it. They will call into the CO, answer pages, or maybe check their voice mail. Or, on rare occasions, they may make a few personal calls which can be very interesting sometimes!

And that's what happened to me. Quite a few times over six months or so, the techs were using my line. Unfortunately, this was my data line, and so I kept getting disconnected from the Internet without, at the time, knowing why.

In addition to voice conversations, there are other things you may hear.

### Data

Where once the most sophisticated device telco installation people carried was the "butt" set, today they may have a small data terminal called Tele-Tech. These little gems

## Sources


Amplifiers, parts, cables  
**Alltronics**  
2300 Zanker Road  
San Jose, CA 95131  
www.alltronics.com

**Electronic Rainbow**  
6227 Coffman Road  
Indianapolis, IN 46268  
www.rainbowkits.com

DTMF Decoders  
**Motron Electronics**  
310 Garfield Street, Suite 4  
Eugene, OR 97402  
www.motron.com

**JDR Microdevices**  
1850 10th Street  
San Jose, CA 95112  
www.jdr.com
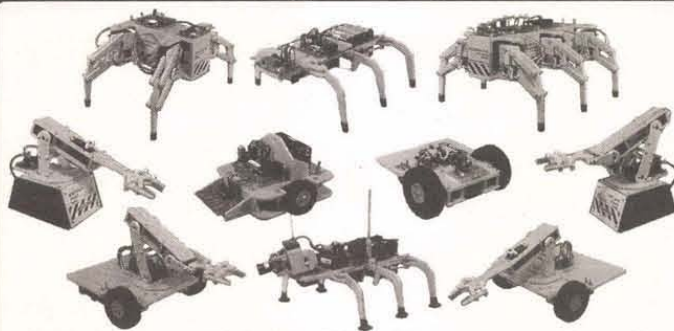
## Build Your Own Intelligent Robot, We Make It Easy!



At Lynxmotion we cater to the beginner. All of our kits are easy to assemble, requiring only common hand tools in the construction process. The detailed assembly manuals include 2D and 3D exploded view diagrams. The kits can be controlled or programmed in an easy to follow BASIC programming language. The technology is here, the costs are affordable, the support is available, join in and become a robot builder!

Lynxmotion, Inc.  
104 Partridge Road  
Pekin, IL 61554-1403  
www.lynxmotion.com



**lynxmotion**

Visit our website or ask for our free catalog!

Tel: 309-382-1816  
Fax: 309-382-1254  
sales@lynxmotion.com  
tech@lynxmotion.com

## FASTER THAN MOTOROLA

**Two-way radio jamming equipment 800/900MHz.** Stop illegal surveillance. **Pager jammers 900MHz.** Stop pagers from going off during school or church service. **Cellular phone jammers.** Stop cellars from going off during school or church service. **PCS jamming, PCS phones.** **Lojack/teletack/boomerang.** Stop illegal tracing/anti-surveillance. **Cordless phone jammers 49MHz/900MHz • Radar jammers Xband • Nextel jammers • Car alarm jammer • CB radio jammer • Garage door jammer • RC radio jammers • AM/FM radio • HF/VHF/UHF radios • 1/8000MHz jamming equipment.**

**This equipment is designed for anti-surveillance customers: embassies, schools, churches, governments, law enforcement.**

**IF YOU DON'T SEE WHAT YOU WANT, WE WILL BUILD IT FOR YOU!!**

*We sell only to specific organizations or for export. Anyone implying illegal activity will be denied assistance and will be reported to law enforcement.*

**Jam RF • 954-561-8128 or www.jamrf.com**



It has been my experience that many telco maintenance people are friendly and will chat with you especially if you know some of the terminology. So, you can always try. Ask if this B-Box goes to your address, or if they can check for multiples, or whatever interests you. I have had some fascinating conversations with telco people. But, of course, they won't tell you everything they know ... Incidentally, if they happen to be having a conversation with their butt set, be polite and wait till they are through rather than interrupting them.

(perhaps like Mr. Bell demonstrating his first working system before Congress), but nevertheless communicate.

### Test Tones

Another of the hidden sounds you may hear are the various tones used for line testing. These may be transmitted at certain intervals, but this will vary from one location to another.

### Tone Slope

This is a series of tones that sounds like a musical scale. It is used to check for line losses at different frequencies. It is quick, lasting less than a second, and sometimes repeats after a few minutes; possibly because the first series indicated some line loss.

### The Milliwatt Test

This is a 1,004 Hz tone at 0 dB tone used to check for line losses, among other things, such as capacitance losses caused by wiretaps and forgotten multiple appearance points. It is very loud, so if you have the volume cranked up, it will definitely get your attention!

### Sweep Tones

This is an audio tone that starts at just under 300 Hz and increases in frequency to a little over 3,000 Hz. Also, the higher end of this tone range detects losses from some inductive devices on the line such as a tap. The reason for this particular frequency range is that telephone



**PHOTO 3**

systems have a bandwidth of 300 to 3,000 Hz. It was also used, so I hear, to trigger or detect an Infinity Transmitter — a type of surveillance device that worked on telephone systems back in the 50s.

Most of these tones are used late at night, and sometimes can cause your phone to "try" to ring. A feeble sound, not quite a normal sounding ring, but one that may wake you up. You have probably experienced this before. Now, you know what it was!

Other tones you might hear include: 440/1,004/2,800 Hz (gain/slope tests); and 2713 Hz to activate Remote Isolation Devices (RIDS), a Maintenance Termination Unit (MTU), or Network Interface Unit (NIU).

### Incoming Calls

When someone calls the line you are monitoring, you will hear a loud low frequency 'buzz' coming from the speaker of the device I will

are used to connect to various telco facilities and I just happened to hear one in use a few months ago. A technician was (again!) accessing the B-Box half a block away that contains the distribution cable leading to my apartment building and I heard the sound of slow analog data (later I learned it was 9600 baud) coming from the speaker. And, as I had a DTMF decoder (Photograph 1) on the line, I was able to get the 800 number the tech had called!

### Crosstalk

We have all heard crosstalk, the faint sounds of other people's conversations that 'leak' into our lines. You may hear this, sometimes, especially in an area where moisture gets into the lines, and even more so if the cables are very old and use cloth insulation. This frequently happens after an unusually heavy rainfall. Here in San Francisco, it was once so bad — during El Nino incidentally — that people in this apartment building could actually converse with each other! It was scratchy, and you had to raise your voice quite a lot

### Telephone Systems Information

<http://mirror.lcs.mit.edu/telecom-archives/>  
Telecom Digest and Archives has a nice selection of links to sites about telephones. Something for everyone.

<http://www.educatorscorner.com/experiments/lwav/signals1.html>  
Here at Educators Corner, you can listen to recorded sounds of various frequencies to use as a reference for the test tones described in this article. And, if you like, you can also listen to helicopters, departing 747s, whales, and jackhammers.

[http://www.cisco.com/warp/public/788/net\\_signal\\_control.html](http://www.cisco.com/warp/public/788/net_signal_control.html)  
From Cisco, an excellent tutorial on the basics of telephone systems.



**Telulex model SG-100A**

**New Features:**  
✓ 21.5 MHz  
✓ .01 Hz steps  
✓ multi-unit phaselock

**BNC/Telulex Div.**

## Any waveform you want!

### ● Synthesized Signal Generator

Clean sinewaves DC-21.5 MHz with .001% accuracy! .01 Hz steps. DC Offset. RS232 remote control.

### ● Arbitrary Waveform Generator


40 Megasamples/Second. 32,768 points. 12 bit DAC

### ● Function Generator

Ramps, Triangles, Exponentials, Noise & more. 0 to 2 MHz in 1 Hz steps. Continuous or Triggered.
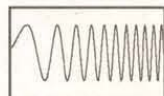
### ● Pulse Generator


Digital waveforms with adjustable duty cycle




DC to 21.5 MHz linear and log sweeps




Int/Ext AM, SSB, Dualtone Gen.

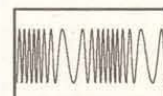

Int/Ext FM, PM, BPSK, Burst

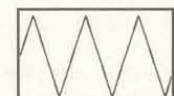


Ramps, Triangles, Exponentials

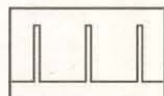

Pulse Generator



Noise

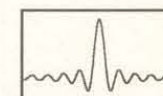

Arbitrary Waveforms



Unlimited Possibilities!

3060 Kerner Blvd., #2  
San Rafael, CA 94901

**Tel** (415) 453-9955

**Fax** (415) 453-9956

<http://www.Telulex.com>

Email: [sales@Telulex.com](mailto:sales@Telulex.com)



describe later in this article. This ringing signal is usually between 20 and 72 Hz (with 20 Hz standard in the US) at a potential of between 40 and 150 volts (with 90 the US standard), depending on the length of the Local Loop. The ring signal duration is one-half to one-and-a-half seconds.

Turn the volume down before you answer or you will get feedback from the speaker. (And maybe a little from the person who called you when they hear the screeching sound!)

## Environmental and Other Monitoring Systems

There are businesses that have facilities that require climate control, meaning a controlled temperature and humidity, but which are frequently unattended. So, they have monitoring systems set up which they can call to get a computer-generated report. Some of them will also open a microphone so that the caller can hear any unusual sounds in the area.

If there should be "trouble" on one of these lines, a telco technician might be notified via their beeper to call in for a 'trouble ticket' and, if the tech happens to use your line, you will hear both them calling in for messages and the synthesized voice of the automated system.

## RTUs: Remote Test Units

There are different types of

remote testing devices, including the Harris-Dracon DATU — Direct Access Test Unit. As I understand it, this is a gizmo that is attached to the distribution frame and can make a direct connection to any pair of wires.

The telco technician calls the access number which is answered, usually on the second ring. It is answered with what is much like an ordinary dial tone, followed by Touch Tones that the technician uses to activate various test functions. One of these is listening on the line — the tech can hear conversations on any line they use the DATU on, which is apparently frequency-inversion scrambled. But we know just how "secure" that is, don't we?

## About the Tones

The numbers (Hz) may not mean anything, and unless you have perfect pitch or happen to have a scope (Photograph 1) on the line as I did in my experiment, you may wonder how you can tell one tone from another.

Some of them can be identified by logging elsewhere on to the web sites listed in the side bar, but as an example, the telephone dial tone is 350 and 440 Hz (together) which is lower in frequency than most test tones.

Others can be heard by dialing telco test lines, which usually have two zeros in the assigned prefix such as 440-00xx or 923.xx00. Since these numbers are considered

to be proprietary (as far as I know), they can't be published here and, at any rate, they tend to change periodically.

## The Device

Okay, already, what the heck is it? Hearing what is happening on your line is done with a simple device called a Listen-Down or Listen-Down-The-Line amplifier. This is nothing more complicated than a small amplified speaker connected to the line through a pair of .01 uF capacitors.

There are two ways to assemble this nifty device. You can get a small transistorized amplifier from any number of places — such as Electronic Rainbow or Alltronics — and connect it to a small speaker from your junk box. But the easiest, fastest, and least expensive method is to use a multimedia computer speaker. No, this doesn't mean tearing into the \$\$ Altec system with the SuperSubWoofer on the family computer which could get you into deep trouble. Most computer stores have low-cost speaker sets. The ones in Photograph 2 cost only \$10.00.

## The Connections

If you are anything like I am, when you start a new project, even a small one, you want to have everything you need to complete it. All you need is:

- Standard RJ-11 modular tele-

phone cable.

- A modular splitter.
- One cable with a plug that fits the amplified speaker audio input.
- Two .01 uF disk ceramic capacitors.
- And a few inches of fine (AWG 22 or so) solid wire.

Clip the phone cable and strip off about two inches of insulation. Carefully trim off the synthetic fibers and wrap the hookup wire tightly around it. Then splice in the leads from the capacitors and solder them. The other ends of the caps go to the speaker cable. The capacitors block the 48-volt DC line voltage while allowing the audio through.

Now, apply power to the speaker, plug the modulator connector into a phone jack using the splitter, turn the volume up, and lift the phone's receiver. You will hear the dial tone coming from the speaker.

## Adding a DTMF Decoder

Should you hear a sleeper and wonder what number they are calling, you can easily add a touch-tone decoder as shown in Photograph 1. They work from an audio signal — they are not connected directly to the phone line which could damage them — so all you need to do is take the audio output that goes from the amplified speaker to the other (left) speaker and plug that into the decoder.

Take your phone off-hook and dial a few numbers while adjusting the volume until you see the digits clearly displayed.

You're done. Now, sit back and listen to the hidden sounds on your telephone line.

If you hear something not covered in this article, I would like to hear from you. **NV**


## About the author

ML Shannon is a San Francisco writer, author of three books on electronic surveillance, and graduate of a two-year technical school in electronics. He has worked "both sides of the fence" as an employee of two corporations who designed and built surveillance equipment, as well as a technician for a professional TSCM countermeasures company.

Shannon has been a guest speaker on surveillance technology before scanner clubs and law enforcement agencies, and has been interviewed on radio talk shows and television.

He is presently at work on a new book, *Cyber-Street Survival* which is a beginner's guide to privacy and security on the Internet.

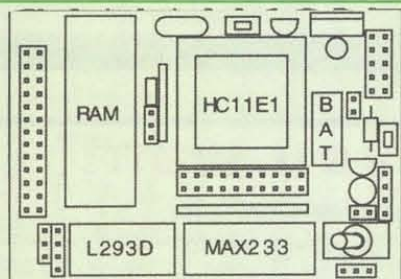He can be reached at P.O. Box 192171, San Francisco, CA 94119-2171 or E-Mail [mshannon@fusion-sites.com](mailto:mshannon@fusion-sites.com).



## SUPER-TCOMP Single Board Computer

- Completely assembled. NOT A KIT!
- Program in C, assembly, IC, etc.
- 32K RAM chip with 10 year battery backup
- 5 volt low drop-out voltage regulator
- Max233 RS232 converter
- Most signals available at expansion ports
- External mode, reset and power connections
- Available options include I/O expansion and LCD board
- Comes with complete instructions
- Very small package: 2.1" x 3.0"
- 1 year limited warranty

----- ONLY \$145 -----

Ray's Robotic Racers (310) 515-6075  
<http://www.teleport.com/~raybutts/>

8+ HOURS

## DIGITAL TELEPHONE RECORDING DEVICE

Voice activated, starts with phone pick up, stops with hang up.

Records both sides of conversations, easily transfers to a PC.

*World's Smallest*, battery operated, extremely reliable, no moving parts, no tape to flip.

Ready to operate, software & accessories included.

Only \$299 + \$6.<sup>95</sup> S/H

ORDER TODAY!

[www.bugged.com](http://www.bugged.com)

PRIVACY ELECTRONICS

5075 Park Boulevard

Pinellas Park, FL 33781

1 877 WIRE TAP

Actual Size

4" Tall 1.4" Wide .75" Thick





# Events

## AUGUST 2000

### AUGUST 4-5

**IL - ELGIN** - Radiofest. Ramada Hotel, 345 River Rd. ARC, POB 1139, LaGrange Park, IL 60526. E-Mail: arci31280@aol.com

### AUGUST 5

**IL - CARLINVILLE** - Hamfest. Macoupin County Fairgrounds. Talk-in: 146.82 or 443.400+103.5PL. Macoupin County ARC, Tim Jones 217-627-2355. E-Mail: KA9VIV at jester25@royell.net  
**MI - ESCANABA** - Hamfest. Delta County ARS, John Anderson WD8RTH, 906-789-6950. E-Mail: wd8rth@arrl.net

**MI - TAWAS** - Hamfest. Isosco County AR Enthusiasts, John Hanley KA8AIP, 517-756-2845. E-Mail: ka8aip@centurytel.net

Web: http://www.oscoda.net/icare/  
**MO - SPRINGFIELD** - Hamfest. Southwest MO ARC, Woodvill Moore W00DY, 417-833-2248. E-Mail: w0ody@arrl.net Web: http://www.smarc.org

**NM - ROSWELL** - Hamfest. Pecos Valley ARC, Vernetta Verasso KC5WKA, 505-627-7777. E-Mail: kc5wka@dfn.com Web: http://www.pvarc.com

**NY - ITHACA** - Hamfest. Tompkins County Airport. 7am-2pm. VE testing. Talk-in: 146.97. Tompkins County ARC, Richard Spingarn AA2UP, 607-387-5251. E-Mail: richard@eagleprint.com Web: http://www.compcenter.com/~tcarc

**OH - COLUMBUS** - Hamfest. Voice of Aladdin ARC, James Morton KB8KJP, 614-846-7790. E-Mail: kb8kjp@cs.com

**PA - LEWISTOWN** - Hamfest. US 522 N. Decatur Township Fire Co. Grounds. Talk-in: 146.91. JVARC and the Decatur Township Fire Co., Richard Yingling, 717-242-1882

**TX - SULPHUR SPRINGS** - Hamfest. Hopkins County ARC, Steve Heller WA0CPP, 903-945-3659. E-Mail: steve@stevheller.com Web: http://www.qsl.net/hcrrc

**VA - VINTON** - Hamfest. William Byrd High School, Washington Ave. 9am-3pm. VE exams. Talk-in: 146.985 (600) W4CA. Roanoke Valley ARC, Dave Miller 540-977-3142. E-Mail: dmiller@rev.net or Fponton@worldnet.att.com Web: http://ourworld.com/serve/home/spages/fcupp/rvarc.htm

### AUGUST 5-6

**WA - SPOKANE** - Eastern WA Section Convention. University High School, 10212 E. 9th Ave. Sat: 9am-5pm, Sun: 8am-12pm. NW Tri-State ARO, Palouse Hills ARC, Inland Empire VHF & Spokane RA, Kamiak Butte Am. Rptr., Betsy Ashleman N7WRQ, 509-448-5821. E-Mail: n7wrq@aol.com Web: http://www.ilea.com/~n7utg

### AUGUST 6

**IN - ANGOLA** - Hamfest. Land of Lakes, Bill Brown WD9DSN, 219-475-5897. E-Mail: sharon.l.brown@gte.net

**NY - FARMINGVILLE** - Hamfest. Radio Central ARC, Neil Heft KC2KY, 631-737-0019. E-Mail: nheft@attglobal.net

**VA - BERRYVILLE** - Hamfest. Clarke County Ruritan Fairgrounds. VE Exams. Talk-in: 146.82. Shenandoah Valley ARC, Irvin Bark W4DHU, 540-955-1745. E-Mail: ibark@visualink.com Web: http://www.vvalley.com/svarc/hamfest

**WI - MARSHFIELD** - HAMNIC. Marshfield Area ARS, Guy Boucher KF9XX, 715-384-4323. E-Mail: guyboucher@tzn.net

### AUGUST 12

**CA - FONTANA** - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves

**IL - QUINCY** - Hamfest. Eagles Alps Grounds, 3737 N. 5th St. 8am-2pm. VEC Testing. Talk-in: 147.63/147.03. Western IL ARC, Jim Funk N9JF, 217-336-4191. E-Mail: jfunk@adams.net Web: http://www.qsl.net/w9awe

**ME - ST. ALBANS** - Hamfest. Piscataquis ARC, George Dean WA1JMM, 207-965-8864. Email: wa1jmm@midmaine.com Web: http://www.qsl.net/parc/

**NY - ROME** - Hamfest. Rome RC, Russell Schorer KB2MAS, 315-853-8739. E-Mail: w4bny@juno.com

**VT - BURLINGTON** - Hamfest. Elks Club on North Ave. 8am-3pm. VE session. Burlington ARC, Renee Berteau N1UXK, 802-893-7660. E-Mail: n1uxk@juno.com

Web: http://www.together.net/~kd1r/fest00.htm  
**WV - HUNTINGTON** - Hamfest. Veterans Memorial Field House, 2590 5th Ave. 8:30am-2pm. VE testing. Talk-in: 146.76. Tri-State ARA, Dwight D. Smith, Sr. WB8JPJ, 304-522-7865. E-Mail: wb8jpp@home.com Web: www.qsl.net/tara

# CALENDAR

The Events Calendar is a free service for publicizing electronic events such as amateur radio hamfests, flea markets, etc. If your organization is sponsoring an event and would like a free listing, contact us at least 60 days in advance. Include your flyer, estimated attendance, name of the person to contact, and phone number.

Complimentary issues are available upon request for distribution to your attendees. A street address for UPS is required.

While we strive for accuracy in our calendar, we can not be responsible for errors or cancellations. The information contained in this column is for the use of the readers of *Nuts & Volts* and may not be republished in any form without the written permission of T & L Publications, Inc.

All listing information should be sent to:

**Nuts & Volts Magazine  
Events Calendar**  
430 Princeland Court  
Corona, CA 92879  
Phone 909-371-8497  
Fax 909-371-3052  
E-mail events@nutsvolts.com

### AUGUST 13

**CA - GOLETA/SANTA BARBARA** - Hamfest. Santa Barbara ARC, Alan Soenke WA6VNN, 805-562-2694. E-Mail: wa6vnn@sbarc.org Web: http://www.sbarc.org

**IA - AMANA** - Hamfest. Amana Outdoor Convention Center. VE Exams. Talk-in: 146.745/145 and 146.520. Cedar Valley ARC, Chuck Bassett N0UTS, 319-378-0448. E-Mail: n0uts@rf.org Web: http://cvarc.rf.org

**IL - PEOTONE** - Hamfest. Hamfests Radio Club, Christine Mack K9RFY, 708-358-1786. E-Mail: christine1@mediaone.net

**IN - GREENTOWN** - Hamfest. Greentown Lions Club Fairgrounds. Kokomo & Grant County ARCS, L.B. (Nick) Nickerson KA6NQW, 765-668-4814. E-Mail: ka6nqwnick@netusa1.net Web: http://www.netusa1.net/~ka6nqwnick/hamfest.html

**MA - ORANGE** - Hamfest. Mohawk ARC, John Doule AE1B, 978-249-5905. E-Mail: ae1b@gis.net

**MI - JACKSON** - Hamfest. Jackson Community College. VE testing. Cascade ARS, Dennis Byrne KC8JLZ, 517-522-4058 or 517-796-6966. E-Mail: byrned@voyager.net

Web: http://www.qsl.net/cars-jxn  
**MN - ST. JOSEPH** - Hamfest. Del-Win Ballroom, 1985 88th Ave. 9am-2pm. VE Exams. Talk-in: 147.01(+). St. Cloud ARC, Linden Scott Hall KA0DAQ, 320-252-4498. E-Mail: lscott@aol.com

Web: http://www.w0sv.org/hamfest.html  
**NJ - BAYVILLE** - Hamfest. Bayville Fire House, Rt. 9. VE Testing. Talk-in: 146.910 out, 146.310 in. PL 127.3. Jersey Shore ARS, Bob Murdock WX2NJ, 732-269-6379. E-Mail: jsarsfest@aol.com

Web: http://members.aol.com/jsarsfest/jsarsfest.html  
**NY - CHEEKTOWAGO** - Hamfest. Leonard Post VFW, Walden Ave. VE Testing. Lancaster ARC, Luke Caliano N2GDJ, 716-634-4667 or 716-683-8880. E-Mail: lcaliano@freeweb.com

Web: http://hamgate1.sunyerie.edu/~larc  
**PA - YORK** - Hamfest. VE testing. Talk-in: 146.700. York ARC, Southern PA Comm. Group, & Hilltop Transmuting Assn., Cecil Mundorff K3DCU, 717-927-6662

### AUGUST 18-19-20

**CANADA - BC - PRINCE GEORGE** - Hamfest. Prince George ARC, Brent Lyons E-Mail: lyonsden@saintmail.net

Web: http://www.pghamfest.dhs.org/

### AUGUST 19

**KS - CHANUTE** - Hamfest. Chanut Area ARC, Charlie Ward WD0AKJ, 316-431-6402

**NJ - OAKLAND** - Hamfest. Ramapo Mountain ARC, Anthony Cassera N2KDZ, 914-732-2731 or 973-839-3564. E-Mail: acassera@intac.com

Web: http://www.intac.com/~hansen/rmarc.htm  
**WA - LONGVIEW** - Hamfest. Cowlitz County Expo Center. 9am-1pm. Talk-in: 147.26+. Lower Columbia ARA, Bob Morehouse KB7ADO, 360-425-6076. E-Mail: kb7ado@aol.com

Web: http://www.qsl.net/cn7p/swapmeet.htm

### AUGUST 20

**CO - GOLDEN** - Convention. Jefferson County Fairgrounds. Denver RC, Ron Taylor K0HRT, 303-989-3978. E-Mail: k0hrt@arrl.net Web: http://www.qsl.net/w0tx

**IN - LAFAYETTE** - Hamfest. Tippecanoe County Fairgrounds. 8am-2pm. Talk-in: 147.135/443.775. Tippecanoe ARA, Bob Martin W9YE, 765-423-1035. Web: www.w9reg.org

**KY - LEXINGTON** - Hamfest. National Guard Armory, adjacent to Lexington airport. 8am-4pm. VE sessions. Talk-in 146.760. Bluegrass ARS,

## COMPUTER SHOWS

**AGI Shows**, 317-299-8827. E-Mail: info@agishows.com http://www.agishows.com

**Blue Star Productions** 612-788-1901. http://www.supercomputersale.com

**Computers And You**, 734-283-1754. www.a1-supercomputersales.com

**Computer Central Shows** 847-412-1900 & 1-888-296-6066. E-Mail: compcent@megsnet.net www.computercentralshows.com

**Computer Country Expo** 847-662-0811 Web: www.ccxpo.com

**Five Star Productions** 810-379-3333. E-Mail: jeff@fivestar www.fivestarshow.com

**Georgia Mountain Productions** 706-838-4827. E-Mail: gamtpro@blrg.tds.net georgiamountain.com

**Gibraltar Trade Center, Inc.** 734-287-2000. Taylor, MI. E-Mail: taylor@gibraltartrade.com www.gibraltartrade.com

John Barnes KS4GL, 606-253-1178. E-Mail: KS4GL@juno.com Web: http://www.qsl.net/k4kgj

**MA - CAMBRIDGE** - Flea at MIT. Albany and Main Sts. 9am-2pm. Talk-in: 146.52 & 449.725/444.725 W1XM/R PL 114.8 (2A). Nick Altenbernd KA1MQX, 617-253-3776 (9-5). Web: http://web.mit.edu/w1xm/www/swapfest.html

**NJ - MULICA HILL** - Hamfest. Gloucester County ARC, Robert Budd KB2EAH, 856-358-6316. E-Mail: johovah@voicenet.com

**OH - WARREN** - Hamfest. Trumbull Campus Kent State Univ., Rt. 45 (Mahoning Ave.) and Rts. 5/82 bypass. Talk-in: 146.970, 443.000. Warren ARA, Renee McCaman KB8SVF, 330-755-2433. E-Mail: mccaman@cboss.com

Web: http://www.onecom.net/wara

### AUGUST 25-26-27

**CT - ENFIELD** - Conference. Eastern VHF/UHF Society & North East Weak Signal Group, Bruce Wood N2LIV, 631-265-1015 or 631-263-9600. E-Mail: bdwood@erols.com

**MA - BOXBOROUGH** - Convention. Holiday Inn Conference Center. Tony Penta W1ABC, 617-248-6996 or 978-887-8887. E-Mail: w1abc@arrl.net Web: http://www.boxboro.org

### AUGUST 26-27

**FL - SARASOTA** - Computer Show. Sarasota Municipal Auditorium, 801 N. Tamiami Trl. Frank Cox, 941-954-0202

**NM - RIO RANCHO** - State Convention. Rio Rancho National Guard Armory, Hwy. 550. Sat: 8am-5pm, Sun: 8am-1pm. VEC Testing. Talk-in: 145.33+ 100 Hz PL, 444.00+ 100 Hz PL. New Mexico Hamvention Committee, Marcus Lieberman KM5EH, 505-836-1724. E-Mail: km5eh@arrl.net Web: http://www.qsl.net/dchf

### AUGUST 26

**MO - COLUMBIA** - Convention. National Guard

**Gibraltar Trade Center, Inc.** 810-465-6440. Mt. Clemens, MI. E-Mail: mtlclemens@gibraltartrade.com www.gibraltartrade.com

**KGP Productions** 1-800-631-0062, 732-297-2526. E-Mail: kgp@mail.com

**MarketPro, Inc.**, 201-825-2229. http://www.marketpro.com

**MarketPro, Inc.**, 301-984-0880. E-Mail: md@marketpro.com http://marketpro.com

**Narisaam Computer Show** 770-663-0983. E-Mail: narisaam@aol.com Web: http://www.showsale.com

**Northern Computer Shows** 978-744-8440. E-Mail: inquiries@ncshows.com Web: ncshows.com

**Peter Trapp Computer Shows** 603-272-5008. E-Mail: www.petertrapp.com

Armory, 5151 Roger Wilson Dr. 8am-2pm. VE testing. Talk-in: 146.76. Central MO Radio Assn., Dewey Bennett W0M0H, 573-445-7030. E-Mail: dbennett01@coirn.org

Web: http://www.qsl.net/~cmra  
**TX - GAINESVILLE** - Hamfest. Gainesville Civic Center. 7am-5pm. VE Exams. Talk-in: 147.34, 443.125. Cooke County ARC, James Floyd N5ZPU, 940-668-7511. email: jfloyd@cooke.net

Web: http://home1.gte.net/rperkins/ccarc.htm  
**WV - WESTON** - State Convention. Jackson's Mill Conference Center. 8am-11pm. VE Testing. Talk-in: 145.390/144.790. WV State AR Council, Ann Rinehart KA8ZGY, 304-768-9534. email: ka8zgy@arrl.net web: http://www.qsl.net/wvsarc

### AUGUST 27

**IL - DANVILLE** - Hamfest. Vermilion County ARA, Terry England W9CAJ, 217-446-6076. E-Mail: w9cau@soltec.net Web: http://members.soltec.net/~w9ema/VCARA/

**IL - WOODSTOCK** - Hamfest. McHenry County Fairgrounds. 6am-3pm. Talk-in: 146.52. Tri-County Radio Group, Inc., Bob Grosse N9KXG, 847-217-7052. E-Mail: n9kxg@hamfest.zzn.com Web: http://www.superhamfest.com

**IN - LA PORTE** - Hamfest. La Porte County Fairgrounds. 7am-1pm. Talk-in: 146.52, 146.61(-) PL 131.8. La Porte ARC, Neil Straub W29N, 219-324-7525. E-Mail: nstraub@nla.net Web: www.geocities.com/siliconvalley/bte/1653

**KS - SALINA** - State Convention. Central KS ARC, Ron Tremblay WA0PSF, 785-827-8149. E-Mail: tremblay@midusa.net

Web: http://www.qsl.net/w0cy  
**MI - LAPEER** - Hamfest. Lapeer County Center Bldg. 8am-4pm. VE testing. LCARA, Charles Conley N8RVG, 810-245-0347. E-Mail: cconley@bigfoot.com

Web: http://www.lapeer.com/lcara



# Events CALENDAR

**MO - ST. CHARLES** - Hamfest. Blanchette Park. 6:30am-1pm. Talk-in: 146.670. St. Charles ARC, Ken Fieser KB0VLN, 314-428-4383. E-Mail: kfieser@aol.com  
**NE - OMAHA** - Hamfest. Millard Social Hall, 10508 S. 144th St. 8am-1pm. Talk-in: 146.34/94. Ak-Sar-Ben ARC, Gerald Gross WA6POZ, 402-891-2481. Email: wa6poz@arrl.net or Ralph Erts W0SMY, email: rests@hotmail.com  
**NY - YONKERS** - Hamfest. Saunders High School, 145 Palmer Rd. 8:30am-2pm. VE testing. Talk-in: 146.265/865. Yonkers ARC, John, 914-963-1021; Paul, 914-237-5589; Dan, 914-667-

0587. E-Mail: w2yrc@hotmail.com  
**PA - NEW KENSINGTON** - Hamfest. Skyview Radio Society, Robert Livrone N3WAV, 724-339-9607. E-Mail: n3wav@arrl.net  
**TN - LEBANON** - Hamfest. Short Mountain Repeater Club, Patsy Pierce K3PAT, 615-395-4488. E-Mail: kq4an@aol.com

## SEPTEMBER 2000

### SEPTEMBER 2

**CANADA - ONTARIO - CARP** - Hamfest. Carp Agricultural Fairgrounds, 3970 Carp Rd. 10am-1pm. Talk-in: VE2CRA 146.940. The Ottawa

ARC, Inc., Greg Danylenko VE3YTZ, 613-236-9291. E-Mail: fleamarket@oarc.net  
**TX - SULPHUR SPRINGS** - Hamfest. Hopkins County ARC, Steve Heller WA0CPP, 903-945-3659. E-Mail: steve@steveheller.com  
 Web: http://www.qsl.net/hcrrc

### SEPTEMBER 2-3

**NC - SHELBY** - Hamfest. Cleveland County Fairgrounds, US Hwy. 74. Shelby ARC, John Ledford W4JL, 704-482-4507. E-Mail: w4jl@shelby.net  
 Web: http://www.shelby.net/n4fan

### SEPTEMBER 8-9

**AR - MENA** - Hamfest. Queen Wilhelmina

Hamfest Assn., Charlotte Lee KC5DOR, 870-642-7656 or 870-642-2234 ext. 107. E-Mail: cbec48@iwon.com

### SEPTEMBER 9

**CA - FONTANA** - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves  
**IN - SPENCER** - Hamfest. Owen County ARA, Kathryn Smith K9INQ, 812-829-2140  
**KY - LOUISVILLE** - State Convention. Bullitt County Fairgrounds. 8am-5pm. FCC exams. Greater Louisville Hamfest Assn., Herbert Rowe W4WQD, 812-294-4905. E-Mail: wd4xl@juno.com  
 Web: http://www.thepoint.net/~glha/  
**MI - GRAYLING** - Hamfest. Hanson Hills Recreation Area, 7601 Old Lake Rd. 8am-12pm. VE Testing. Talk-in: 145.13. ARA of Hansen Hills, John Schultz N8YSS, 517-348-4966. E-Mail: jschultz@i2k.net  
 Web: http://www.arahh.org/swapshop.html  
**MN - RUSH CITY** - Hamfest. East Central MN ARC, Larry Jilek KA0MEN, 320-358-4205. E-Mail: lj@ecenet.com  
**NY - BALLSTON SPA** - Hamfest. Saratoga County Fairgrounds. 7am-3pm. VE Testing. Talk-in: 146.40/147.00 and 147.84/147.24. Saratoga County RACES Assn., Inc., Darlene Lake N2XQG, 518-587-2385. E-Mail: lake@capital.net  
 Web: http://www.capital.net/users/lake

### SEPTEMBER 9-10

**FL - MELBOURNE** - Hamfest. Platinum Coast ARS, Tim Madden KI4TG, 321-724-9339. E-Mail: hamfest@pcars.org

### SEPTEMBER 10

**MA - SOUTH DARTMOUTH** - Hamfest. Southeastern MA ARA, Bill Miller K1IBR, 508-996-2969. E-Mail: billmiller@netzero.net  
**NY - BETHPAGE** - Hamfest. Briarcliffe College, 1055 Stewart Ave. 8:30am-2pm. VE testing. Talk-in: W2VL 146.85 repeater (136.5 PL). Long Island Mobile ARC, Ed Muro KC2AYC, 516-520-9311. E-Mail: hamfest@limarc.org  
 Web: http://www.limarc.org  
**PA - BUTLER** - Hamfest. Butler Farm Show Grounds. Talk-in: 147.360 +600. Butler County ARA, Gerald Wetzel, W3DMB, 724-282-6777. E-Mail: w3dmb@arrl.net  
 Web: http://www.cfcorp.com/bcara/

### SEPTEMBER 15-16-17

**IL - PEORIA** - Hamfest. Exposition Gardens. 6am-4pm. FCC Exams. Talk-in: 147.075+, 53.990 (-1.7), and 146.76(-). Peoria Area ARC, Ron Morgan KB9NW, 309-692-3378 or 309-694-2469. E-Mail: kb9nw@juno.com  
 Web: http://www.w9uvi.org

### SEPTEMBER 16

**AR - LITTLE ROCK** - Hamfest. North Little Rock Community Center, 2700 North Willow St. Talk-in: 146.940. 444.200+ (114.8 PL). CAREN, Scott Derden K5SCD, 501-258-1881. E-Mail: k5scd@arrl.net  
 Web: http://carenclub.webjump.com

**CA - SANTA ROSA** - Hamfest. Lewis Adult Education Center, Corner of Lewis Rd. and Lomitas Ave. VE Session. Sonoma County RAs, Inc., Rick Reiner K6ZWB, 707-575-4455. Web: http://www.cdsl.net/scra/

**GA - DALLAS** - Hamfest. Paulding Meadows Park. 8am-2pm. Talk-in: 146.895+ 77Hz, 224.700. Paulding County ARC, Inc., Bill Houston WD4LUQ, 770-445-9191. E-Mail: Bhouston@worldnet.att.net

**IL - ROLLING MEADOWS** - Convention. Holiday Inn Holiday, 3405 Algonquin Rd. Northern IL DX Assn., Bill Smith W9VA, 847-945-1564. E-Mail: w9va@aol.com

**MI - GRAND RAPIDS/CALEDONIA** - Hamfest. 9757 Duncan Lk. Ave. 8am-1pm. VE Exams. Talk-in: 147.260/R. CTCSS 94.8 Hz or 146.52 simplex. Grand Rapids ARA, Lowell ARC, & MI ARA, Lee Burgess W8MLB, 616-458-9297. E-Mail: hamfest@w8dc.org Web: http://www.w8dc.org

**NY - WHITE PLAINS** - Hudson Division Convention. Westchester County Center. 8am-2pm. Talk-in: 147.05 PL 114.8. Westchester Emergency Communications Assn., Thomas Raffaelli WB2NHC, 914-741-6606. E-Mail: wb2nhc@weca.org

**PA - SCHNECKSVILLE** - Hamfest. Schnecksville Fire Dept. Talk-in: 146.70 (PL151.4)/R, 444.90 (PL151.4)/R. The Delaware Lehigh ARC, Inc., Carl Seier, 610-261-0403. E-Mail: aa3ix@arrl.net Web: http://www.kutztown.edu/faculty/chuk/dlarc/

### SEPTEMBER 16-17

**AK - ANCHORAGE** - State Convention. Anchorage ARC, John Bury KL7QZ, 907-349-8754. E-Mail: bury@gci.net  
 Web: http://k17aa.akconnect.com  
**PA - YORK** - Hamfest. York Hamfest Foundation, John Shaffer W3SST, 717-764-8193 or 717-764-

## Tired of Expensive Inkjet Cartridges ?

# Save 90% on Inkjet Inks !

Printer (Call for Others Not Listed!)	# of Refills		Cost/Refill		Kit Price	
	Black	Color	Black	Color	Black	Color
HP 500 Series, 400, Officejet 300, 350, Fax	7	14	4.71	2.85	32.95	39.95
HP 600 Series, Officejet 500, 570, 600	7	14	4.71	3.21	32.95	44.95
HP 820C, 855C, 870C, 1000C, 1150C, Copier 120, 210	6	12	6.67	3.33	39.95	39.95
HP 720C, 722C, 712C, 880C, 890C, 895C 1120C, 1170C	6	12	6.67	3.75	39.95	44.95
Canon BJ-10, 200, 210, 240, 250 Apple SWriter 1200, 1500	14	20	2.15	2.00	29.95	39.95
Canon BJC-4000 Series, C2500, C3000, C3500, C5000	60	60	0.50	0.67	29.95	39.95
Canon BJC-6000	14	8	2.85	1.67	39.95	39.95
Canon BJC-600, 610, 620 Apple SWriter Pro	20	13	1.50	3.07	29.95	39.95
Epson Stylus Color, Color Pro, Pro XL	12	12	2.50	3.33	29.95	39.95
Epson Stylus Color II, IIs, 1500 (Black)	15	15	2.00	2.66	29.95	39.95
Epson Stylus Color 500, 200	20	17	1.50	2.35	29.95	39.95
Epson Stylus Color 400, 600, 800, 850, Photo / 440, 640	20	17	1.50	2.65	29.95	44.95
Lexmark JP 1000, 1020, 1100, ExecJet II, IIC, Medley 4C	10	17	3.00	2.35	29.95	39.95
Lexmark JetPrinter 3200, 5700, 5000, Z11, Z31	15	17	2.67	2.35	39.95	39.95
Compaq IJ700, IJ900, Xerox XJ8C, XJ9C	15	17	2.67	2.35	39.95	39.95
Xerox Home Center 450C, XJ6C Inkjet	22	12	1.36	3.33	29.95	39.95

## SAVE 30 - 50% on New Compatible Cartridges New Lower Cartridge Pricing!

Printer	BLACK CARTRIDGE	COLOR CARTRIDGE
(CALL FOR OTHERS NOT LISTED !!)		
Canon BJC-4000/5000/2000 Series, C2500, C3000	\$4.95	\$11.95
C3500, C5000, C5500 Apple StyleWriter 2400, 2500	\$4.95	\$11.95
Canon BJC-600, 610, 620 Apple StyleWriter Pro	\$4.50 (9cc)	\$4.50 @ (9cc)
Hi-Capacity Canon BJC-600, 610, 620	\$4.95 (15cc)	\$4.95 @ (12cc)
Canon BJC-70, BJC-80	\$9.95 (3-pak)	\$14.95 (3-pak)
Epson Stylus Color, Color Pro, Pro XL	\$10.50	\$14.95
Epson Stylus Color II, IIs, 200	\$10.95	\$14.95
Epson Stylus Color 400, 500, 600, 800, 850, 1520, Photo	\$10.95	\$14.95
Epson Stylus Color 440, 640, 660, 740, 760, 860	\$10.95	\$14.95
Epson Stylus Color Photo 750, 900, 1200	\$10.95	\$15.95

- BULK Inks, Refill Accessories
- Glossy card stock & Coated Paper
- 2 - 3 Day Shipping

**Quality Inks for:**  
**HP • Epson • Lexmark**  
**Canon • Apple • DEC**

**Call or see us online!**

Monday - Friday  
 8:30 - 5:30 PST 10:30 - 7:30 EST

**Inkjet**

**Southwest**



**www.inkjetsw.com**

(480) 668-1069 Fax

**1-800-447-3469**

(480) 668-0959



# Events CALENDAR

4805. E-Mail: w3sst@yorkhamfest.org  
Web: <http://www.yorkhamfest.org>

## SEPTEMBER 17

**CT - NEWTOWN** - Hamfest. Edmond Town Hall, Rt. 6. 9am-2pm. Talk-in: 146.67(-) PL 100. Candlewood ARA, Seab Lyon AA1MY, 914-831-3124. E-Mail: sslyon@att.net

**MA - CAMBRIDGE** - Flea at MIT. Albany and Main Sts. 9am-2pm. Talk-in: 146.52 & 449.725/444.725 W1XM/R PL 114.8 (2A). Nick Altenbernd KA1MQX, 617-253-3776 (9-5). Web: <http://web.mit.edu/w1xm/www/swapfest.html>  
**OH - CINCINNATI** - Hamfest. Kolping Center. 8am-4pm. VE exams. Talk-in: 146.88. Greater Cincinnati ARA, Jim Weaver KB8JE, 513-459-0142. E-Mail: kb8je@arrl.net

**PA - YORK** - Hamfest. York County Vo-Tech School. VEC testing. York Hamfest Foundation, 717-764-8193. E-Mail: w3sst@yorkhamfest.org  
Web: <http://www.yorkhamfest.org>

## SEPTEMBER 23

**NY - HAMBURG** - Western NY ARRL Section Convention. Erie County Fairgrounds, Rt. 62. 8:30am-4:30pm. Harold Smith K2HC, 716-424-7184. E-Mail: info@buffalohamfest.org  
Web: <http://www.buffalohamfest.org>

**NY - MARGARETVILLE** - Hamfest. Behind the A&P. VE Exams. Talk-in: 146.520 simplex, 146.985, 449.125. Margaretville ARC, Lester Bourke KB2DCE, 914-586-3186 or 914-586-2324. E-Mail: bourke@catskill.net

Web: <http://www.catskill.net/marc>  
**TX - WEBSTER** - Hamfest. Webster Civic Center. 8am-3pm. Talk-in: 442.750+, 146.64. Clear Lake ARC, Kyle Swarts KD5HQD, 713-666-5854. E-Mail: kd5hq@mindspring.com

Web: <http://www.clarc.org/swapfest.htm>  
**WA - WALLA WALLA** - Hamfest. Walla Walla ARC, Mary Hayter KC7PNE, 509-522-5227. E-Mail: kk7sr@arrl.net

## SEPTEMBER 23-24

**IL - GRAYSLAKE** - Hamfest. Lake County Fairgrounds, Rts. 45 & 120. Sat: 8am-4pm, Sun: 8am-3pm. VEC Testing. Talk-in: 146.16/76 MHz (107.2 Hz PL). Chicago FM Club, Mike Brost WA9FTS, 708-457-0966. E-Mail: mbrost@cin.net  
Web: <http://www.chicagofmclub.org>

**VA - VIRGINIA BEACH** - Roanoke Division Convention. Virginia Beach Pavilion. Sat: 9am-5pm, Sun: 9am-4pm. Talk-in: 146.970. Tidewater Radio Conventions, Art Thiemens AA4AT, 757-484-2857. E-Mail: aa4at@arrl.net  
Web: <http://www.vahamfest.com>

## SEPTEMBER 24

**FL - NEW PORT RICHEY** - Hamfest. New Port Richey Recreational Center, 6630 Van Buren Rd. 9am-3pm. Suncoast ARC, Ron Wright N9EE, 727-376-6575. E-Mail: n9ee@akos.net

**MD - BOWIE** - Hamfest. Prince George's Stadium. VEC testing. Talk-in: 147.105, 146.529. FAR, Dan Blasberg KA8YPY, 301-345-7381. E-Mail: Blasberg@Bellatlantic.net  
Web: <http://www.amateurradio-far.org>

**NY - YONKERS** - Flea Market. Lincoln High School, Kneeland Ave. 9am-3pm. VE Exams. Talk-in: 440.425 PL 156.7, 223.760 PL 67.0, 146.910, 443.350 PL 156.7. Metro 70cm Network, Otto Supliski WB2SLQ, 914-969-1053. E-Mail: wb2slq@juno.com

Web: <http://www.metro70cmnetwork.com>  
**OH - CLEVELAND** - Hamfest. 8am-2pm. VE exams. Talk-in: 146.73/R PL 110.9. Hamfest Assn. of Cleveland, Ron Nichols N8LZA, 1-800-CLE-FEST or 216-999-7388. E-Mail: info@hac.org Web: <http://www.hac.org>

## SEPTEMBER 29-30

**PA - TREVOSE** - Convention. Mt. Airy VHF Radio Club, John Sortor KB3XG, 610-584-2489. E-Mail: johnkb3xg@aol.com  
Web: <http://www.ij.net/packrats>

## SEPTEMBER 30

**NY - HORSEHEADS** - Hamfest. Chemung County Fairgrounds. 6am-3pm. FCC exams. Talk-in: 146.70-444.20. ARAST, Dave Lewis, 607-589-7636. E-Mail: info@arast.org, hamfest@arast.org, or winterfest@arast.org

**SD - SIOUX FALLS** - Hamfest. Old National Guard Armory, Sioux Empire Fairgrounds. VE Testing. Talk-in: 146.895. Sioux Empire ARC, Will Graving KE0Z, 605-647-2606. E-Mail: graving@iwn.net Web: <http://www.qsl.net/w0zwy>

## OCTOBER 2000

### OCTOBER 1

**IA - WEST LIBERTY** - Hamfest. Muscatine County Fairgrounds. VE Exams. Talk-in: 146.31/91, 146.25/85, 146.52 local. Muscatine ARC & IA City ARC, Steve Fowler KA9AQR, 309-537-3678. E-Mail: sfowler@winco.net  
Web: <http://www.qsl.net/kc0ags/hamfest.html>

**IN - BEDFORD** - Hamfest. Lawrence County 4-H Fairgrounds. Hoosier Hills Ham Club, John Scheiwe KB9LTI, 812-279-0050.

E-Mail: chairman@hoosierhillshamfest.org  
Web: <http://www.hoosierhillshamfest.org>  
**PA - WRIGHTSTOWN** - Hamfest. Middletown Grange Fairgrounds, Penns Park Rd. Pack Rats, Joe Keer KU3T, E-Mail: ku3t@amsat.org Web: <http://www.ij.net/packrats>

### OCTOBER 6-7

**NH - ROCHESTER** - Hamfest. Fairgrounds. Hoss Traders, Joe, 207-469-3492

### OCTOBER 6-7-8

**AZ - SCOTTSDALE** - Southwest Div.

Convention. Scottsdale ARC, Walt Schuknecht N7IZM, 480-947-0338. E-Mail: n7izm@arrl.net  
**OK - BROKEN ARROW** - Hamfest. Broken Arrow ARC, Joe Horn KC5VPO, 918-451-0028. Web: <http://www.qsl.net/w5bbs/hamfest>

### OCTOBER 7

**FL - ORLANDO** - Hamfest. Bahia Temple, 2300 Prembrook Dr. Talk-in: 147.390. Ed KY4E, 407-660-0936. E-Mail: ky4e@excite.com

**MO - WARRENSBURG** - Hamfest. Warrensburg Area ARC, Denise Haye N0PVS, 816-697-3426. E-Mail: we0g@microlink.net

Web: <http://www.callto/waarc>

**NJ - TEANECK** - Hamfest. Fairleigh Dickinson University. 8am-2pm. FCC Exams. Talk-in: 146.19/79 and 146.52 simplex. Bergen ARA, Jim

Joyce K2ZO, 201-664-6725. E-Mail: jjjoyce@cybernex.net  
Web: <http://www.bara.org>

### OCTOBER 8

**CT - WALLINGFORD** - State Convention. Mountaintop Special Event Facility. 9am-3pm. Talk-in: 147.36/96. Nutmeg Hamfest Alliance, Gordon Barker K1BIY, 860-342-3258. E-Mail: k1biy@juno.com  
Web: <http://www.qsl.net/nutmeghamfest>  
**MI - DIMONDALÉ** - Hamfest. The Summit, 9410 Davis Hwy. 8am-2pm. VE testing. Talk-in: 145.390 (-600) and 146.520. Central MI ARC & Lansing Civil Defense Repeater Assn., J. Ervin Bates W8ERV, 517-676-2710. E-Mail: w8erv@arrl.net  
Web: <http://www.qsl.net/CMARC/hamfair.html>

## New REWORK STATION from Xytronic


your price leader in quality Soldering and Desoldering Tools

**TWZ60**  
Hot Tweezers  
available for SMD  
chip removal



**\$99.95**

**Xytronic 988**  
**\$465.00**

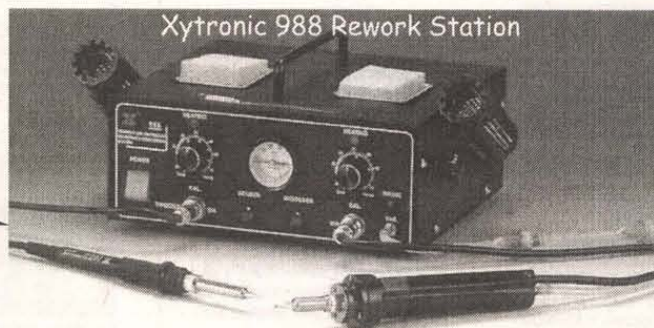

**HAP60**  
Hot Air Pencil  
Available for SMD  
chip removal



**\$79.95**

## Xytronic 988TP \$599.00

Total Package includes Tweezers and Hot air Pencil

For more info go to  
[www.howardelectronics.com/xytronic/988.html](http://www.howardelectronics.com/xytronic/988.html)  
Free Trials Available On-Line

### Letter from a Very Satisfied Customer

When I first unpacked the solder station I was impressed with its weight and feel. I fired it up and within a few seconds it was preheated and ready to go. I began to solder and loved the feel of the solder pencil. The heat is very adjustable and can be set to suit your needs. I have enjoyed soldering this last week. It's nice to not have the iron get so hot in your hand while soldering. Then it was finally time to desolder. The pump sounds smooth and has good power. At first I had a hard time working with it because of the pump staying on the extra few seconds, but after desoldering a few parts I got used to it. I just had to retrain my technique. Now when I use it I like that I can begin desoldering right away without unclogging it first. After I am done I use the cleaning stick and put it in the rest. So far it's always ready to go the next time I need it. I would attribute that to the pause mode. I have gone long periods of time between uses. I just push the button and within seconds it reheats to selected temperature and I am ready to go. After one week of use I am very impressed. It's a very good unit at a very good price! Thank You, Keith

Order On-Line for 5% savings or call us Toll Free at 1-800-394-1984

Visa - M/C - Discover - A/E - COD - Terms to Qualifying Companies  
60 Day Money Back Total Satisfaction Guarantee

**HOWARD ELECTRONIC**  
**HE** INSTRUMENTS INC  
Your Desoldering Specialists

6222 N. Oliver Kechi, KS 67067  
Toll Free U.S. and Canada  
**1-800-394-1984**

[www.howardelectronics.com](http://www.howardelectronics.com)  
sales@howardelectronics.com  
International (316) 744-1993  
or Fax (316) 744-1994



## 'SX-1SD' Debugger+Programmer


Qualified by and inhouse tool for  
Scenix Semiconductor

- In-system debugger for SX18/20/28/48/52
- Built in programmer
- Full speed emulation
- Real-time in-system code execution and breakpoint
- Frequency synthesizer from 25khz to 75mhz / 120mhz\*
- External oscillator support to 90 mhz / 100mhz\*
- Source level debugging for SASM, SXC and more
- Selectable internal frequencies
- External break and clock inputs
- Conditional animation break and Software animation trace
- IDE runs under Win 95/98/2000/NT4 via parallel port
- Comes with SASM Assembler, SXDEMO board, SX28AC device and 18-pin, 28-pin SDIP headers


Now  
supporting the  
100 mhz SX

From  
**\$295\***

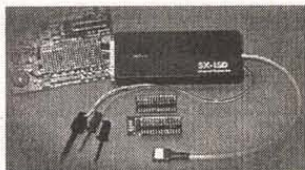- \* SX-1SD ..... \$295 (synthesize to 75mhz, external OSC support to 90-95mhz)
- \* SX-1SD100 ... \$350 (synthesize to 120mhz, external OSC support to above 100mhz)



## Also Available...

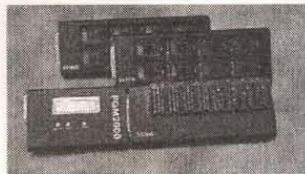

### PGM2000 Gang Programmer

- Stand alone 8 gang programmer
- Parallel Port Interface for on-line operation
- Different 8-socket DIP, SOIC, SSOP, TQFP, PQFP adapters for all SX18/20/28/48/52
- Adjustable programming voltages in 0.1V
- Codes and fuse reside securely in EEPROM of Master Control Unit
- Comes with Win 95/98/2000/NT4 software
- Also supports other processors via different 8-socket adapter modules
- Starts at \$900 with one 8-up DIP adapter



### PGM-SX Programmer

- Parallel Port Interface
- 40-pin ZIF socket to carry device to be programmed or program in-circuit
- Win 95/98/2000/NT4 software
- Comes with SASM assembler
- Optional SOIC, SSOP, TQFP and PQFP programming sockets
- PGM-SX \$149, SMT adapters \$120

**AdvancedTransData**  
14330 Midway, #128, Dallas, Texas  
Tel 972.980.2667 Fax 972.980.2937  
Email: atc1@ix.netcom.com

[www.adv-transdata.com](http://www.adv-transdata.com)

Write in 39 on Reader Service Card.

## HAM GEAR FOR SALE



**2.4GHz ATV — 8 channel TRANSMITTERS AND RECEIVERS.** 35mW output power, 1 video channel, 2 audio, SMA connectors. NTSC/PAL compatible. Includes 1/4 wave rubber duck antenna. Standard frequencies are: 2398, 2405, 2412, 2416, 2420, 2428, 2435, 2442 MHz. Custom frequencies are available. See ad in this section for power amplifier. **\$79/each for transmitter. \$79/each for receiver.** Seabrook, 972-480-0060 (Texas, CST) or E-Mail: [main@480i.com](mailto:main@480i.com) Web: [www.480i.com](http://www.480i.com)



**2.4GHz POWER** amplifier with power supply. 10-40 mW input, 1 (one) watt output with in-line SMA connectors and built-in heat sink. Approx. 2" x 2" x 5/8" size. Frequency range 2.3GHz-2.5GHz. **\$189/each.** Compatible with all ATV product lines. See our website for more info on accessories and transmitter and receiver modules. Seabrook, 972-480-0060 (Texas, 9-6PM CST). E-Mail: [main@480i.com](mailto:main@480i.com) Web: [www.480i.com](http://www.480i.com)



**1.2GHz ATV — 8 channel TRANSMITTERS AND RECEIVERS.** 75mW output power, 1 video channel, 2 audio, SMA connectors. NTSC/PAL compatible. Includes 1/4 wave rubber duck antenna. Standard frequencies are: 1250, 1255, 1260, 1265, 1270, 1275, 1280, 1290 MHz. Custom frequencies are available. **\$79/each for transmitter. \$79/each for receiver.** Seabrook, 972-480-0060 (Texas, 9-6PM CST). E-Mail: [main@480i.com](mailto:main@480i.com) Web: [www.480i.com](http://www.480i.com)

**WANTED: MILITARY** capacitors, resistors, transistors, diodes, ICs, semi's, etc. Please fax/E-Mail excess lists & RFQs 818-769-1002 fax 818-769-1084. [electmatind@earthlink.net](mailto:electmatind@earthlink.net) & <http://www.militarycomponents.com>

**WANTED: ROCKWELL**-Collins HF-80 equipment, 851S-1, 237B-3 log periodic, Collins literature. Jim Stitzinger 805-259-2011, 805-259-3830 (fax), [bfi-jfs@smartlink.net](mailto:bfi-jfs@smartlink.net)

## HAM GEAR WANTED

## CB — SCANNERS

**CB MODIFICATIONS!** Frequencies, books, kits, high-performance accessories, plans, repairs, amplifiers, 10-meter conversions. The best since 1976! Catalog \$3. CBI, Box 1898NV, Monterey, CA 93942. [www.cbintl.com](http://www.cbintl.com)

**CBs, ACCESSORIES, SCANNERS, ANTENNAS, MICROPHONES, COAX.** Best prices! Call 1-800-821-2769 for current flyer. We also carry NIMH batteries and chargers. <http://www.thomas-distributing.com> **THOMAS DISTRIBUTING**, 128 Eastwood, Paris, IL 61944.

**EXPORT RADIOS** & accessories, scanners, microphones, power supplies, amps, repairs, modifications, much more! Here 15 yrs! Picture price sheets \$1 (refundable). Galaxy, Box 1202, Akron, OH 44309.

**CB RADIOS, EXPORT RADIOS, AMPLIFIERS, CONNEX, COBRA, GALAXY, SUPERSTAR, PALOMAR, TEXAS STAR, SHOOTING STAR,** echo boards, antennas, noise toys, test meters, accessories, power microphones and much more. Catalog \$3 (refundable). B & M Electronics, 3600 Cty. Rd. 126, Waterloc, AL 35677. E-Mail: [BMElectronics@aol.com](mailto:BMElectronics@aol.com)

## MUSIC & ACCESSORIES

**www.cctvco.com**  
E-MAIL: [SALES@CCTVCO.COM](mailto:SALES@CCTVCO.COM)  
**1-800-323-8746**

**MONITOR**  
93<sup>00</sup>  
BLACK & WHITE  
12" 1000 LINES  
ECL - 1202  
MANY SIZES AVAILABLE

**BLACK & WHITE BULLET CAMERA**  
WATERPROOF  
79<sup>00</sup>  
420 LINES  
ECL - 554  
ECL - 377

**DIGITAL COLOR CAMERA**  
DIGITAL COLOR (DSP)  
350 LINES  
2 LUX  
ECL - 552  
99<sup>00</sup>

**MINI DIGITAL COLOR CAMERA**  
350 LINES  
ECL - 554  
2 LUX  
METAL HOUSING  
78<sup>00</sup>

**COLOR MICRO BOARD CAMERA**  
DIGITAL (WITH DSP)  
350 LINES  
32 MM X 32 MM  
2 LUX \* PINHOLE LENS  
ECL - 454P  
87<sup>00</sup>

**2.4 GHZ VIDEO TRANSMITTER**  
500' \* 4 CHANNELS  
ECL - 2400MT  
2.5' L X 1.5' W X .5' H  
89<sup>00</sup>

**BLACK & WHITE MINE DOME**  
3.5" \* 420 LINES  
ECL - 372  
59<sup>00</sup>

**OUTDOOR ALUMINUM HOUSING & BRACKET**  
WITH HEAT SHIELD  
ECL - 601S  
45<sup>00</sup>

**BLACK & WHITE CAMERA**  
420 LINES  
ECL - 375  
69<sup>00</sup>

**BLACK & WHITE MICRO BOARD CAMERA**  
420 LINES  
32MMX32MM  
1 LUX  
ECL - 11P  
PINHOLE LENS  
34<sup>00</sup>

**PIR CAMERA**  
HIDDEN (COVERT)  
420 LINES  
1 LUX  
WORKING PIR  
96<sup>00</sup>

**4 CHANNEL RECIEVER**  
135<sup>00</sup>  
2.4 GHZ  
WITH POWER SUPPLY  
ECL - 2400SR

**SAMSUNG STR960**  
960 HOUR TIME LAPSE  
REORDER  
DIAMOND-HEAD SYSTEM  
ON SCREEN DISPLAY  
TIME DATE ALARM  
AUDIO INPUT (ICAI)  
POWER SOURCE 110 VAC  
(FREE VOLT)  
580<sup>00</sup>

**PLASTIC WALL BRACKET**  
7" ADJUSTABLE P/T  
ECL - 206  
45<sup>00</sup>

**MINI METAL BRACKET**  
SWIVEL HEAD  
CAMERA MOUNT  
ECL - 203AL  
50<sup>00</sup>

**QUAD SEQUENTIAL OR FULL SCREEN**  
FREEZE FRAME MODE  
15V ADAPTER INCLUDED  
REAL TIME B/W QUAD  
ECL - 4000  
125<sup>00</sup>

We Have  
**MONTHLY SPECIALS!**

Phone or Fax us to be placed on our mailing list  
**1-800-323-8746**  
Fax (305) 635-3175



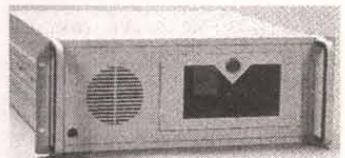
## COMPUTER HARDWARE

**ISO7816 PROGRAMMER** built \$150. Kit \$125. No software. Blank smart cards \$20.00 or 8/\$100. Tony 419-385-3100.




**DIGITAL CAMERA** with 2000 x 1600 megapixel resolution, 4MB memory, more, only \$199. Polaroid ColorShot printer, print picture perfect from digital camera or PC using inexpensive Polaroid instant film \$99. (Retail for \$199.) Lexmark 1200 x 1200 dpi color Jetprinter (highest resolution on the planet) only \$49 after \$40 rebate! Details or to place an order call 847-657-1160 or [www.saveaware.com](http://www.saveaware.com)



**19" RACKMOUNT ATX PC chassis**, \$169 (with ad). 972-242-8087, [www.cti-tx.com](http://www.cti-tx.com)



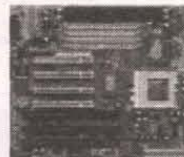**533MHz PII Celeron computer system \$499!** Details or to place an order call 847-657-1160 or [www.saveaware.com](http://www.saveaware.com)



**500MHz AMD K6-11 3D CPU and Pentium motherboard super combo deal** including AGP 3D 8MB video, sound. All I/O ports, 56K modem/voice/fax, LAN, ATX or normal power connectors, baby AT motherboard fits almost all cases, CD-ROM disc w/drivers, Corel 8 Suite & many FREE applications, 2 year motherboard warranty, only \$159. Same as above but with PII 533MHz Celeron CPU, AT or ATX style motherboard \$229! Memory 32MB \$49, 64MB \$79. More items available. Order now 847-657-1160 or [www.saveware.com](http://www.saveware.com)

**BRAND NAME** low-end Pentium computers starting at \$50. Call Jerry W2GIA, Disks N Data, 1-800-833-6893 or E-Mail: [dndcom@earthlink.net](mailto:dndcom@earthlink.net)



**SONY PLAYSTATION GAME ENHANCER, mod-chip function plays backup COPY of CD.** You do not need to have original to play backup. Simply plug the enhancer in back of playstation! Skips both Sony logos, many preloaded cheat codes. More \$29. MOD-CHIP plays backups, works with all models and games \$19. Quantity prices available. Order now 847-657-1160 or [www.saveware.com](http://www.saveware.com)

# Test Equipment Connection Corporation

Test Equipment Connection is looking to purchase your excess or underutilized electronic test and measurement equipment. We buy the largest variety of electronic test equipment in the industry.

## WE BUY TEST EQUIPMENT




RENT

REPAIR



TRADE

SELL

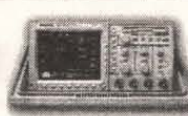

CALL: 800.615.8378

FAX: 800.819.8378

[WWW.TestEquipmentConnection.COM](http://WWW.TestEquipmentConnection.COM)

Specialist in Hewlett-Packard, Tektronix, and many more manufacturers.

Write In 40 on Reader Service Card.

## COMPUTER SOFTWARE

**FREE IBM DISK CATALOG** of quality Shareware and CD-ROMs. **MOM 'N' POP'S SOFTWARE** <ASP>, PO Box 15003-N, Springhill, FL 34609-0111. 352-688-9108. [momnpop@gate.net](mailto:momnpop@gate.net)

**FMSTUDY32 FM**, LPFM allocation studies. Manage FCC database on your PC! Manual included, \$39.95. Demo, info, special Web pricing at <http://members.xoom.com/fmstudy>



**WINDOWS 95B only \$39!** 10 pack \$290, Windows 98SE (second edition) only \$119! Order now 847-657-1160 or [www.saveware.com](http://www.saveware.com)

**CAM & MOTION SW/HW:** Z-trace, PCB toolpath, Plotcam motion control, step drivers. [www.megabits.net/ddt](http://www.megabits.net/ddt) FAX 321-452-7197, 321-459-2729. [heater@megabits.net](mailto:heater@megabits.net)

## Miniature Transmitters and Receivers

### 2 Button / 3 Channel Transmitter



**RF300T**

1....\$22.95  
5....\$19.95 ea  
10....\$16.95 ea

**RF300XT**

1....\$25.95  
5....\$22.95 ea  
10....\$19.95 ea

- 300' (XT), 150' (T) Range
- Frequency: 318 MHz
- 59,049 Settable Security Codes
- 12 Volt Battery and Keychain Included
- Current Draw: 4.8 ma
- Fully Assembled in Case
- Dimensions: 1.25" x 2.0" x .5"
- Push both buttons for the 3rd Channel
- Slide Button Cover Included

- Alarm Systems
- Garage / Gate Openers
- Lighting Control

- Magic Props
- Medical Alert
- Monitoring Systems

- Industrial Controls
- Surveillance Control
- Motor Control

### 4 Button / 15 Channel Transmitter



**RF304XT**

1....\$27.95  
5....\$24.95 ea  
10....\$21.95 ea

- 250' Range
- Frequency: 318 MHz
- 6,561 Settable Security Codes
- 12 Volt Battery and Keychain Included
- Current Draw: 4.6 ma
- Fully Assembled in Case
- Dimensions: 1.35" x 2.25" x .5"
- Push combination of buttons to achieve up to 15 channels

### 2-4 Data / 3-15 Channel Receivers



**RF300RL  
RF300RM**

1....\$27.95  
5....\$24.95 ea  
10....\$22.95 ea

**RF304RL  
RF304RM**

1....\$29.95  
5....\$26.95 ea  
10....\$23.95 ea

- Compatible with 300/4 Transmitters
- 11-24 volts DC Operating Voltage
- 13 ma. Current Draw
- Latching (L) or Momentary (M) Output
- Kits Available (subtract \$5.00 ea.)
- Dimensions: 1.25" x 3.75" x .5"
- 2 (300) / 4 (304) Output Data Lines
- Binary to Dec / Hex Converter can achieve up to 15 channels

- Schematics Available
- Receiver Board Layout Available
- Custom Design Consulting Available

**Visitect Inc.**

(510) 651-1425 Fax: (510) 651-8454  
P.O. Box 14156, Fremont, CA 94539


Email: [Support@Visitect.Com](mailto:Support@Visitect.Com)  
Visa / Mastercard, COD

Write In 41 on Reader Service Card.

Nuts & Volts Magazine/AUGUST 2000 39



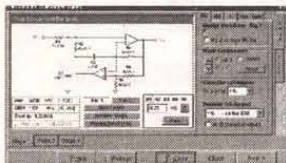**UNDERGROUND CDs:** Hacking, phreaking, free energy, health, anti-gravity, time travel, way-cool electronics projects, music & books. <http://www.hi-techstuff.com>



**WWW.SCHEMATICA.COM** for professional freeware and shareware. Active and passive filter design, 555 designer, linear simulators.

**www.rascom1.com WIN98 UTILITIES.** Web site blocking firewall, keypad program launcher, demos, and special offers! E-Mail: [rascom@mediaone.net](mailto:rascom@mediaone.net)

## COMPUTER EQUIPMENT WANTED

**WANTED: FOR** historical museum, pre-1980 microcomputers, magazines, and sales literature. Floyd, VA 24091-0341 (540-763-3311/540-382-2935).

**HP CALCULATORS** wanted: models 10, 70, calculator watch, others for private collection. Cash paid. Bob Morrow, 765-855-2348, [rkmorrow@aol.com](mailto:rkmorrow@aol.com)

**DEC EQUIPMENT WANTED!!!** We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dialog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 OR fax 937-847-2350.

**WANTED: MILITARY** capacitors, resistors, transistors, diodes, ICs, semi's, etc. Please fax/E-Mail excess lists & RFQs 818-769-1002 fax 818-769-1084. [electmatind@earthlink.net](mailto:electmatind@earthlink.net) & <http://www.militarycomponents.com>

**www.nutsvolts.com**

## TEST EQUIPMENT

**FEITEK PROVIDES** repair, calibration and traceable certifications of test equipment. Free estimates. We buy, sell and trade all makes of test equipment. Visa and MasterCard accepted. Check out our inventory and specials at [WWW.FEITEK.COM](http://WWW.FEITEK.COM) 2752 Walton Road, St. Louis, MO 63114, 314-423-1770.

**KENTRONIX TEST EQUIPMENT SPECIALS.** Check our WEB site at <http://www.kentronix.com> for monthly specials. We are also looking to buy test equipment, coaxial and waveguide components, manuals, etc. Contact Brian at 732-681-3229 or FAX 732-681-3312. E-Mail: [brian@kentronix.com](mailto:brian@kentronix.com)

**DEC EQUIPMENT WANTED!!!** We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dialog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 OR fax 937-847-2350.

**POOR MAN'S** Spectrum Analyzer/Monitor Receiver Kit. 2 to 1,700 MHz. Basic kit only \$98. Now available with switched resolution filters, tracking generator and direct digital frequency readout. Works with ANY scope or IBM compatible computer. Send stamped envelope for details. Science Workshop, Box 310B, Bethpage, NY 11714. <http://www.science-workshop.com>

**WANTED: MILITARY** capacitors, resistors, transistors, diodes, ICs, semi's, etc. Please fax/E-Mail excess lists & RFQs 818-769-1002 fax 818-769-1084. [electmatind@earthlink.net](mailto:electmatind@earthlink.net) & <http://www.militarycomponents.com>

**BROWSE OUR** Web site and check out the "monthly special." TDL Technology, Inc., [www.zianet.com/tld](http://www.zianet.com/tld)

**TEST EQUIPMENT** technicians needed: calibration and repair techs. Three full-time openings. We are located in Broomfield, Colorado, between Boulder and Denver. We perform electronic and physical/dimensional calibrations. Please send resume to [irl@calibration.com](mailto:irl@calibration.com)



**POCKET TESTBENCH**, inexpensive RS-232 instrument, with scope, logic, counter, generator modes. Also, products for embedded development. Oricom Technologies, 303-449-6428. [www.sni.net/~oricom](http://www.sni.net/~oricom)

**AFFORDABLE HP** power sensor repair! Most 8481As repaired for \$305 or less. We also handle 478As and many others. Call or fax for more information. Willamette RF, Inc., 541-754-7226, FAX 541-753-4629.

**HP 8621B** plug-in wanted. Contact Dan Marshall, [ddaustin@inetport.com](mailto:ddaustin@inetport.com) or 512-453-1133.

## SECURITY

**SURVEILLANCE-COUNTERSURVEILLANCE:** I buy and sell used equipment. Steve 410-879-4035.

**Sell Nuts & Volts in your store!**

Contact us for complete details.

phone 909-371-8497

fax 909-371-3052

E-Mail [distributors@nutsvolts.com](mailto:distributors@nutsvolts.com)

## Lightwave 2000 Flashlight \$29.95

Four super-bright white LEDs replace the bulb you'd find in a traditional flashlight, providing a long-lasting high-intensity light. LED lights mean your flashlight will last about 14 times longer than a regular flashlight, and these flashlights are waterproof and shockproof. Ideal for short-range use in cars, planes, etc. Flashlight requires 3 AA batteries (included). Manufacturer's limited lifetime warranty even includes the LED lights!

## Geophone

vibration sensing kit

Detect a fly stomping across the desk!



Well maybe not that sensitive, but almost. These vibration sensors made by Geosource® were used in oil exploration to determine geological statistics. They are made with a magnet suspended in a coil and are very sensitive to vibration. Compact size, the unit measures approx. 1.6" high and 1.2" dia. The kit includes a geophone vibration sensor along with parts to build a basic detector that will light an LED. In addition we include a schematic that will show you how to operate a relay. The sensitivity is adjustable, so you can set it to detect elephants and other small creatures. Similar units were used by our armed forces to detect enemy troop movements...the perfect device to alert you to the pitter patter of little Leroy's feet! Unit sensitivity can be set high enough to detect a business card dropped on a table, and we've made it work with vibrations up to 40 feet away! Earthquake or Aunt Agatha...you decide! It's a fun gadget with many uses.

COMPLETE GEOSENSOR KIT.....\$9.95  
GEOSENSOR UNIT ONLY.....\$7.95


**NO TAN LINES!!!  
AMAZING MINI  
MICRO FM RADIO!  
\$7.50**

Much lighter than a heavy jam box with really good sound! This tiny radio (1.5"x1.06"x0.38") has a seek button, reset control, and an on/off switch. Personal listening has never sounded better! Ideal for ballgames, beaches, and work-outs. Battery and nugget style ear-phones included.



Reading this little tiny space will get you a free gift with purchase...go to our website, place your order online, and click on the Nuts & Volts box on our home page!!

## Light-UP Favorites!

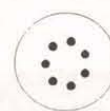

The RF Bug is always a favorite just \$15.00 for a little blinking disk that is triggered by RF within a short range.

## The Photon Microlight II

is a super bright keychain LED flashlight, push to light or switch on for continuous bright illumination. Available in a variety of colors. Blue, Green, White, or Turquoise \$17.50; Red, Yellow, or Orange \$13.50



## SPECTRUM LED A RAINBOW OF LIGHT! \$5.95

Imagine an LED capable of producing all three primary colors in the same package! The entire spectrum, including near-white, can be created! Imagination becomes reality with this T-1-3/4 multi-color LED. Here's the technology: a red chip, a green chip, and two blue chips encased in a diffused T-1-3/4 package. Using various current combinations, you can produce red, orange, yellow, green, aqua, blue, violet or white light! Detailed spec sheet included. What can you do with these (beyond the obvious amaze your friends!)? Create a single indicator system, designate various controls by color, make a multi-color bargraph, make your project something out of the ordinary with multicolor LEDs!

**www.gatewayelex.com**




8123 PAGE BLVD \* ST. LOUIS, MO 63130 \* (314)427-6116  
9222 CHESAPEAKE DR. \* SAN DIEGO, CA 92123 \* (619)279-6802  
2525 FEDERAL BLVD. \* DENVER, CO 80211 \* (303)458-5444  
MAIL ORDERS CALL TOLL-FREE 1-800-669-5810  
FAX ORDERS (314)427-3147

rv0700

THE FINE PRINT: PRICES SUBJECT TO CHANGE WITHOUT NOTICE \* GATEWAY IS NOT RESPONSIBLE FOR PRINTING ERRORS \* MASTERCARD, VISA AND DISCOVER ACCEPTED \* YES, WE'LL TAKE YOUR CHECK - SORRY, NO C.O.D.s \* \$10 MERCHANDISE MINIMUM ON MAIL ORDERS \* SUPPLY OF SOME ITEMS IS LIMITED \* PRICES DO NOT INCLUDE SHIPPING \* UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. \* How do I set my laser printer on auto?






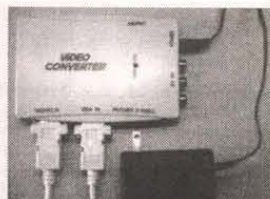


**USE PC MONITOR AS SECURITY MONITOR.** The VGA-801 accepts standard NTSC or PAL inputs for display on any existing VGA/SVGA computer monitor. Small compact size. Over 600 lines of resolution, twice that of standard TV monitor! **\$69 each.** Dealers welcome. MATCO, Inc., 1-800-719-9605; Fax 847-619-0852; E-Mail: sales@mat-co.com Website: www.mat-co.com



**SCANNING MOTOR — A-330SC** with universal mounting bracket accepts all standard 1/4 x 20 threaded CCTV cameras. No tilt, just PAN. 75 degrees of continuous motion with a scan rate of 5 seconds per cycle. 110 volt indoor operation, but can be adapted for outdoor use. Includes 12 foot power cord. Perfect solution to triple your effective camera viewing angle! **\$39/each, or \$25/each** in qty. of 4. Small size, 3-1/2"D x 2"H. MATCO, Inc., Schaumburg, IL. 1-800-719-9605. E-Mail: sales@mat-co.com Website www.mat-co.com

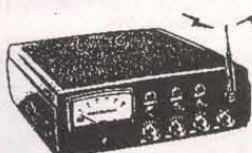

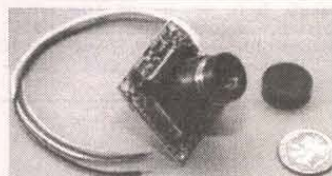**COUNTER-SURVEILLANCE=\$250 HR!** Electronic eavesdropping is unbelievably widespread! Are you sure you're safe? Learn how others (without prior experience) earn **\$250 HR** in the fascinating field of COUNTER-SURVEILLANCE! For FREE catalog call: **1-800-732-5000.** HTTP://WWW.SPY-CITY.COM



**LOW VOLTAGE B/W high RES 430 line CAMERA** with optional black low-profile swivel adjustable enclosure. Pin hole or Std. lens type, 6, 8, and 12mm lens are available. 1/3" CCD, 3.6mm/F2.0 lens included; works from **7.5-13 VDC**, highest voltage range in market. 0.08 lux, IR sensitive; 1.27" x 1.27" x 0.5"D pinhole or 1" deep standard. **\$49 each SPECIAL PRICE FOR JUNE.** Enclosure: \$8; optional lens: \$18. Dealers welcome. MATCO, Inc. 1-800-719-9605. Fax 847-619-0852. E-Mail: sales@mat-co.com Website: www.mat-co.com



**WEATHER RESISTANT OUTDOOR CAMERAS.** WVR-700 type, high impact tempered glass with stand. Black & white (430 lines), or color (420+ lines) available. Standard 3.6mm lenses with optional lenses of 6, 8, and 12 mm at \$20 extra. **B/W \$119/each. Color \$179/each.** Small compact size with sun shield. MATCO, Inc., 1-800-719-9605. E-Mail: sales@mat-co.com Website www.mat-co.com



**CCD BULLET CAMERAS B/W & COLOR.** AX-800 series, weather resistant high impact design with swivel bracket. Will work with Matco's scanning motor. 3/4" diameter x 3" long approx. B/VV: 400 line/0.2 lux. **\$89/each.** Color: 350 lines/2 lux, **\$139/each.** MATCO, Inc., 1-800-719-9605. E-Mail: sales@mat-co.com Website www.mat-co.com



**INFRARED FILTER ELIMINATES 99.9% OF ALL VISIBLE LIGHT — IR-9000.** All B/W CCD cameras are IR sensitive. Place a 25 watt or less light behind the 3" x 3" filter, and you will see in the DARK. **\$18/each.** Purchase 2 for **\$30.** MATCO, Inc., 1-800-719-9605. E-Mail: sales@mat-co.com Website www.mat-co.com



**AS-1004.** FCC approved, 2.4GHz transmitter & receiver with audio! Capable handling total of 4 wireless cameras, range: >300'. Built-in camera, 400 TV line. **\$219 per system.** Additional cameras at **\$129/each.** Matco, Inc. 1-800-719-9605 Fax: 630-350-9546. E-Mail: nsales@mat-co.com Web site www.mat-co.com



## Doppler Direction Finder

Track down jammers and hidden transmitters with ease! This is the famous WAZEBY DFE featured in April 99 QST. Shows direct bearing to transmitter on compass style LED display, easy to hook up to any FM receiver. The transmitter - the object of your DF'ing - need not be FM, it can be AM, FM or CW. Easily connects to receiver's speaker jack and antenna, unit runs on 12 VDC. We even include 4 handy home-brew "mag mount" antennas and cable for quick set up and operation! Whips can be cut and optimized for any frequency from 130-1000 MHz. Track down that jammer, win that fox hunt, zero in on that downed Cessna - this is an easy to build, reliable kit that compares most favorably to commercial units costing upwards of \$1000.00! This is a neat kit!

DDF-1, Doppler Direction Finder Kit ..... \$149.95

## Wireless RF Data Link Modules

RF link boards are perfect for any wireless control application; alarms, data transmission, electronic monitoring...you name it. Very stable SAW resonator transmitter, crystal controlled receiver - no frequency drift! Range up to 600 feet, license free 433 MHz band. Encoder/decoder units have 12 bit Hottel HT-12 series chips allowing multiple units all individually addressable, see web site for full details. Super small size - that's a quarter in the picture! Run on 3-12 VDC. Fully wired and tested, ready to go and easy to use!

RX-433 Data Receiver ..... \$16.95 TX-433 Data Transmitter ..... \$14.95 RXD-433 Receiver/Decoder ..... \$21.95 TXE-433 Transmitter/Encoder ..... \$19.95

## World's Smallest TV Transmitters



We call them the 'Cubes'.... Perfect video transmission from a transmitter you can hide under a quarter and only as thick as a stack of four pennies - that's a nickel in the picture! Transmits color or B&W with fantastic quality - almost like a direct wired connection to any TV tuned to cable channel 59. Crystal controlled for no frequency drift with the high power 100 mW unit goes up to 1/4 mile. Their very light weight and size make them ideal for balloon and rocket launches, R/C models, robots - you name it! Units run on 9 volts and hook-up to most any CCD camera or standard video source. In fact, all of our cameras have been tested to mate perfectly with our Cubes and work great. Fully assembled - just hook-up power and you're on the air! One customer even put one on his dog!

C-2000, Basic Video Transmitter ..... \$89.95 C-2001, High Power Video Transmitter ..... \$179.95

## CCD Video Cameras

Top quality Japanese Class 'A' CCD array, over 440 line line resolution, not the off-spec arrays that are found on many other cameras. Don't be fooled by the cheap CMOS single chip cameras which have 1/2 the resolution, 1/4 the light sensitivity and draw over twice the current! The black & white models are also super IR (Infrared) sensitive. Add our invisible to the eye, IR-1 illuminator kit to see in the dark! Color camera has Auto gain, white balance, Back Light Compensation and DSP! Available with Wide-angle (80°) or super slim Pin-hole style lens. Run on 9 VDC, standard 1" pin-p video. Use our transmitters for wireless transmission to TV set, or add our IB-1 Interface board kit for super easy direct wire hook-up to any Video monitor, VCR or TV with A/V input. Fully assembled, with pre-wired connector.

CCDWA-2, B&W CCD Camera, wide-angle lens ..... \$69.95 CCDPH-2, B&W CCD Camera, slim fit pin-hole lens ..... \$69.95 CCDCC-1, Color CCD Camera, wide-angle lens ..... \$129.95 IR-1, IR Illuminator Kit for B&W cameras ..... \$24.95 IB-1, Interface Board Kit ..... \$14.95

## AM Radio Transmitter

Operates in standard AM broadcast band. Pro version, AM-25, is synthesized for stable, no-drift frequency and is settable for high power output where regulations allow, typical range of 1-2 miles. Entry-level AM-1 is tunable, runs FCC maximum 100 mW, range 1/4 mile. Both accept line-level inputs from tape decks, CD players or mike mixers, run on 12 volts DC. Pro AM-25 includes AC power adapter, matching case and bottom loaded whip antenna. Entry-level AM-1 has an available matching case and knob set that dresses up the unit. Great sound, easy to build - you can be on the air in an evening!

AM-25, Professional AM Transmitter Kit ..... \$129.95 AM-1, Entry level AM Radio Transmitter Kit ..... \$29.95 CAM, Matching Case Set for AM-1 ..... \$14.95

## Mini Radio Receivers

Imagine the fun of tuning into aircraft a hundred miles away, the local police/fire department, ham operators, or how about Radio Moscow or the BBC in London? Now imagine doing this on a little radio you built yourself - in just an evening! These popular little receivers are the nuts for catching all the action on the local ham, aircraft, standard FM broadcast radio, shortwave or WWV National Time Standard radio bands. Pick the receiver of your choice, each easy to build, sensitive receiver has plenty of crystal clear audio to drive any speaker or earphone. Easy one evening assembly, run on 9 volt battery, all have squelch except for shortwave and FM broadcast receiver which has subcarrier output for hook-up to our SCA adapter. The SCA-1 will tune in commercial-free music and other 'hidden' special services when connected to FM receiver. Add our snazzy matching case and knob set for that smart finished look!

AR-1, Airband 108-136 MHz Kit ..... \$29.95 HFRC-1, WWV 10 MHz (crystal controlled) Kit ..... \$34.95 FR-1, FM Broadcast Band 88-108 MHz Kit ..... \$24.95 SR-1, Shortwave 4-11 MHz Band Kit ..... \$29.95 SCA-1 SCA Subcarrier Adapter kit for FM radio ..... \$27.95 FR-6, 6 Meter FM Ham Band Kit ..... \$34.95 FR-10, 10 Meter FM Ham Band Kit ..... \$34.95 FR-146, 2 Meter FM Ham Band Kit ..... \$34.95 FR-220, 220 MHz FM Ham Band Kit ..... \$34.95 Matching Case Set (specify for which kit) ..... \$14.95

## PIC-Pro Pic Chip Programmer

Easy to use programmer for the PIC16C84, 16F84, 16F83 microcontrollers by Microchip. All software - editor, assembler, run and program - as well as free updates available on Ramsey download site! This is the popular unit designed by Michael Covington and featured in Electronics Now, September 1998. Connects to your parallel port and includes the great looking matching case, knob set and AC power supply. Start programming those really neat microcontrollers now...order your PICPRO today!

PIC-1, PICPRO PIC Chip Programmer Kit ..... \$59.95

**Order Toll-free: 800-446-2295**

Sorry, no tech info, or order status at 800 number

For Technical Info, Order Status  
Call Factory direct: 716-924-4560

**RAMSEY ELECTRONICS, INC.**  
793 Canning Parkway Victor, NY 14564

See our complete catalog and order  
on-line with our secure server at:  
**www.ramseyelectronics.com**

## 1 GHz RF Signal Generator



A super price on a full featured RF signal generator! Covers 100 KHz to 999.9999 MHz in 10 Hz steps. Tons of features; calibrated AM and FM modulation, 90 front panel memories, built-in RS-232 interface, +10 to -130 dBm output and more!

Fast and easy to use, its big bright vacuum fluorescent display can be read from anywhere on the bench and the handy 'smart-key' has great analog feel and is intelligently enabled when entering or changing parameters in any field - a real time saver! All functions can be continuously varied without the need for a shift or second function key. In short, this is the generator you'll want on your bench, you won't find a harder working RF signal generator - and you'll save almost \$3,000 over competitive units!

RSG-1000B RF Signal Generator ..... \$1995.00

## Super Pro FM Stereo Transmitter

Professional synthesized FM Stereo station in easy to use, handsome cabinet. Most radio stations require a whole equipment rack to hold all the features we've packed into the FM-100. Set freq with Up/Down buttons, big LED display. Input low pass filter gives great sound (no more squeals or swishing from cheap CD inputs!) Limiters for max 'punch' in audio - without over mod, LED meters to easily set audio levels, built-in mixer with mike, line level inputs. Churches, drive-ins, schools, colleges find the FM-100 the answer to their transmitting needs, you will too. Great features, great price! Kit includes cabinet, whip antenna, 120 VAC supply. We also offer a high power export version of the FM-100 fully assembled with one wait of RF power, for miles of program coverage. The export version can only be shipped if accompanied by a signed statement that the unit will be exported.

FM-100, Pro FM Stereo Transmitter Kit ..... \$249.95 FM-100WT, Fully Wired High Power FM-100 ..... \$399.95

## FM Stereo Radio Transmitters

No drift, microprocessor synthesized! Great audio quality, connect to CD player, tape deck or mike mixer and you're on-the-air. Strappable for high or low power! Runs on 12 VDC or 120 VAC. Kit includes snazzy case, whip antenna, 120 VAC power adapter - easy one evening assembly.

FM-25, Synthesized Stereo Transmitter Kit ..... \$129.95

Lower cost alternative to our high performance transmitters. Great value, easily tunable, fun to build. Manual goes into great detail about antennas, range and FCC rules. Handy for sending music thru house and yard, ideal for school projects! Too - you'll be amazed at the exceptional audio quality! Runs on 9V battery or 5 to 15 VDC. Add matching case and whip antenna set for nice 'pro' look.

FM-10A, Tunable FM Stereo Transmitter Kit ..... \$34.95 CFM, Matching Case and Antenna Set ..... \$14.95 FMAC, 12 Volt DC Wall Plug Adapter ..... \$9.95

## RF Power Booster

Add muscle to your signal, boost power up to 1 watt over a freq range of 100 KHz to over 1000 MHz! Use as a lab amp for signal generators, plus many foreign users employ the LPA-1 to boost the power of their FM transmitters, providing radio service through an entire town. Runs on 12 VDC. For a neat finished look, add the nice matching case set. Outdoor unit attaches right to the antenna for best signal - receiving or transmitting, weatherproof, too!

LPA-1, Power Booster Amplifier Kit ..... \$39.95 CFM, Matching Case Set for LPA-1 Kit ..... \$14.95 LPA-1WT, Fully Wired LPA-1 with Case ..... \$99.95 FMBA-1, Outdoor Mast Mount Version of LPA-1 ..... \$59.95

## FM Station Antennas

For maximum performance, a good antenna is needed. Choose our very popular dipole kit or the Comet, a factory made 5/8 wave coilinear model with 3.4 dB gain. Both work great with any FM receiver or transmitter.


TM-100, FM Antenna Kit ..... \$39.95 FMA-200, Vertical Antenna ..... \$114.95

**VISA MasterCard AMERICAN EXPRESS DISCOVER**

**ORDERING INFO:** Satisfaction Guaranteed. Examine for 10 days, if not pleased, return in original form for refund. Add \$6.95 for shipping, handling and insurance. Orders under \$20, add \$3.00. NY residents add 7% sales tax. Sorry, no CODs. Foreign orders, add 20% for surface mail or use credit card and specify shipping method.


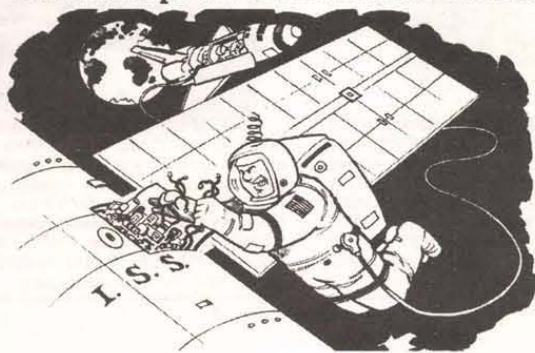
## Callbacks up here can be a matter of life and death.



Technicians at NASA's Space Shuttle Logistics use the **CapAnalyzer 88A** to be sure equipment is in perfect condition before being launched where service calls could be somewhat of a problem. The **CapAnalyzer 88A** is also used by NBC TV, General Motors, Sears Service, Time Warner Communications, Panasonic, Matsushita Industrial, and Pioneer Electronics technicians, as well as thousands of independent TV, computer monitor, VCR and industrial service technicians. They prefer the **CapAnalyzer 88A** because it checks electrolytic capacitors for leakage and ESR *in-circuit*, accurately.

Check [www.eds-inc.com/88users.html](http://www.eds-inc.com/88users.html) for actual users' comments as they compare their own **CapAnalyzer** to the "wizards" and "z-meters" they already own. No unsoldering to check out-of-circuit, no mistaking a

shorted or leaky cap as good, as other "ESR" meters do, no guessing about whether a value is good or bad. With the exclusive three-color comparison chart right on the front panel, auto-discharge, multi-beep alert, and one-handed tweezer test probe, even your grandmother could find defective caps in that problem PWM power supply, TV, computer monitor, VCR, or industrial control board in just seconds. And because it's handheld you can service anything anywhere. It's no wonder that almost 60% of **CapAnalyzer** sales are by referrals, or service managers buying additional units. In fact, our distributors tell us it's the most asked-for-by-name piece of test equipment they sell.


So stop wasting time and come back down to Earth. You can have your own **CapAnalyzer 88A** for only \$179. With our exclusive 60-day satisfaction-or-money-back guarantee, you risk nothing. Prepare to be amazed: your only problem will be running out of work as you take care of all of those "dogs" that you've been sitting on. We're **Electronic Design Specialists**. We make test equipment designed to make you money. Check out [www.eds-inc.com](http://www.eds-inc.com) for all of the details. Available worldwide, at your distributor now, or call 561-487-6103. (And thanks to all our customers for making us #1! -Dave)

Write in 44 on Reader Service Card.

**DEALERS & OEMs only. Highest quality CCTV products**, not cheap imports. See our line card at [www.ddaustin.com](http://www.ddaustin.com) If you've been lied to, ignored, or haven't found an experienced distributor, contact Detection Dynamics. 512-453-1133. We are not for individuals, hobbyists, or spy shop customers. We are for security professionals & volume users.

**SEEKING DISTRIBUTORS FOR SECURITY PRODUCTS.** Matco, Inc., Schaumburg, IL 630-350-0299. [www.matco.com](http://www.matco.com)

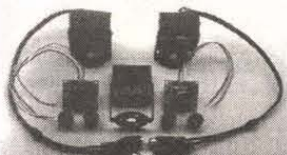**ALARMLAND.COM SECURITY** devices for professionals. Motion detectors, panels, contacts, CCTV, and more. Fax your order to 732-840-1390.



**COLOR — LOW LIGHT 2 LUX CCD** pin hole and standard lens available, only 1.37" x 1.37". \$109 each, enclosure \$10 extra. Sony sensor: Matco, Inc., 1-800-719-9605 Fax: 630-350-9546. E-Mail: [nsales@matco.com](mailto:nsales@matco.com) Web site [www.matco.com](http://www.matco.com)




**40 DAYS and 40 NIGHTS RECORDER.** TLR-6960 time lapse, can be activated by either contact closure or continuous duty operation with standard T-120 tape. Special price \$499. Matco, Inc., Schaumburg, IL 1-800-719-9605. E-Mail: [nsales@matco.com](mailto:nsales@matco.com) Web site [www.matco.com](http://www.matco.com)

Subscribe to Nuts & Volts 1800 783-4624

## TELEPHONE LISTENING DEVICE WITH 12 HR. RECORDER

FCC Approved

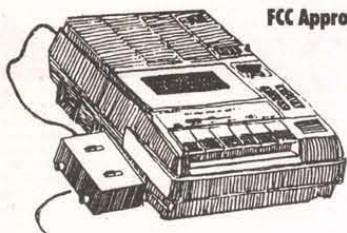

Record telephone conversations in your office or home. Starts automatically when phone is answered, records both sides of phone conversation. Recorder stops when phone is hung up. \$99.95 + \$7 shipping. For telephone listening device separately \$19.95 + \$2 ship.

For comprehensive 50 page catalog of Micro Video, VHF transmitters, Surveillance, and Counter-surveillance and much more! Send \$3.00

Call 321-725-1000

**USI CORP**

P.O. Box N2052 Melbourne, FL 32902  
COD'S OK

## PRIMECELL

IF YOU NEED NEW BATTERIES FOR YOUR ELECTRONIC EQUIPMENT  
DON'T PITCH EM - SEND THEM FOR REBUILDING! - SAVE \$ \$

CUNARD ASSOC. INC., 9343 US RT 220, Bedford, PA 15522

- WE INSTALL NEW Ni-CAD OR Ni-MH BATTERIES INTO YOUR ORIGINAL CASE.
- WE IMPROVE CAPACITY TO BETTER THAN ORIGINAL.
- WE FIX WHAT CAN'T BE FOUND. (OR AFFORDED)
- WE PROVIDE QUICK SERVICE / EXTENDED LIFE FOR OLDER EQUIPMENT
- WE OFFER FREE QUOTES. / FREE RETURN IF QUOTE IS REFUSED.
- WE PROPERLY DISPOSE OF YOUR OLD CELLS BY RECYCLING.
- WE GIVE YOU A 12 MONTH WARRANTY.
- WE WILL BE HERE WHEN YOU NEED US / EST. 1986
- WE SAVE YOU \$\$\$ MONEY \$\$\$

\* NO JOB IS TOO LARGE OR TOO SMALL ..... VOLUME DISCOUNTS AVAILABLE

GENERAL ELECTRIC	UNIDEN	RADIO SHACK
19A704850P (1200mAh) \$ 34.95	APX690 1050 \$ 29.95	HTX Packs \$ 29.95
19A704860P (1800mAh) \$ 39.95	1000 1010 1070 \$ 34.95	New 8.4V pack & chgr
PL19D429763 (777)G1/3 \$ 37.95	1100 1200 Series \$ 36.95	1500mAh nimh \$ 34.95
19A705293P 344A4506P \$ 34.95	BP205 650mAh \$ 19.95	
	BP200 1500mAh \$ 24.95	
	SC150 1500mAh \$ 22.95	
MAYON SA-1155 1160 \$ 39.95		
TAD 1450 1510 1520 \$ 21.95		
MOTOROLA	ICOM	KENWOOD
P200 HT600 MT1000	BP2 / BP3 / BP22 \$ 18.95	PB2 / KNB3 \$ 29.95
NTN 4585 4824 5414 \$ 37.95	BP5 / BP23 / 24 \$ 24.95	PB21/21H \$ 14.95
NTN 5447 5521 5545 \$ 37.95	BP7 / CM7 / BP8 \$ 32.95	PB25/H26 \$ 24.95
NLN 5860 NTN 4327 \$ 39.95	BP180 / CM79 \$ 34.95	
MIDLAND	YAESU	CORDLESS DRILLS
70-B10 B16 B19 B21 \$ 39.95	FNB 3 4 12 14 16 \$ 32.95	Any brand 7.2V \$ 18.95
B25 B26 B32 B36 B60 \$ 39.95	FNB19 21 26 27 38 \$ 32.95	Any brand 9.6V \$ 29.95
	FNB 10 11 17 25 35 \$ 23.95	Any brand 12.0V \$ 32.95
		Any brand 14.4V \$ 37.95
		Any brand 18.0V \$ 45.95
		COMPUTER PACKS
		Send battery for quote.

FOR INFORMATION ABOUT YOUR REQUIREMENTS ..... CONTACT US:  
PHONE OR FAX: (814) 623-7000 E-MAIL TO: [PRIMECELL@AOL.COM](mailto:PRIMECELL@AOL.COM)  
SEND YOUR PACKS FOR FREE QUOTATION VIA UPS, RPS OR US MAIL  
VISIT OUR WEB SITE <http://members.aol.com/primecell/primecell.htm>

**BATTERY REBUILD SERVICE**


MANY OTHERS AVAILABLE - WRITE OR CALL  
**FREE CATALOG**  
ADD \$ 4.50 SHIPPING & HANDLING PER ORDER



**QUAD VIDEO CABLE MODULATOR.** CVS-600 inserts 4 color or black & white composite video signals on unused cable channels, 81 thru 95. Watch 4 remote security cameras from any TV in your home! Built-in signal amplifier and comb filter eliminates any ghosting and actually **IMPROVES** existing video! Only one unit needed with existing cable system. \$199/each and \$169/each in qty. of 4. MATCO, Inc., 1-800-719-9605. E-Mail: [sales@matco.com](mailto:sales@matco.com) Website [www.matco.com](http://www.matco.com)

**CONSUMERTRONICS 120+** exciting manuals: Electronics, computers, Internet, phones, energy, radionics, financial (including stocks), crime-fighting, security, survival, phenomena, **SPECIAL PROJECTS**. Catalog \$3. PO Box 23097, Albuquerque, NM 87192. [www.tsc-global.com](http://www.tsc-global.com)

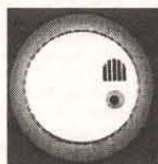**SEE ADMART SECTION**, pages 76 and 77 for other MATCO products, including wireless systems.



**HIDDEN CAMERA!** Looks like a smoke detector, **actually** is a 3.6 mm B/W wide angle lens. Lightweight, put anywhere. **Only \$69.95+ S&H. ORDER TODAY.** Privacy Electronics, 1-877-WIRE-TAP. [WWW.BUGGED.COM](http://WWW.BUGGED.COM)

## SATELLITE EQUIPMENT



**FREE BIG** dish catalog. Low prices! Systems, upgrades, parts, and "4DTV." Skyvision, 1010 Frontier Dr., Fergus Falls, MN 56537. [www.skyvision.com](http://www.skyvision.com) Call 1-800-543-3025.



**BEST PRICING** on 18" satellite TV systems for home and RV. DISH Network DirectTV, multi-room viewing options, accessories, more. [www.skyvision.com](http://www.skyvision.com) Call 1-800-543-3025.

**WANTED: MILITARY** capacitors, resistors, transistors, diodes, ICs, semi's, etc. Please fax/E-Mail excess lists & RFQs 818-769-1002 fax 818-769-1084. [electmatind@earthlink.net](mailto:electmatind@earthlink.net) & <http://www.militarycomponents.com>

**FREE FLYER** on DBS files, hacking, hardware info. Smart card socket \$5 ea. New Atmel 89C52 \$10 ea. Bill 1-800-879-9657.

**FREE SATELLITE TV SYSTEM. USE THIS CERTIFICATE #S-18231100 AND CALL 626-568-0903.**

**PRACTICAL ANTENNA HANDBOOK**, by Joseph Carr. The most popular book on antennas ever written, widely known as "the antenna builder's bible." Only \$49.95! **10% discount to Nuts & Volts subscribers.** Call 1-800-783-4624 to order using Visa or MasterCard.

Continued on page 58



# HANDHELD SATELLITE/CELL PHONE FROM GLOBALSTAR

**F**irst, a little history is due. Everyone is talking about the apparent failure of the Iridium satellite/terrestrial portable phone system that went silent after just a few months of very unprofitable operation. I personally tested one of the Iridium phones down in Mexico; and when the satellite-based system was up, phone calls went through as advertised.

There was absolutely no background hiss off the low-earth-orbit satellite connection, but I must say voice quality sounded a bit mechanical — a little bit less-natural sounding than digitized phone calls using terrestrial PCS micro cell phones.

And, the Iridium handset was anything but micro — it had an interchangeable back that housed much of the satellite transmit and receive circuitry, and it wasn't until you switched out the back with the required terrestrial cell system electronics would the Iridium phone get a bit scaled down.

But probably the biggest question about the Iridium system was exactly how much was it going to cost to make a phone call from another country, or out at sea, or within the coastal waters of our own country. Numerous phone calls to the reps for Iridium could only give us vague answers, so it may have been no wonder

that travelers and mariners held up their purchase of Iridium equipment until pricing could be confirmed.

And I guess now the big question is what to do with the satellites, whizzing around the earth every 100 minutes in the "OFF" mode. With the billions spent to put all of the Iridium satellites up in their low-earth orbits, I can't believe they will all be soon relegated as space junk to come down on purpose in fireballs.


## GLOBALSTAR NOW ON THE AIR

Say who? Globalstar USA is an indirect subsidiary of Vodafone Air Touch Plc., and has exclusive rights to sell Globalstar satellite service across the continental United States. Globalstar USA owns and operates the land-based portion of the Globalstar network throughout the United States, Canada, Mexico, and — good news for mariners — the Caribbean. Globalstar is lead by founding partner Loral Space & Communications, which is a partnership of the world's leading telecommunications service providers and equipment manufacturers, including the Qualcomm handheld, satellite/terrestrial, portable phone I operated during these tests.

Just as important as the 48 low-earth-orbit satellites in space is the network of Globalstar land-based, public-switched, telephone ground stations to receive the mutual uplink/downlink "bent pipe" signal to and from your little battery-operated handheld. While Globalstar has an agreement with service providers in over 100 countries throughout the world, the all-important "mutual view" land stations presently serve North America and parts of Central and South America, as well as Europe, South Africa, and Asia. As of Feb. 2000, this gives available service to customers in 21 countries, with Globalstar planning to introduce service in more than 80 countries by mid-year.

These all-important land stations are called "gateways," and the 13th gateway just came up on the air in Venezuela, providing mobile satellite telephone service across all of Venezuela, as well as neighboring countries like Guyana, Suriname, French Guyana, and a number of French southern Caribbean islands.

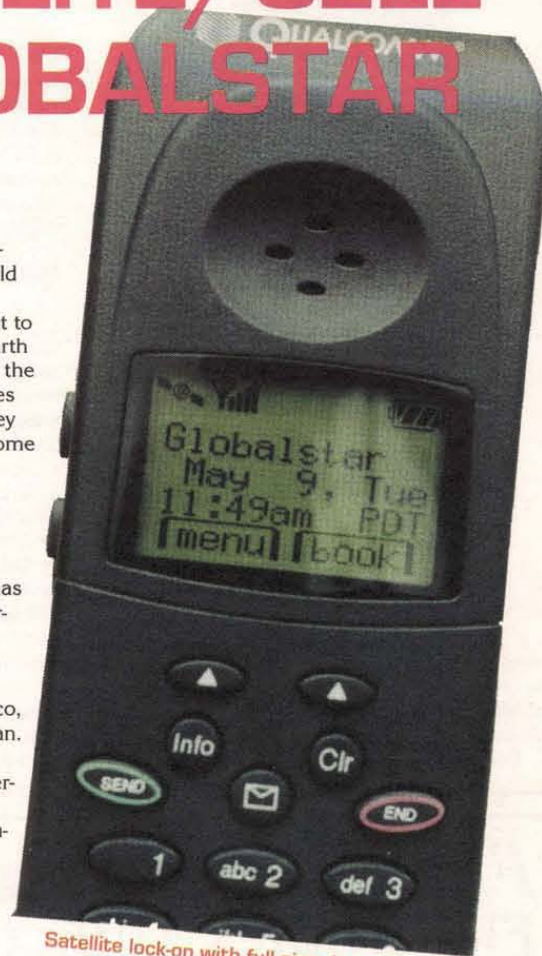While it is certainly impressive to see a global view of 48 low-earth satellites spinning around as the world turns beneath it, it doesn't mean that the Globalstar portable phone in the satellite mode will have a mutual view of the same exact satellite the land station may receive.



Satellite lock-on with full signal strength.

You may visualize the reception area of these low-earth-orbit satellites by tuning in the NASA TV channel during the next Space Shuttle and International Space Station mission. What you might see out the window of the shuttle is pretty close to the signal capture area of a low-earth-orbit satellite. At 500 miles up, the


---

**With the billions spent to put all of the Iridium satellites up in their low-earth orbits, I can't believe they will all be soon relegated as space junk to come down on purpose in fireballs.**

---


satellite could see approximately 1,700 miles to the north, 1,700 miles to the south, 1,700 miles to the east, and 1,700 miles to the west. (You can estimate distance to the horizon in miles by converting miles of altitude to feet of altitude, and then taking the square root of this for your range in miles to the visible horizon. For the radio horizon at microwave frequencies, you might add an additional 10 percent.)

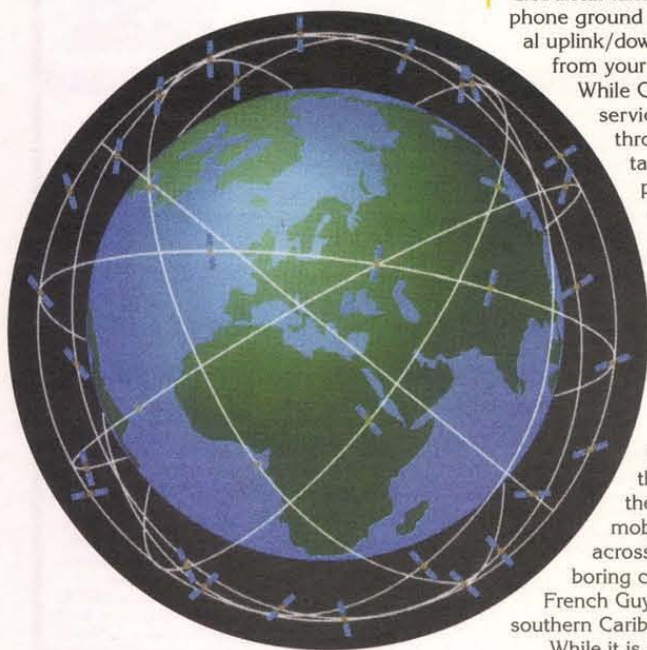For sailors, 48 satellites circling the world does not mean worldwide and oceanwide complete coverage. The earth-bound gateway stations are positioned strategically to pick up the



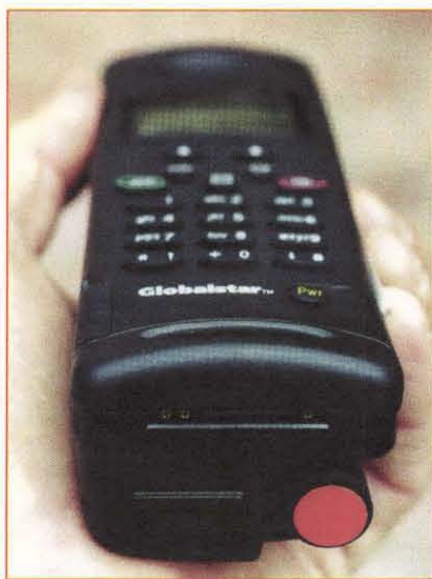**Globalstar's 48-Satellite Low Earth Orbit Constellation**





**The Qualcomm handset will soon support satellite and cell computer calls.**

greatest anticipated volume of incoming signals from those areas of the world where local terrestrial cell phone coverage is either not available or simply impractical due to terrain.

For West Coast sailors, the Texas gateway

station may lose a mutual view of your hand-held Globalstar portable when you are beyond halfway to Hawaii.

"There is no gateway on Hawaii," comments Tom Geller, Senior Account Executive for GSI Group. "But there is plenty of blue water cruising coverage for mariners and sailors, and we invite everyone to look at our present coverage map at [http://www.globalstarusa.com/h\\_06.shtml](http://www.globalstarusa.com/h_06.shtml). We presently have 13 gateways in operation," adds Geller, indicating the enthusiastic response he recently received from boaters and sailors at a recent marine show.

## HOW GOOD?

The Qualcomm handheld phone, Model GSP1600, was an amazing piece of cellular and satellite technology — you get the works all inside this single, compact, portable, analog/digital handset. There are no bulky backs to strap on like Iridium, and no other expensive additions to buy to get the system up and running on your local analog cellular service, or your local digital cellular service, or up to a satellite using digital technology pioneered by Qualcomm. Qualcomm digital is Code Division Multiple Access (CDMA), and AMPS (Advanced Mobile Phone System) is the traditional high-fidelity analog service in the 800 MHz cellular bands.

In our local Southern California AMPS service, talk-and-listen fidelity was spectacular, and best of all, no annoying echoes or delays in the conversation. During our reviews, no one knew I

was on a portable cell phone.

With the push of a button, the system can switch over to the digital network, and talk-and-listen clarity was without any background noise at all, like AMPS, but the conversation had slight delays and both my transmit and receive voice conversations sounded a bit brassy and hollow, typical of any digital cell phone system. It was tough to carry on a fast-paced conversation in the digital mode.

With one more push of a mode button, I switched over to the satellite mode and, within a couple of seconds, the little LCD readout indicated a superb satellite signal, and there was the dial tone. The dial tone sounds exactly like the dial tone in a cell phone set, and I needed to do a double-take to insure I was indeed working off of the secondary Tootsie Roll-sized satellite antenna. As soon as I put my hand around the bigger satellite antenna, I could see the signal just about disappear. Sure enough, I was indeed working off of a low-earth-orbit satellite. My phone call went through just as fast as a typical cell phone call, and there was absolutely no major delay in the conversation to what I had experienced with the old Iridium system. With Iridium, dial tones and keypad tones sounded strangely different, but with the Qualcomm Globalstar system, everything sounded just like I was going through a local cell site.

## BUT HOW LONG?

During repeated tests, we were able to get

## FREE to all Electronics Addicts

\$199 To All Others!

when you mention this special offer #NV2000

For the first time ever we've decided to offer a proprietary software package titled, "Basic Electronics Concepts" to the general public. (Until now, the software hasn't been available to the public, at any price!)

Over 1500 Electronics teachers nationwide use this exact software package to teach Junior High through Graduate Students the basics of electronics, teaching them step by step. The total course of instruction is over 10 full hours and teaches all about resistors, potentiometers, photocells, capacitors, speakers, silicon diodes, SCRs, NPN transistors, PNP transistors, transistor oscillators, and IC timers!

We sell this package day in and day out for \$199 to teachers, parents, and hobbyists that want a detailed, complete method of teaching electronics to themselves, friends or children.

Here's our offer: As part of our "Grand Opening", for a limited time every first time order on the web will receive a copy of this incredible software absolutely free!

We have a limited quantity of the software program in stock, at last check, approximately 1136 units, so place your order today!

Here's a few of the 117 different kits that you can build that we offer ONLINE:

**Color Organs • FM Transmitter Kits Amplifier Kits • Strobe Light Kits Alarm Kits • Radios Kits • Meter Kits Keypad Lock Kits • Infrared Kits and more!**

We carry national brands and guarantee that your order will arrive promptly and be exactly what you expected! **ORDER NOW!**

**Build a kit today!**


PHONE: 877-606-8766

FAX: 800-470-1606

24 Hour Ordering on the web:  
[www.HobbyTron.com](http://www.HobbyTron.com)

**HOBBY TRON**.com

## RF Data Modules

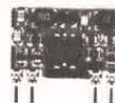

### AM TRANSMITTER

- Small size: 17.78 x 11.43mm
- CMOS/TTL input
- No adjustable components
- Low Current, 4mA typical
- 418MHz or 433.92MHz OOK
- Simple to integrate - simply add antenna, data and power
- Range up to 250ft.
- Wide supply range, 2-14Vdc
- SAW controlled - stability
- Also available in DIL package

AM-RT5 ..... \$12.10



### AM RECEIVER

- Compact size: 38.1 x 13.7mm
- On-board data recovery, CMOS
- Low current, 2.4mA typical
- 2kHz data rate, CMOS/TTL output
- 5Vdc operation
- On 418MHz or 433.92MHz (4xx)
- No adjustable components
- Patented Laser Trimmed component
- High stability
- Sensitivity: -105dBm
- Available also in 0.8mA version

AM-HRR3-4xx ..... \$10.95



### FM TRANSCIVER

- Only 23 x 33 x 11mm
- Up to 40k bps data rate
- 19200 baud with ASCII
- Up to 500ft. range
- 5v operation
- 0.25mW into 50
- 418 or 433MHz FM
- Fast 1ms enable
- Direct interface to 5V CMOS
- Auto TX/RX changeover

BIM-4xx-F ..... \$87.36

### RS232 TRANSCIVER MODULES



- 4,800 to 38,400 bps half duplex
- 3-wire RS232 interface
- µController with user EEPROM
- RS232 interface protected to ±15kV
- Data packetizing performed by user
- Auto TX/RX changeover
- 418 MHz and 433MHz versions
- Range up to 500ft. (0.25mW ver.)
- 0.25mW & 10mW versions
- Reset switch and status LED's
- 7.5-15V dc via DB9 connector, 20mA

BIM-4xx-RS232 .... \$139.30



- Up to 19,200 bps half duplex
- 3 wire RS232 interface
- Range up to 500ft
- Transparent data packetizing
- Supports 8 or 9 bit protocols
- Self test function
- Reset Switch & Status LED's
- 1/4 wave wire antenna on board
- Available in a Simplex Tx/Rx pair (RTcomTX & RTcomRX)
- 7.5V-15Vdc operation

Transceiver..... RTcom-4xx..... \$247.90  
Transmitter..... RTcom-Tx-4xx..... \$ 87.15  
Receiver..... RTcom-Rx-4xx..... \$105.52



**ABACOM**  
TECHNOLOGIES



Tel: (416)236-3858  
Fax: (416)236-8866  
[www.abacom-tech.com](http://www.abacom-tech.com)  
[abacomtech@compuserve.com](mailto:abacomtech@compuserve.com)



about three and a half hours talk time in the satellite mode, with a full day of standby time waiting for an incoming phone call. In the digital mode to a local provider, we could go for almost five hours talk time, and three days standby time. In the AMPS mode, we achieved a little over two and a half hours talk time, and about 14 hours standby.

They supply a charger with a nifty retractable 110 VAC blade assembly that allows you to easily plug in and get a fast recharge. There is also an accessory 12-volt, cigarette-lighter adapter cable, too, for charging and running the equipment in your vehicle or boat.

Another one of our tests was purposely taking the equipment into an area with no cellular coverage. We would use it in the automatic mode and see whether or not it could detect cell dropout, and switch over to satellite. At the bottom of Zion Canyon, it did just that! We were amazed that we could get satellite signals so deep down in the valley. And out on the water, as soon as we cruised well beyond cellular shoreside coverage, the unit quietly switched over to the satellite mode, and didn't miss a beat!

## DATA YET?

Data capabilities are coming, up to 9.6 KBPS, including E-Mail, file transfer, FAX, and

short message service. They say it's going to be the fall before the digital interconnects may take place.

## OKAY, HOW MUCH?

At last we get firm answers to this question on a satellite portable phone system! Globalstar USA offers three distinct domestic pricing plans based on a monthly service charge and fees for satellite connection and use. The basic plan is \$29.99 per month, plus \$1.69 per minute for gabbing offshore or way down in Mexico off of the satellite. If you do a lot of talking, another plan is \$169.99 per month and includes 100 minutes of satellite air time, with each additional minute at \$1.49. And if you really plan to do a lot of yakking off the satellite, they have another plan for \$370.00 that includes 250 minutes of satellite air time, with additional minutes at \$1.39. Add to these amounts your roughly \$30.00 per month to subscribe to local cellular digital or analog coverage that will meet your requirements for staying in touch with this same equipment through your local cell phone provider.

The 11-ounce Qualcomm tri-mode phone has a suggested retail price of \$1,500.00 and, if you want to go with a fixed satellite



One phone for satellite and earth comms.

## GLOBALSTAR NEEDS CUSTOMERS

The demise of the small Iridium satellite phone has cast a shadow on Globalstar's bid to be successful in low-earth-orbit, portable, satellite phone service. In a recent *Wallstreet Journal* report, customers may hold off going with the Globalstar system after they have heard the war stories about friends and acquaintances literally "stuck" with useless Iridium handsets.

In an interview with Antony Bruno in the April issue of *RCR*, a Globalstar spokesman, Mac Jeffery, was quoted, "...If Iridium hadn't happened, we wouldn't be having this conversation — we are paying for their sins ..."

"Analysts turned against us quick," he said. "Everything is exactly as it was before, the only factor that changed was Iridium ... Iridium really spooked people," adds Jeffery.

Analysts calculate it will take about a half-million subscribers by the end of this year to keep Globalstar looking good for continued service. Even one-quarter million subscribers could keep their future looking good. But if less than 100,000 subscribers indeed sign up for Globalstar service and take on the \$1,500.00 phone, Globalstar would be well short of its projected success in this endeavor.

Chances are Globalstar users will begin to see some sort of rebates as marketing efforts get into full swing this summer. Just like Magellan Orbcomm data communicators, Orbcomm users were turned into sales personnel when Orbcomm gave away many months of free airtime to help attract new users to the system. At one point, the handset was being offered "free" for those users that would sign up for three years of monthly service.

So stay tuned into Globalstar — chances are summer specials will keep this new low-earth-orbit communications service viable and affordable, all from a little handset not much larger than a traditional cell phone.



## Quality Used Test Equipment

90 DAY WARRANTY Parts & Labor - 10 DAY TRIAL PERIOD

### HEWLETT PACKARD

105B, Quartz Oscillator, aging < 5 x 10 <sup>-10</sup> per day	\$700
11720A, Pulse Modulator, 2-18 GHz, >80dB on/off ratio	\$300
11975A, 2-8GHz Amplifier (use w/ 11970 series mixers)	\$1500
214B, 10 MHz Pulse Generator, 200W Pulse/500	\$700
2225A, Thinkjet Printer, HP/II	\$150
3314A, Arbitrary/Function Generator	\$900
339A, Distortion Analyzer	\$700
3456A, 6.5 digit Multimeter, HP/IB, cal'd with cert	\$450
3468B, 5.5 digit Multimeter, HP/II	\$300
3852A, Data Acq/Control Unit	\$800
435B, Power Meter w/11730A sensor cable, HP/IB	\$300
436A, Power Meter w/11730A sensor cable, HP/IB	\$550
5004A, Signature Analyzer	\$200
5087A-033, Distribution Amp, 10MHz in/out, 12-chan	\$1000
5180A, Waveform Digitizing Recorder, 20MHz	\$250
5315B-04, 100 MHz Counter	\$200
5328A-011-020-030, 512 MHz Counter w/DVM, HP/IB	\$225
5334A-060, 100 MHz Counter, front & rear input, HP/IB	\$300
5335A, 200 MHz Counter, HP/IB	\$525
5335A-10-40, 200 MHz Counter, Oven Oscillator, HP/IB	\$675
5335A-10-20-30-40, 1.3GHz Counter, Oven/DVM/HP/IB	\$900
54501A, 100MHz, 4-chan Digitizing O'Scope w/HP/IB	\$1100
6034L, Autotriggering Pwr Sup, 60V/10A/200W HP/IB	\$575
6038A, Autotriggering Pwr Sup, 60V/10A/200W HP/IB	\$1250
6253A, Dual Pwr Sup, 0-20V@3A	\$250
6255A, Dual Pwr Sup, 0-40V@1.5A	\$300
6267B, Pwr Sup, 0-40V@30A	\$450
6268B, Pwr Sup, 0-60V@30A	\$600
6271B, Pwr Sup, 0-60V@3A	\$175
6274B, Pwr Sup, 0-60V@15A	\$650
6284A, Pwr Sup, 0-20V@3A	\$100
6289A, Pwr Sup, 0-40V@1.5A	\$100
6294A, Pwr Sup, 0-60V@1A	\$100
7550A, Graphics Plotter, HP/IB	\$200
8112A, 50MHz Programmable Pulse Generator, HP/IB	\$2200
8340A, Synthesized Sweep Generator, 0.01-26.5GHz	\$14000
8350B, Sweep Generator Mainframe	\$1200
83522A, RF Plug-in, 0.1-2.4 GHz RF Plug-in	\$2400
83592B, RF Plug-in, 0.1-20 GHz RF Plug-in	\$7000
8481A, Power Sensor, DC-18GHz, -30 to +20dBm	\$450
8494G, Prog Attenuator, DC-4GHz, 0-11dB, SMA	\$300
8496G, Prog Attenuator, DC-4GHz, 0-110dB, SMA	\$300
8496H, Prog Attenuator, DC-18GHz, 0-110dB, SMA type	\$400
8498A, High Pwr Atten, 25W, DC-18GHz, 30dB	\$400
8501A, Storage Normalizer w/cable (use w/8505A)	\$750
8502A, Transmission Reflection Test Set, 0.5-1300MHz	\$700
8505A, Network Analyzer, 0.5-1300MHz	\$2500
8566A, Spectrum Analyzer, 100Hz-22GHz, HP/IB	\$9000
8566B, Spectrum Analyzer, 100Hz-22GHz, HP/IB	\$18000
8569B, Spectrum Analyzer, 0.01-22GHz, HP/IB	\$4500
8660C/86632B/86603A, 2.6GHz Synth Sig Gen	\$1800
8660D/86632B/86603A, 2.6GHz Synth Sig Gen	\$3200
8903B-001, Audio Analyzer, 20 Hz-100 KHz, rear input	\$1500

9411B, Switch Controller, HP/IB	\$450
9413A, VHF Multi-Port Switch	\$450
E1406A, VXI Command Module	\$525
E1499A, VXI V/382 Controller	\$550
R486A, Thermistor Mount, 26.5-40GHz	\$400

### TEKTRONIX

2445, 150 MHz O'Scope, 4-Channel	\$800
AM503, Current Probe Amplifier	\$250
CFG280, 11MHz Function Gen/100MHz Counter (new)	\$600
P6452, Data Acquisition Probe (use w/ DAS9100)	\$150
P6460, Data Acquisition Probe (for 1240/1241 Analyzer)	\$125
PS503A, Triple Pwr Sup, 0 to +/-20V@1A, 5V@1A	\$150
SG504, Leveled Sine Wave Generator	\$1850
TD5460-1M, 350 MHz Digital O'Scope, 4-Channel, extra memory, includes 2 new P6138A probes & manuals	\$3500
TMS01, 500-series Power Module	\$100
TMS03, 500-series Power Module	\$125

### MISCELLANEOUS

Austron 2100, Lorin-C Timing Receiver	\$1000
Cablesan 256, Programmable Cable Assembly Tester	\$475
Cablesan 512, Programmable Cable Assembly Tester	\$750
EIP 548A, Microwave Counter, 10 Hz-26.5 GHz	\$1800
EMI TCRI60T30, Pwr Sup, 0-160V@30A	\$650
ENI 3200L, RF Power Amp, 0.25-150MHz, 200W	\$7000
ESI SR1030 Resistance Transfer System, 0.1Ω-1MΩ, includes 6 resistor banks, PC101, SPC102, and 2 SB103	\$6500
ESI SR1030-1K, Resistance Standard, 1KΩ/step	\$875
Fluke 5200A, AC Voltage Calibrator	\$1000
Fluke 5440B, DC Calibrator, calibration verified	\$2800
Fluke 6080A/AN, Synth Signal Gen, 0.5-1024MHz, AM, FM, Phase, and Pulse-Mod, High Spectral Purity	\$3200
Fluke 752A, Reference Divider	\$1750
Fluke 845AB, High Impedance Null Detector	\$300
Fluke 87, 4.5-digit RMS Handheld DMM	\$225
Fluke 8922A, Digital RMS Voltmeter, 2 Hz-11 MHz	\$400
Heise 711B, Digital Pressure Gauge, 0 to 30 PSI, 0.5%	\$250
Heise CC (18inch), Pressure Gauge, 0.1% to 1500psi	\$250
Heise CC (18inch), Pressure Gauge, 0.1% to 2000psi	\$250
Hughes 117704F000, TWT Amp, 12-18GHz, 10W	\$800
Krohn-Hite 3550, Filter, Hi/Lo Pass, Band Pass & Reject	\$275
Lambda LQ530, Digital Pwr Sup, 0-10V@14A	\$125
Lambda LQ531, Digital Pwr Sup, 0-20V@8.6A	\$125
Lambda LQ421, Dual Dig Pwr Sup, 0-20V@1.7A	\$125
L&N 4223B, Standard Resistor, 0.001Ω	\$1800
L&N 4385, Shunt Box, 8 ranges (0.75A to 15A), 0.02%	\$250
Racal-Dana 1996, Counter, 1.3GHz, Oven Osc, GPIB	\$275
RF Power Labs M102L, RF Amp, 30Hz-100MHz, 2W	\$400
Rockland 852, Dual Hi/Lo Pass Filter	\$450
Solartron 7061, DMM, 7-1/2 Digit	\$800
Sorensen DCR300-3B, Pwr Sup, 0-300V@3A	\$550
Wavetek 2001, Sweep Generator, 1-1400MHz	\$375
Wavetek 271-02, 12MHz Pulse/Func Gen, GPIB	\$400
Wavetek 859, 50 MHz Prog Pulse Generator, GPIB	\$575

Visit our website at [www.testequipmentplus.com](http://www.testequipmentplus.com)

### TEST EQUIPMENT PLUS

(800) 834-6068, FAX (520) 575-6936  
3331 W. Bright Terrace, Tucson, AZ 85741





# Globalstar

phone set-up, you could spend up to \$2,500.00 for a system aboard your yacht or major land cruiser.

## AND SPEAKING OF LAND

We also tested the Qualcomm phone in the satellite mode in hilly terrain with plenty of trees to obscure the satellite signal. Globalstar builds into their satellite system "path diversity" — a way of taking each call and carrying it by several satellites, allowing for a soft handoff in case one of the satellites loses track of your signal if you should go behind a big pine.

The new satellite maintains the transmission of the original signal to the appropriate terrestrial gateway where the call is then routed locally through terrestrial communications infrastructure. And I am told that the local gateway station with Texas as the one we were going through usually routes calls via land lines and will always try and electronically and automatically avoid sending the call back up to a geostationary satellite so as to minimize echoes and time delays. With the old Iridium system, it was cumbersome to talk through a satellite. With Globalstar, it's just like cellular!

## AND THE FUTURE IS ...

We will continue to see Globalstar work for more gateway land stations in order to expand the usable range to satellites and gateways. However, these expensive gateway stations will only go up if there is a perceived demand for

service in an area presently in a shadow. A few sailors a month might not justify setting up that Hawaiian station as of yet but, if the service really takes off among mariners, we might see a Hawaii gateway in our future. Since this is a major sailing route, I would think that this system would attract plenty of new users.

Popular sailing routes will certainly attract the potential cruise line business, plus commercial freight and fishing vessels, too. Hopefully this will encourage investors to add additional gateway earth stations with a mutual view of the satellite that the sailor will see.

I believe that the user of Qualcomm's Code Division Multiple Access (CDMA) technology will continue to be a pacesetter in digital communications to come. While there is also Time Division Multiple Access (TDMA) technology out there, CDMA seems to have many strong advantages.

For our readers with technical questions, Globalstar invites everyone to log onto their web site and look at the coverage maps plus post questions about their service. A list of Globalstar dealers can be found by calling **Globalstar USA at 1-877-SATPHONE (877-728-7466).**

I was reluctant to give back the demonstra-

**Qualcomm  
GSP  
1600  
tri-mode  
satellite  
handset.**



tion phone because it was so simple to operate, and un-clumsy like other satellite portable phones I had operated a few months earlier. I believe that Globalstar is here to stay and, if you are traveling within satellite coverage with mutual view of the ground stations, do consider Globalstar as a three-way phone system with great promise! **NV**

## Turn Your Multimedia PC into a Powerful Real-Time Audio Spectrum Analyzer

### Features


- 20 kHz real-time bandwidth
- Fast 32 bit executable
- Dual channel analysis
- High Resolution FFT
- Octave Analysis
- THD, THD+N, SNR measurements
- Signal Generation
- Triggering, Decimation
- Transfer Functions, Coherence
- Time Series, Spectrum Phase, and 3-D Surface plots
- Real-Time Recording and Post-Processing modes

### Applications

- Distortion Analysis
- Frequency Response Testing
- Vibration Measurements
- Acoustic Research
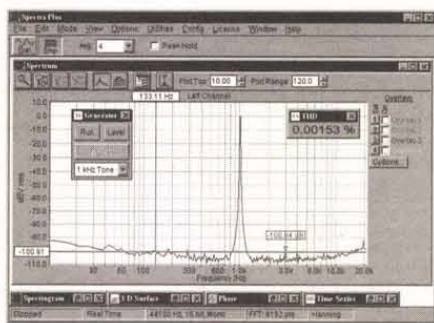
### System Requirements

- 486 CPU or greater
- 8 MB RAM minimum
- Win. 95, NT, or Win. 3.1 + Win.32s
- Mouse and Math coprocessor
- 16 bit sound card



**Priced from \$299**

(U.S. sales only — not for export/resale)

**DOWNLOAD FREE 30 DAY TRIAL!**

[www.spectraplus.com](http://www.spectraplus.com)

**PHS** Pioneer Hill Software  
24460 Mason Rd.  
Poulsbo, WA 98370  
a subsidiary of Sound Technology, Inc.



**Spectra Plus**  
FFT Spectral Analysis System

Sales: (360) 697-3472

Fax: (360) 697-7717

e-mail: [pioneer@telebyte.com](mailto:pioneer@telebyte.com)

**Metric**  
Equipment Sales, Inc.

**800-432-3424**

Fax: 510-264-0886

[www.metricsales.com](http://www.metricsales.com)

**RENT • BUY • SELL**  
Yes, we will buy your surplus equipment!

**Scopes, Meters, Analyzers, Power Supplies, Signal Generators, Counters, Recorders and more**

Hewlett-Packard, Tektronix, Fluke, Dranetz, TTC, Anritsu, Wavetek, Keithley, and more

**Test & Measurement Instruments**

**Over 7000 Models • 6-Month Warranty**

**Save 30-90% • 5-Day Free Trial**



# Win

Each month, **11** lucky names will be drawn!!

## with Nuts & Volts

As a paid subscriber to Nuts & Volts,  
you will be automatically entered each  
month in our prize drawing!

Join

**TODD PHILLIPS** of Frankfort, KY  
**PETER HANTOS** of Los Angeles, CA  
**SAUL NORMAN** of New York, NY  
**ARON BACS** of Burke, VA  
**WES STAFFORD** of Ripley, WV  
**MEL PARKER** of Dacula, GA

**FRANK PHILIP** of Campbell, OH  
**KEVIN HOSHAU** of Stratford, IA  
**RICHARD BOGDAN** of  
Schaumburg, IL  
**HENRY VEITH** of Metairie, LA  
**CHUCK HAYES** of Phoenix, AZ

This month's sponsor ...

### GENERAL DEVICE INSTRUMENTS

**1-800-760-3820**  
**WWW.GENERALDEVICE.COM**

GDI will be providing a Rommaster II — a 32 Pin, Universal Programmer by XEL-TEK. Retail value \$199.00!! Features include printer port interfaces, parallel communication, uses address 278H, 378H, 3BCH, easy interface to LAPTOP, PC, PS/2 or compatibles, mouse support, user-friendly menu-driven software interface, high-speed programming, plus cost-effective hardware and flexible software.

**NETCOM** (page 19) will continue to provide prizes monthly!

**To Subscribe** — Just fill in and mail the card supplied in the magazine or call our toll free order line at **(800) 783-4624** with a Visa or MasterCard.

If you do not wish to order a subscription, but would like to be entered in our drawing, simply send or E-Mail your name, address, and telephone number to *Nuts & Volts*, 430 Princeland Ct., Corona, CA 92879 or [drawing@nutsvolts.com](mailto:drawing@nutsvolts.com). No phone entries accepted. All orders/entries must be received by the last day of the month to be included in that particular month's drawing.

When Visiting Disney World And Sea World...  
Come To The World Of Electronic Surplus!

**SKYCRAFT**

PARTS & SURPLUS, INC.  
ORLANDO, FLORIDA



Located At The Intersection Of I-4  
And Fairbanks Avenue.

Self-Service Retail Outlet Featuring Commercial  
And Government Electronic Surplus Including:

- |                    |                       |
|--------------------|-----------------------|
| ★ WIRE             | ★ COAX                |
| ★ SWITCHES         | ★ RELAYS              |
| ★ RESISTORS        | ★ HARDWARE            |
| ★ TRANSISTORS      | ★ CAPACITORS          |
| ★ TRANSFORMERS     | ★ PANEL METERS        |
| ★ TEST EQUIPMENT   | ★ CIRCUIT BOARDS      |
| ★ NI-CAD BATTERIES | ★ INTEGRATED CIRCUITS |

\*\*\*\*\*

**We Buy Surplus  
Electronic Parts —  
FAX your list.**

[www.skycraftsurplus.com](http://www.skycraftsurplus.com)

FAX 407/647-4831

PH 407/628-5634


P.O. BOX 536186

ORLANDO, FLA. 32853-6186

**HOURS:**  
Monday - Friday 8:30-6:00  
Saturday 8:30-5:00



### The Pocket Programmer

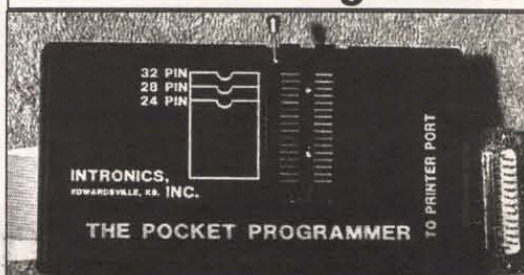

The portable programmer that uses the printer port of your PC instead of an internal card. Easy to use software that programs E(E)prom, Flash & Dallas Ram. 27(C)/28(C)/28F/ 29F/29CXXXX & 25XX series from 16K to 8 Megabit with a 32 pin socket. Adapters available for Pic, MCU's 874X, 875X, 40-Pin X 16 & Serial Eprom's, PLCC, 5-Gang, 82/74 Prom's and Eprom Emulator to 32K X 8.  
Only \$129.95

Same Name, Address & Phone Number for 16 Years....  
Now isn't that Amazing ?

**Intronics, Inc.**

Box 13723 / 612 Newton St.

Edwardsville, KS 66113

Tel. (913) 422-2094

Fax (913) 441-1623 Visa / Master Charge / Amex

Add \$5.00 COD

Add \$4.00 Shipping



# A Tethered *Backyard* Explorer-Bot

by Karl Lunt

*Why use a wire tether?  
Why not use RF links?*

I've had a lot of fun recently running Tacklebot around in my backyard. Long-time readers of my past "Amateur Robotics" column will recognize Tacklebot as a machine I built using a sturdy, plastic fishing tackle box as a frame. If you haven't yet seen Tacklebot, stop by my web page at [www.seanet.com/~karllunt](http://www.seanet.com/~karllunt) and check it out.

Basically, Tacklebot consists of two Dayton 2L011 gearhead motors bolted to a length of 1/4-inch aluminum plate, in turn, bolted to the underside of a large tacklebox. The robot uses a large single caster up front, giving it a three-point support system. Electronics consist of a 68hc11 BOTBoard+ (BB+), a motor controller made of power MOSFETs and DPDT relays, and a

National Semiconductor SimpleSwitcher® power supply board. You can find all the details of Tacklebot's construction in my book, *Build Your Own Robot!*, so I'm not going to go into a lot of detail here.

But I am going to discuss the tether I hooked to Tacklebot to give me remote control over my robotic explorer. Adding a simple tether — in the form of a long cable with suitable connectors — to an easily-constructed robot frame can give you a powerful, fun-to-run machine with little cost or work.

Long-time 'bot builders are probably asking, "Why use a wire tether? Why not use RF links?" A tether solves some nasty problems that crop up when you try to go wireless. First, a wire teth-

er is simple and cheap to build. I paid \$25.00 for 100 feet of flexible, tough 10-conductor shielded cable at the local surplus store. This bought me a video link, a serial communications link, and a 12 VDC power conduit. In one stroke, I eliminated two sets of RF connections and added a power link that I could never have made wireless.

A wire tether also offers a means of recovering a fallen robot that has gone someplace you can't or won't go. I ran Tacklebot into the crawl-space under my house during its testing phase, and a couple of times I had to drag the machine out by its tether when it got stuck. Sure, I could have crawled down there after it, but that's not the point. Had I been exploring a dangerous or impossibly small area, I would have had a tough time recovering my robot. In this case, a wire tether offers a big advantage over wireless links.

Finally, you can build a wire tether in just an evening or two, and spend the rest of your time playing with your robot. I've built a few wireless links in my day, and they always seem to take longer to install and cost more than I planned. They do have their purposes, but the name of the game is "play" and you can play faster by adding a wire tether. After you have played with your tethered robot for a while, you can always add wireless links later.

## Design of a wire tether

The tether I built for Tacklebot carries three signals; refer to the accompanying diagram of a wire tether design (Figure 1). The RS-232 serial link handles commands from my laptop PC and data returned by the robot. The video link hooks to a small black and white video camera mount-




A look at Tacklebot's rear apron, showing the main power switch, motor power switch, DB-25 tether connector, and battery charger jack.


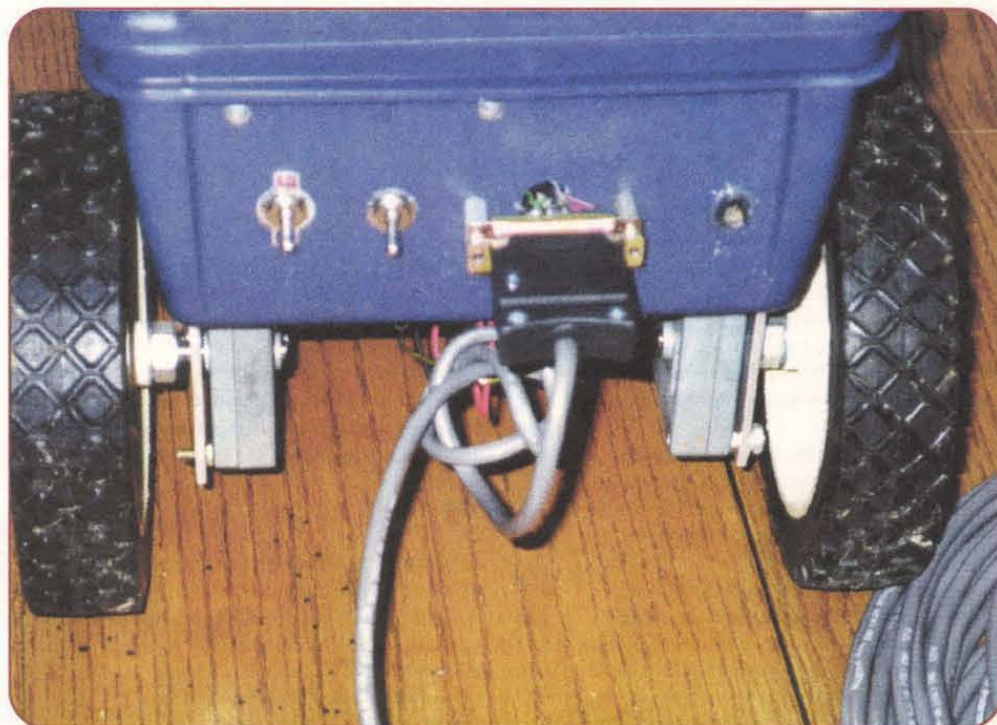
## Ready to go!

I've tied the tether's cable through the restraining loop underneath the robot's frame, then hooked the tether to the DB-25 connector on the rear apron. All I need now is to apply power and do some exploring.



ed on the front edge of the robot. The 12 VDC power link provides the 120 mA of current needed by the video camera, so the camera doesn't add an extra drain on the robot's batteries.

The cable I chose for my tether contains 10 26 AWG wires and a separate drain wire with shield. I used two wires each for the 12 VDC and ground signals to make sure they had a low resistance down the 100-foot length of cable. Thus, I need a total of seven wires for my tether signals, leaving me three spares for extra features later.

I chose to terminate each end of the cable in a DB-25 connector; I put a female connector on the robot end of the cable and a male on the computer end. I realize that this connector scheme is far larger than it needs to be, but I was in a hurry and the stores were closed. I would have preferred DB-15s, but I had DB-25s laying around, so that's what I used.

When you build your cable, be sure to add good-quality hoods to the connectors at each end. These only cost a buck or so, and will protect the connections from casual moisture and physical damage. Get the hoods that provide strain relief, because the cable will get a good workout and it's a royal pain tracking down failures caused by fatigued connections.

The RS-232 signals used in the tether are your basic serial communications signals. The video signal is the NTSC video generated by the B/W camera. Normally, you would use coax for this signal, but this is a fairly short run, and I

haven't seen any problems with the signal displayed on my video monitor. In fact, the security system that used this camera originally included about 60 feet of small-gauge zipcord wire for signal transmission, so I figured my cabling would be good enough.

When I first designed this tether, I had envisioned another use for the 12 VDC power link. I was going to build a simpler frame than Tacklebot; a frame consisting only of motors and electronics, but no batteries. The robot would take its motor power from the 12 VDC feed in the tether. This would let me build a much lighter, smaller frame and give me more useful power from the motors, which wouldn't have to waste so much torque lugging batteries around.

For various reasons, I had to abandon this idea and rework Tacklebot instead. But building such a frame appeals to me. It would make a great club project, and could serve as the springboard for a fully wireless robot. And you wouldn't have to bother with battery chargers, extra weight, or the added size required for those big batteries.

I used a Radio-Shack lump-in-the-line 12 VDC power supply as the source of the power feed in my tether. It is rated for an amp or so of current, well beyond the needs of my video camera. The model I'm using

— 273-1653 — even includes a push-button circuit breaker on the top; this came in very handy at least once, and spared me having to replace some fried components.

### A simple pan head

Mounting a video camera on a robot lets you get a whole new view of the world. Seen from a height of about 16 inches, my backyard looks very alien and jungle-like. But driving a robot around with a camera that can only look forward can prove challenging. You can't look to the side to see how close you are to a wall or shrub, and you can't look sideways to gauge your rate of travel. Thankfully, adding a pan head to your camera takes nothing more than a



## EPROM+

A device programming system for design, repair and field service

- ◆ EXCEPTIONAL POWER FOR THE PRO
- ◆ EASY-TO-USE FOR THE NOVICE

**Here's what you get:** A rugged, portable programming unit including the power pack and printer port cable both of which store inside the case. A real printed user and technical manual which includes schematic diagrams for the programming unit plus diagrams for all technology family adapters\*. Comprehensive, easy-to-use software which is specifically designed to run under DOS, Windows 3.1, 95 and 98 on any speed machine. The software has features which let you READ, PROGRAM, COPY and COMPARE plus much more. You have full access to your system's disk including LOADING and SAVING chip data plus automatic processing of INTEL, HEX, MOTOROLA S-RECORD and BINARY files. For detailed work the system software provides a full screen buffer editor including a comprehensive bit and byte tool kit with more than 20 functions.

**Broad device support:** Including FIRST GENERATION EPROMS (2708, TMS2716\*, 25XX etc.) SECOND GENERATION EPROMS (2716-27C080)(8 MEG), 40 and 42 PIN EPROMS\* (27C1024-27C160)(16 MEG) EEPROMS (2816-28C010) PLUS ER5901, FLASH EPROMS (28F29C, 29EE, 29F)(32 MEG), NVRAMS (12,20,X2210/12) 8 PIN SERIAL EPROMS\* (24, 25, 85, 93, 95, 80011A) PLUS ERI400/MS8657\* BIPOLAR PROMS\* (74S/82S), SERIAL FPGA CONFIGURATORS (17CXXX) MICROS\* (874X, 875X, 87C5X, 87C75X, 89C) ATMEL MICROS\* (89S, 90S)(AVR) PIC MICROS\* 8, 18, 28, 40 PIN (12CXXX, 16C5X, 6X, 7X, 8X PLUS FLASH & 17C) MOTOROLA MICROS\* (68705P3/U3/R3, 68HC705C8/C9/J2/P9, 68HC711E9/D3)

□ Includes step-by-step tutorial plus explanation of EPROM fundamentals  
□ 1 YEAR WARRANTY - 30 DAY MONEY BACK GUARANTEE  
\*REQUIRES SNAP-IN ADAPTER (ORDER FACTORY DIRECT OR BUILD YOURSELF)

# \$289

\$5.00 SHIPPING • \$5.00 C.O.D.  
VISA • MASTERCARD • AMEX

ANDROMEDA RESEARCH, P.O. BOX 222, MILFORD, OHIO 45150  
(513) 831-9708 FAX (513) 831-7562

website - [www.arlabs.com](http://www.arlabs.com)

email - [arlabs@worldnet.att.net](mailto:arlabs@worldnet.att.net)

MADE IN THE U.S.A.

You can reach me by E-Mail at:  
[karllunt@seanet.com](mailto:karllunt@seanet.com)

Or hit my web site at:

[www.seanet.com/~karllunt](http://www.seanet.com/~karllunt)

My web site also includes details on ordering my new book, *Build Your Own Robot!* (A. K. Peters, Ltd.; ISBN 1-56881-102-0; \$34.00).



hobby servo motor and some tinkering. Refer to the accompanying diagram of a simple camera pan head (Figure 2).

I started with a Futaba S-148 servo motor, available at most large hobby stores and through the mail from outlets such as Tower Hobbies. This motor provides 42 oz-inches of torque, features a compact design that is easy to mount, and uses standard servo timing pulses for control. Most of the computer boards we use in the Seattle Robotics Society, including the BB+, are already designed to control up to four of these motors, and they are a mainstay of many SRS designs.

When you buy a Futaba servo motor, you also get a package of various control horns and attachments. I started with two control horns. The 1-3/8th inch round horn, mounted on the top of the pan head, holds the bolt that threads into the mounting hole on the underside of my video camera. I drilled a suitable mounting hole on the control horn to hold this bolt. I also drilled out holes for three sets of 4-40 spacers and hardware. I then drilled matching holes in a 1-1/2 inch four-point horn so I could bolt the two horns together as shown.

Next, I put the bolt for mounting the camera into the larger hole on the round control horn, ran a nut down on it to hold the bolt firmly in place, then spun a second nut onto the bolt. Finally, I put the small servo control horn screw (not shown here) into the center mounting hole of the lower control horn. You will use this screw

## A tether solves some nasty problems that crop up when you try to go wireless.

to fasten the pan head assembly to the servo motor shaft. Note that you can push a small Phillips screwdriver through the center of the upper control horn to reach the control horn screw; this gives you access when you need to tighten the screw to the servo shaft.

### Final assembly

I had to do some slicing and dicing on Tacklebot's lid to make room for the pan head servo. The tacklebox is made of tough but flexible plastic, which drills easily and can, with effort, be cut with an Exacto knife. Be very careful while hacking on this plastic with a knife; you can easily slip and cut yourself.

I drilled and cut a hole for the servo motor shaft in the lid of the tacklebox, near the robot's front end. I then positioned the motor and measured for a 1/8th-inch hole on either side of the motor, near the center of the motor frame. I stuck a suitably-sized piece of double-sided foam tape to the face of the servo motor, then used these two holes for a nylon wire-tie to clamp the motor firmly to the inside lid of the tacklebox.

Mounting the tether connector to the outside rear face of the robot frame required more cutting and hacking. I drilled two holes for #4 hardware in a suitable location, then bolted the DB-25 male connector to the outside of the box, using appropriate spacers and hardware. Be sure to use wide #4 washers on the hardware that mounts to the plastic of the tacklebox, to spread the load when you tighten down the screws. This prevents the screwheads or the nuts from drilling right through the plastic and popping out.

I also drilled a large hole between the DB-25 mounting holes, so I could run the wiring harness from the DB-25 connector to the inside of the box. Once I got the wiring inside, I added appropriate connectors for the various signals,

Close-up of Tacklebot's video camera and pan head. The servo-mounted pan head and the camera's field of view combine to provide 180 degrees of coverage.

then dressed them to the proper points inside the robot frame.

I knew I would eventually need to drag the robot around by this tether, and the DB-25 connectors wouldn't stand the strain. So I used a pair of heavy-jawed nippers to cut apart a stout coat hanger. I then used pliers to twist a four-

### PICmicros & BASIC

PicBasic Compiler - \$99.95

PicBasic Pro Compiler - \$249.95

Now it's even easier to program the fast and powerful Microchip PICmicros. The PicBasic and PicBasic Pro Compilers convert your English-like BASIC programs to files that can be put directly into a PICmicro. True compilers for faster, longer programs. BASIC Stamp™ I/II\* libraries. For mid-range PIC12C67x, 14Cxxx, 16C55x, 6xx, 7xx, 8x, 87x, 9xx and high-end 17Cxxx (PicBasic Pro only).

\*BASIC Stamp is a registered trademark of Parallax Inc.

New! PIC-XI  
Experimenter/  
Lab Board

Assembled - \$199.95  
Kit with parts - \$139.95  
Bare PCB only - \$49.95

EPIC Plus PIC Programmer - \$59.95

Programs PIC12C5xx, 67x, 14Cxxx, 16C505, 55x, 6xx, 7xx, 8x, 87x and 9xx.  
Optional ZIF adapters for DIP, SOIC, MQFP, PLCC.  
Runs off two 9-volt batts or optional AC adapter.  
Includes programming software and assembler.

PICProto  
Prototyping Boards

Get it wired quicker! High-quality blank prototyping boards for PICmicros. Holds PICmicro, 5V reg, caps, oscillator, DB9-25, large proto area. \$8.95 - \$19.95

microEngineering Labs, Inc.

Box 7532 Colorado Springs CO 80933  
(719) 520-5323 (719) 520-1887 fax  
<http://www.melabs.com>

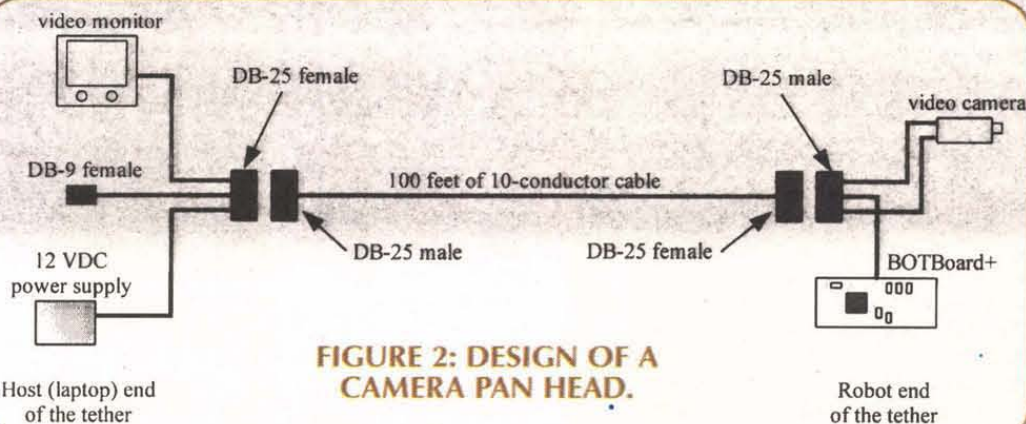


FIGURE 2: DESIGN OF A CAMERA PAN HEAD.



inch length of this wire into a suitable shape that I could bolt to the metal plate on Tacklebot's underside. By using the heavy bolts already holding the motors, I made a strong metal loop to which I could fasten the tether cable. I can either use a wide wire-tie to fasten the tether to the loop, or just knot the cable around the loop. Either way, I have a sturdy mechanical hook-up for the tether, which also provides strain relief for the electrical connection.


### Now, the firmware

I intended to run Tacklebot around my backyard by sending single-key commands from my laptop over the RS-232 cable. The laptop side of the equation was easy; I could just crank up that old standby, ProComm. But the robot side would

require some firmware for my 68hc11 BOTBoard+, and that means SBasic.

Those of you who followed my earlier column are no doubt familiar with my SBasic compiler. It lets me write small, fast programs in a friendly dialect of Basic, without having to resort to 68hc11 assembly language. It isn't a full-featured Basic, like some of the Microsoft products, but it has plenty

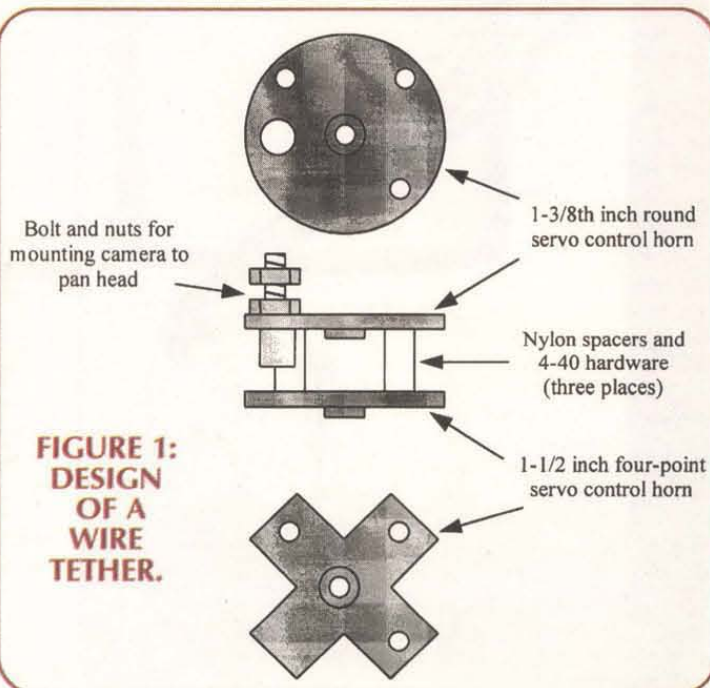You can build a wire tether in just an evening or two, and spend the rest of your time playing with your robot.



VISIT US ON THE WEB AT:  
<http://www.candhsales.com>  
email: [candhsales@earthlink.net](mailto:candhsales@earthlink.net)

**C and H SALES COMPANY**  
2176 E. Colorado Blvd. • Pasadena, CA 91107

**TOLL FREE:  
1-800-325-9465**

**FREE  
148 PAGE  
CATALOG!**

C & H SALES COMPANY HAS BEEN IN BUSINESS FOR OVER FIFTY YEARS.  
WE'RE THE BEST SOURCE FOR GREAT BUYS ON ITEMS LIKE THESE - AND MORE!

#### ELECTRONIC COUNTER

HEWLETT PACKARD,  
Model 5328A. Universal  
counter. Usable to 100  
MHz, 100 ns single shot resolu-  
tion. Has frequency, period, period average, ratio, total-  
ize, scale functions. Two input channels provide individual  
slope, polarity and level settings. Has 9 digit LED  
readout. Input power 100-240 VAC 48-66 Hz 100 VA  
max. Dimensions: 17" wide x 17-1/4" deep x 3-1/2"  
high.

Stock #TE9808

\$250.00

#### MILLIOMETER

HEWLETT PACKARD,  
Model 4328A.  
Designed to measure  
very low resistances.  
Measurement range  
1m ohm to 100 ohms.  
Resolution 20 u ohms.  
Analog meter readout. Ideal for  
measuring contact resistance of switches or relays. This  
unit is also useful for measuring the resistivity of semi-  
conductor devices. (Requires special 4 terminal probes  
which are not supplied, but probably are available from  
Hewlett Packard.) Power input: 115-230 VAC 48-66 Hz,  
5 VA max. Dimensions: 5-1/8" wide x 11-1/2" deep x  
6-1/2" high.

Stock #TE9812

\$200.00

#### PRECISION LINEAR WAY BEARING

This assembly consists of a linear ball bearing track rail  
and two ball bearing slider elements. 280mm long with  
14 countersunk holes for rail mounting. Stainless steel.

Stock #BR2002

\$57.50

#### DIAPHRAGM PUMP

THOMAS  
INDUSTRIES  
Single diaphragm  
oil-less pump. Motor  
rated 115 VAC 60 Hz.  
Pump output is 0.69  
cfm free air. Max. continuous operating pressure 20 psi.

Stock #PC9904

\$49.50

#### SOLA CONSTANT VOLTAGE TRANSFORMER

SOLA ELECTRIC, #93-13-150. Harmonically neutralized  
constant voltage transformer. Rated at 500 watts. Input  
voltage 95 to 130 VAC 60 Hz. Output voltage 120 VAC.  
This unit is designed for rack or bench mounting. The  
meters on the front panel indicate output current and  
input/output voltage. A toggle switch is provided for  
selection of input or output voltage. The input voltage is  
connected at the rear of the unit via a covered electrical  
panel. Two standard 3-wire grounded electrical outputs  
are supplied on the front and rear panels. Dimensions:  
19" wide x 14-1/4" high x 10-1/4" deep. Weight 59 lbs.

Stock #STR9900

\$225.00

## LOWEST COST LCD'S ON EARTH

#### VIDEO LCD

4 Inch Video NTSC \$150  
Sharp P/N 4LU4E  
Composite NTSC & RGB Input  
12:00 OR 6:00 Viewing Angle  
Integrated Backlight & Inverter  
Extended Temp: -10 to +60 C  
Brightness: 260 nits  
Power Consumption: 4.3 Watts  
Contrast: 50 to 1

#### CHARACTER LCD

OPTREX DMF-5005N-EW  
240 x 64 Graphic EL Backlit STN \$30  
OPTREX DMF-5005N  
240 x 64 Graphic Reflective STN \$30  
SANYO DM2023-7G1  
2 x 20 Character Reflective STN \$8  
SHARP LM20A21  
2 x 20 Character Reflective STN \$8  
VIKAY 2035TNLD NOTW-D  
2 X 16 Character LED Backlit STN \$8

#### LCD MONITOR

10.4" DSTN or 12.1" TFT  
Analog SVGA Input  
Autosync  
Auto Sizing  
Automatic Expansion of VGA  
images to SVGA (On 12.1")  
Very Aggressive Pricing  
Starting under \$500!

#### TOUCH MONITOR

EarthVue 10.4  
10.4" VGA TFT  
Analog VGA Input  
105 Nit Brightness  
RS-232 Touch Screen Option  
Only 9.9"W x 7.7"H x 1.5"D  
Ideal For Factory Automation  
Fully Articulating Ball Mount  
Only \$1095 With Touch

#### LCD DISPLAYS

6.3" Mono STN \$60  
9.4" Mono Reflective \$60  
8.4" TFT \$250  
9.4" DSTN \$150  
10.4" TFT \$350  
10.4" DSTN \$240

NoteBook Screens  
340 Models In Stock  
Obsolete Screens Stocked  
Hard To Find LCD? Call!

#### CONTROLLERS

ISA  
PCI  
PC/104  
NTSC  
Analog VGA  
Complete LCD Kits with LCD,  
Controller & Cable Starting  
under \$200



**EARTH**

Computer Technologies

"The World Leader In LCD Recycling"


Ph: (949) 361-2333 Fax: (949) 361-2121  
<http://www.flat-panel.com>

☒ Master Charge ☒ Visa ☒ American Express ☒ Discover

Call us first if you have surplus inventories of electronic, optical, or mechanical items for disposal

**WE BUY & SELL!**



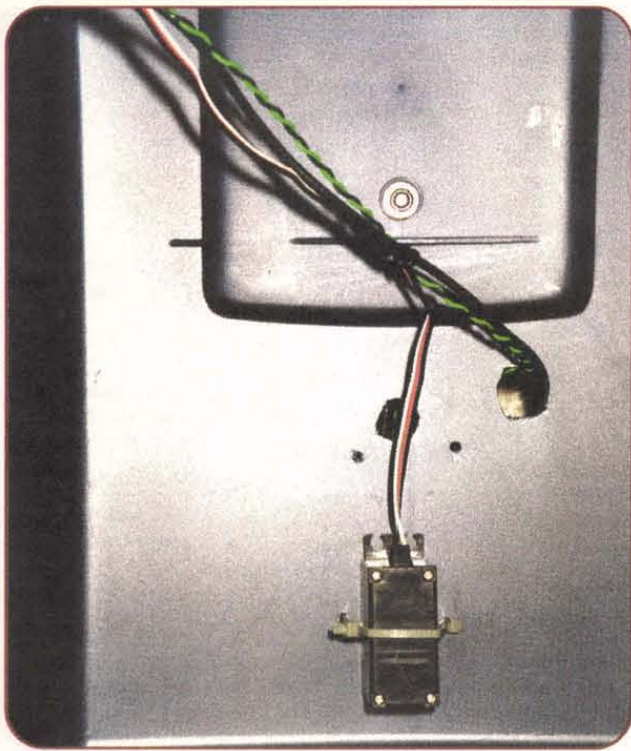

A view of the lid's inside, showing how I mounted the camera's pan head servo. The cable leading to the servo carries the control signal and 5 VDC, while the two cables going out of the lid's top carry power to the camera and return the video signal.

of power for running 'bots, and best of all, it's free. Just hit at my web site and download a copy, complete with the needed 68hc11 assembler.

The design for Tacklebot's firmware began with an earlier version of my Tacklebot firmware. I changed a few elements to give me more control over the robot's speed, and I also added commands for positioning the camera's pan head. Refer to the accompanying listing for details (Figure 3).

When the robot powers up, the firmware starts at label MAIN. After initializing the real-

time interrupt (RTI) subsystem and setting up the motors, it sends a brief message to the user, then waits in a loop for the user to enter a 'G.' This prevents the robot from taking off as soon as I apply power to the motors.

Once I've entered this simple password, the firmware enters a large loop that accepts a character, tests it, and executes the appropriate command. Numbers from 1 to 7 change the position of the camera's pan head; the number 4 moves the camera to the center position. The letters r, l, f, and b let me move the robot right, left, forward, and backward. I can also enter a space to stop the robot.

Since Tacklebot can move at a pretty good clip, I also added the q and z commands to set the speed of the motors. Note that entering either letter stops the motor but sets the speed variable for the next motion command. Finally, the e and c commands turn lights on and off, though I don't actually have lights hooked up yet.

As you can see, the firmware is pretty simple, yet it provides ample control for exploring my backyard. Even though the 68hc811e2 chip that I used in my BB+ only has 2K bytes of EEPROM for program storage, this code weighs in at less than 1K, leaving me plenty of room for more features.

```

=====
'
' tackle02.bas
'
' This code supports the motors and pan head. It also accepts
' one-key commands over the serial port (SCI).

include "regs11.lib"
include "servos.bas"

'
' Motor control constants, used by the RTI ISR code to support the
' motors. These constants assume the motors connect as follows:
'
' PB0 1 means right motor goes forward, 0 means no motion
' PB1 1 means right motor reverses, 0 means no motion
' PB2 1 means left motor goes forward, 0 means no motion
' PB3 1 means left motor reverses, 0 means no motion
'
' Note that having PB0 and PB1 both high, or PB2 and PB3 both high, is
' an illegal state, and might damage the drive electronics.

const RMTR_FWD = $01
const RMTR_REV = $02
const LMTR_FWD = $04
const LMTR_REV = $08
const RMTR_STOP = 0
const LMTR_STOP = 0

const SPEED_HALF = $eeee
const SPEED_FULL = $ffff

const PAN_TOC = TOC2
const PAN_CW = $fdc0
const PAN_CCW = $ef80
const PAN_CENTER = $f500
const PAN_INC = (PAN_CW - PAN_CCW) / 6

'
' Variables
'
declare rmtr
declare lmtr
declare rpwm
declare lpwm
declare t
declare k
declare wait
declare n

declare panloc
declare panchg
declare speed

'
' Real-time interrupt (RTI) interrupt service routine
'
' This ISR supports down-counting timers, such as WAIT. It also
' supports PWM of both motors, through the RPWM and LPWM pattern
' variables and the two motor control variables, RMTR and LMTR.
'
' This routine assumes port b controls the motors. See the constant
' declarations above for pin assignments.

interrupt $fff0
pokeb tfig2, $40
if wait <> 0
    wait = wait - 1
endif
t = 0
if rpwm and 1 = 1
    t = rmtr
endif
if lpwm and 1 = 1
    t = t or lmtr
endif
pokeb portb, ((peekb(portb) and $f0) or t)
rpwm = rroll(rpwm)
lpwm = rroll(lpwm)
end

' RTI ISR
' rearm rti
' need to decrement wait?
' if so, do it
' assume no motor voltage
' if right motor is on...
' show it
' if left motor is on...
' show it
' set the motors
' roll masks for next time

'
' SetMotor change the direction of the current motion
'
' Invocation: gosub SetMotor, LeftDir, RightDir
'
' Note: This routine momentarily disables interrupts while it changes
' the low-level motor variables lmtr and rmtr.

SetMotor:
interrupts off
rmtr = pull()
lmtr = pull()
interrupts on
return

'
' no interrupts
' save new direction values
' allow interrupts

'
' SetSpeed change the speed of the current motion
'
' Invocation: gosub SetSpeed, LeftSpeed, RightSpeed

```



# World's Smallest 68HC11 Microcontroller Module!

## MicroStamp11™

- tiny 1-inch x 1.4-inch module
- 5V regulator, 8MHz crystal
- choice of 8K or 32K EEPROM
- plugs into your breadboard like a DIP
- SCI, SPI, OC, IC, timer, interrupts, and more
- all I/O lines brought out to versatile 20-pin connector
- easy programming/code-loading with Docking Module
- 8K Starter Package #MS11SP8K.....\$49\*
- 32K Starter Package #MS11SP32K.....\$60\*
- additional modules from \$34 each


\* Includes MicroStamp11, documentation, PC software, serial cable & Docking Module. Add \$5 for shipping & handling

**Technological Arts**

Phone: (416) 963-8996

Fax: (416) 963-9179

**www.technologicalarts.com**

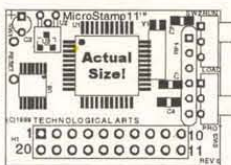

**Possible Applications:**

- remote telemetry
- micro robotics
- smart sensors
- many more!

Visa/MasterCard  
Discover/Amex

## ELECTRONIC MILITARY SURPLUS



## FAIR RADIO SALES

WEBSITE: fairradio.com

E-MAIL: fairradio@wcoil.com

PHONE: 419-227-6573

FAX: 419-227-1313

1016 E. Eureka - Box 1105

Lima, OH 45802

VISA. MASTERCARD. DISCOVER

Address Dept. NV

## AB-1244/GRC MAST KIT

Has twelve aluminum alloy on steel sections form sturdy, yet lightweight 30 foot 1.7" dia mast. Kit includes five each lower and upper sections, one ea lower and upper adapter sections, gin pole swivel base, four ea 36 and 42 ft guy ropes, four guy stakes, two guy rings plus 2.5 pound sledge hammer. Part of OE-254/GRC antenna set; 30 lbs sh. NEW, \$139.50 NYLON BAG for above. New, \$39.50; See Web for details.

## SERVICE MONITOR

Singer Model CSM-1 Communications Service Monitor: Signal Generator 50 KHz - 512 MHz, Frequency Meter, and Amplitude Modulation meter; 0-30% & 0-100%. 17.1x16.2x9.2, 50 lbs sh., used repairable with op's manual, \$250.00

Allow money for shipping on merchandise.

**SEND FOR OUR 2000 CATALOG !!**

Radios - Test Equipment - Tubes - Antennas

## That's a wrap

I've presented here the highlights of my latest additions to Tacklebot, a tethered robot suit-

able for outdoors exploration. You can build on these ideas for your own robot, and the program listing should help you in your firmware design. Be sure to visit my web site for SBasic, and to

see some pictures of Tacklebot in its earlier incarnation.

*And above all, have fun with this hobby!*

NV

\* Note: This routine momentarily disables interrupts while it changes the low-level motor variables lpwm and rpwm.

SetSpeed:

```
interrupts off
rpwm = pull()
lpwm = pull()
interrupts on
return
```

' no interrupts  
' save new PWM values

' allow interrupts

\* GetKey() read a char from the serial port

\* This routine returns 0 if no key is available or the key if one was available.

GetKey:

```
push inkey()
if peek(0) > 0
    place 0, peek(0) and $ff
endif
return pull()
```

' check for key and save it  
' if got a key...  
' mask off bit 8  
' return the key (or 0)

main:  
pokeb baud, \$30  
pokeb scsr2, \$0c

' 9600 baud  
' turn on rcvr and xmtr

```
print "tackle02"
gosub SetSpeed, 0, 0
gosub SetMotor, LMTR_STOP, RMTR_STOP
gosub InstallServo, PAN_TOC
poke PAN_TOC, PAN_CENTER
```

' start with motors stopped  
' connect to the servo motor  
' move to center position

```
print
print "Press 'G' to begin...";
```

' instruct the user

```
pokeb portb, 0
pokeb tflg2, %01000000
pokeb tmsk2, %01000000
```

' all port b lines low  
' set up RTI  
' arm RTI

```
wait = 0
interrupts on
```

' allow interrupts

```
do
    k = usr(GetKey)
    loop until k = 'G'
    print
    print "Ready to rock!"
```

' wait for user to enter a key  
' must enter a G

```
do
    do
        k = usr(GetKey)
        loop until k <> 0
        panchg = 0
        select k
            case '1'
            case '2'
            case '3'
```

' do forever...  
' get a key  
' loop until something to do  
' based on key...  
' 1-7 aligns the camera pan head

```
case '4'
case '5'
case '6'
case '7'
panloc = PAN_CCW + (PAN_INC * (k - '1'))
poke PAN_TOC, panloc
endcase
```

```
case " " ' space means stop motors
gosub SetSpeed, 0, 0
gosub SetMotor, LMTR_FWD, RMTR_FWD
print "Stop ";
endcase
```

```
case 'f' ' f means forward
gosub SetSpeed, speed, speed
gosub SetMotor, LMTR_FWD, RMTR_FWD
print "Forward ";
endcase
```

```
case 'b' ' b means backward
gosub SetSpeed, speed, speed
gosub SetMotor, LMTR_REV, RMTR_REV
print "Backward ";
endcase
```

```
case 'r' ' r means right turn
gosub SetSpeed, speed, speed
gosub SetMotor, LMTR_FWD, RMTR_REV
print "Right ";
endcase
```

```
case 'l' ' l means left turn
gosub SetSpeed, speed, speed
gosub SetMotor, LMTR_REV, RMTR_FWD
print "Left ";
endcase
```

```
case 'q' ' q sets full speed
speed = SPEED_FULL
gosub SetSpeed, 0, 0
print "Full speed ";
endcase
```

```
case 'z' ' z sets half speed
speed = SPEED_HALF
gosub SetSpeed, 0, 0
print "Half speed ";
endcase
```

```
case 'e' ' e means lights on
pokeb portb, peekb(portb) or $30
print "Lights on ";
endcase
```

```
case 'c' ' c means lights off
pokeb portb, peekb(portb) and $cf
print "Lights off ";
endcase
```

print "What? "; ' no idea...

endselect  
loop



# Taking Things Apart:

## The Joy of Microcontroller Disassembly

I like to take things apart. I love that special joy of discovering how something works from the inside out. For me, this is as true for software as it is for hardware. One of the things I like best about working with microcontrollers is the tight coupling

between the assembly code and what happens on the pins. But there is a part of the experience that is opaque, the part between the assembly code and the execution, the Machine Code.

Too many times, I've found a bunch of poorly organized hex files on a disk, or pulled a hex file off an

unlabeled chip with no idea what it does. All I have is a mess of hexadecimal numbers. Through careful disassembly, these can be turned back into human-readable programs. Call me a nerd, but I've found that teasing understanding out of the mystery of machine code is extremely satisfying, not to mention educational.

This article will describe the basic concepts you need to understand how a disassembler works. I will focus on the Microchip instruction set for the ever-popular PIC 16C84 and the Intel INHX8M hex file format, but the ideas hold true for any microcontroller. The conclusion of this article, appearing in next month's issue, will describe how to actually write a disassembler using the delightful Python programming language.

### Examining Assembly Language

The first thing to understand is the difference between assembly language and a high-level language like Basic or C. Assembly opcodes, or mnemonics, are very close to the commands the machine actually understands. They typically do very simple things (especially in a Reduced Instruction Set Computer or RISC chip such as the PIC) like 'ADD RegisterQ, 20' or 'JUMP end-loop.'

Complicated actions are built up out of a bunch of these simple commands. A line in an assembly-language program is very consist-

tent. It may have a label, an opcode, one or two arguments, and possibly a comment. High-level languages tend to have commands that are built out of many assembly commands like 'FOR a = 1 to 10' or 'SEROUT 1,12,300,14,' making it relatively easy to do complicated activities.

A compiler turns these commands into assembly language for the programmer. Many programmers prefer working in assembly language because they can control the efficiency and size of the program better than a compiler can.

Once the assembly language program is written, it is put through an assembler. An assembler is a program that turns the assembly-language source code into the set of bits that is machine code.

Assemblers are available from a number of sources with a variety of features, but the essential function of producing machine code is always the same. Assemblers will usually provide an option to generate either a collection of the bytes laid out as they will be on the chip, which is an object file or a file specially formatted for use with a programming device, which is often an Intel Hex File. Both file types represent machine code.

For the purpose of narrowing the discussion, I will use the Intel Hex File format in my description of disassembly, but the principles are the same for either type of file.

An assembly language program is readable by humans with a little training. (See Listing 1 for an example program.) Careful use of whitespace, variable names, and labels can make it much easier to understand. Many assemblers allow macros — or defined sequences of commands — to be used in code, as well. This simplifies programming and can simulate many of the features of a high-level language. I will stick to straight-assembly language as we look at examples to keep things simple.

When the assembler turns the assembly opcodes into hexadecimal sequences, it will optionally produce a listing file, as well (see Listing 2). This file shows the assembly language program side by side with the hex bytes it is turned into. It also shows the address of each command. This is

:100010001030AB000230AC00AA0AAA1D1128AA01B8

Number of data bytes

End of File Indicator

CRC Checksum

10 0010 00 1030AB000230AC00AA0AAA1D1128AA01 B8

Figure 1 —  
The Intel Hex File  
(INHX8M)  
format

Starting address of data

Data Bytes


INSTRUCTION	DESCRIPTION	MSB -> LSB
ADDWF f,d	Adds w register value with register f value, stores the result in d (0 = w, 1 = f)	00 0111 dfff ffff
ANDLW k	ANDs w register value with literal value k, stores the result in w	11 1001 kkkk kkkk
BSF f,b	Sets bit number b in register f	01 01bb bfff ffff

Table 1 — Example PIC instruction formats

Listing 3 — The  
Intel Hex File of our  
example
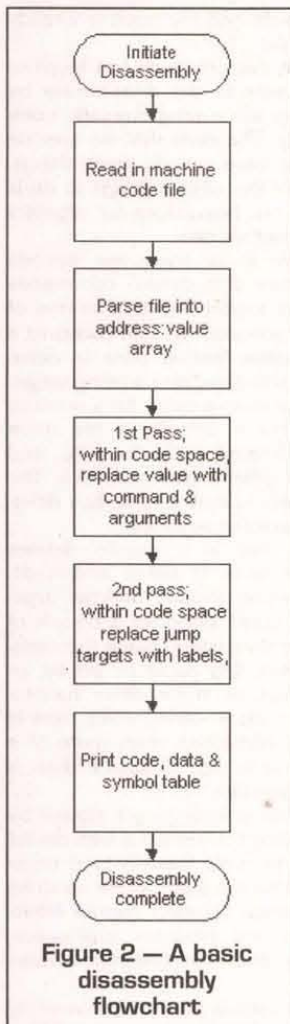
```
:100000008316003086000030850083120030AA007D
:100010001030AB000230AC00AA0AAA1D1128AA01B8
:10002000AA0A2A082B0786001030AB07AB1F1A2834
:10003000AB01AB002B082A078600AC0AAC1D2228B6
:0C004000AC01AC0A2C0885000C28630001
:00000001FF
```





in a number of ways depending on the chip's technology, but it generally involves a special device used to program the chip such as an EPROM programmer or 'burner.' Most of these devices feed one byte or word (two bytes) at a time to the chip. Lots of manufacturers and hobbyists have produced programmers, but almost all of them use a standard format designed to make it easy to feed the bytes to the chip.

A number of formats are used; arguably the most common is the Intel Hex File format INHX8M. (I'll just refer to it as Intel Hex Format.) For brevity's sake, I will focus on only this format. Other formats serve a similar purpose and are easy to understand if you start with the Intel Hex Format first.

The basic format of the Intel Hex File is very simple (see Figure 1). A colon starts a line followed by a byte specifying the number of data bytes on the line. Next is the starting address for the data on the line. A byte follows that defines whether this is the end-of-file or not. The data bytes come next. A CRC checksum of the line is the last byte on the line. Lines can be variable in length.

### A Multipass Disassembler

Our first step in disassembly (see Figure 2) is to strip out the meaningful bytes from the hex file (see Listing 3) and assign them addresses. Using

ADDR	WORD	LABEL	OPERAND	ARG1, ARG2	
0000	1683		BSF	STATUS, 0x5	; Restart Vector
0001	3000		MOVLW	0x0	
0002	0086		MOVWF	PORTB/TRISB	
0003	3000		MOVLW	0x0	
0004	0085		MOVWF	PORTA/TRISA	; Interrupt Vector
0005	1283		BCF	STATUS, 0x5	
0006	3000		MOVLW	0x0	
0007	00AA		MOVWF	0x2a	
0008	3010		MOVLW	0x10	
0009	00AB		MOVWF	0x2b	
000A	3002		MOVLW	0x2	
000B	00AC		MOVWF	0x2c	
000C	0AAA	TARG_1:	INCF	0x2a, F	
000D	1DAA		BTFS	0x2a, 0x3	
000E	2811		GOTO	TARG_4	
000F	01AA		CLRF	0x2a	
0010	0AAA		INCF	0x2a, F	
0011	082A	TARG_4:	MOVF	0x2a, W	
0012	072B		ADDWF	0x2b, W	
0013	0086		MOVWF	PORTB/TRISB	
0014	3010		MOVLW	0x10	
0015	07AB		ADDWF	0x2b, F	
0016	1FAB		BTFS	0x2b, 0x7	
0017	281A		GOTO	TARG_3	
0018	01AB		CLRF	0x2b	
0019	00AB		MOVWF	0x2b	
001A	082B	TARG_3:	MOVF	0x2b, W	
001B	072A		ADDWF	0x2a, W	
001C	0086		MOVWF	PORTB/TRISB	
001D	0AAC		INCF	0x2c, F	
001E	1DAC		BTFS	0x2c, 0x3	
001F	2822		GOTO	TARG_2	
0020	01AC		CLRF	0x2c	
0021	0AAC		INCF	0x2c, F	
0022	082C	TARG_2:	MOVF	0x2c, W	
0023	0085		MOVWF	PORTA/TRISA	
0024	280C		GOTO	TARG_1	
0025	0063		SLEEP		

### SYMBOL TABLE

ADDR	SYMBOL
000C	TARG_1
0011	TARG_4
001A	TARG_3
0022	TARG_2
0000	IND0
0001	TMR0/RTCC/OPTION
0002	PCL
0003	STATUS
0004	FSR
0005	PORTA/TRISA
0006	PORTB/TRISB
0008	EEDATA/EECON1
0009	EEADR/EECON2
000A	PCLATH
000B	INTCON

Listing 4 — Disassembler output

an extremely useful tool for verifying what is really being put onto the chip.

An assembly language opcode and its arguments fit into a very specific set of bits. In the PIC 16C84 family, 14 bits are allotted to hold the command and arguments. The format of these bits is carefully defined (see Table 1.) These bits — or the bits collected together as bytes — constitute the machine code, usually viewed in hexadecimal notation.

Labels and comments are not stored in the machine code. A label represents which number, or address, in the program a command is at; this can be reconstructed from the sequence of commands by the machine. The comment is for humans and the machine doesn't care about it so it never makes it into the machine code.

### The Intel Hex File

Once the machine code is ready as a set of bits, it needs to be moved onto a chip to be useful. This can happen

## They Wrote The Book

The A+ Certification Exam Guide was developed by IBM, the company which set the standard for Personal Computing. It consists of two large volumes and a CD-ROM disk.


If your goal is to become a certified Computer Service Technician, the Guide is the only reference you should need to successfully prepare for the certifying exam. Over 2,000 pages, it is thorough, yet not cumbersome to use. And once you become a certified Technician, it is still useful as a reference.

The A+ Certification Exam Guide was written by training-education specialists with the experience necessary to guide you through the information that is key to passing the exam. Difficult concepts are clearly explained, and topics and skills stressed on the exam are pointed out. In addition, the volumes include helpful graphics, diagrams, tables and charts.

The CD-ROM disk, which is part of the two volume set, not only contains the entire contents of both volumes, but also, hundreds of very useful sample test questions. There are also Self-Assessment sections at the end of each chapter in the Guide.

This 2-volume set is also a tremendous reference work for anybody who wants to know how PCs work or what to do when they don't work.

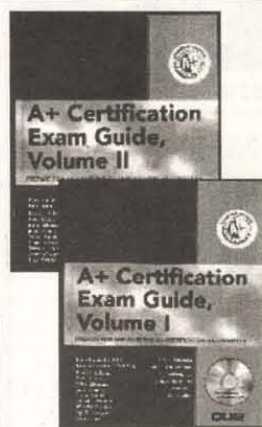The A+ Certification Exam is sponsored by CompTIA.



REGULAR PRICE: \$199<sup>99</sup>



This special price won't last long!!!

ORDER NOW!!!

800-854-7393

WEBSITE: [www.graymarkint.com](http://www.graymarkint.com)

Graymark®





```
STATUS equ 03
PORTA equ 05
PORTB equ 06
TRISA equ 05
TRISB equ 06
RPO equ 05
```

```
LED1REG equ 02a
LED2REG equ 02b
LED3REG equ 02c
```

```
wdtoff
```

```
bsf STATUS,RPO ;init ports
movlw 00
movwf TRISB
movlw 00
movwf TRISA
bcf STATUS,RPO
```

```
movlw 00 ;init led*reg
movwf LED1REG
movlw 010
movwf LED2REG
movlw 002
movwf LED3REG
```

```
loop incf LED1REG ;inc led1reg
      btfss LED1REG,3 ;skip next if >= 8
      goto led1 ;jump
      clrf LED1REG ;clear led1reg
      incf LED1REG ;ledreg1 = 1
```

### Listing 1 — A simple assembly-language program

```
led1 movf LED1REG,w ;move led1reg to w
      addwf LED2REG,w ;combine with led2reg
      ;in w

      movwf PORTB ;output on portb

      movlw 010 ;setup w with increment
      addwf LED2REG,f ;inc led2reg (high nibble)
      btfss LED2REG,7 ;skip next if >= 8
      goto led2 ;jump
      clrf LED2REG ;clear led2reg
      movwf LED2REG ;ledreg1 = 0x10
      movf LED2REG,w ;move led2reg to w
      addwf LED1REG,w ;combine with led1reg
      ;in w

      movwf PORTB ;output on portb

      incf LED3REG ;inc led3reg
      btfss LED3REG,3 ;skip next if >= 8
      goto led3 ;jump
      clrf LED3REG ;clear led3reg
      incf LED3REG ;led3reg = 1
      movf LED3REG,w ;move led3reg t

      movwf PORTA ;output on porta

      goto loop ;do it all over again

      sleep

      END
```

the format of the hex file as a guide, this is quite simple. Each line from the hex file is taken in turn.

We parse the line by taking the starting address from the line and using it as the address of the first byte. In the case of the PIC 14 bit instruction set, we have to use two bytes to represent an opcode. The additional two bits of the high byte are ignored.

We then use the byte count from the line to determine how many additional bytes to work

through, incrementing the address count for each byte. Since we are disassembling PIC 14 bit instructions, we won't assign a new address to each byte, but for each word.

We now have a list of machine codes with addresses. Either as a second step, or concurrently with our first step, we can turn the machine code into recognizable opcode mnemonics. This process involves using a sieve to sort through the bits of the machine code to make a match with an

opcode. The opcodes are typically grouped into sets of opcodes that share bit patterns. This makes it easy to rapidly determine, by checking a couple of bits which group, then by checking additional bits to narrow further and so on. When we finally reach the target opcode, we can parse the arguments out of the bits, as well.

When this process is complete, we have an addressed list of recognizable opcode mnemonics with arguments. The simplest version of a first pass disassembly is

complete and the result is already useable!

At this point, we can begin to add value to the disassembly by adding some programmatic complexity. The code that we execute in our sieve can do many things. One of the easiest things to do is swap out hex values for registers wherever we can.

We know from our opcode structure that certain commands always expect registers as one of the arguments. We can construct a subroutine lookup table to determine which register is being targeted and swap a name for a number.

This is actually a tad more complicated with the PIC and many other microcontrollers. The problem is that the PIC has different banks of registers.

A flag in a register defines which bank is being addressed. The same register address argument could stand for a couple of different registers. Since the register bank flag could be set by an interrupt or some other hard-to-track code, knowing which bank is being addressed takes more of a microcontroller simulator than a disassembler.

This is easy to get around by replacing the hex value with the list of all possible (usually two) registers. This is a place where we strike a balance between human intelligence and program intelligence, rather than over-program a solution.

A second pass of disassembly allows even more interesting things to be done, the best of which is adding labels to our code and then replacing the hex values after jumps with the names of the labels we created. This makes the disassembled code much more readable.

We do this by running through the results of our first pass and collecting all the targets of jump commands. We then use this list to create unique labels at each of the addresses in our list of targets. We can then replace all of the jump targets with the unique label names we created.

We can also produce one of the other useful items that an assembler produces: a symbol table. This is a simple table of associations between names and numbers.

The names may be labels and the numbers addresses, or the names may be registers and the numbers the register number.

When writing assembly language, it's also possible to assign names to addresses or values for the sake of readability. Disassemblers can easily provide the label and register associations.

## World Passing You By?

Are you interested in Microprocessors & Embedded Control Systems? If not you should be! Look around, just about everything these days has an embedded microprocessor in it. TVs, cars, radios, traffic lights & even toys have embedded computers controlling their actions. The Primer Trainer is the tool that can not only teach you how these devices operate but give you the opportunity to program these types of systems yourself. Examples & exercises in the Self Instruction manual take you from writing simple programs to controlling motors. Start out in Machine language, then move on to Assembler, & then continue on with optional C, Basic, or Forth Compilers. So don't be left behind; this is information you need to know!

**Examples Include:**

- Measuring Temperature
- Using a Photocell to Detect Light Levels
- Making a Waveform Generator
- Constructing a Capacitance Meter
- Motor Speed Control Using Back EMF
- Interfacing and Controlling Stepper Motors
- Scanning Keypads and Writing to LCD/LED Displays
- Bus Interfacing an 8255 PPI
- Using the Primer as an EPROM Programmer
- DTMF Autodialer & Remote Controller (New!)





The PRIMER is only \$119.95 in kit form. The PRIMER Assembled & Tested is \$169.95. This trainer can be used stand alone via the keypad and display or connected to a PC with the optional upgrade (\$49.95). The Upgrade includes: an RS232 serial port & cable, 32K of battery backed RAM, & Assembler/Terminal software. Please add \$5.00 for shipping within the U.S. Picture shown with upgrade option and optional heavy-duty keypad (\$29.95) installed. Satisfaction guaranteed.

**EMAC, inc.**  
11 EMAC WAY, CARBONDALE, IL 62901  
618-529-4525 Fax 457-0110 BBS 529-5708  
World Wide Web: <http://www.emacinc.com>

1985 - 1998  
OVER  
12  
YEARS  
OF SERVICE

## PIC'n Books

### LEARN ABOUT PIC MICROCONTROLLERS

See Table Of Contents: <http://www.sq-1.com>  
Secure Online Ordering is Available

PIC is a trademark of Microchip Technology Inc.

**SQUARE 1 ELECTRONICS**

Voice (707) 279-8881 Fax (707) 279-8883

<http://www.sq-1.com>



The variable names are not provided since the computer has no way of knowing what arbitrary numbers a human might like to see as a name.

Many microcontrollers also have special registers that are set via the hex file. An example on the PIC 16C84 would be the register that defines — among other things, what kind of oscillator is being used — the config word (address 0x2007). This register is at a consistent location outside of the range of addresses defined as holding code, so we can spot it in the hex file and decode it into the flags that are set or cleared.

The disassembly listing can describe the status of these flags, or even reproduce the commands an assembler would want to see if you were trying to work with the register in code.

Now we have an assembly lan-

guage program (see Listing 4) that is quite readable. It has clearly labeled opcode mnemonics, registers, and jump labels. This code could be used by an In-Circuit Emulator (see the Jan. 99' *Nuts & Volts*, "Your Hottest Tool May be ICE!") to single step through code, understand how a complicated

interrupt scheme is set up, or any number of other educational purposes.

In the conclusion of this article next month, I'll show how a disassembler can be written. I'll use Python, the open-source language that is considerably easier to read than many other languages.

I'll describe the operations needed to do multipass disassembly and even demonstrate how to have the program create a symbol table and comment some lines. A working disassembler will be provided with source so that experimenters can adapt it to their own needs. **NV**

### Disassembly Resources

#### The Simtel.Net MS-DOS Collection Disassemblers

<http://www.eunet.bg/simtel.net/msdos/disasm-bydate.html>

#### XDASM - Universal Cross Disassembler

<http://www.datasynceng.com/xdasmdoc.htm>

#### Programmers Heaven Assembler Zone

Assemblers/Disassemblers Filelist

<http://www.programmersheaven.com/zone5/cat25/index.htm>

### Open Directory — Computers: Programming: Disassemblers

<http://dmoz.org/Computers/Programming/Disassemblers/>

### PIC Resources

#### Microchip

<http://www.microchip.com/>

#### the PIC archive

<http://come.to/thepicarchive>

#### Microchip Net resources

<http://www.geocities.com/SiliconValley/Way/5807/>

LOC OBJECT LINE SOURCE TEXT  
CODE  
VALUE

```
00000003 00001 STATUS equ 03
00000005 00002 PORTA equ 05
00000006 00003 PORTB equ 06
00000005 00004 TRISA equ 05
00000006 00005 TRISB equ 06
00000005 00006 RPO equ 05
00000007
0000002A 00008 LED1REG equ 02a
0000002B 00009 LED2REG equ 02b
0000002C 00010 LED3REG equ 02c
00011
00012
Warning[207]: Found label after column 1. (wdtoff)
0000 00013 wdtoff
00014
0000 1683 00015 BSF STATUS,RPO
0001 3000 00016 MOVLW 00
0002 0086 00017 MOVWF TRISB
0003 3000 00018 MOVLW 00
0004 0085 00019 MOVWF TRISA
0005 1283 00020 BCF STATUS,RPO
00021
00022
0006 3000 00023 movlw 00 ;init led*reg
0007 00AA 00024 movwf LED1REG
0008 3010 00025 movlw 010
0009 00AB 00026 movwf LED2REG
000A 3002 00027 movlw 002
000B 00AC 00028 movwf LED3REG
00029
Message[305]: Using default destination of 1 (file).
000C 0AAA 00030 loop incf LED1REG ;inc led1reg
000D 1DAA 00031 btss LED1REG,3 ;skip next if >= 8
000E 2811 00032 goto led1ok ;jump
000F 01AA 00033 clrf LED1REG ;clear led1reg
Message[305]: Using default destination of 1 (file).
0010 0AAA 00034 incf LED1REG ;ledreg1 = 1
0011 082A 00035 led1ok movf LED1REG,w ;move led1reg to w
0012 072B 00036 addwf LED2REG,w ;combine with
;led2reg in w
00037
0013 0086 00038 movwf PORTB ;output on portb
00039
0014 3010 00040 movlw 010 ;setup w with
;increment
0015 07AB 00041 addwf LED2REG,f ;inc led2reg (high
;nibble)
0016 1FAB 00042 btss LED2REG,7 ;skip next if >= 8
0017 281A 00043 goto led2ok ;jump
0018 01AB 00044 clrf LED2REG ;clear led2reg
0019 00AB 00045 movwf LED2REG ;ledreg1 = 0x10
001A 082B 00046 led2ok movf LED2REG,w ;move led2reg to w
001B 072A 00047 addwf LED1REG,w ;combine with
;led1reg in w
00048
001C 0086 00049 movwf PORTB ;output on portb
00050
```

### Listing 2 — The List file output from an assembler

```
Message[305]: Using default destination of 1 (file).
001D 0AAC 00051 incf LED3REG ;inc led3reg
001E 1DAC 00052 btss LED3REG,3 ;skip next if >= 8
001F 2822 00053 goto led3ok ;jump
0020 01AC 00054 clrf LED3REG ;clear led3reg
Message[305]: Using default destination of 1 (file).
0021 0AAC 00055 incf LED3REG ;led3reg = 1
0022 082C 00056 led3ok movf LED3REG,w ;moveled3reg t
00057
0023 0085 00058 movwf PORTA ;output on porta
00059
0024 280C 00060 goto loop ;do it all over again
00061
0025 0063 00062 sleep
00063
00064 END
```

### SYMBOL TABLE

LABEL	VALUE
LED1REG	0000002A
LED2REG	0000002B
LED3REG	0000002C
PORTA	00000005
PORTB	00000006
RPO	00000005
STATUS	00000003
TRISA	00000005
TRISB	00000006
_16C84	00000001
led1ok	00000011
led2ok	0000001A
led3ok	00000022
loop	0000000C
wdtoff	00000000

### MEMORY USAGE MAP ('X' = Used, ' ' = Unused)

0000 : XXXXXXXXXXXXXXXX XXXXXXXXXXXXXXXX XXXXXX

All other memory blocks unused.

Program Memory Words Used: 38  
Program Memory Words Free: 986

Errors : 0  
Warnings : 1 reported, 0 suppressed  
Messages : 4 reported, 0 suppressed



## MILITARY SURPLUS ELECTRONICS

**WANTED: MILITARY** capacitors, resistors, transistors, diodes, ICs, semi's, etc. Please fax/E-Mail excess lists & RFQs 818-769-1002 fax 818-769-1084. [electmatind@earthlink.net](mailto:electmatind@earthlink.net) & <http://www.militarycomponents.com>

**Sell Nuts & Volts**  
in your store and earn \$\$\$!  
E-Mail distributors@nutsvolts.com

## AUDIO — VIDEO — LASERS

**BROADCAST VIDEO** equipment wanted: all types, new or old. Please call, Jon with info. 1-800-539-2859.

**WANTED: PRO** video equipment, VCRs, switchers, cameras, etc. Advanced Media 702-874-1911.

**SYNC-A-LINK UNIVERSAL video sync generators.** For more details phone 918-479-6451, E-Mail: [rlc@sstelco.com](mailto:rlc@sstelco.com) or write to **Sync-A-Link**, PO Box 4, Locust Grove, OK 74352.

**QUAD VIDEO CABLE MODULATOR.** CVS-600 inserts 4 color or black & white composite video signals on unused cable channels, 81 thru 95. Watch 4 remote security cameras from any TV in your home! Built-in signal amplifier and comb filter eliminates any ghosting and actually **IMPROVES** existing video! Only one unit needed with existing cable system. \$199/each and **\$169/each** in qty. of 4. MATCO, Inc., 1-800-719-9605. E-Mail: [sales@mat-co.com](mailto:sales@mat-co.com) Website [www.mat-co.com](http://www.mat-co.com)


**FREE LASER CATALOG.** Helium-Neon, Argon, ruby, visible laser diode modules, lightshows, holography, laser pointers. Lowest prices. Midwest Laser Products, PO Box 262, Frankfort, IL 60423. 815-464-0085 [www.midwest-laser.com](http://www.midwest-laser.com)



**ANTIQUE VIDEO TRANSFER SERVICE:** transfer any 2" QUADRUPLUX tape. Affordable fast! Phone/fax 415-821-7500 or 415-821-3359. 5001 Diamond Heights Blvd., San Francisco, CA 94131-1621.



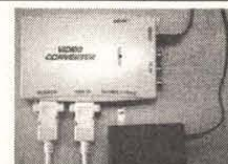**STEREOSCOPE VR** is a stereo multiplexer that creates 3D stereoscopic video from two genlock cameras. Stereoscope VR comes with LCS glasses and driver. 90 day warranty \$247 or write to **Sync-A-Link**, PO Box 4, Locust Grove, OK 74352. Phone 918-479-6451, E-Mail: [rlc@sstelco.com](mailto:rlc@sstelco.com)



**USE PC MONITOR AS SECURITY MONITOR.** The VGA-801 accepts standard NTSC or PAL inputs for display on any existing VGA/SVGA computer monitor. Small compact size. Over 600 lines of resolution, twice that of standard TV monitor! **\$69 each.** Dealers welcome. MATCO, Inc., 1-800-719-9605; Fax 847-619-0852; E-Mail: [sales@mat-co.com](mailto:sales@mat-co.com) Website: [www.mat-co.com](http://www.mat-co.com)

## CABLE TV

**BRAND NEW** basic converters, 550MHz w/remote, \$9.95 ea. 10 lot min. Call 706-657-4445.

**DISCOUNT CABLE converters, bullet snoopers, all makes and models: Genuine unmodified General Instrument, Jerrold, Tocom, Scientific Atlanta, Zenith, Pioneer, Panasonic and more. Best warranty. Free catalog 1-800-243-0962.**

**CABLE PARTS for all makes and models, raw boxes at low prices. Call 1-888-817-8100 [www.chip place.com](http://www.chip place.com)**

**NEW! CABLE converter electronic service equipment and supplies for most cable converter boxes. Highest service, lowest prices. Call Ken Erny Electronics. 24 hr. order and information hot line 516-389-3536.**



**NOTCH FILTERS** 110, 108.5, 106.5, 97.5 75dB deep notch. \$19.95 ea., 1-5 qty. \$15.95 ea., 6-10 qty. \$11.95 ea., 11-20 qty. \$9.95 ea., 21 or more qty. Call 24 hr. order and information hot line 516-389-3536.

**CABLE CONVERTERS.** Original equipment with remote. Like new. Lowest prices. Guaranteed, ready to go. Limited models. Call for flyer 412-833-0773.

# ALL ELECTRONICS

C O R P O R A T I O N

## 150 Watt Power Supply

Power Switch Corporation  
# PVI 150-39-PRV  
Input:  
100 - 240 Vac.  
Outputs:  
5 Volts @ 8 Amps  
12 Volts @ 8 Amps  
Maximum output achieved with 20 CFM forced air cooling. New, open-frame switching power supply. 7.13" x 4" x 1.9" high. UL, CSA. **CAT # PS-150 \$8.50 each**

## 40 RPM 115 Vac Motor

Cramer Co. # 105VA150-E  
40 RPM, 115 Vac gear motor.  
1.83" diameter x 1.18" body.  
Mounting ears on 2.1" centers.  
0.25" diameter x 1" long shaft.  
Prepped with a 1.25" long pin through the hole in the drive shaft. Pin is removable.  
4" long pigtail leads. UL, CSA. **CAT # ACM-108 \$2.50 each**

## MINIATURE S.P.D.T. LEVER SWITCH

(ON) OFF (ON) Alps # SSCF2136LX  
S.P.D.T., center-off miniature lever switch. Spring-action lever returns to center-off position. 0.49" x 0.43" plastic body. Lever extends 0.375" beyond body. Mounting flange extends 0.24". Solder-loop terminals. Large quantity available. **CAT # LSW-1 4 for \$1.00**  
100 for \$20.00  
1250 for \$150.00 (12¢ each)

## 16 Character X 2 Line LCD with Backlight

Daewoo # 16216L-5-VSO  
5 x 7 dot format.  
2.56" x 0.54" viewing area.  
3.15" x 1.41" module size.  
LED backlight. Includes hook-up/spec sheet. **CAT# LCD-53 \$7.50 each**

## 12 VDC 2.5 Amp Switching Adaptor

Plug-in-wall regulated switching power supply. Ideal for cameras, scanners, cell phones, computers or any devices sensitive to power fluctuations. Input: 100 - 240 Vac. 6 foot output cord has a coax DC power plug (2.1mm id, 5.5mm od). Tip positive. Ferrite snap-bead for EMI suppression. Compact, 3.23" x 2.23" x 1.38" UL, CSA, CE. **CAT # PS-1225 \$15.00 each**  
10 for \$12.50 each  
100 for \$10.00 each

## Modular CD Racks

Organize your CDs or CD ROMs with these high-impact, black plastic CD storage racks. Slots for 12 jewel cases. Each 12 CD module can interlock vertically and horizontally with other modules. Can be free-standing or wall mounted. **CAT# CDR-3 \$2.00 each**  
10 for \$17.50

## Laser Level

Accurate and easy to use for short and long distance leveling. Center the bubble, and anything that intersects the beam is at exactly the same height. Use it to match heights in large rooms or across buildings. Set and align electrical and plumbing fixtures, cabinets and shelves. Rugged, black anodized aluminum housing with pocket clip. Locking push button switch to prevent unintended actuation. Includes two AAA batteries. **CAT # LL-1 \$16.95 each**

QUALITY Parts  
FAST Shipping  
DISCOUNT  
Pricing

CALL, WRITE, FAX  
or E-MAIL For A  
Free 96 Page  
CATALOG.  
Outside the U.S.A.  
send \$3.00 postage.

## 3 Outlet Lighter Cord w/ Battery Monitor

Three foot cord with LED lighted, fused, 10 Amp plug at one end and three outlet jacks at other end. Jack assembly has red, yellow and green LEDs to indicate battery condition. Can be mounted via mounting ears (4.7" centers) or double-sided tape (included). Mounting ears fold out of way if not in use. **CAT # CLP-44 \$3.75 each**

## Ionizer

Seawise Industrial Ltd.  
Model # SW750. Input: 120 Vac  
Output: 7.5 KV 60 Hz. The main component in a household ionization unit. 2.2" x 1" x 0.86" thick with a mounting tab that extends 0.75" from the unit. UL recognized. **CAT # SW-750 \$4.50 each**

## Blue & White Ultrabrights

BLUE / water clear 1200 mcd  
45 degree viewing angle. **\$3.50 each CAT # LED-58**  
10 for \$27.50  
WHITE / water clear 1800 mcd  
**\$3.50 each CAT # LED-48**  
10 for \$27.50

## Motorized Potentiometer Dual 10K Linear Taper

Alps Electric # 726T-10KBX2  
Dual 10K linear pot powered by a small reversible 6 Vdc gearhead motor. Pot and motor assembly are 1" square x 1.7" long excluding shaft and bushing. 6 mm flattened shaft is 0.5" long. 9mm threaded bushing. PC pins and mounting tabs for pc board mounting. **\$4.00 each CAT # MPOT-10K**  
10 for \$35.00

ORDER TOLL FREE **1-800-826-5432**  
Shop ON-LINE [www.allelectronics.com](http://www.allelectronics.com)

MAIL ORDERS TO:  
**ALL ELECTRONICS CORP.**  
P.O. BOX 567 • VAN NUYS, CA 91408-0567

FAX (818) 781-2653 • INFO (818) 904-0524  
E-MAIL [allcorp@allcorp.com](mailto:allcorp@allcorp.com)

NO MINIMUM ORDER • All Orders Can Be Charged to Visa, Mastercard, American Express or Discover • Checks and Money Orders Accepted by Mail • Orders Delivered in the State of California must include California State Sales Tax • NO C.O.D. • Shipping and Handling \$5.00 for the 48 Continental United States • ALL OTHERS including Alaska, Hawaii, P.R. and Canada Must Pay Full Shipping • Quantities Limited • Prices Subject to change without notice.

**MANUFACTURERS - We Purchase EXCESS INVENTORIES... Call, Write, E-MAIL or Fax YOUR LIST.**



**UNMODIFIED CABLE CONVERTERS.** Zenith ST1600, ST1086, ST300, Panasonic 175, 145 vol. & non-vol. Regal RR-92 & RC 83, DP5, DP7, DRZ, 5503 VIP, SA 8580. Guaranteed low prices. Please call for more converters 405-631-1856.

**POSITIVE NOTCH FILTERS.** All channels available. Starting at \$16 each. Order by single channel #. Top quality non-tunable metal cylinder type. 75dB deep on the notch. Need to block the video on a cable channel? Order a negative notch filter. We carry a large stock on all channels for dealers and vendors. VISA, MASTERCARD, DISCOVER, and UPS COD for established customers. Quantity pricing on 5 or more. 100 pcs. \$7 each. Open 8am to 5pm CST, Monday-Friday. All sales must comply with FCC 1996 Cable Act. On the web go to **WWW.GOFILTERS.COM "THE FILTER COMPANY"**. Call for all orders **1-800-235-8080**.

**TOCOM UNMODIFIED** 5503 cable converters, untouched, \$6 ea. 10 lot min. Call 706-657-4445.

**UNMODIFIED CABLE** converters. SA 8590, \$24.95 ea. 10 lot min. Call 706-657-4445.

**ZENITH UNMODIFIED** converters. ST 1600, \$29.95 ea. 10 lot min. Call 706-657-4445.

**SA UNMODIFIED** cable converters. 8550 @ \$9.95 ea., 8570 @ \$19.95 ea. 10 lot min. Call 706-657-4445.

**NEW IN BOX 860MHz** analog converters. Enjoy the newest technology CATV equipment can offer along with superior quality all in one unit. Channel output 3 or 4. HRC, IRC, standard switchable. Includes 1 set of audio/video cables, 1 RF quick connect cable and remote control. Parental control, sleep timer, last channel recall, memory 1 thru 4, and volume control are all available on remote. Minimum order taken for 10 pcs. at \$59.95 each. \$49.95 for 50 pc. order. Significant savings on larger quantities. Call 706-657-4445.

**UNMODIFIED JERROLD DPV-5 CONVERTERS, \$25 ea. 10 lot min. Call 651-426-4435.**

**ONE STOP SHOP: FOR ALL YOUR CABLE NEEDS.** UNMODIFIED DPBB-7312, CFT 2014, CFT 2224; S/A 8550 TO 8600; ZENITH: ST 1601, PIO BA 6310. CALL FOR BEST PRICES. JERROLD 550 AND PANASONIC HAND REMOTES ONLY \$2.95 EACH. ALSO, UNIVERSAL 3-I REMOTE WORKS ON CFT UNITS \$3.95 EACH. CALL FOR FREE CATALOG. 405-631-5153.

**ATTN: CABLE BROKERS. THE FOLLOWING UNMODIFIED CONVERTERS FROM CB SYSTEMS FIELD-PULL AVAILABLE IN 100-LOT. ZENITH ST-1600 \$25 EA., JERROLD DPV-5 \$15, DPV-7 \$19, CFT 2014 \$45, S/A 8600 \$49, PIO-BA 9515 \$65. MANY OTHER RAW EQUIPMENT, WE CAN LOCATE FOR YOU. CALL 405-634-1535.**

**NEW 125 CHANNEL VOLUME CONVERTER \$59.** PANASONIC TZPC-175 \$39 (RAN). BUY FACTORY DIRECT & SAVE. DEALERS WELCOME. 405-616-0100.

**RAW CONVERTERS:** Pio 5135 \$45; Zenith ST 1600 (99 channel) \$65; S/A 8590 (10 button) \$65, 8590 (11 button) \$75; Tocom 5503 VIP (400MHz) \$35, Tocom 5507 \$45; CFT 2014 \$85, CFT 2224 \$115; DPBB-7 \$75; S/A 8600 \$95. Also, hand remotes as low as \$2.95. Call for items not listed. 405-634-1535.

**UNMODIFIED DPV-7 \$35, CFT 2014 \$65, S/A 8600 \$65. POWER-UP, 30-DAY WARRANTY. MINIMUM 10-LOT, CALL FOR OTHER ITEMS NOT LISTED. 405-692-4982.**

**RAW UNTOUCHED PIO-9515 SCREEN & CLEAN, \$89. MINIMUM 10-LOT. 1-800-354-7719.**



**QUAD VIDEO CABLE MODULATOR.** CVS-600 inserts 4 color or black & white composite video signals on unused cable channels, 81 thru 95. Watch 4 remote security cameras from any TV in your home! Built-in signal amplifier and comb filter eliminates any ghosting and actually **IMPROVES** existing video! Only one unit needed with existing cable system. \$199/each and **\$169/each** in qty. of 4. MATCO, Inc., 1-800-719-9605. E-Mail: sales@mat-co.com Website [www.mat-co.com](http://www.mat-co.com)

**CABLE PARTS!** Computer parts. Call for great prices or visit us on the Web: [HTTP://WWW.CB-Electronics.com](http://WWW.CB-Electronics.com) or call 1-800-436-8630.

**THE WIZARD SAYS** check out our prices. Cable parts and huge sale on raw boxes. 1-888-79-CHIPS. [www.chipwizards.com](http://www.chipwizards.com)


**UNMODIFIED ORIGINAL** equipment. Jerrold, SA, 125 channel converters. Lowest prices guaranteed. Dealers only. SA 8580 as low as \$35. Call now 214-476-7177.

## TELEPHONE/FAX

**PHONE SYSTEMS WANTED!!!** We buy AT&T MERLIN, SYSTEM 25/75/85 and other AT&T phone systems. Please call for a quote or fax us your equipment list. **KEYWAYS, INC.**, 937-847-2300 or FAX 937-847-2350.

**SOHO PHONE** systems and KSU-less phones. We carry Panasonic, BBS Telecom, Bizfon, and more. Tools, connectors, wire and so much more. Fax: 732-840-1390 or [alarmland.com](http://alarmland.com)

# Catch The Bus

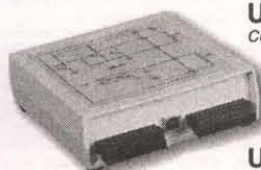

**USB Relay Module**  
Control 8 to 16 "form C", 1 Amp relays  
**USB Opto Module**  
8 to 32 opto-isolated Inputs and Outputs  
**USB Digital Module**  
Industry standard 50 pin interface  
**USB Temperature Module**  
Measures temperature over multiple remote sensors

## J-Works, Inc

12328 Gladstone St., Unit 4  
Sylmar, CA 91342  
(818) 361-0787 Voice  
(818) 270-2413 Fax


Visit our Web site for free information on all our products  
<http://www.j-works.com>  
E-mail [sales@j-works.com](mailto:sales@j-works.com)

Write in 48 on Reader Service Card.
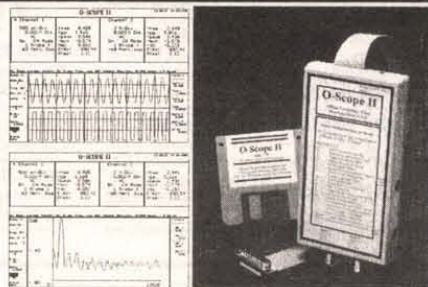
# Digital Storage Oscilloscopes

From \$99.00

**ATC modules** turn your PC into a full-function DSC, spectrum analyzer, logger, & DVM. Units DC to 50MHz. O-Scope II now in Windows 3.1, 95/98, NT and DOS.



O-Scope Ip \$189.  
O-Scope II \$349.  
Specialty probes call.

ATC is a stocking distributor for Pico Technology LTD which offers scope modules to 100MSPS, resolutions from 8 to 16 bit. Pico offers PC based data loggers from 1 to 22 channels, 8 to 16 bit and the Enviromon environmental monitoring system.

**Pico products - call**

The DFA-5, low cost differential amplifier, cuts through common mode noise problems to reveal low voltage signals. With gains from 1X to 1000X and band widths from 20KHz to 1.2MHz, DFA-5 is the test accessory to help you work with signals from 5 Volts to 5 microVolts. Only \$129.00.

**Serial Port Problems ???**  
Check out Serial !! Our lowcost serial channel analyzer only \$99.00.

**Allison Technology Corporation**

2006 Finney Vallet Rd., TX. 77471 U.S.A.  
800-980-9806 or 281-239-8500  
<http://www.atcweb.com> [atc@accesscomm.net](mailto:atc@accesscomm.net)



The RF Connection  
213 North Frederick Ave.  
Suite 11NV  
Gaithersburg, MD USA  
20877

<http://www.therfc.com/>

**Complete Selection of MIL-Spec Coax, RF Connectors and Relays**

UG-21B/U N Male for RG-213/214.....\$5.00  
UG-21D/U N Male for RG-213/214.....\$3.25

N Connectors for 9913/Flexi4XL/9096

UG-21B/9913.....\$6.00 Pins Only.....\$1.50  
UG-21D/9913.....\$4.00 Extra Gasket......75

Amphenol 83-1SP-1050 PL-259.....\$0.90  
UG-176/U Reducer RG-59/8X .25 or 5/1.00  
UG-175/U Reducer RG-58/58A .25 or 5/1.00  
Silver Teflon PL-259/Gold Pin.....\$1.00 or 10/\$9.00

MIL-Spec Coax Available (Teflon, PVC IIA)

New Product: Belden 9913F. 9913 with High Density PE Foam dielectric, stranded center cond. and Duobond III Jacket.....80/ft or \$76.00/100ft

Also New: 9092, RG8X with Type II Jacket Intro Price.....\$23.00/100ft

**Call for Specials of the Month**

Full Line of Audio Connectors for Icom, Kenwood, and Yaesu

8 Pin Mike Female.....\$2.50  
8 Pin Mike Male Panel.....\$2.50  
13 Pin DIN for Kenwood.....\$2.75  
8 Pin DIN for Icom.....\$1.00  
8 Pin DIN for Kenwood.....\$1.50

Prices Do Not Include Shipping

Orders 800/783-2666  
Info 301/840-5477  
FAX 301/869-3680

## Software for learning & designing

This new range of products, from Matrix Multimedia in the UK, includes resources and tools to help you learn about electronics and helping you to design electronic products and systems.



A complete course in electronics: Made up of 3 CD ROMs: Electronic Circuits & Components, Digital Electronics, and Analog Electronics.



A complete course in programming the PICmicro series of microcontrollers: the PICtutor CD ROM and development board. Comprehensive tutorials, assembler / send package, and flexible development board.



A course in Filter design: Filters CDROM.



A complete Electronics CAD suite: CADPACK includes software for schematic capture, circuit simulation, circuit animation and even PCB layout.



A scalable digital logic simulator: Digital Works allows complex digital logic circuits to be built and tested on-screen for learning logic design and



each program / CD ROM \$50 \$99 \$300  
PICtutor CD + development board \$149 \$300 -

CD ROMs now available from all Velleman distributors

Complete product descriptions available at: [www.matrixmultimedia.co.uk](http://www.matrixmultimedia.co.uk)

or order immediately at:  
Bright Future  
6540 Cedarview Court,  
Dayton Ohio 45459-1214  
Tel: (937) 438 5373 Fax: (937) 438 3229

Write in 49 on Reader Service Card.

Write in 50 on Reader Service Card. 59



## COMPONENTS

**WANTED: MILITARY** capacitors, resistors, transistors, diodes, ICs, semi's, etc. Please fax/E-Mail excess lists & RFQs 818-769-1002 fax 818-769-1084. [electmatind@earthlink.net](mailto:electmatind@earthlink.net) & <http://www.militarycomponents.com>

**MATCO WILL design, engineer, and** develop a 2.4GHz wireless 8 channel solution for your remote applications. FCC approved. Matco, Inc., Schaumburg, IL 1-800-719-9605. E-Mail: [nsales@matco.com](mailto:nsales@matco.com) Web site [www.matco.com](http://www.matco.com)



**AMAZING! 35c TOGGLE SWITCHES.** Brand new. Rated 6Amp/125V. Hardware included. 1/4" panel hole. SPDT or DPDT, on-on or on-off-on. Minimum 100pcs/package. Visa or MC, no COD. Gateway Products Corporation, 1-800-830-9195.

**SEE OUR** ad on 4-channel 2.4GHz wireless systems in the AdMart section on page 76. Matco, Inc.

**WANT TO Buy:** ICs, military & aircraft relays, diodes, transistors, Cannon, TRV, Amp, Burndy, Deutsch, Bendix connectors, electronic test equipment & most components. Hoffer Electronic Ent., 818-718-1165, FAX 818-341-5506. E-Mail: [Hoffel165@aol.com](mailto:Hoffel165@aol.com)

## MICROCONTROLLERS

**ATMEL 89CXXXX** programmer, IBM parallel port, C++ source code, schematics, \$250 + S/H. E-Mail: [cbanni3061@aol.com](mailto:cbanni3061@aol.com)

**WANTED: MILITARY** capacitors, resistors, transistors, diodes, ICs, semi's, etc. Please fax/E-Mail excess lists & RFQs 818-769-1002 fax 818-769-1084. [electmatind@earthlink.net](mailto:electmatind@earthlink.net) & <http://www.militarycomponents.com>



**PIC & ATMEL PROGRAMMERS** from \$17.95 and \$29.95! Visit [www.electronics123.com](http://www.electronics123.com) for complete details. Amazon Electronics, Inc. Toll free 1-888-549-3749.



**PROGRAM PICs in BASIC.** Complete package to get started includes: PicBasic compiler, EPIC programmer, cable, batteries, PIC16F84. \$159.95. [www.elproducts.com](http://www.elproducts.com)

**ATMEL AVR MICROCONTROLLER** board with integrated programmer. \$30 US. <http://www.avrboard.com> 1-877-62-MICRO.

## ANTIQUE ELECTRONICS


**WANTED: FOR** historical museum, pre-1980 microcomputers, magazines, and sales literature. Floyd, VA 24091-0341 (540-763-3311/540-382-2935).

**WANTED: MILITARY** capacitors, resistors, transistors, diodes, ICs, semi's, etc. Please fax/E-Mail excess lists & RFQs 818-769-1002 fax 818-769-1084. [electmatind@earthlink.net](mailto:electmatind@earthlink.net) & <http://www.militarycomponents.com>

**WANTED: EIAJ R/R 1/2"** color VTR. Excellent operating condition only, please. 415-821-3359, fax 415-821-7500.

**CRYSTAL SETS.** Parts, plans, books, kits. Largest source in the world. Catalog \$2. B. TURKE, PMB 270, 5030 Champion Blvd. G-6, Boca Raton, FL 33496.

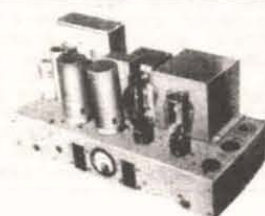**RADIO TUBES** and phono. needles. 870-347-2281.



**ALWAYS WANTED** Western Electric theatre amps, speakers, horns, drivers, and tubes. Also seeking vintage tube equip. by Marantz, McIntosh, and Tannoy. Chong Ong, 10223 Valentino Dr., #7304, Oakton, VA 22124. Tel: 703-255-3218, Fax: 703-255-3718. E-Mail: [ongkt88@erols.com](mailto:ongkt88@erols.com)

## AVIATION ELECTRONICS

**BUY, SELL, trade,** avionics equipment, Collins, King, Sperry: test equipment, IFR, Litton LTN series INUs. 941-625-3222 P. 941-625-0494 F. E-Mail: [avionics@afcon.net](mailto:avionics@afcon.net)

**WANTED: MILITARY** capacitors, resistors, transistors, diodes, ICs, semi's, etc. Please fax/E-Mail excess lists & RFQs 818-769-1002 fax 818-769-1084. [electmatind@earthlink.net](mailto:electmatind@earthlink.net) & <http://www.militarycomponents.com>



### STEEL ENCLOSURES

Features include ventilation holes, self-adhesive rubber feet. Front and rear panels are 0.05" aluminum alodine painted white. Top and bottom covers are 0.04" phosphated steel painted black.

- 2.5" x 6" x 7" GC3119A \$14.00
- 2.5" x 17" x 11" GC3119F 21.00
- 3.5" x 8" x 7" GC3119G 15.00
- 3.5" x 17" x 11" GC3119K 26.00



### RG-58 CABLE

25 feet long, with BNC connector on each end. 97W023 \$8.95 each

### 16-BIT MFM HARD DRIVE CONTROLLER

DTC P/N 5280. 97C045 \$4.95 each



### 20 OHM 50 WATT RESISTOR

97P007 \$3.25 each



### ANTI-STAT MAT

Approx. 21 1/2" x 11 1/4" (55cm x 30cm), with alligator clip. Handy size for many jobs. BM-204A \$19.95 each



### ATARI 1020 COLOR PRINTER

For all Atari 8-bit computers. (Not PC-compatible!) Package includes: printer, power supply, software, pens, paper and interface cable. These are new units in factory sealed boxes. 94C037 \$14.95 each



### RED PROJECTION LENS

Used in rear-screen projection TV sets. Also useful for photography and laser light shows. Focal length = 75mm; diameter = 75mm. 99L001 \$24.95 each



### COLMAN GEARMOTOR

25RPM @ 12VDC, 100mA. Measures 2.25"D x 1.25"L, with shaft 0.125"D x 0.75"L. Mfr. #FYQF-33700-40-5. 20M009 \$19.95 each


### GEAR REDUCTION DRIVE WITH 12VDC MOTOR

Output 8 RPM, max. torque 30 in. lb. shaft 5/16" dia. x 1-1/16" long. Dimensional diagram enclosed. Made by Multi Products. 20M011 \$14.95 each


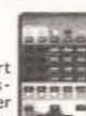
### SOLENOID VALVE

Teflon body for high purity and/or reactive chemicals - gas or fluid. 24VDC coil. 0.25" NPT ports, 30 psi working press. Two way (common to NO or NC). Dimensions: 1.625" diameter x 4" height. 99B001 \$34.95



### INFRARED KIT

Includes part #97V012 (assembled transmitter unit with forty-seven buttons) and receiver kit. Receiver kit includes PC board, IR detector, amplifier IC, and all components. Finished unit detects signal from transmitter and converts it to a serial TTL compatible signal. 93V010 \$19.95 each



### MAGNET DRIVE PUMP

1/25HP, 230 VAC, 50/60 Hz, 0.7A. March model MDXT-3. 99U003 \$49.95 each



### 24VDC MOTOR with STIRRER

Approx. 2400RPM and 250mA, no load. 1 1/2" dia x 3 1/4" long. Stirrer is 8 1/2" max. below top of neck, fits into bottle with 1-3/16" ID mouth. Merkle-Korff Ind. part 127E13010. 20M005 \$19.95 each



### STEPPER MOTOR DRIVER

Will drive two bipolar stepper motors up to 2A per phase. Board has the following ICs: 74HC00, 3702C, L298N, 74HC138, 74HC573WM, MS6264L-10FC, 74HC374, TL555C, PCA82C200T, HCTL-2000, 24LC16B, 9200ACA, 7705AC, AMD485, D78C10AGF. Approx. 1 1/2"W x 5"L board with DB-15M connector. Sorry, no docs. 99C001 \$14.95

### TVAUDIO DEMODULATOR

Originally used in cable TV application, this subassembly takes channel 3, 4 or 5 signal and demodulates the audio. Comes with documentation and schematics, plus additional schematics to build add-on video demodulator board. 92A028 \$9.95 each



### BAKER'S DOZEN LENSES

600 diopter meniscus lens, ~25mm (1"). Good optical quality - used in photo booths. 20L002 79¢ each 20L003 Tube (13) - \$7.95

### 500W VARIAC

Variable AC voltage power supply. Input 110 VAC @ 5A, 60Hz. Output 0-130 VAC voltmeter. 5A fuse and a 6' cable. P/N AECC-590VR. 99N006 \$59.95



### 2000W VARIAC

Input: 110VAC @ 20A, 60Hz. Output: 0-110VAC selectable. This unit has handles. P/N AECC-2090VR. 99N008 \$129.95



### G-I UNIVERSAL REMOTE CONTROL

General Instruments XRC110. 44-button transmitter controls up to four units, i.e., TV, VCR, Cable Box, Digital Audio Tuner. Easily programmed as your needs change. Indicator lights show which device is being controlled. Volume control may be programmed to work even though the rest of the transmitter is in a different mode. Works with equipment from many manufacturers. Will do a "code search" for the correct code. Batteries and detailed instructions. 98V011 \$9.95 each

### SPECIALTY COAX CABLE

Used for 16-Ohm impedance matching in transistor RF amplifiers. Stranded center cord, polyethylene insulation, tinned copper braid shell, black PVC insulation, 0.125" outside diameter. 20W006 60¢/ft.

### "SEXY FETS"

IRFM250 "N" channel hexfet, rated 200 Volts, 0.100 Ohm, 27.4 Amps. These are mil-spec parts in TO-254AA packages. Ref: MIL-S-19500/592. Full documentation included. 95I003 \$14.95 each



### RESISTOR RIOT

1/8, 1/4, 1/2 Watt, power, precision, fixed, adjustable, etc. Thousands of pieces. 20P003 5 Lbs. for \$9.95



# ALLTRONICS

2300-D Zanker Road - San Jose, CA 95131-1114

(408) 943-9773 - Fax (408) 943-9776

Download our New Catalog: <http://www.alltronics.com>

Store Hours: 9-6 M-F & 10-3 Sat. - Pacific Visa, MC, AmEx Accepted All Sales Final. California Residents Add Sales Tax. Shipping Additional on All Orders. Prices Subject to Change Without Notice. Prices Good 60 Days from Date of Publication





# Do You Repair Electronics?

For only \$7.95 a month, you'll receive a wealth of information:

Repair data for TV, VCR, monitor, audio, camcorder, & more.

Over 100,000 constantly updated problem/solutions plus...

- TechsChat live chat room.
- Private user discussion forums.
- Automated email list server.
- UL/FCC number lookup.
- Hot tips bulletin board.
- Manufacturer information.

To access RepairWorld, direct your internet browser to <http://www.repairworld.com>

## RepairWorld.com

Electronix Corp. 1 Herald Sq. Fairborn, OH 45324 (937) 878-9878

Write in 54 on Reader Service Card.

### PUBLICATIONS

**WANTED: MILITARY** capacitors, resistors, transistors, diodes, ICs, semi's, etc. Please fax/E-Mail excess lists & RFQs 818-769-1002 fax 818-769-1084. [electmatind@earthlink.net](mailto:electmatind@earthlink.net) & <http://www.militarycomponents.com>



**OUT-OF-PRINT TECHNICAL BOOKS.** [www.johnsontechbooks.com](http://www.johnsontechbooks.com) 805-525-8955. [sales@johnsontechbooks.com](mailto:sales@johnsontechbooks.com)

**BASIC STAMP 2** users: "Inside the BASIC Stamp II" tells how the PBASIC interpreter works, how code is stored in EEPROM, how to optimize code for space and speed. 160 pages, 50 illustrations, many examples. See <http://members.aol.com/stamp2book> Send \$29.95 check or money order (US funds) to Brian Forbes, PMB 326, 19672 Stevens Creek Boulevard, Cupertino, CA 95014-2465.


### ROBOTICS

**ROBOT BOOKS.COM** visit our web site for reviews of robotics books, plus robot kits, toys, movies, and magazines! [www.robotbooks.com](http://www.robotbooks.com)

**ARobot KIT** from Arrick Robotics uses the BASIC Stamp II. Quality metal construction. Easy to assemble and very expandable. \$235. <http://www.robotics.com/arobot>



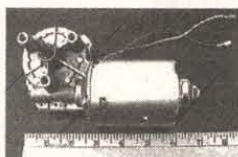**MOTOR CONTROLLERS**, PWM, 12V, 24V, 35A, many features from \$35 plus S&H. Info: 570-735-5053. Details: <http://divelec.tripod.com> Toll free orders (only) 1-877-679-1865.



**GEARHEAD MOTORS**, 24V, 35 RPM. Manufacturer rated 900 pounds. \$10 plus S&H. Info: 570-735-5053 Details: <http://divelec.tripod.com> Toll free orders (only) 1-877-679-1865.

**ROBOTS WANTED:** Dead or alive, whole or parts. Marvin (Iowa Precision), Gemini, RoPet, Hubot, RB5X, Newton SynPet, ComroTot, ELAMI, ITSABOX, HeathKit (HERO JR, I, 2000, or Arm Trainer), Androbots (TOPO, BOB, Fred, and Androman), Rhino, Maxx Steele, Omnibots, etc. Also looking for robot prototypes, options, and literature, will pay cash. Please E-Mail [rdoerr@bizserve.com](mailto:rdoerr@bizserve.com) Call 810-777-1313 or write to: Robert Doerr, 26308 Cubberness, St. Clair Shores, MI 48081.

### PLANS — KITS — SCHEMATICS

### Lowest Dealer Price Available

	5+	10+	20+
Refurb. Panasonic 145	\$45	\$40	\$35
Regal w/Remote	\$38	\$35	\$30
BC4535 86 Channel	\$30	\$28	\$25
Oak Sigma 99 Channel	\$45	\$40	\$35
75 Channel Converter	\$18	\$18	\$18
Zenith ST1600 w/Remote	\$75	\$70	\$65
Panasonic Converters Model-175 (550MHz)	\$65	\$55	\$45

Six month's warranty on this model only

Call us today to satisfy all your cable equipment needs!

**SAM'S ELECTRONICS**  
**1-405-631-1856**

All Cable Equipment is unmodified.

## DesignNotes.com

Your Design Resource on the Web

Improve Your Design Skills, Find Project Advice and More

### Enter Our Monthly Design Contest!

Win \$100 and become eligible for our \$1,200 Grand Prize

### Visit Our Online Forum

One of Our Most Popular Site Features  
Practical Solutions without all the Chit Chat

On-Line Tutorials  
Including Free Access to the *Electronics & Interface Companions On-Line*  
During June & July 2000

Internet Distributor for  
**Xeltek**  
Universal Device Programmers

Program EPROM's, Micro's, PLD's, PAL's, Flash.  
Over 5000 Vendor parts.  
Prices Starting at \$195

Share What You Know and Learn What You Don't

Visit Us at  
[www.designnotes.com](http://www.designnotes.com)

Write in 52 on Reader Service Card.

## SINGLE CHIP COMPUTER!

Zero External Components  
Built-in BASIC / Assembly  
RS232 Program Download  
1K flash, 64ee, 3irq, 2timers  
15 I/O bits, A/D comparator  
20mips, faster than pic8051  
20 pin DIP part #MV1200

**\$1.99** OEM (1K) EVAL KIT (\$1) \$7.00



### NEW! 8K SUPER CHIP

Improved BTERP with 40 times the BASIC program capacity  
40 pin DIP part #MV8515 - 32 I/O, 12 irq, 3 timers, bus  
8K flash, 512 ee, 512 sram - Watchdog with internal osc.  
**\$5.40 OEM (1k), Eval Kit \$19.00**

## PC SOLID STATE DISK

**\$21 OEM (1k), EVAL \$75**  
FLASH, NVRAM, ROM  
256K-16M DIP/PCMCIA

## \$95 UNIVERSAL PROGRAMMER

FLASH, EPROM, NVRAM, EEPROM  
to 8meg (27080). Adapters for micros, PLCC, etc. Parallel port version for notebooks. FAST and EASY TO USE.

## PC WATCHDOG!

NO MORE HANGUPS..  
Reboots PC on hardware or software hangup..  
oem \$21, eval \$75



## LCD VGA \$27

OEM (1k), eval \$95  
640x480 controller  
use with PC or SBC

## \$27 MINI PC

\$27 OEM, Eval \$95, includes:  
DOS, 3 ser, 2 par, rtc, NVram,  
Built-in LED display, ISA bus,  
Keyboard and LCD interfaces.  
COMPLETE !!!  
Not a "core" or "engine". All  
utilities and tutorial included.  
Use Turbo C, BASIC, MASM.  
386 version: \$42 oem, \$195 eval



**WWW.STAR.NET/PEOPLE/-MVS**  
MVS Box 850  
Merr., NH 03054  
(508) 792 9507

5yr Limited Warranty  
Free Shipping  
Mon-Fri 10-6 EST

Write in 53 on Reader Service Card.

## Electro Mavin

Great Buys - Great Products - Great Gadgets  
Check Out Our Great WebSite at

**<http://mavin.com>**

For Computer Items, Hobbies Projects,  
Microwave Goodies and Some of the  
Greatest Prices on the Web....

800-421-2442 or FAX 310-632-3557

E-Mail

[john@mavin.com](mailto:john@mavin.com) or [sean@mavin.com](mailto:sean@mavin.com)





**CIRCUIT BOARDS.** Low-cost, precision-made PC boards from your CAD program files (no photoplots required). Single and double-sided with contour routing. Ideal for RF/analog/digital prototypes. Full details at <http://www.pcbmilling.com> E-Mail: [feedback@pcbmill.com](mailto:feedback@pcbmill.com) FAX: 703-818-0071.

**TEST EQUIPMENT** kits. If you liked Heathkit, you will love Technology Systems, 4 Prospect Pl., Torrington, CT 06790.

**CONSUMERTRONICS 120+** exciting manuals: Electronics, computers, Internet, phones, energy, radionics, financial (including stocks), crime-fighting, security, survival, phenomena, **SPECIAL PROJECTS.** Catalog \$3. PO Box 23097, Albuquerque, NM 87192. [www.tsc-global.com](http://www.tsc-global.com)

**200+ ELECTRONIC PROJECTS.** Secure WEB ordering @ [www.matcopublishing.com/plans1.htm](http://www.matcopublishing.com/plans1.htm) or send \$1 (refundable) for catalog. MATCO-5A, POB 509, Roseville, MI 48066-0509.

**SMART CARD** applications CD-ROM \$50. Blank smart cards \$20 or 8/\$100. Tony 419-385-3100.

## MANUALS — SCHEMATICS WANTED

**DISK AND/or** service manual to install Creative CR-563-R, CD-ROMA, sound card #2210. Alex Siegel, 51 Tracy Ave., Totowa, NJ 07512.

## MISCELLANEOUS ELECTRONICS FOR SALE

**FREE FLYER** on DBS, cable TV, phones, credit cards, schematics, health items. Bill 1-800-879-9657.



**SOLAR-POWERED FAN HAT.** Baseball type hat with solar powered fan. Great for sports fans, golfers, etc. Available in red or blue. \$19 plus \$2.00 shipping. CA residents add 7.75% sales tax. Visa/MC/Disc/Amex OK. H.T. Orr Computer Supplies, 249 Juanita Way, Placentia, CA 92670. 714-528-9822, 1-800-377-2023, FAX 714-993-6216.

**HIGH QUALITY TOOLS AND STAINLESS STEEL HARDWARE.** European and American screwdrivers, nutdrivers, pliers, hex-keys, balldrivers, and more! Wiha, Bondhus, and Knipex. Stainless cap screws, machine screws, nuts, washers, U-bolts, and eyes. Free catalog. Robert Mink Import-Export, Box 6437V, Fair Haven, NJ 07704. Telephone or fax 732-758-8388. E-Mail: [w2tv@compuserve.com](mailto:w2tv@compuserve.com)

**HARD-TO-find parts:** big screen screens, keypads, picture tubes, flybacks, tuners, CRT sockets, & modules for all TVs. 912-272-6561. Scarborough TV, 1422 Old River Road, East Dublin, GA 31027.



**ANAHEIM WIRE PRODUCTS. DISTRIBUTOR OF ELECTRICAL WIRE AND CABLE** since 1973. Items available from our stock: Hook up wire, Automotive primary wire, GXL, SXL, Plenum cable, Teflon wire, Multi-conductor cable, Irradiated PVC, SO-CORD, Mil-Spec wire, Building wire, Welding cable, Battery cable, Telephone wire, Shrink tubing, Cable ties, Connectors. Wire cut & strip to specs. If interested, please call 1-800-626-7540. FAX: 714-563-8309. Visa/MC/Amex. SEE US ON THE INTERNET: <http://www.anaheimwire.com> OR E-Mail: [info@anaheimwire.com](mailto:info@anaheimwire.com)

**NUCLEAR ELECTRONICS (NIM, CAMAC),** PMTs, optics, high vacuum, and high voltage components and equipment. Guaranteed quality at reasonable cost. OE Technologies, Box 703, La Madera, NM 87539. Ph: 505-583-2482, Fax: 505-583-9190, E-Mail: [oetech@newmexico.com](mailto:oetech@newmexico.com) <http://www.oetech.com>

**TV/PC-Pedaler™** Now you can burn some calories while watching TV, playing a video game, or using your computer. Patent pending exerciser easily connects to your TV or computer, you must pedal to view the screen. For info go to [www.tvpedaler.com](http://www.tvpedaler.com)

## MISCELLANEOUS ELECTRONICS WANTED


**DEC EQUIPMENT WANTED!!!** We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dialog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.,** 937-847-2300 OR fax 937-847-2350.

**WANTED: AVIONICS** test equipment, IFR, 600A, 401L, others, Collins, King, Sperry, North Atlantic, Litton INUs LTN series, rate and tilt tables, air data test sets, 941-625-3222 P. 941-625-0494 F. E-Mail: [avionics@afcon.net](mailto:avionics@afcon.net)

## PIC Real-time 'Emulator' and Programmer for
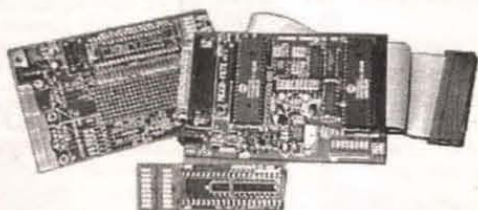
# \$159

Introducing **PIC-ICD** = Debugger + Programmer + Demo Board = \$159



**PB-87X probe for RICE17A now shipping**  
supports 16F87x, 16C66/67/76/77

Featuring on-the fly data capture break with 2-level trigger and pass count support, stop watch function and real-time data bus capture - complete system for \$775

- For PIC16F87X and emulates most PIC16C6X/7X
- In-circuit run-time debugging
- Real-time code execution
- High speed parallel port interface
- Built-in device programmer
- 2.5V to 6.0V operating range
- One level real-time breakpoint
- Two external break inputs
- Conditional animation break
- Run, step, run to Cursor, etc.
- Operating frequencies from 32khz to 20mhz
- Runs under PICICD IDE (Win 95/98/2000NT) or MPLAB™ (Win 95/98)
- Source level and symbolic debugging
- Software animation trace captures 3 user-defined variables in addition to opcode, W, STATUS, FSR registers and corresponding instructions
- Comes with ICD Debug module, demo board, 40-pin and 28-pin emulator headers, cable, power adapter, IDE software and printed user's guide



**Full-feature, real-time RICE17A Emulator System, from \$595**

- 64K program memory, 32K trace
- 12-clip external probe - break input, break output, trigger output, 8 logic traces and ground
- Source level debugging
- Unlimited software breakpoints and trigger points
- New PB-87x probe provides on-the-fly data break with 2-level trigger and pass count, stopwatch and databus capture
- Supports PIC12/16/17
- Low voltage emulation
- Self-diagnostic test board
- Optional PIC Time Stamp for \$59



**Single Socket PIC Programmers and Adapters**

- PGM16N supports all PIC12/14/16
- PGM17 supports all PIC17
- One 40-pin ZIF socket for all DIP parts
- Optional surface mount sockets for all package types which are compatible with all PIC programmers
- Emulation headers in SOIC, PLCC and QFP packages
- Win 95/98/NT hosting software
- DOS software for PGM17

**Advanced TransData**  
14330 Midway, #128, Dallas, Texas  
Tel 972-980-2667 Fax 972-980-2937  
Email: [atc1@ix.netcom.com](mailto:atc1@ix.netcom.com)




**Stand Alone Gang Programmer from \$900**

- New flash based firmware makes new device support a snap
- Production quality 8-gang programmer for PIC, SX, ST6 and more
- Approved by IC manufacturers
- Stand-alone chip duplication
- LCD and LEDs display program functions and results
- Codes reside securely in EEPROM of control module
- Custom all programming voltages in 0.1v increments

Visit the Ultimate Source for PIC Tools at  
[www.adv-transdata.com](http://www.adv-transdata.com)



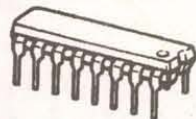**WANTED: TUBES**, radios, transmitters, receivers, gyros, bearings, connectors, relays, lamps, synchros. Hyness Company, 709B Delair Road, Monroe Twp., NJ 08831. Phone: 609-395-1116, FAX 609-395-1117.



**WANTED: EXCESS ELECTRONIC COMPONENTS, BOARD-LEVEL COMPONENTS; MILITARY COMPONENTS; ICs, MEMORY, TRANSISTORS, DIODES, CAPS, RELAYS, ETC. CALL LPS 562-439-2453 FAX 562-439-0453.**

**WANTED: MILITARY** capacitors, resistors, transistors, diodes, ICs, semi's, etc. Please fax/E-Mail excess lists & RFQs 818-769-1002 fax 818-769-1084. electmatind@earthlink.net & http://www.militarycomponents.com

**WANTED: BALANCING** machines & vibration analyzing equipment manufactured by the following: Spectral Dynamics, Hofmann, Bentley Nevada, Schenck, IRD Mechanical, Gishott. Contact Mike Park at E.T. Balancing, 12823 Athens Way, Los Angeles, CA 90061. 310-538-9738, FAX: 310-538-8273.

**WANTED: X-BAND** radar equipment. Military, civilian, working or not, parts, TMs, etc. Box 10215, Pittsburgh, PA 15232.

**WANTED: TISSA** Sci. calculator in good working order, will pay. Hugh M. Adams, hugh@emcst.com 1011 Hondo Ave., Apt. D, Fort Walton Beach, FL 32547-3823, 850-864-2414.

## BBS & ONLINE SERVICES


**WANTED: MILITARY** capacitors, resistors, transistors, diodes, ICs, semi's, etc. Please fax/E-Mail excess lists & RFQs 818-769-1002 fax 818-769-1084. electmatind@earthlink.net & http://www.militarycomponents.com

## EDUCATION

**MAGICIAN IS** available to solve your RF problem. I will teach you in my laboratory how to do it. Young engineers and technicians are welcome. SMT prototyping up to 3GHz for customers. Minaret Radio, John Horvath ph: 909-943-3676.
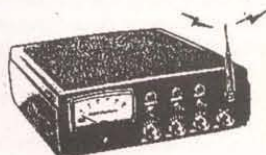
## BUSINESS OPPORTUNITIES

**WANTED: MILITARY** capacitors, resistors, transistors, diodes, ICs, semi's, etc. Please fax/E-Mail excess lists & RFQs 818-769-1002 fax 818-769-1084. electmatind@earthlink.net & http://www.militarycomponents.com



**COUNTER-SURVEILLANCE=\$250 HR!** Electronic eavesdropping is unbelievably widespread! Are you sure you're safe? Learn how others (without prior experience) earn **\$250 HR** in the fascinating field of COUNTER-SURVEILLANCE! For FREE catalog call: **1-800-732-5000**. HTTP://WWW.SPY-CITY.COM

**WANTED: SERVICE** technician, process engineer, or electronics engineer to evaluate products for cleaning electronic components and equipment. Good part-time income opportunity. 714-972-9200; E-Mail: taemerald@aol.com

## REPAIRS — SERVICES

**PRINTED CIRCUIT** design by professional with 30+ years: conventional, multilayer, downhole, fine line. Prototype and production fabrication. Reverse engineer existing 2-layer board. Toll free 877-236-3223. www.circuit-applied-tech.com

**WANTED: MILITARY** capacitors, resistors, transistors, diodes, ICs, semi's, etc. Please fax/E-Mail excess lists & RFQs 818-769-1002 fax 818-769-1084. electmatind@earthlink.net & http://www.militarycomponents.com

**CABLE CONVERTER REPAIR:** Quality repair service for all name brands. If you're tired of the runaround you're getting from the company you purchased it from, or they're out of business. Give us a call for fast and courteous service. Have model and problem ready. Sorry no box, chip, or IL repairs. **Highview Engineering 815-245-3735** or E-Mail: HIGHENG1@AOL.COM ask for George.

**PATENT YOUR HARDWARE/SOFTWARE INVENTIONS.** Experienced registered patent agent can help you. Quick, efficient, economical, confidential service. Call 909-599-0801.

**(E)EPROM PROGRAMMING** done quickly and economically. One day turn around typical. Simple copy \$3 per device. Also prototyping, design, and consulting services available. Call or send SASE to: **Luzer Electronics, 4023 North Bayberry, Wichita, KS 67226. 316-687-2127, FAX 316-687-3103.**

**CIRCUIT BOARDS** for projects, prototypes, short runs. From your artwork. Low rates. Atlas Circuits 704-735-3943. www.pcbatlas.com

# Roger's Systems Specialist

24895 Avenue Rockefeller  
Valencia California 91355

Place an **Order** on our Newly Updated **WebSite** and receive a **FREE** mouse!

(800)366-0579  
(661)295-5577  
fax(661)295-8777



Computer • Telecommunications  
Network • Audio • Video

www.rogerssystems.com

## CAT. 5 CABLE



Also available  
in many  
colors!!

Grey

TE-038-L5	3ft. Straight Patch	\$1.75
TE-068-L5	7 ft. Straight Patch	\$2.00
TE-128-L5	14ft. Straight Patch	\$3.00
TE-258-L5	25ft. Straight Patch	\$5.00
TE-508-L5	50 ft. Straight Patch	\$8.00
TE-758-L5	75ft. Straight Patch	\$14.00
TE-108-L5	100 ft. Straight Patch	\$16.00

## USB CABLES

CC-USB-6	6ft. USB "A"-A" M/M	\$5.00
CC-USB-AB6	6ft. USB "A"-B" M/M	\$5.00
CC-USB-AB10	10ft. USB "A"-B" M/M	\$6.00
CC-USB-AB15	15ft. USB "A"-B" M/M	\$8.00
CC-USB-X6	6ft. USB "A"-A" M/F	\$6.00
CC-USB-X10	10ft. USB "A"-A" M/F	\$6.00



CC-USB-PP \$25.00

USB to Parallel Printer

## IEEE-1394 FIREWIRE



\$5.00

FW-6X4-6  
FW-4X4-10

6ft 6pin x 4pin.....\$5.00  
10ft 4pin x 4pin.....\$12.00

\$20.00 min. Order required  
Add \$4.50 shipping for prepaid orders  
Prices subject to change without notice  
All major credit cards accepted  
Special offers only valid on items in stock  
Call for quantity discount  
No out of state checks accepted

## S-VGA Extensions

male/female  
black

CC-VGA-4C	6FT.....	\$6.00
CC-VGA-5C	10FT.....	\$8.00
CC-VGA-25CX	25FT.....	\$16.00
CC-VGA-50CX	50FT.....	\$25.00
CC-VGA-100CX	100FT.....	\$44.00

## S-VGA Switch Box Cable

male/male  
black

CC-VGA-3C	6FT.....	\$6.00
CC-VGA-9C	10FT.....	\$8.00
CC-VGA-11C	25FT.....	\$16.00
CC-VGA50MM	50FT.....	\$25.00
CC-VGA100MM	100FT.....	\$44.00

These premium VGA cables are made with 75 ohm coaxial cables. They are triple shielded to support extremely high bandwidth and unsurpassed protection against interference. Furthermore, our premium cables are Plug-N-Play ready and are compatible with the latest technology.

## ADD ON CARDS



Call for more information  
on any of these cards!!

CA-PPGA-S1  
IO-398  
IO-400  
SD-884  
USB-PCI  
VD-466  
VD-488

PPGA Celeron CPU Slot 1 adaptor...\$10.00  
ISA 8bit Single Parallel IEEE Card...\$12.00  
PCI 32bit Single Parallel IEEE Card...\$33.00  
16bit ISA Sound Card ESS Chip...\$14.00  
USB x PCI Add on Card...\$27.00  
S-VGA SIS 4MB PCI Video Card...\$31.00  
Savage4 32MB AGP 12bit 3D Video Card...\$99.00

## Multi-PC Controller

w/keyboard & mouse emulation  
Easy to select by push button

HD15-S-VGA  
PS/2 KEYBOARD  
PS/2 MOUSE

CC-PS2-VGA6 Cable Kit  
with this Item \$12.00

DS-HD2-66EM 2-WAY \$49.00  
DS-HD4-66EM 4-WAY \$69.00

## USB HUB

4-port USB hub with power & cable  
Full compliance w/USB spec. Rev 1.0.  
LED indicator for fault or dummy USB port.  
Transmission for 5 meter cable segment.  
Plug & Play capability for outside peripherals.  
Support UHCI and OHCI spec.  
One year factory warranty!



TM-USB-4HUB

\$39.00

## Electronic CPU Switch

DS-102-KMMPS

\$99.00 kit

Includes:  
One MiniView KVM switch  
2 Sets of Premium Grade KVM Cables  
One PS/2 to AT keyboard adapter  
One PS/2 to Serial mouse adapter  
One User Guide  
Features:  
Keyboard & mouse emulation for error  
Free PC booting  
No external power required  
Works virtually with any operating system  
Fully hot pluggable



## SLOT FAN

Extends your computer life.  
Ball Bearing

Takes up only one of the PCI/ISA slots.  
Special designed turbine fan gives you great performance and quietness.




\$12.00

TM-FAN-SLOT

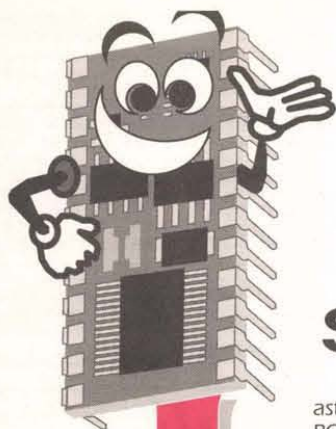CPU's-Motherboards-HardDrives  
Memory-SCSI Adaptors-SCSI Cables  
CD burners-CD's & Rewritable CD's  
And Much Much More!!!!





by Jon Williams

# Stamp Applications

## STAMPS IN THE LAB — PART 2

Putting the Spotlight on BASIC Stamp Projects, Hints, and Tips

Last month, our Stamp program did its processing and served up information without asking. This month, we've gone to the other extreme: the Stamp sits and waits for a command before doing anything. Can we find a happy middle ground?

Last month, we had some fun by keeping our PC connected to the Stamp and displaying information with a neat little program from SelmaWare called Stamp Plot Lite. Later, we went on to create a Visual Basic program that was compatible with Stamp Plot Lite output statements.

In both cases, the Stamp acted as an "information provider" and just pumped out data. There will be times though, when we want to ask the Stamp for a specific piece of information. We may also want to set some information in the Stamp that affects its behavior. That's what we're going to do this month.

### Building a Two-Way Street

Since we can't learn to swim without getting wet, let's jump right in. Take a look at the Stamp program in Listing 1 (if you don't have a Parallax BASIC Stamp Activity Board, you can build an equivalent circuit using the schematics provided last month).

After the obligatory setup and initialization, the program waits on some serial input from the PC — in this case, coming in on the programming port (defined as Pin 16). The input, specifically, is going to start with a question mark and be followed by a hexadecimal number. This (hex) number is our query; it tells the Stamp what we want.

Why do it this way? Well, there are a couple of reasons. By using the HEX modifier in the SERIN function, we're able to receive data in the form of ASCII text. This data could come from a Visual Basic program, but we haven't written that yet. Since we want to be sure the Stamp code is

working as expected before we tackle the PC side of things, it would be nice if we could use some other tool to do our testing. With this technique, we can. Since the Stamp is expecting a string input, we can use a general-purpose terminal program to see if things are working. We can even use a

DEBUG terminal in the Windows version of the Stamp editor.

Let's go back to our SERIN function and discuss the details. First, SERIN waits for the "?" character to arrive, ignoring everything else until that happens. The question mark, then, is what signifies the start of a query. Once a question mark arrives, the HEX modifier causes the Stamp to look for valid hex characters (0-9, A-F). The arrival of any non-hex character (usually a carriage return [Enter] when using a terminal) tells the Stamp to stop accepting input (to the variable called param in our case) and continue on.

What has actually happened is that the Stamp has used the SERIN function to do a text-to-numeric conversion. Pretty cool, huh? Now that we have a command, we can use standard IF-THEN logic statements to see if it is valid for our particular program. (Since there are so many possible commands and they are not numerically contiguous, using BRANCH to jump to the requested routine becomes a bit awkward.) If the command isn't valid, a message and the offending input is displayed.

Could we have used "?ID" instead of "?F0" to get the Stamp's identification string? Yes, technically we could have, but it becomes very tedious in PBASIC programming. The reason is that the Stamp can't do direct string comparisons. What we would have to do is compare the input, character-by-character, to see if it's valid. And to be user-friendly, we'd have to allow uppercase and lowercase entries — doubling the number of comparisons. Since the HEX modifier of SERIN is not case-sensitive, our program will work if we enter "?F0" or "?f0" or any upper/lower combination.

For an example of character-by-character string comparisons in the Stamp, take a look at Jon Richards' networking demo at [www.jdrichards.com](http://www.jdrichards.com).

The Stamp responds to a request by sending a text string by using DEBUG. Remember that DEBUG in the BS2 is the same as SEROUT on pin 16 at 9600 baud. Each of the response strings consists of a label, the equal sign, the value of that particular parameter, and finally, a carriage return. When using a terminal program, the output is easily readable. Something like this:

```
ID=Parallax BS2
```

The carriage return at the end of the output gives us a new line when using a terminal program and serves as an "end of input" when we process the input with our own program (like Stamp Plot Lite does). The equal sign will be used as a delimiter when we do our own processing. We'll use it to distinguish the label from its value.

Most of our queries are requests for information. Two of them, however, can modify information that is stored in the Stamp. Let's look at those.

The first one is "?F1" which will allow us to write a string value to the Stamp's EEPROM (in a location called ID). When F1 is received as a command value, the program jumps to the subroutine called SetID. On entry to SetID, the EE pointer called addr is initialized, then the Stamp waits for a character to arrive. Notice that no modifier is used here. Since terminal programs and the Stamp represent characters using ASCII codes, we don't have to do anything special. When a character does arrive, it is written to the EE and the address pointer is incremented. If the last character was a carriage return (13), the program outputs the new string (using the code at ShowID), otherwise it loops back and waits for another character.

The second modifying query is "?B1" which allows us to set the status of four LEDs. Take a look at the subroutine called SetLEDs. This time, we're going to use the BIN modifier of SERIN. What this means is that our valid inputs are going to be "1" (LED is on) and "0" (LED is off). Since the hardware uses active low outputs, we're forced to invert the data. That's easily handled with the complement operator (~).

Figure 1 shows an actual online session with this Stamp program using the DEBUG terminal. If you're not using the Windows Stamp



Figure 1



# STAMP APPLICATIONS

## STAMPS IN THE LAB — PART 2

' Nuts & Volts - Stamp Applications  
' August 2000 (Listing 1)

```
' =====
' Program... POLLSTMP.BS2
' Author.... Jon Williams
' Started... 25 MAY 2000
' Updated... 29 JUN 2000
' =====
```

```
' -----[ Program Description ]-----
' This program waits for a text command from the PC and responds with a
' string that contains the name of the data and its current value.
'
' If the ATN line is opened, this program will work with any general-
' purpose terminal program (i.e., HyperTerm). To read the temperature you
' would type the characters '?', 'A', '1', followed by a carriage return.
```

```
' -----[ Revision History ]-----
'
```

```
' -----[ I/O Definitions ]-----
```

```
SIOPin CON 16 ' serial I/O on programming port
Rst CON 13 ' DS1620.3
Clk CON 14 ' DS1620.2
DQ CON 15 ' DS1620.1
```

```
' -----[ Constants ]-----
```

```
Baud96 CON 84 ' 9600-8-N-1 (matches DEBUG)
CmdID CON $F0 ' get string ID
CmdSet CON $F1 ' set string ID
CmdTmp CON $A0 ' get DS1620 - display raw count
CmdTmpC CON $A1 ' get DS1620 - display in C
CmdTmpF CON $A2 ' get DS1620 - display in F
CmdStat CON $B0 ' get digital output status
CmdLEDS CON $B1 ' set LED outputs
```

```
' DS1620 commands
RTmp CON $AA ' read temperature
WTHi CON $01 ' write TH (high temp register)
WTLi CON $02 ' write TL (low temp register)
RTHi CON $A1 ' read TH
RTLi CON $A2 ' read TL
StartC CON $EE ' start conversion
StopC CON $22 ' stop conversion
WCfg CON $0C ' write configuration register
RCfg CON $AC ' read configuration register
```

```
' -----[ Variables ]-----
```

```
cmd VAR Byte ' command from PC/terminal
addr VAR Byte ' EE address pointer
eeDat VAR Byte ' EE data
param VAR Word ' parameter from PC
char VAR param.LOWBYTE
tmpIn VAR Word ' raw data from DS1620
halfBit VAR tmpIn.Bit0 ' 0.5 degree C indicator
sign VAR tmpIn.Bit8 ' 1 = negative temperature
tempC VAR Word ' degrees C in tenths
tempF VAR Word ' degrees F in tenths
potVal VAR Word ' reading from BSAC pot
buttons VAR Nib ' BSAC input buttons
```

```
' -----[ EEPROM Data ]-----
```

```
ID DATA "Parallax BS2", CR ' CR-terminated string
```

```
' -----[ Initialization ]-----
```

```
OUTC = %1111 ' turn off LEDs (active low)
DIRC = %1111 ' make port C all outputs

HIGH Rst ' alert the DS1620
' use with CPU; free run mode
SHIFTOUT DQ,Clk,LSBFIRST,[WCfg,$10]
LOW Rst
PAUSE 10 ' pause for DS1620 EE write cycle
HIGH Rst
' start temp conversion
SHIFTOUT DQ,Clk,LSBFIRST,[StartC]
```

LOW Rst

```
' -----[ Main ]-----
Main: ' wait for a command
cmd = 0
SERIN SIOPin,Baud96,[WAIT ("?"),HEX cmd]
```

' check for valid command

```
IF cmd = CmdID THEN ShowID
IF cmd = CmdSet THEN SetID
IF cmd = CmdTmp THEN ShowTemp
IF cmd = CmdTmpC THEN ShowTempC
IF cmd = CmdTmpF THEN ShowTempF
IF cmd = CmdStat THEN ShowStat
IF cmd = CmdLEDS THEN SetLEDS
```

```
BadCommand:
DEBUG "Invalid Command: ",HEX2 cmd,CR
GOTO Main
```

```
' -----[ Subroutines ]-----
```

```
ShowID: DEBUG "ID=" ' label output
addr = ID ' point to first character of ID
GetEE: READ addr, eeDat ' read a character from EEPROM
DEBUG eeDat ' print the character
addr = addr + 1 ' point to next character
IF eeDat <> CR THEN GetEE ' if not CR, read another
GOTO Main
```

```
SetID: addr = ID ' point to ID location
GetC: SERIN SIOPin,Baud96,[char] ' get character from PC
WRITE addr, char ' write character to EEPROM
addr = addr + 1 ' point to next location
IF char <> CR THEN GetC ' if not CR, wait for another
GOTO ShowID ' confirm new ID
```

```
ShowTemp:
GOSUB GetTemp
DEBUG "DS1620=",DEC tmpIn,CR ' send raw temp to PC
GOTO Main
```

```
ShowTempC:
' will only return temps above freezing (0 C)
GOSUB GetTemp
IF sign = 0 THEN NoNegC
tmpIn = 0
NoNegC: ' convert raw count to 10ths C
tempC = tmpIn * 5
DEBUG "TempC=",DEC (tempC/10),".",DEC (tempC//10),CR
GOTO Main
```

```
ShowTempF:
' will only return temps above freezing (32 F)
GOSUB GetTemp
IF sign = 0 THEN NoNegF
tmpIn = 0
NoNegF: ' convert raw count to 10ths F
tempF = (tmpIn * 9) + 320
DEBUG "TempF=",DEC (tempF/10),".",DEC (tempF//10),CR
GOTO Main
```

```
ShowStat:
' show LED status
DEBUG "Status=", BIN4 -OUTC, CR
GOTO Main
```

```
SetLEDS:
' wait for output bits
' - as binary string
SERIN SIOPin,Baud96,[BIN param]
OUTC = ~param.LOWNIB ' set the outputs
GOTO ShowStat ' confirm new outputs
```

```
GetTemp:
HIGH Rst ' alert the DS1620
SHIFTOUT DQ,Clk,LSBFIRST,[RTmp] ' read temperature
SHIFTOUT DQ,Clk,LSBFIRST,[tmpIn/9] ' get the temperature
LOW Rst
RETURN
```



# STAMP APPLICATIONS

## STAMPS IN THE LAB — PART 2

editor, you can use any generic terminal program instead (make sure that Local Echo is disabled). Each command is terminated with a carriage return (Enter on the PC keyboard). For "7F1" and "7B1", a space was used as the separator between the command and the data. And don't forget the SERIN DEC modifier. If you develop a program (like this one) where you can enter data from a terminal, using the DEC modifier will make it easy.

### More BASIC to BASIC

Now that we have a Stamp project that will respond to requests, we can use Visual Basic to create a program that handles or even automates them for us. This is a pretty simple process; in fact, we only have to make a very small addition to the code that we created last month.

Essentially, we just have to build a command string for each of our functions

and send it to the Stamp. What we have to keep in mind though is that the MSComm control in VB does not have the pacing parameter that the Stamp's SEROUT function has and we're going to be forced to code around this. We need some pacing between characters because we're using SERIN modifiers and, in the case of the ID string, we're writing the characters to the Stamp's EEPROM as they come in. These processes take time.

Listing 2 is the VB code for a small demo program (see Figure 2) that takes advantage of a couple of the features of our Stamp project. This program will allow us to get and set the identification string and set the BSAC LEDs.

Remember that Visual Basic is event-driven, that is, nothing happens until something happens. In our case, things get started when we connect to the Stamp (Connect on the Port menu) and then click on one of the buttons. Let's go through one.

When we click on the button labeled "Read," a subroutine called

```
' Nuts & Volts - Stamp Applications August 2000 (Listing 2)
' =====
' Program... PolledStamp.VBP
' Author.... Jon Williams
' Started... 25 MAY 2000
' Updated... 2 JUL 2000
' =====

Option Explicit

Dim rxBuffer As String      ' response from Stamp
Dim roundRobin As Byte     ' polling control
Dim okayToClose As Boolean  ' okay to quit program?

Private Declare Function timeGetTime Lib "winmm.dll" () As Long

Private Sub cmdIDRead_Click()
    SendStr ("7F0")
End Sub

Private Sub cmdIDWrite_Click()
    SendStr ("7F1 " & Trim(txtIDString.Text))
End Sub

Private Sub cmdSetLEDs_Click()
    Dim x As Integer
    Dim ledStr As String

    ledStr = ""
    For x = 0 To 3
        If chkLED(x).Value = 1 Then
            ledStr = ledStr & "1"
        Else
            ledStr = ledStr & "0"
        End If
    Next

    SendStr ("7B1 " & ledStr) ' send command and status
End Sub

Private Sub Form_Load()
    Dim x As Integer

    ' setup form
    Me.Left = (Screen.Width - Me.Width) / 2
    Me.Top = (Screen.Height - Me.Height) / 2
    Me.Caption = App.Title

    ' clear ID text
    txtIDString.Text = ""
    cmdIDRead.Enabled = False
    cmdIDWrite.Enabled = False

    ' uncheck LEDs
    For x = 0 To 3
        chkLED(x).Value = 0
    Next
    cmdSetLEDs.Enabled = False

    ' setup comm object
    With MSComm1
        .CommPort = 1
        .Settings = "9600,N,8,1" ' setup for DEBUG
        .DTREnable = mnuPortResetStamp.Checked
        .RTSThreshold = 1 ' process one char at a time
        .InputLen = 1 ' grab one char at a time
    End With

    .InputMode = comInputModeText ' input will be strings
    .SThreshold = 0 ' don't wait to send
    End With

    okayToClose = True
End Sub

Private Sub Form_QueryUnload(Cancel As Integer, UnloadMode As Integer)
    Cancel = Not (okayToClose)
End Sub

Private Sub Form_Unload(Cancel As Integer)
    If MSComm1.PortOpen Then MSComm1.PortOpen = False
End Sub

Private Sub mnuFileExt_Click()
    Unload Me
End Sub

Private Sub mnuPortComX_Click(Index As Integer)
    ' deselect last port
    mnuPortComX(MSComm1.CommPort).Checked = False
    ' select new
    MSComm1.CommPort = Index
    mnuPortComX(Index).Checked = True
End Sub

Private Sub mnuPortConnect_Click()
    Dim x As Byte

    If okayToClose And (Not (MSComm1.PortOpen)) Then
        ' open the port
        On Error GoTo PortError
        MSComm1.PortOpen = True
        ' update the title bar
        Me.Caption = App.Title & " [Connected]"
        ' update port menu
        For x = 1 To 4
            mnuPortComX(x).Enabled = False
        Next
        mnuPortConnect.Caption = "&Disconnect"
        ' enable form controls
        cmdIDRead.Enabled = True
        cmdIDWrite.Enabled = True
        cmdSetLEDs.Enabled = True
    Else
        ' close the port
        MSComm1.PortOpen = False
        ' update the title bar
        Me.Caption = App.Title
        ' update port menu
        For x = 1 To 4
            mnuPortComX(x).Enabled = True
        Next
        mnuPortConnect.Caption = "&Connect"
        ' disable form controls
        cmdIDRead.Enabled = False
        cmdIDWrite.Enabled = False
        cmdSetLEDs.Enabled = False
    End If
    Exit Sub
PortError:
End Sub
```



# STAMP APPLICATIONS

## STAMPS IN THE LAB — PART 2

cmdIDRead\_Click is executed. This subroutine calls SendStr with the data "7F0" (read the ID). If we jump down to SendStr, we see that it sends each character of the passed string with a five-millisecond delay in between them. Once all of the characters have been sent, it completes the transmission with a carriage return (13).


One of the details that we have to deal with when using the Stamp's programming port for general serial communications is that it echoes back everything that it receives. What this means is that every character we send to the Stamp through the programming port comes back in on the receive line. When a character arrives, the MSCmm1\_OnComm subroutine gets called.

MSCmm1\_OnComm collects all incoming characters in a string called rxBuffer until it sees a carriage return. When that happens, it passes the buffer to the subroutine (cleverly called) ProcessBuffer for handling.

ProcessBuffer looks at the first character of the incoming string. If it's a "7" we

know that the string is the command we just sent and it can be discarded. If the first character is something else, we'll check it for "=" and parse the label and its parameter. A Select-Case structure lets us iterate through available labels and deal with the parameter. In the case of "ID", we send the parameter to the Identification text box. Prove to yourself that this works by clearing the text box and then clicking on "Read."

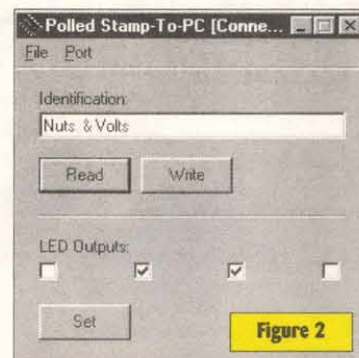This is a simple demo and doesn't do a lot — but is a very good shell for any application of this sort that you might want to develop. And you can always



```
MsgBox "Could not open Com" & Trim(Str(MSCmm1.CommPort)) & ". " & _
vbCr & "Please select another port.", _
vbExclamation + vbOKOnly, App.Title
```

```
On Error GoTo 0
```

```
End Sub
```

```
Private Sub mnuPortResetStamp_Click()
```

```
    mnuPortResetStamp.Checked = Not (mnuPortResetStamp.Checked)
    MSCmm1.DTREnable = mnuPortResetStamp.Checked
```

```
End Sub
```

```
Private Sub MSCmm1_OnComm()
```

```
    Dim newChar As String
```

```
    Select Case MSCmm1.CommEvent
```

```
        Case comEvtReceive
```

```
            newChar = MSCmm1.Input
```

```
            If newChar = Chr(13) Then
```

```
                ProcessBuffer (rxBuffer)
```

```
                rxBuffer = ""
```

```
            Else
```

```
                rxBuffer = rxBuffer & newChar
```

```
            End If
```

```
        ' process other events here
```

```
    End Select
```

```
End Sub
```

```
Private Sub ProcessBuffer(ByVal buffer As String)
```

```
    Dim leadChar As String
```

```
    Dim delimPos As Integer
```

```
    Dim label As String
```

```
    Dim param As String
```

```
    ' get leading character
```

```
    leadChar = Mid(buffer, 1, 1)
```

```
    If leadChar = "?" Then
```

```
        ' echoed query - ignore
```

```
    Else
```

```
        ' process the response
```

```
        delimPos = InStr(1, buffer, "=")
```

```
        If delimPos > 0 Then
```

```
            ' extract label and parameter
```

```
            label = UCase(Trim(Mid(buffer, 1, delimPos - 1)))
```

```
            param = Trim(Mid(buffer, delimPos + 1))
```

```
            ' process known responses
```

```
            Select Case label
```

```
                Case "ID"
```

```
                    txtIDstring.Text = param
```

```
                Case "DS1620"
```

```
                    ' process raw temperature
```

```
                Case "TEMPC"
```

```
                    ' display celcius temp
```

```
                Case "TEMFF"
```

```
                    ' display fahrenheit temp
```

```
                Case "STATUS"
```

```
                    ' confirm LED status
```

```
                Case Else
```

```
                    ' unknown label
```

```
            End Select
```

```
        Else
            ' buffer has no delimiter
            ' (error message)
        End If
    End If
```

```
End Sub
```

```
Public Sub Delay(milliseconds As Single)
```

```
    Dim timeout As Single
```

```
    timeout = milliseconds + timeGetTime()
```

```
    Do Until timeGetTime() >= timeout
```

```
        DoEvents
```

```
    Loop
```

```
End Sub
```

```
Private Sub SendStr(ByVal txBuf As String)
```

```
    Dim x As Integer
```

```
    ' can't quit while transmitting
```

```
    okayToClose = False
```

```
    For x = 1 To Len(txBuf)
```

```
        MSCmm1.Output = Mid(txBuf, x, 1)
```

```
        ' give Stamp time to receive and process the character
```

```
        Delay (5)
```

```
    Next
```

```
    ' add CR to end of command
```

```
    MSCmm1.Output = Chr(13)
```

```
    okayToClose = True
```

```
End Sub
```

```
Private Function Dec2Bin(ByVal decValue As Long) As String
```

```
    Dim tmpBin As String
```

```
    Dim testBit As Long
```

```
    tmpBin = ""
```

```
    testBit = 1
```

```
    Do
```

```
        If (testBit And decValue) > 0 Then
```

```
            tmpBin = "1" & tmpBin
```

```
            decValue = decValue - testBit
```

```
        Else
```

```
            tmpBin = "0" & tmpBin
```

```
        End If
```

```
        testBit = testBit * 2
```

```
    Loop While (decValue > 0)
```

```
    Dec2Bin = tmpBin
```

```
End Function
```

```
Private Function Bin2Dec(ByVal binValue As String) As Long
```

```
    Dim temp As Long
```

```
    Dim binLen As Integer
```

```
    Dim x As Integer
```

```
    temp = 0
```

```
    binLen = Len(binValue)
```

```
    For x = 1 To binLen
```

```
        ' add bit value if "1"
```

```
        If Mid(binValue, x, 1) = "1" Then
```

```
            temp = temp + 2 ^ (binLen - x)
```

```
        End If
```

```
    Next
```

```
    Bin2Dec = temp
```

```
End Function
```



# AMAZING MICROVIDEO!

## SUPERCIRCUITS.COM

America's #1 Microvideo Source

### LIPSTICK VIDEO CAMERAS

**MICRO COLOR CAMERA**  
1" X 1"  
350 TVL  
\$89.95!!



**STEALTHY SUPER PINHOLE**  
\$69.95



**FREE CATALOG! CALL US TODAY AND GET YOURS!**

**WOW!**

**FREE PLUG & PLAY CABLES**  
1 YEAR WARRANTY



**AMAZING!**



**STEALTHY SEE-IN-THE-DARK**  
WEATHERPROOF WITH 56 IR LED'S \$139.95



.04 LUX  
460 TVL  
2 YEAR WARRANTY

**CCTV VIDEO CAMERA**  
\$79.95!

SONY CHIPSET

**WORLD'S SMALLEST! LISTED IN 1999 GUINNESS BOOK OF RECORDS**

**AMAZING!**

**MICRO VIDEO CAMERA**  
\$59.95!



**WIRELESS VIDEO**



**WORLD'S SMALLEST VIDEO CAMERA & TRANSMITTER**  
700 FOOT RANGE \$299.95  
1 YEAR WARRANTY

**UNBEATABLE DEAL!**



350 Lines of Resolution  
**TINY 1.25" COLOR CAMERA-PLUG & PLAY-ONLY \$69.95!!**

### WIRELESS VIDEO

\$89.95



2.4 GHz AUDIO/VIDEO  
TRANSMITTER, RECEIVER  
W/ 700 FOOT RANGE  
PART 15 FCC APPROVED

### NIGHTVISION VIDEO CAM



**ULTRA PINHOLE VIDEO CAMERA-EASY CONCEALMENT**  
\$109.95

### AMAZING NEW UNDERCOVER VIDEO

CAP CAM \$149.95  
GLASSES CAM  
TIE CAM  
BAG CAM  
PAGER CAM



SONY GV-A500HI-8 VCR WITH 4" TFT MONITOR \$979.95

### MINI TIME/DATE OVERLAY



**MINI REALTIME B/W QUAD**

TINY SIZE, 12 VDC/120  
1 YEAR WARR- \$149.95

**\$34.95**

1 YEAR WARRANTY

**STEALTHY PINHOLE VIDEO CAMERA \$34.95**  
410 TVL, 0.5 LUX, 1.2"

**1-800-335-9777 ext NV**

Or fax us at 512-260-0444

[www.supercircuits.com](http://www.supercircuits.com)

**Free Catalog- Call Us Today And Get Yours**

**1-800-335-9777**

Write in 30 on Reader Service Card.

[www.supercircuits.com](http://www.supercircuits.com)

## STAMP APPLICATIONS STAMPS IN THE LAB — PART 2

automate the polling by adding a timer to the project and using it to send a command. You can also use the PC's clock to create scheduled polling events. It's up to you now. With this basic communications infrastructure in place, there's no reason not to partner your PC and Stamps on sophisticated projects.

### Can We Do Both?

Last month, our Stamp program did its processing and served up information without asking. This month, we've gone to the other extreme: the Stamp sits and waits for a command before doing anything. Can we find a happy middle ground?

Yes we can — with caution. We might, for example, create a device that normally runs on its own but has the facility to display and set parameters. In this case, we could use an input to indicate Run or Review mode. When the input (switch) is set to Review, the program would jump to a section that waits for an input query (like Main in this month's program).

When we do this, we'll want to add the timeout parameter to the SERIN function. On a timeout, the program would jump to the Run/Review switch check. If back in Run, the program would go back to its normal operations, otherwise it would continue waiting for some input from the PC.

One of the neat things about using the event-driven serial input of VB is that we don't have to wait around for a specific number of characters to arrive. If you're using the Stamp's programming port of serial communications, be careful not to mix polled commands to the Stamp with spontaneous serial data.

Remember what we just covered: When using the Stamp programming port, the PC's serial transmit pin gets tied back to its serial receive pin. Our VB program deals with this by checking the first character of the buffer for the query character. If we allow the Stamp to spontaneously transmit in a normally polled situation, however, that transmission could take place right in the middle of our polling sequence, corrupting the buffer. And since the Stamp can't receive and transmit serial data at the same time, the incoming data would be missed. Again, be cautious and try not to mix spontaneous and polled communications.

### Comm Control For Everyone

I erred last month when I stated that you had to have the Professional or Enterprise editions of Visual Basic to the MSComm control. There is a work-around for those of you that are using the Learning edition or use a language other than VB.

Serial communications guru Richard Grier has created a free control that you can use with VB (and other programming languages that support ActiveX controls) called XMComm. XMComm uses the MSComm control internally and has all its capabilities. On top of that, it also supports XModem communications for sending files between two computers. Richard has written an excellent book called *Visual Basic Programmer's Guide to Serial Communications*. This book, along with Jan Axelson's *Serial Port Complete* should be on your desk if you intend to do any serious serial-communications programming.

### What's Next?

What I do know is that I don't know for sure except that I'm toying with some Stamp-based robotics ideas. I've got my ideas, but I'd really rather hear yours. Drop me a note and we'll see what we can come up with. Until then, Happy Stamping. **NV**

### Resources:

**Jon Williams**

3718 Valley View Lane, #3040  
Irving, TX 75062  
(972) 659-9090  
[jonwms@aol.com](mailto:jonwms@aol.com)

**Parallax**

599 Menlo Drive, Suite 100  
Rocklin, CA 95756  
(888) 512-1024  
[www.parallaxinc.com](http://www.parallaxinc.com)

**Richard Grier**

*Visual Basic Programmer's Guide to Serial Communications*  
[www.mabry.com](http://www.mabry.com)

**XMComm control**

[ourworld.compuserve.com/homepages/richard\\_grier](http://ourworld.compuserve.com/homepages/richard_grier)

**Jan Axelson**

*Serial Port Complete*  
[www.lvr.com](http://www.lvr.com)



**CALL TOLL FREE**

(800) 292-7711  
Orders Only

Se Habla Español

# C&S SALES

Secure On-line Ordering @ [cs-sales.com](http://cs-sales.com)

**CALL OR WRITE  
FOR OUR  
FREE**

64 PAGE CATALOG!  
(800) 445-3201

## Digital Multimeters

### Elenco Model M-1740



**\$34.95**  
11 Functions:  
• Freq. to 20MHz  
• Cap. to 20µF  
• AC/DC Voltage  
• AC/DC Current  
• Diode Test  
• Transistor Test  
• Meets UL-1244 safety specs.  
Model M-2760N  
(9 functions)

### Elenco Model LCR-1810



**\$99.95**  
• Cap. 0.1pF to 20µF  
• Inductance 1µH to 20H  
• Resistance 0.01Ω to 2.000MΩ  
• Temperature -20°C to 750°C  
• DC Volts 0 - 20V  
• Freq. up to 15MHz  
• Diode/Audible Continuity Test  
• Signal Output Function  
• 3 1/2 Digit Display

### Elenco Model LCM-1950



**\$69.95**  
• Large 1 3/4 Digit LCD  
• Autoranging Freq. to 4MHz  
• Cap. to 400µF  
• Inductance to 40H  
• Res. to 4.000MΩ  
• Logic Test  
• Diode & Transistor Test  
• Audible Continuity Test

### Fluke 87III



**\$319**  
Features high performance AC/DC voltage and current measurement, frequency, duty cycle, resistance, conductance, and capacitance measurement.

## Deluxe Soldering Stations

### Elenco SL-5 Series

Electronically controlled, ideal for professionals, students, and hobbyists. Available in kit form or assembled.

**As Low As  
\$29.95**

Works w/ any iron! Turn any soldering iron into a variable iron.

Quantity Discounts Available



#### Features:


- Cushion Grip Handle
- Soldering Iron (optional) with Grounded Tip for Soldering Static-Sensitive Devices. Easily Replaceable. Uses Long-Life, Plated Conical Tip.
- Heavy Steel, Non-Slip Base.
- Iron Holder Funnel - Reversible, left or right side.
- Steel Tray for Sponge Pad.
- Sponge Pad.

## Test Equipment

### 10 Function 1.3GHz Universal Counter Elenco Model F-1300

- Frequency .05Hz - 1.3GHz 3 Ranges
- Period - Can read 60Hz to 60.000000 F=1/T
- Totalize - Counts to 999,999,999
- RPM - 3 to 2099994 RPM
- Duty Cycle
- Max/Min/AVG with Time
- Stop-watch set .2 sec. to 100 hrs.
- Math Functions
- Timer - 2 sec. to 99 days
- Pulse Width - 0.1ms to 66666.6ms

**\$229.95**

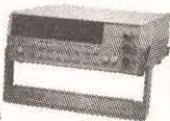

### Elenco 3MHz Sweep Function Generator with built-in 60MHz Frequency Counter Model GF-8046

**\$195.95**



This sweep function generator with counter is an instrument capable of generating square, triangle, and sine waveforms, and TTL, CMOS pulses over a frequency range from 0.5Hz to 3MHz. GF-8025 - Without Counter \$139.95

### 20MHz Sweep / Function Generator with Frequency Counter Model 4040

- 0.2Hz to 20MHz
- AM & FM Modulation
- Burst Operation
- External Frequency Counter to 30MHz
- Linear and Log Sweep



21.5MHz Model 4070 \$1295  
10MHz Model 4017 \$325  
5MHz Model 4011 \$255 **\$445** **BK PRECISION**

### Elenco Handheld Universal Counter 1MHz - 2.8GHz Model F-2800



**\$99**

#### Sensitivity:

- <1.5mV @ 100MHz
- <5mV @ 250MHz
- <5mV @ 1GHz
- <100mV @ 2.4GHz

Features 10 digit display, 16 segment and RF signal strength bargraph. Includes antenna, NiCad battery, and AC adapter.

C-2800 Case w/ Belt Clip.....\$14.95

### Elenco RF Generator with Counter (100kHz - 150MHz) Model SG-9500



**\$225**

Features internal AM mod. of 1kHz, RF output 100mV - 35mHz. Audio output 1kHz @ 1V RMS. SG-9000 (analog, w/o counter) \$124

### Elenco Quad Power Supply Model XP-581

4 Fully Regulated Power Supplies in 1 Unit



**\$85**

4 DC Voltages: 3 fixed: +5V @ 3A, +12V @ 1A, 1 variable: 2.5 - 20V @ 2A • Fully Regulated & Short Protected • Voltage & Current Meters • All Metal Case


### Elenco Power Supply Model XP-603



**\$85**

- 0-30VDC @ 3A Output
- 3A Fused Current Protection
- Current Limiting Short Protection
- 0.025Ω Output Impedance
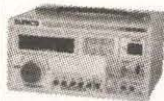
### Elenco 10Hz - 1MHz Digital Audio Generator Model SG-9300



**\$225**

Features built-in 150MHz frequency counter, low distortion and sine/square waves. SG-9200 (w/o counter) \$124

## Ordering Information:

Model SL-5 - No Iron. (Kit SL-5K) **\$29.95**

Model SL-5-40 - Includes 40W UL Iron. (Kit SL-5K-40) **\$35.95**

Model SL-5-60 - Includes 60W UL Iron. (Kit SL-5K-60) **\$36.95**

Limited Time Offer: **FREE SP-1A Solder Practice Kit w/ Kit Order!**

Weller WLC-100 - Variable Power Control 5 - 40 watts **\$34.95**

### Elenco Model SL-30



**\$84.95**

- Tip temperature changeable from 300°F (150°C) to 900°F (480°C).
- Temperature is maintained within +10°F of its preset temperature.
- The tip is isolated from the AC line by a 24V transformer.
- The tip is grounded to eliminate static charges.

SL-10 - Same as SL-30 w/o digital display **\$59.95**

### Weller Model WTCPT Controlled Output Soldering Station


- Transformer powered soldering station complete w/macro style, low voltage, temperature controlled soldering iron.
- PT Series soldering tips come in a variety of shapes and sizes in three standard temperature ranges: 600°F, 700°F, & 800°F.
- 0-24V output - 60 watts.
- Special "closed loop" method of controlling maximum tip temperature.



**\$125**

## Elenco Oscilloscopes

Free Dust Cover and 2 Probes

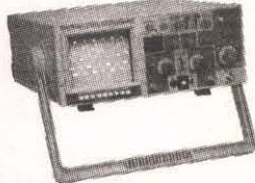

S-1325 25MHz Dual Trace \$325  
S-1330 25MHz Delayed Sweep \$439  
S-1340 40MHz Dual Trace \$475  
S-1345 40MHz Delayed Sweep \$569  
S-1360 60MHz Delayed Sweep \$725  
S-1390 100MHz Delayed Sweep \$995

### DIGITAL SCOPE SUPER SPECIALS


DS-203 20MHz/10Ms/s Analog/Digital.....\$695  
DS-303 40MHz/20Ms/s Analog/Digital.....\$850  
DS-603 60MHz/20Ms/s Analog/Digital.....\$950

## Elenco Educational Kits

### Model XK-150

Digital / Analog Trainer

**\$89.95**

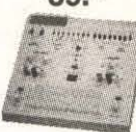

- 830-pin Breadboard
- 8 Data Switches
- 8 LED Buffered Readouts
- Built-in Function Generator (sine and square wave)
- Built-in Clock Generator
- Variable Power Supply +125V to 15VDC @ .25A -125V to -15VDC @ .25A +5VDC @ .25A +30VAC center-tapped at 15VAC @ .25A

### Model AR-2N6K

2 Meter / 6 Meter Amateur Radio Kit

**\$34.95**



### Model AK-700

Pulse/Tone Telephone Kit

Flashing Neon Lights

Great School Project

**\$15.95**



### Model M-1005K

DMM Kit

**\$15.95**



- Transistor Test
- Diode Test
- Overload Protection
- Pocket Size

### Model AM-780K

Two IC Radio Kit

**\$11.95**



### Model AK-870

Radio Control Car Kit

**\$24.95**



### Model MX-901

Electronic Crystal Radio

**\$6.95**



- Solderless
- No Batteries Req.

## CCTV Cameras

Cameras have 420 lines (360 color) of resolution, 0.08 Lux, 3.6mm/F2 90° field of view. Power requirement is 12VDC @ 100mA (order SC-1).

### MONOCHROME CAMERAS

### COLOR CAMERAS



**\$69**

SC-12 - 35mm Lens (1.25"x1.25")

**\$69**

SC-15 - Pin Lens (1.25"x1.25")

**\$69**

Add \$10 for lens • Add \$10 for audio

**\$109**

Accessories:

SC-1 - 12V 100mA adapter

SC-2 - 50' cable w/ connectors



**\$69**

SC-20 Pin Lens

**\$69**

360 Lines 1.25" x 1.25"

Infrared Sensitive, Audio Included

Add \$10 for case

**\$19.95**

Call for complete catalog.

**\$109**

Call for complete catalog.

## Guaranteed Lowest Prices

UPS SHIPPING: 48 STATES 5%  
OTHERS CALL FOR DETAILS  
IL Residents add 8.25% Sales Tax

**SEE US ON THE WEB**

## C&S SALES, INC.

150 W. CARPENTER AVENUE  
WHEELING, IL 60090  
FAX: (847) 541-9904 (847) 541-0710  
<http://www.cs-sales.com>

## 15 DAY MONEY BACK GUARANTEE

## 2 YEAR FACTORY WARRANTY



# FET PRINCIPLES AND CIRCUITS

## Part 4

### Field-Effect Transistors

by Ray Marston

Ray Marston looks at practical VMOS power FET circuits in this final episode of this four-part series.

For a complete selection of JFETs, Transistors, and MOSFETs, check out Linear Systems on Page 17.

Part 1 of this series explained (among other things) the basic operating principles of those enhancement-mode power-FET devices known as VFETs or VMOS. This final episode of the series takes a deeper look at these devices and shows practical ways of using them.

#### A VMOS INTRODUCTION

A VFET can, for most practical purposes, be simply regarded as a high-power version of a conventional enhancement-mode MOSFET. The specific form of VFET construction shown in Figure 17 in Part 1 of this series was pioneered by Siliconix in the mid-1970s, and the devices using this construction are marketed under the trade name 'VMOS power FETs' (Vertically-structured Metal-Oxide Silicon power Field-Effect Transistors). This 'VMOS' name is traditionally associated with the V-shaped groove formed in the struc-



Figure 1. Symbol of Siliconix VMOS power FET with integral zener diode gate protection.

ture of the original (1976) versions of the device.

Siliconix VMOS power FETs are probably the best known type of VFETs. They are available as n-channel devices only, and usually incorporate an integral zener diode which gives the gate a high degree of protection against accidental damage; Figure 1 shows the standard symbol used to represent such a device, and Figure 2 lists the main characteristics of five of the most popular members of the VMOS family; note in particular the very high maximum operating frequencies of these devices.

Other well-known families of 'Vertically-structured' power MOSFETs are those produced by Hitachi, Supertex, and Farranti, etc. Some of these V-type power MOSFETs are available in both n-channel and p-channel versions and are useful in various high-performance complementary audio power amplifier applications.

#### THE VN66AF

The best way to get to know VMOS is to actually 'play' with it, and the readily available Siliconix

Device type number	$P_{TOT}$ (max) (W)	$I_D$ (max) (A)	$V_{DS}$ (max) (V)	$V_{GS}$ (max) (V)	$V_{TH}$ (min-max) (V)	$g_m$ (typ) (mmho)	$C_{IN}$ (max) (pF)	$f_T$ (typ) (MHz)
VN10KM	1	0.5	60	5	0.3 - 2.5	200	48	—
VN1010	1	0.5	100	15	2V max	200	48	—
VN48AF	12.5	2	40	15	0.8 - 2	250	50	600
VN66AF	12.5	2	60	15	0.8 - 2	250	50	600
VN88AF	12.5	2	80	15	0.8 - 2	250	50	600

Figure 2. Major parameters of five popular n-channel Siliconix VMOS power FETs.

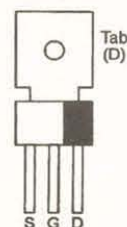


Figure 3. Outline and pin connections of the TO202-cased VN66AF power FET.

VN66AF is ideal for this purpose. It is normally housed in a TO202-style plastic-with-metal-tab package with the outline and pin connections shown in Figure 3.

Figure 4 lists the major static and dynamic characteristics of the VN66AF. Points to note here are that the input (gate-to-source) signal must not exceed the unit's 15V zener rating, and that the device has a typical dynamic input capacitance of 50pF. This capacitance dictates the dynamic input impedance of the VN66AF; the static input impedance is of the order of a million megohms. Figures 5 and 6 show the VN66AF's typical output and saturation characteristics. Note the following specific points from these graphs.

(1) The device passes negligible drain current until the gate voltage reaches a threshold value of about 1V; the drain current then increases non-linearly as the gate is varied up to about 4V, at which point the drain current value is about 400mA; the device has a square-law transfer characteristic below 400mA.

(2) The device has a highly linear transfer characteristic above 400mA (4V on the gate) and thus offers good results as a low-distortion class-A power amplifier.

## ACP'S 99th GIANT COMPUTER SWAP★MEET

Orange County's Original!  
All Day Sunday 8am-2pm  
Sept 24th  
FREE Admission & Parking  
Shop 100's of Sellers

in ACP's Giant Parking Lot!!!


Advanced Computer Products, Inc.

ACP SUPER★STORE  
Since 1976

1310 E. Edinger  
Santa Ana, CA  
714-558-8813  
www.acpsuperstore.com
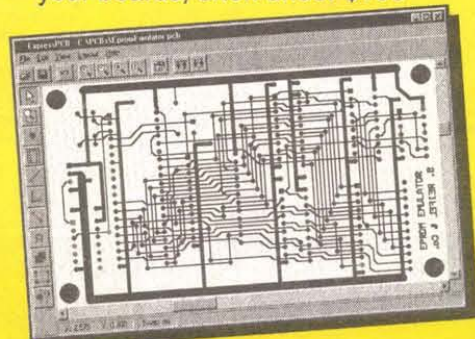
## PCB LAYOUT Software For Windows - FREE

- 1 Download our board layout software
- 2 Design your 2 sided plated-through PCB
- 3 Send us your layout over the Internet
- 4 In 2-3 business days, UPS delivers your boards, often under \$100



www.expresspcb.com



# FET

(3) The drain current is controlled almost entirely by the gate voltage and is almost independent of the drain voltage so long as the device is not saturated. A point not shown in the diagram is that, for a given value of gate voltage, the drain current has a negative temperature coefficient of about 0.7% per °C, so that the drain current decreases as temperature rises. This characteristic gives a fair degree of protection against thermal runaway.

(4) When the device is saturated (switched fully on) the drain-to-source path acts as an almost pure resistance with a value controlled by the gate voltage. The resistance is typically 2R<sub>0</sub> when 10V is on the gate, and 10R when 2V is on the gate. The device's 'off' resistance is in the order of megohms. These features make the device highly suitable for use as a low-distortion high-speed analog power switch.

## DIGITAL CIRCUITS

VMOS can be used in a wide variety of digital and analog applications. It is delightfully easy to use in digital switching and amplifying applications; Figure 7 shows the basic connections. The load is wired between the drain and the positive supply rail, and the digital input signal is fed directly to the gate terminal. Switch-off occurs when the input goes below the gate threshold value (typically about 1.2V). The drain ON current is determined by the peak amplitude of the gate signal, as shown in Figure 5, unless saturation occurs. In most digital applications, the ON current should be

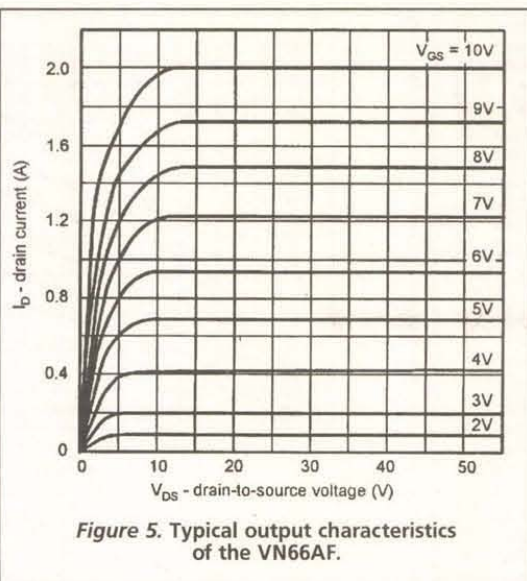


Figure 5. Typical output characteristics of the VN66AF.

chosen to ensure saturation.

The static input impedance of VMOS is virtually infinite, so zero drive power is needed to maintain the VN66AF in the ON or OFF state. Drive power is, however, needed to switch the device from one state to the other; this power is absorbed in charging or discharging the 50pF input capacitance of the VN66AF.

The rise and fall times of the output of the Figure 7 circuit are (assuming zero input rise and fall times) determined by the source impedance of the input signal, by the input capacitance and forward transconductance of the VMOS device, and by the value of  $R_L$ . If  $R_L$  is large compared to  $R_S$ , the VN66AF gives rise and fall times of roughly 0.11nS per ohm of  $R_S$  value. Thus, a 100R source impedance gives a 11nS rise or fall time. If  $R_L$  is not large compared to  $R_S$ , these times may be considerably changed.

A point to note when driving the VN66AF in digital applications is that its zener forward and reverse ratings must never be exceeded. Also, because of the very high frequency response of VMOS, the device is prone to unwanted oscillations if its circuitry is poorly designed. Gate leads should be kept

STATIC	Max drain-to-source voltage	60V
	Max drain-to-gate voltage	60V
	Max continuous drain current	2A
	Max pulsed drain current	3A
	Max continuous forward gate current	2mA
	Max pulsed forward gate current	100mA
	Max continuous reverse gate current	100mA
	Max reverse gate-to-source (zener) voltage	15V
	Max dissipation at 25°C case temperature	15W
	Gate threshold voltage	0.8V min, 2.0A typ.
DYNAMIC	Zero-gate-voltage drain current at 25°C	10µA max
	On-state drain current at V <sub>GS</sub> = 10V	1.0A min, 2.0A typ.
	Temperature operating and storage range	-40 to +150°C
	Forward transconductance (typical)	250 mmho
	Input capacitance (typical)	50pF
	Reverse transfer capacitance (typical)	10pF
	Common-source output capacitance (typical)	50pF
	Typical switching times, 25V supply, 23R load, 0-10V gate drive from a 50R source	
	Turn-on delay	2nS
	Rise time	2nS
	Turn-off delay	2nS
	Fall time	2nS

Figure 4. Major static and dynamic characteristics of the VN66AF.

short, or be protected with a ferrite bead or a small resistor in series



## REFILL INKS FOR INKJET PRINTERS

Refill your old cartridge and save. All refill kits come with instructions and needed materials for refilling inkjet cartridges. Success guaranteed. Available for the following:

**CANON BC-01, BC-02** CANON BJ10e, APPLE STYLEWRITER, BJ-200 Single, Black, \$8.00. **CANON BJC-600** (BC-201) Single Black or Single Colors (3 refills) \$8.00. **CANON BJ-130/300/330 & IBM Exec Jet** (Cart #BJL-481 & BJL-642) Black - 3-bottle kit \$22.00. **CANON BJC-210/240** (BC-05 Cart) 3-color kit (3 refills each color for BC-05) \$24.00. **CANON BJC-4000** and Apple Stylewriter 2400 Black 3-bottle kit (3 refills BC-20, 9 refills BCI-21 black, 30 refills BCI-11 black, 10 refills BCI-10) \$19.00. **CANON BJC-4000/BJC70** and Apple Stylewriter 2400 Tri-color kit - 6 refills each color for BCI-21 or 15 refills each color for BCI-11 \$24.00. **CANON BJC-800/820/880** 3-bottle kit (for BJI-643B) \$19.00. **CANON BJC-800/820/880** 3-bottle tri-color kit (Cart #BJL-643CMY) \$24.00. **EPSON STYLUS COLOR PRINTER** (Cart S020034) Single Triple black \$19.00; Tri-color kit (Cart S020036) 2 refills each color \$24.00. **EPSON STYLUS COLOR II** (S020047) Triple Black \$19.00 (S020049). Tri-color (2 refills each color) \$24.00. **EPSON STYLUS COLOR 400, 500, & 600** (S020093) Triple black (7 refills total) \$19.00. **EPSON STYLUS COLOR 200, 500** (S020097) Tri-color 3 refills each color \$24.00. **EPSON STYLUS COLOR 400, 600, 800, 1520** Tri-color (S020089) 3 refills each color \$24.00. **EPSON STYLUS 800/1000** (S020025) 3-refill kit, black, \$19.00. **EPSON STYLUS COLOR 440 AND 640** Black refill kit. (S020187) 4 refills plus free vacuum bottle \$19.00. **EPSON STYLUS COLOR 440, 640, AND 740** (S020191) Color refill kit. 4 refills of each color \$24.00. **HP DESKJET 500/550/560** (51608A, 51633A, 51626A) Black single refills \$8.00. **HP DESKJET 500/550/560**. Black 3-bottle kit \$19.00. **HP DESKJET 500C/550C/560C**. Tri-color kit (5 refills each color) \$24.00. **HP DESKJET 1200C, DESIGNJET 650** (Cart #HP 51640B) Black Three pack (3 refills) \$19.00. **HP DESKJET 1200C/1600C, DESIGNJET 650** (Cart #HP 51640 C,M,Y). Tri-color kit (one refill each color) \$24.00. **HP DESKJET 600/660** (HP 51629A) Black three pack \$19.00. **HP DESKJET 600C/660C**. (HP 51649A) Tri-color (5 refills each color) \$24.00. **HP DESKJET 855C/1600C** (HP 51645A) Black three pack \$19.00. **HP DESKJET 855C** (HP 51641A) Tri-color kit (2 refills each color) \$24.00. **HP PAINTJET and PAINTJET XL** (51606A) Black 3-bottle kit \$19.00. **HP PAINTJET and PAINTJET XL** (51606C) Tri-color kit \$24.00. **HP PAINTJET XL300** (C1645A & C1656A) Black 3-refill kit \$19.00. **HP PAINTJET XL300** Tri-color kit (1 refill each color) HP 51639C,M,Y \$24.00. **HP THINKJET, QUIETJET, KODAK DICONX 150** (51604A or 92261A) black 5 refills \$9.00. **IBM/Lexmark/Execjet/4076** (1380620) black 3-refill kit \$19.00. **IBM/Lexmark ExecJet IIC, WinWriter 150 C** (Cart #1380619) 4 refills each color \$24.00. **Lexmark 3200, 5000, 5700, 7000, 7200, Optra 45 and Z51** (12A1970) 3 refills Black \$19.00. **Lexmark 3200, 6000, 5700, 7000, Optra 45 and Z51** (12A1980) 4 refills each color \$24.00. **SNAP AND FILL SYSTEM** - Permits refilling HP 51626A (black for HP 500-series) and HP 51629A (black for HP 600-series) cartridges without making a hole in the cartridge. Consists of special cartridge holder, syringe, plastic tubing, and directions. **STARTER KIT** - with ink for 3 refills \$28.00. **EXTRA INK FOR SNAP & FILL SYSTEM** (black only) 4-oz. bottle \$18.00; 8-oz. bottle \$34.00. Specify whether for HP 51626A or HP 51629A.

## HARD-TO-GET PRINTER RIBBONS

Gorilla Banana, Commodore 1525 \$8.00; Adam Coleco \$12.00; TI-850/855 \$6.00; Centronics 700 Zip Pack \$5.00; C. Itoh Prowriter Jr., Riteman C+/F+ \$6.00; Riteman Inrunner \$8.00; Commodore MPS-801 \$5.00; MPS 803 \$5.00; Decwriter LA30/36 \$4.00; Apple Scriber \$4.00; Manniman Tally Spirit 80, Commodore 1526 \$5.00; Epson JX-80 4-Color \$14.00; Printronix P-1013 \$11.00; Star SJ144 color 3-pack \$29.00. ALSO HEAT & TRANSFER RIBBONS AND PAPER FOR PRINTING T-SHIRTS.

Over 300 different ribbons in stock. All ribbons new, not re-inked. Fully guaranteed. Order directly or send SASE for complete list.

Add \$4 per order shipping. CA residents add 7.75% sales tax. On ribbon orders over \$50 deduct 10% discount.

## H.T. ORR Computer Supplies

249 Juanita Way, Placentia, CA 92870-2216

714-528-9822 • 800-377-2023 • FAX 714-993-6216

<http://www.extremeplay.com/occomp/orr.htm>

Write in 138 on Reader Service Card.

Nuts & Volts Magazine/AUGUST 2000 71

## ON SCREEN DISPLAY-CHARACTER OVERLAY BOARD

Need to display more text than your LCD module can handle? OSD-232 is the solution! From any RS-232 serial source like a PC or Basic Stamp, display 28 columns by 11 rows of information (308 characters total) directly onto any NTSC or optional PAL baseband (video in) television or VCR. OSD-232 can overlay monochrome text onto an incoming video source or display colored text on a self-generated colored background screen.

OSD-232 \$99.00

We accept Visa and Mastercard.


Intuitive Circuits, LLC

2275 Brinston • Troy, MI 48063

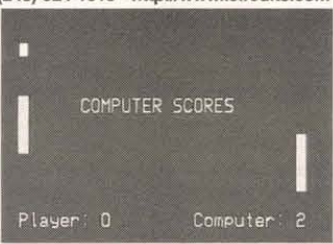(248) 524-1918 • <http://www.icircuits.com>



OSD-232 on board a radio controlled airplane



An OSD-232 video game programmed in BASIC

Write in 136 on Reader Service Card.



# TEKLAB INC. WANTED

BUYING \$10 MILLION DOLLARS  
WORTH OF TEST EQUIPMENT!

Hewlett Packard	Hewlett Packard	Hewlett Packard	Rohde&Schwarz	Fluke
1143A.....\$365	6552A.....\$585	8562E.....\$20,039	AMIC.....\$6,747	2625A.....\$1,328
11667A.....\$325	6574A.....\$1,239	8563E.....\$22,677	CMD55.....\$14,947	2645A.....\$1,364
11792A.....\$1,376	66000A.....\$762	8564E.....\$31,629	CMD57.....\$11,363	5500A.....\$4,650
11974U.....\$4,257	66101A.....\$592	8565E.....\$44,070	CMD80.....\$17,965	5520A.....\$10,432
16442A.....\$1,565	66102A.....\$537	85718B.....\$1,000	CTS55.....\$4,054	5790A.....\$7,188
16518A.....\$1,600	66103A.....\$429	85719A.....\$689	FSEA20.....\$10,940	6062A.....\$1,550
16522A.....\$3,182	6612B.....\$408	8590L.....\$3,540	FSEA30.....\$21,776	6080A.....\$1,433
16533A.....\$1,916	6621A.....\$1,069	8591C.....\$6,198	FSEB20.....\$19,452	
16557D.....\$5,535	6622A.....\$1,366	8591E.....\$5,667	FSEB30.....\$29,732	
1660CS.....\$4,074	6623A.....\$1,336	8593E.....\$10,047	FSEK30.....\$39,453	
1662AS.....\$2,542	6624A.....\$1,792	8594E.....\$7,228	FSEM20.....\$17,601	
16700A.....\$4,231	6626A.....\$4,010	8595E.....\$7,880	FSEM30.....\$25,649	
16702A.....\$4,862	6629A.....\$2,603	8596E.....\$9,141	SME03.....\$9,659	
6717A.....\$9,102	6632B.....\$775	8643A.....\$3,404	SME06.....\$15,612	
3245A.....\$1,599	66332A.....\$981	8644B.....\$11,655	SMIC03B.....\$10,698	
33120A.....\$843	6653A.....\$1,068	8645A.....\$13,637	SMT03.....\$5,487	
34401A.....\$487	6654A.....\$1,068	8648A.....\$2,139	SMT06.....\$10,564	
3458A.....\$3,362	6673A.....\$1,788	8648B.....\$3,518	SMY01.....\$1,914	
346A.....\$564	6674A.....\$1,659	8648C.....\$4,363	SMY02.....\$2,537	
346B.....\$511	6683A.....\$2,396	8648D.....\$4,896		
346C.....\$756	6812A.....\$2,253	8662A.....\$6,775		
34970A.....\$567	6812B.....\$2,939	8663A.....\$15,639		
35670A.....\$7,808	6813A.....\$3,121	8664A.....\$17,260		
3589A.....\$9,606	6834B.....\$6,175	8665A.....\$15,154		
3708A.....\$7,505	70911A.....\$7,712	8665B.....\$24,718		
37702A.....\$3,608	81103A.....\$2,430	8713C.....\$5,623		
37718A.....\$9,046	81106A.....\$800	8714C.....\$6,795		
41421B.....\$999	8110A.....\$3,162	8714ES.....\$13,329		
41422A.....\$1,381	81110A.....\$3,541	8720D.....\$31,990		
41425A.....\$587	8114A.....\$3,954	8720ES.....\$33,243		
41426A.....\$3,784	8133A.....\$21,733	8722D.....\$45,912		
4156A.....\$17,275	81530A.....\$1,681	8722ES.....\$43,823		
4156B.....\$23,728	81531A.....\$1,214	87512A.....\$1,088		
41800A.....\$439	8153A.....\$1,226	8753D.....\$15,237		
4278A.....\$2,512	83050A.....\$8,665	8753E.....\$16,922		
4284A.....\$4,622	83206A.....\$4,365	8753ES.....\$18,232		
4338B.....\$1,278	83220C.....\$3,804	8757D.....\$3,750		
4352B.....\$30,983	83236B.....\$4,400	8920B.....\$8,237		
4395A.....\$11,478	83480A.....\$5,253	8922P.....\$18,516		
43961A.....\$1,109	83484A.....\$6,480	8922S.....\$14,610		
4396B.....\$14,772	83485A.....\$6,028	8924C.....\$26,190		
53131A.....\$736	83640A.....\$18,273	89431A.....\$13,062		
53181A.....\$674	83640B.....\$22,311	89441A.....\$34,986		
53310A.....\$4,891	83650B.....\$30,880	8970B.....\$4,515		
5347A.....\$3,009	83711B.....\$9,333	8990A.....\$7,972		
5348A.....\$1,950	83712B.....\$11,609	8991A.....\$6,473		
5350B.....\$1,592	83732B.....\$18,492	E3631A.....\$474		
5373A.....\$10,593	83752A.....\$11,842	E3632A.....\$407		
54522A.....\$4,921	83752B.....\$11,854	E3633A.....\$657		
54602B.....\$786	8449B.....\$4,622	E4402B.....\$7,374		
54610B.....\$1,074	8481A.....\$330	E4404B.....\$10,157		
54615B.....\$2,443	8481D.....\$458	E4406A.....\$16,264		
54645D.....\$1,713	8482B.....\$367	E4418A.....\$1,214		
54845A.....\$14,051	85024A.....\$733	E4418B.....\$1,612		
6010A.....\$1,128	85025D.....\$633	E4419A.....\$2,069		
6015A.....\$1,739	85025E.....\$516	E4420B.....\$3,439		
6030A.....\$1,941	85027D.....\$2593	E4421A.....\$4,571		
6031A.....\$1,688	85032B.....\$812	E4421B.....\$5,665		
6032A.....\$1,814	85033D.....\$1,272	E4422A.....\$4,184		
6035A.....\$2,053	85052D.....\$1,667	E4422B.....\$5,864		
60501B.....\$604	8508A.....\$2,385	E4425B.....\$8,220		
60502B.....\$747	85107B.....\$54,767	E4426A.....\$4,075		
60504B.....\$906	8517B.....\$16,246	E4432B.....\$8,661		
60507B.....\$1,101	8560E.....\$15,767	E4433B.....\$9,528		
6050A.....\$901	8561E.....\$19,164	E7405A.....\$17,069		
6063B.....\$848	8562A.....\$9,199	E8285A.....\$32,424		
6543A.....\$453	8563A.....\$9,699	E4419B.....\$2,223		

**Check Out These  
BUY PRICES!**  
Options pay even more

Tektronix	Tektronix
2712.....\$2,682	TDS784D.....\$10,901
11801B.....\$10,338	TDS794D.....\$22,207
11801C.....\$11,223	TDS820.....\$5,362
1502C.....\$2,428	TLA714.....\$5,584
370A.....\$14,313	TLA7D1.....\$3,504
371A.....\$16,135	TLA7D2.....\$6,795
AM503B.....\$560	TLA7N3.....\$4,994
AWG2021.....\$5,185	TLA7N4.....\$8,116
AWG510.....\$7,305	TL5216.....\$8,635
AWG520.....\$14,904	TSG130A.....\$1,127
AWG610.....\$17,147	VM700A.....\$2,951
CSA803C.....\$7,462	VM700T.....\$8,679
CTS850.....\$7,773	8003A.....\$1,525
DG2020A.....\$4,293	80301.....\$309
GB1400.....\$35,116	80303.....\$391
HFS9003.....\$5,658	80304.....\$524
P6245.....\$446	80320.....\$329
PS2520G.....\$400	80323.....\$411
SD22.....\$2,581	80324.....\$544
SD24.....\$6,346	80503.....\$1,090
SD26.....\$4,054	80504.....\$3,090
ST112.....\$8,849	8542C.....\$1,648
ST2400A.....\$22,947	8650A.....\$1,950
TDS220.....\$382	
TDS3032.....\$1,392	
TDS3034.....\$2,850	
TDS3054.....\$5,149	
TDS340.....\$573	
TDS350.....\$880	
TDS360.....\$1,492	
TDS380.....\$1,941	
TDS460A.....\$3,164	
TDS510A.....\$3,376	
TDS520D.....\$4,016	
TDS540B.....\$3,168	
TDS540C.....\$5,592	
TDS540D.....\$7,466	
TDS640A.....\$2,610	
TDS640B.....\$8,138	
TDS684C.....\$9,193	
TDS694C.....\$22,748	
TDS754D.....\$8,591	
TDS784C.....\$8,755	

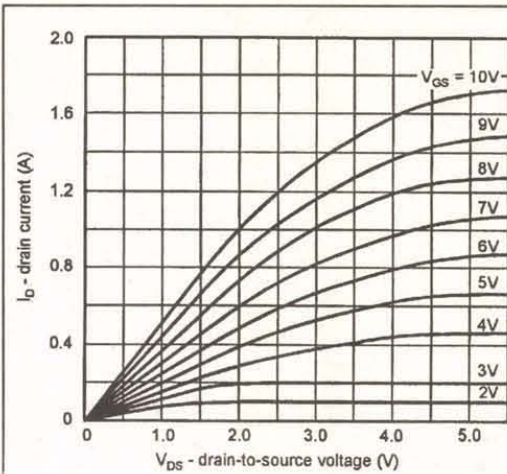


Figure 6.  
Typical  
saturation  
characteristics  
of the  
VN66AF.

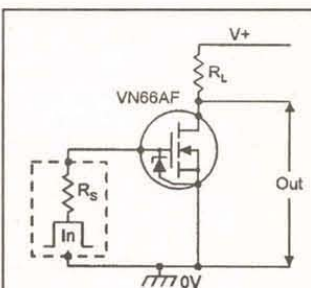


Figure 7. Basic VMOS digital switch or amplifier.

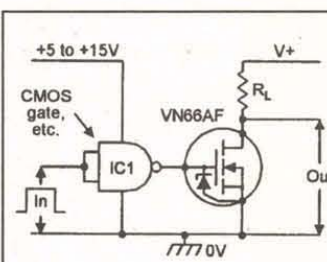


Figure 8. Methods of driving VMOS from CMOS.

with the gate.

VMOS can be interfaced directly to the output of a CMOS IC, as shown in Figure 8. Output rise and fall times of about 60ns can be expected, due to the limited output currents available from a single CMOS gate, etc. Rise and fall times can be reduced by driving the VMOS from a number of CMOS gates wired in parallel, or by using a special high-current driver.

VMOS can be interfaced to the output of TTL by using a pull-up resistor on the TTL output, as shown in Figure 9. The 5V TTL output of this circuit is sufficient to drive 600mA through a single VN66AF. Higher output currents can be obtained either by wiring a level-shifter stage between the TTL output and the VMOS input, or by wiring a number of VMOS devices in

# FET

Weeder  
Technologies



RS-232  
Stackable

www.weedtech.com

Data Book Available

850-863-5723

**Digital I/O Module** - 14 I/O pins individually configured for input or output. Turn on/off relays. Sense switch transitions, button presses, 4x4 matrix decoding using auto-debounce and repeat. One-shot pulse output with user programmable length. \$49


**Analog Input Module** - 8 input pins. 12-bit plus sign self-calibrating ADC reads voltages from 0 to 4095 mV using 1 mV resolution. Supports single-ended, differential, or pseudo-differential modes. Software programmable alarm trip-points for each input. \$59

**Stepper Motor Driver** - Drives a unipolar stepper motor rated up to 25VDC @ 2A. Uses automatic self-generated parabolic acceleration/deceleration curves for smooth start and stop motion. Software programmable ramp-rate and speed. 24-bit absolute motor position counter. Limit-switch input. \$59

**Pulse Counter/Timer** - Read frequency from 0.50000 to 1,500.00 Hz using floating decimal point and 5-digit resolution throughout range. Measure period, RPM, duty cycle, pulse length, velocity of a projectile using a pair of trip wires. Accumulate pulse count. \$69

**Multi-Drop Peripheral Interface** - Connect a third-party RS-232 peripheral, such as a bar-code scanner, force-gage, multi-meter, etc., onto the multi-drop bus. Appended header character identifies which of up to 32 devices is sending data to the host PC. Host uses header character to address each peripheral. \$59

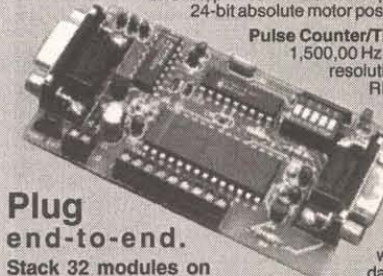Plug  
end-to-end.  
Stack 32 modules on  
the same RS-232 cable.



**GUARANTEED PAYMENT  
WITHIN 15 DAYS**


Quantities required are dependent on prior purchases.

Check out the updated list at: [www.teklab.cc](http://www.teklab.cc)


email: [sellnow@teklab.cc](mailto:sellnow@teklab.cc)

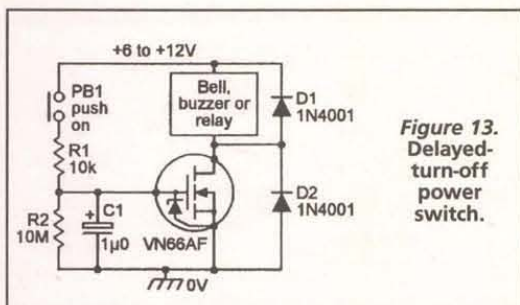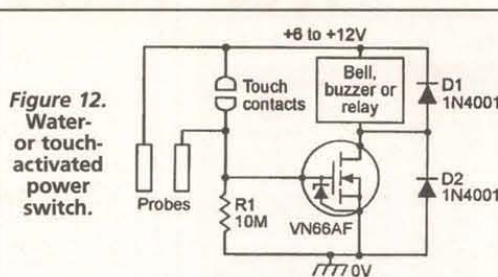Phone: 561-334-0600 FAX: 561-334-0655

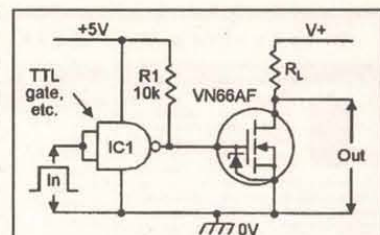





**Figure 13.**  
Delayed-  
turn-off  
power  
switch.



**Figure 12.**  
Water-  
or touch-  
activated  
power  
switch.



**Figure 9.** Method of driving  
VMOS from TTL.

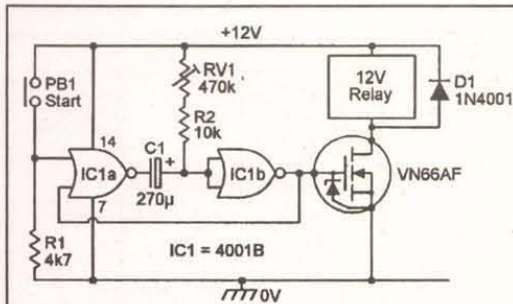

**Figure 14.**  
Simple  
relay-output  
timer circuit.

parallel, as shown in Figure 10.

When using VMOS in digital switching applications, note that if inductive drain loads such as relays, self-interrupting bells or buzzers, or moving-coil speakers are used, clamping diodes must be connected as shown in Figure 11, to damp inductive back-EMFs and thus protect the VMOS device against damage.


## SOME DIGITAL DESIGNS

Figures 12 to 15 show a few simple but useful digital applications of the VN66AF. The water- or touch-activated power switch of Figure 12 could not be simpler: when the touch contacts and water probes are open, zero volts are on the gate of


the VN66AF, so the device passes zero current. When a resistance (zero to 10s of megohms) is placed across the contacts (by contact with skin resistance) or probes (by water contact), a substantial gate voltage is developed by potential divider action and the VN66AF passes a high drain current, thus activating the bell, buzzer, or relay.

In the manually activated delayed-turn-off circuit of Figure 13, C1 charges rapidly via R1 when push-button switch PB1 is closed, and discharges slowly via R2 when PB1 is open. The load thus activates as soon as PB1 is closed, but does not deactivate until some 10s of seconds after PB1 is released.

In the simple relay-output timer circuit of Figure 14, the VMOS device is driven by the output of a manually triggered monostable or one-shot multivibrator designed around two gates of a 4001B CMOS IC; the relay turns on as soon as PB1 is closed, and then turns off auto-

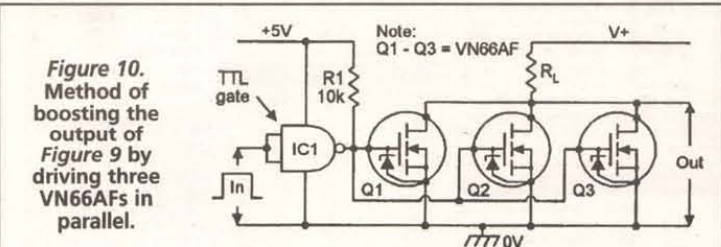

**Figure 10.** Method of  
boosting the  
output of  
Figure 9 by  
driving three  
VN66AFs in  
parallel.

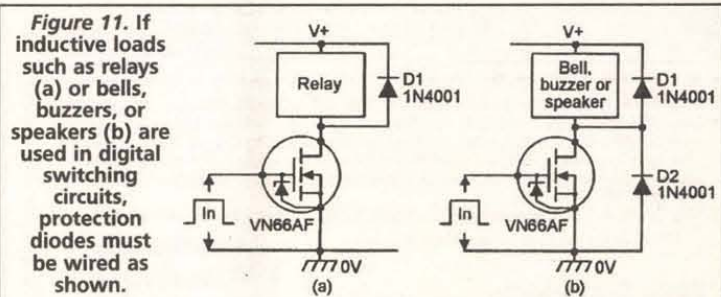

**Figure 11.** If  
inductive loads  
such as relays  
(a) or bells,  
buzzers, or  
speakers (b) are  
used in digital  
switching  
circuits, protection  
diodes must  
be wired as  
shown.

# FET

## HOT NEW PRODUCTS!!!



Phone Manager - Reverse Caller ID. Now you can keep track of outgoing numbers. Records length, time and date of call. Keep track of the children, the wife, or the phone company. Easy hookup via phone jack.

**New low price \$79.95**

Phone and Internet Voice Changer - This device is new to the market and provides realistic sounding voices. It allows you to interface directly to your phone jack, or computer via patch cord and mic.

**Intro price \$129.95**



Order directly from our website at [www.electronickits.com](http://www.electronickits.com)  
We also have over 200 Electronic Plans, Kits and Spy Products  
Carl's Electronics Inc. [sales@electronickits.com](mailto:sales@electronickits.com)

Write in 135 on Reader Service Card.

# SAME DAY PROTOS


Modem Gerber files before 9 AM EST.

We ship the boards same day.

Multilayers NEXT DAY.
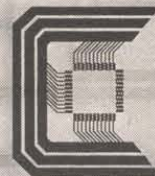
## Service:

- Instant Quotes
- Routing / Scored Panels
- Single / Double / Multi-Layers
- Blind and Buried Vias
- SMOBC and LPI
- Electrical Testing
- Thru Hole or SMT
- Carbon Ink / Peelable Mask
- Nickel and Gold Plating
- UL Approved



**CHICAGO CIRCUITS CORPORATION**

Manufacturer of Printed Circuit Boards

2685 UNITED LANE

ELK GROVE VILLAGE, IL 60007

E-MAIL: [sales@chicagocircuits.com](mailto:sales@chicagocircuits.com)

TEL: (847) 238-1623 • FAX: (847) 238-9160

MODEM: (847) 238-1728

Write in 140 on Reader Service Card.

Nuts & Volts Magazine/AUGUST 2000 73



### COLLIMATING LENS

This economical collimating lens assembly consists of a black anodized aluminum barrel that acts as a heat sink, and a glass lens with a focal point of 7.5mm. Designed to fit standard 9mm laser diodes. Simply place diode in the lens assembly, adjust beam to desired focus, then set with adhesive.

STOCK#	1-9	10-24	25+
LSLENS Lens Assembly	24.99	23.74	21.37

### DIODE/TRANSISTOR TESTER KIT

This dynamic tester allows checking of transistors & diodes in circuit. Identifies NPN or PNP transistors. Checks all types, small or large power. Identifies anode or cathode of diodes.

STOCK#	1-9	10-24	25+
DT100K	24.99	23.74	21.37

### ANTI-STATIC FOAM CLEANER

A thick, foaming cleaner for use in static sensitive applications. Safe for plastics and fiberglass. Use on computer cases and all office equipment. Also cleans soft fabrics. 5 oz. aerosol can.

STOCK#	1-9	10-24	25+
S81102	1.99	1.89	1.70

### EPROMS

STOCK#	1-24	25-99	100+
2716	2.99	2.84	2.56
2732	4.49	4.27	3.84
2732A-20	5.49	5.22	4.70
2764-20	5.39	5.12	4.61
2764-25	4.49	4.27	3.84
2764A-20	3.49	3.32	2.99
2764A-25	2.99	2.84	2.56
2764-15	2.99	2.84	2.56
27256-15	4.79	4.55	4.10
27256-15	2.99	2.84	2.56
27512-25	3.09	2.94	2.65
27C512-25	2.99	2.84	2.56
27C010-15	2.79	2.65	2.39
27C020-15	3.49	3.32	2.99
27C040-12	5.49	5.22	4.70
27C080-12	10.99	10.44	9.40

### Popular I.C.'s

STOCK#	1-24	25-99	100+
7400	.39	.37	.33
74LS00	.19	.18	.16
4017	.29	.28	.25
7805T	.33	.31	.28
7812T	.33	.31	.28
LM317T	.49	.47	.42
LM386N-1	.33	.31	.28
NE555N	.24	.23	.21
LM741N	.24	.23	.21
NE5532N	.55	.52	.47
68HC705CBP	8.99	8.54	7.69
8749	17.99	17.09	15.38
62256LP-10	2.79	2.65	2.39
2816	2.79	2.65	2.39

### FM MICROPHONE KIT

Transmit your voice on any FM radio. Range up to 1000'. Case included.

STOCK#	1-9	10-24	25+
K30	15.99	15.19	13.67

### What Do We Have ?

- I.C.'s
- Oscillators
- Crystals
- Diodes
- Tools
- Laser Diodes
- Vises
- Resistors
- Capacitors
- Connectors
- Trim pots
- Kits
- Vises
- LED's
- Transistors
- And more!

### GADGETEER'S GOLDMINE

This exciting collection of electronic projects features experiments ranging from magnetic levitation and lasers to high-tech surveillance and digital communications.

STOCK#	1-9	10-24	25+
TB3360	24.99	23.74	21.37

• Order Line — (800) 824-3432 • International — (724) 495-1230 • Fax Orders — (724) 495-7882  
 • Technical Support — (724) 495-1231 • No Minimum Order — (Orders under \$20 subject to \$5 charge)  
 • UPS 3 day, Blue, Red, & Fed. Ex. Shipping Available (Call for charges) • PA Res. Add 7% Sales Tax  
 • Open Mon-Fri 9:00 AM - 5:00 PM (EST) • Corporate Accounts / Quantity Discounts Available • We accept M/C, VISA, Discover & American Express with no surcharge • Call for FREE Catalog (\$2.00 Outside U.S.)  
 • We Carry A Complete Line Of Electronic Components • Email - [unielec@aol.com](mailto:unielec@aol.com)  
 Visit us on the web! [www.unicornelectronics.com](http://www.unicornelectronics.com)

**Unicorn Electronics**  
 1142 State Route 18  
 Aliquippa, PA 15001

**FREE SHIPPING!!** on pre-paid orders

Write in 137 on Reader Service Card.

## Serial in, graphics out. Almost too easy.


These serial displays take RS-232 at 2400 or 9600 baud and produce stunning text and graphics on a supertwist LCD screen. See our complete line at [www.seetron.com](http://www.seetron.com). All models are in stock for immediate delivery.

### G12032 120x32-pixel LCD

SGX-120L **\$99.00**  
 Same size as 2x16 text LCD  
 Editable font(s) in 4 sizes  
 Up to 6 screens in EEPROM  
 Easy terminal protocol



(3.2 x 1.4 in.)

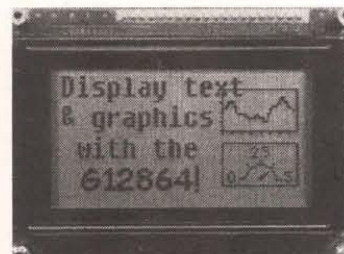


(3.7 x 2.8 in.)

### G12864 128x64-pixel LCD


BOX-128L-1 **\$199.00**  
 Large, sharp LCD  
 Editable font(s)  
 Up to 14 screens in flash  
 Separate text, graphics layers  
 DB9 connector built in  
 AC adapter jack built in  
 Easy terminal protocol

**www.seetron.com**


Scott Edwards Electronics, Inc. ph 520-459-4802 fx 520-459-0623 [nrv@seetron.com](mailto:nrv@seetron.com)

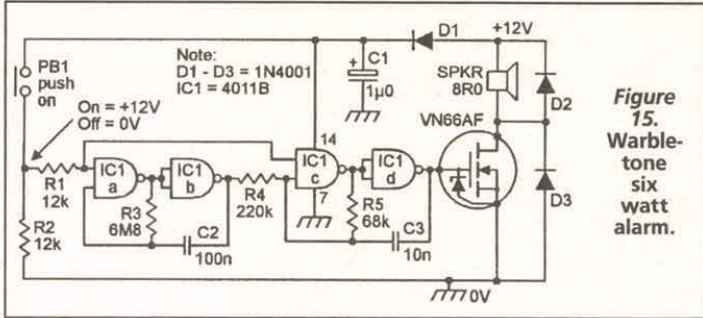


**Figure 15.**  
Warble-tone six watt alarm.

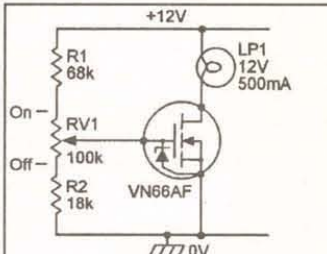

**Figure 16.** Simple DC lamp dimmer.

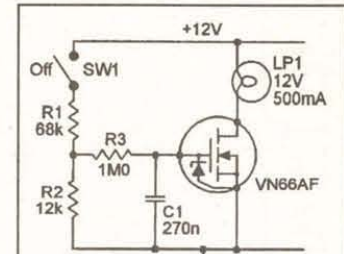

**Figure 17.** Soft-start lamp switch.

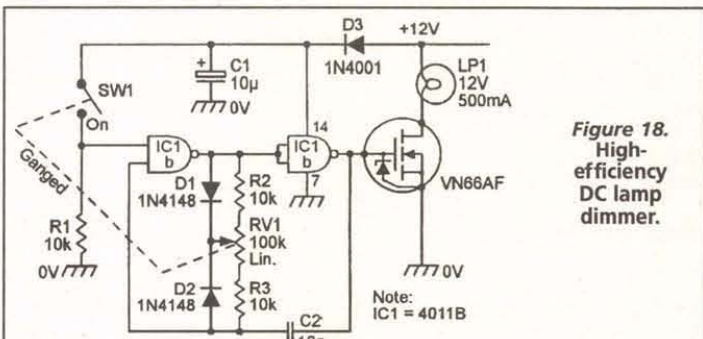

**Figure 18.**  
High-efficiency DC lamp dimmer.

matically again some pre-set 'delay time' later. The delay is variable from a few seconds to a few minutes via RV1.


Finally, Figure 15 shows the practical circuit of an inexpensive but very impressive alarm-call generator that produces a 'dee-dah' sound like that of a British police car siren. The alarm can be turned on by closing PB1 or by feeding a 'high' voltage to the R1-R2 junction. The circuit uses an 8R0 speaker and generates roughly six watts of output power.

### DC LAMP CONTROLLERS

Figures 16 to 18 show three simple but useful DC lamp controller circuits that can be used to control the brilliance of any 12V lamp with a power rating of up to six watts. A VMOS power FET can, for many purposes, be regarded as a voltage controlled constant-current generator; thus, in Figure 16, the VMOS drain current (and thus the lamp brightness) is directly controlled by the variable voltage of RV1's slider. The circuit thus functions as a manual lamp dimmer.

The Figure 17 circuit is a simple modification of the above design,
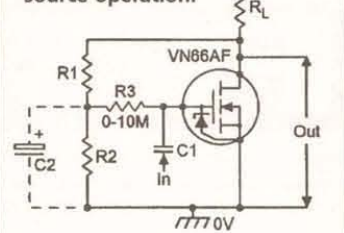
### Figure 19. Biasing technique for linear common source operation.



the action being such that the lamp turns on slowly when the switch is closed as C1 charges up via R3, and turns off slowly when the switch is opened as C1 discharges via R3.

The Figure 18 circuit is an efficient 'digital' lamp dimmer which controls the lamp brilliance without causing significant power loss across the VMOS device. The two 4011B CMOS gates form an astable multi-vibrator with a mark/space ratio that is fully variable from 10:1 to 1:10 via





RV1; its output is fed to the VN66AF gate, and enables the mean lamp brightness to be varied from virtually fully-off to fully-on. In this circuit, the VMOS device is alternately switched fully on and fully off, so power losses are negligible.

## LINEAR CIRCUITS

VMOS power FETs can, when suitably biased, easily be used in either the common source or common drain (voltage follower) linear modes. The voltage gain in the common source mode is equal to the product of  $R_L$  and the device's  $g_m$  or forward transconductance. In the case of the VN66AF, this gives a voltage gain of 0.25 per ohm of  $R_L$  value, i.e., a gain of x4 with a 16R load, or x25 with a 100R load. The voltage gain in the common drain mode is slightly less than unity.


A VMOS power FET can be biased into the linear common source mode by using the standard enhancement-mode MOSFET biasing technique shown in Figure 19, in which the R1-R2 potential divider is wired in the drain-to-gate negative feedback loop and sets the quiescent drain voltage at roughly half-supply value, so that maximal signal level swings can be accommodated before clipping occurs.

When — in the Figure 19 circuit — R3 has a value of zero ohms, the circuit exhibits an input impedance that, because of the AC negative feedback effects, is roughly equal to the parallel values of R1 and R2 divided by the circuit's voltage gain ( $R_L \times g_m$ ). If R3 has a finite value, the input impedance is slightly less than the R3 value, unless AC feedback-decoupling capacitor C2 is fitted in place, in which case, the input impedance is slightly greater than the R3 value.

Figure 20 shows how to bias the VN66AF for common drain (voltage follower) operation. Potential divider R1-R2 sets the VMOS gate at a quiescent value slightly greater than half-supply voltage. When the R3 value is zero, the circuit input impedance is equal to the parallel values of R1 and R2. When the R3 value is finite, the input impedance equals the R3 value plus the parallel R1-R2 values. The input impedance can be raised to a value many times greater than R3 by adding the C2 'bootstrap' capacitor to the circuit.

Finally, Figure 21 shows a practical example of a VMOS linear application. The circuit is wired as a class-A power amplifier which, because of the excellent linearity of the VN66AF, gives remarkably little distortion for so simple a design. The VN66AF


**Figure 21.**  
Simple class-A  
audio power  
amplifier gives  
1% THD at 1W.

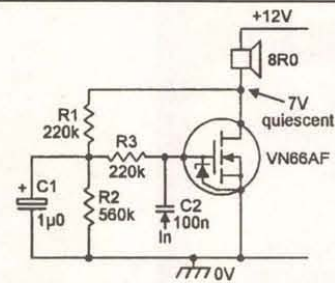

must be mounted on a good heatsink in this application. When

the design is used with a purely resistive 8R0 load, the amplifier

**Figure 20.**  
Biasing  
techniques for  
linear common  
drain (voltage  
follower)  
operation.

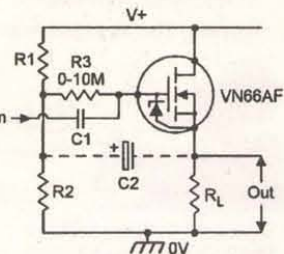

bandwidth extends up to 10MHz.  
NV

## AMAZING DEVICES

### Laser Window Bounce Listening System

Powerful listening system, yet simple in operation. You shine a LASER at a window and intercept the reflected beam with our ultra-sensitive filtered OPTICAL RECEIVER. Vibrations on the window from internal sounds and voices are now clearly heard. Range can be up to several hundred meters depending on the output power of the laser and optics used.

LLR30 Optical RECEIVER with voice filter.....	\$99.95	LLR3K Kit of Optical Receiver.....	\$69.95
LLR40 Higher performance with low noise preamp, basic optics and deluxe headset.....	\$199.95		
CWL10 10 mw ClassIIIB Invisible IR LASER for 500'.....	\$199.95	CWL1K Kit of LASER.....	\$149.95
LM650P5 5 mw ClassIIIA Visible Red Laser Module for up to 100'.....	\$19.95		
LM650P10 10 mw ClassIIIB Visible Red Laser Module for up to 200'.....	\$69.95		

### Gravity Motor

Electrical charge reactions produce the effect of "anti gravity." You build a model craft from simple parts and levitate it with our ion power source. Battery or 115vac operation. Great science or fascinating research project. Includes our gravity handbook.

GRA3 Plans/Book.....	\$20.00
GRA3K Power Source Kit.....	\$99.95
GRA30 Assembled Above.....	\$149.95

### TAKE CONTROL Using Electronic Hypnosis

Electronic circuitry induces hypnotic as well as ALPHA relaxed mind states. Place subjects under your control

HYP2 Plans.....	\$10.00
HYP2K Kit/Plans.....	\$49.95
HYP20 Ready to Use.....	\$69.95
MIND2 Plans for Mind Control.....	\$15.00
MIND2K Kit/Plans.....	\$49.95
MIND20 Ready to Use.....	\$79.95

### Therapeutic Pulsar

Complex Magnetic waves are claimed to produce many health benefits. Board level experimental device is sold for research purposes only.

THMAG10 Lab Assembled.....	\$24.95
----------------------------	---------

### Cybernetic Ear!

Provides that "extra edge" for many listening applications. Enhances 3 to 4x of normal.

CYBEREAR.....	\$19.95
---------------	---------

### Mini TESLA Coil

Lights up a 4' fluorescent tube-all without any contact! Yet only 3" tall!

MTC1K Kit/Plans.....	\$19.95
MTC10 Assembled.....	\$34.95

### Telephone Line Grabber

Listen to your premises. Break in to calls Control household appliances. Remote dial long distance calls from anywhere!

TELCON4 Plans.....	\$10.00
TELCON4K Kit/Plans.....	\$129.95
TELCON40 Ready to Use.....	\$169.95

### Tesla Coil

Produces 30" Sparks Create a spectacular display of nature own lightning. Many amazing experiments possible. See in action on our web site!

BTC4 Plans.....	\$20.00
BTC4K Kit.....	\$799.95
BTC40 Ready to Use.....	\$999.95
Smaller Version (8-10" Sparks)	
BTC3 Plans.....	\$15.00
BTC3K Kit.....	\$349.95
BTC30 Ready to Use.....	\$449.95

### Pain Field Pistol

Caution! Do not aim at people! Blast out rodents with high power ultrasonics. Handheld and battery operated with all controls. Rental units available.

PPP1 Plans.....	\$8.00
PPP1K Kit/Plans.....	\$49.95
PPP10 Ready to Use.....	\$79.95

### Amazing Gravitron

Remarkable true levitation without any tethering or external sources of energy. Winning science project. Includes self starter

GRV10 - Anti Gravity Top.....	\$39.95
GRV30 - Super Levitator.....	\$49.95

### Hover Board

28 pages of data related to the most revolutionary advance in transportation. Cutting edge R&D

HOVER Plans and Data.....	\$25.00
---------------------------	---------

### Transistorized TESLA Coil

Amazing and bizarre effects turn a normal light bulb into a spectacular plasma display! With adjustable frequency control. Safe 12vdc input

TCL5 Plans.....	\$8.00
TCL5K Kit/Plans.....	\$59.95
TCL50 Assembled and Tested.....	\$99.95

### Attention! High Voltage Modules

Battery powered for hovercraft, plasma guns, anti gravity, force fields, pyrotech

MINIMAX4 4KV.....	\$19.95
MINIMAX3 3KV.....	\$17.95
MINIMAX2 2KV.....	\$14.95

### Ion Ray Guns

Star Wars Technology Directs Energy Projects electric shocks without contact! Conduct many weird and bizarre experiments. Handheld battery operated and easy to operate.

IOG7/9 Plans.....	\$10.00
IOG7K Kit/Plans.....	\$99.95
IOG70 Assembled/Testing.....	\$149.95
Higher Powered Device	
IOG9K Kit/Plans.....	\$129.95
IOG90 Assembled/Testing.....	\$199.95

### Semi-Cond Burning Lasers

10mw to 2 Watts of continuous output! Use for directed beam of heat. Illumination source for night vision, laser window bounce IR driver for ultra-bright green lasers.

CWL5K Kit/Plans minus diode.....	\$199.95
CWL50 Assembled minus diode.....	\$299.95
LD34 CW 3/4 W 980nm diode.....	\$249.95

### Nightstar Night Viewer

Sees in total darkness

- 35000x Light Gain
- Over 100 yds Recognition
- Built in IR Illuminator
- 20 degree Field of View
- 20 Hours Battery Life
- Spectral Response 810-840 nm.

NSTAR10 - Ready to Use.....	\$239.95
-----------------------------	----------

### Jacobs Ladder

Pyrotechnical traveling fiery plasma expands over 3" before evaporating into space. Solid state circuitry with adjustable arc control. 115/230 volt operation. Uses safe high frequency energy.

JACK1 Plans.....	\$8.00
JACK1K Supply, Mtg Blks, Ladders.....	\$149.95
JACK10 Ready to Use.....	\$249.95

### 3 Mi FM Voice Transmitter

Crystal clear performance. Many applications. Easy to assemble

FMV1K Parts and plans.....	\$39.95
----------------------------	---------

See Our "Action" Web Site at  
[www.amazing1.com](http://www.amazing1.com)

Experiment with and Construct Lasers, Phasers, Hypnosis, Mind Control, TESLA COILS, Time Travel, Rail Guns, Magnetic Cannons, Coil and Sleeve Guns, Super High Gravity Pulses, Explode Wires and Water, Antigravity, Levitation, Mass Warping, Magnetic Can Crushing, Plasma Propulsion, High Energy Radio Frequency Guns (Herf), EMP, Lattice Snapping, Force Fields, Ion Ray Guns and all Types of Electrical Pyrotechnics, Plasma and Neon Displays, Sound Blasters, Ultrasonics, Super Hearing, Long Range Transmitters, Jammers, Personal and Property Protection, Surveillance Plus More!!

### Ultra Bright Green Laser visible over a mile!!

30 to 50x brighter than the red pointers. Shirt pocket sized pen .55" x 6.3" Full 5mw. Operates for hours from two "AAA" batteries. Call for pricing as we will not be undersold!!!!!!

### 6 Easy FM Xmtr Projects!

- 1 Super Sensitive Ultra Clear 1 Mile+ Voice Transmitter.
- 2 1 Mile+ Telephone Transmitter.
- 3 Line Powered Phone Transmitter Never Needs Batteries!!
- 4 Tracking/Homing Beacon Beeping Transmitter
- 5 Video/Audio Retrocaster 1 Mi.
- 6 TV/FM Radio Disrupter. Neat Prank! Discretion Required

Includes Hints Using Wireless Devices

COMBOX Plans Above 6 Projects.....	\$49.95
COMBOP Plans Above 6 Projects.....	\$10.00

### Shock Force Field Vehicle Object Electrifier

Hand shock balls, wands. Mini circuit is easily hidden. Great payoff for those wise guys.

SHK1K Kit/plan.....	\$19.95
---------------------	---------

### Mind&Brain Controllers

Incredible device Turbo charges memory. Boost mental powers, Controls stress, Speeds up healing processes and Uncover hidden potentials. High quality unit with many features.

BWPLUS-APOLLO Ready to use.....	\$189.95
BWII- EINSTEIN Lower cost unit.....	\$129.95

### Burning Cutting Lasers

Current and Future Weapons Systems

We Stock Parts!

LC3 Plans Poor Mans CO <sub>2</sub> System.....	\$15.00
LC7 Plans Lab CO <sub>2</sub> System 30W+.....	\$20.00
LAGUN2 Plans Nd:Yag, Ruby 6Kw.....	\$20.00

All Three Plans for only.....\$25.00!!

### PLASMA FIRE SABER

Patented Moving Light Concept Defies all Logic as it Appears to Evaporate into Space!! Duplicate the STAR WARS effect

Replaceable Blades, Override Switch Interactive Sound Module Available on Request

SAB15K - Kit 15" Display.....	\$29.95+\$5.00 s&h
SAB24K - Kit 24" Display.....	\$59.95+\$5.00 s&h
SAB36K -Kit 36" Display.....	\$129.95+\$15.00 s&h


Specify Color:  
photon blue, starfire red  
phaser green, neon red

# FET

Information Unlimited PO Box 716 Amherst N.H. U.S.A. 03031  
1 800 221 1705 Orders/Catalogs Only! Fax 1 603 672 5406 Information 1 603 673 4730 Free Catalog on Request  
Pay by MC,VISA,Cash, Check, MO, COD. Add \$5.00 S&H plus \$5.00 if COD. Overseas Contact for Proforma


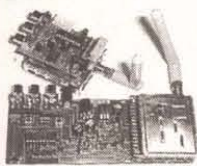
## 2.4 GHz Wireless Transmitter & Receiver



**\$89-\$159**  
per pair

- Microwave 2.3 GHz to 2.5 GHz
- **NEW!!** 8 Channel Version
- Audio, Video (NTSC + PAL)
- Frequency Development Kit Available

### MATCO

OEM Sales 630-350-0299  
General Sales 847-605-1020  
www.mat-co.com

## MFM COMMUNICATIONS

### NOW IN STOCK —

- Magnetic Strip Reader/Writers
- Mobile Mag-Strip Readers
- 7816 Programmers


### PLUS

*A wide range of  
cellular accessories*

### 24 HOUR DELIVERY

Tel/Fax: 011441342312403  
http://members.aol.com/  
mfmcom123/index.htm

## SBC2000-074

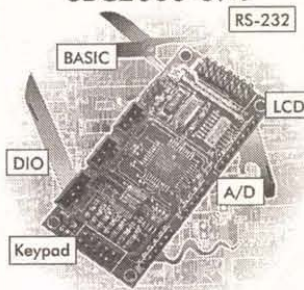

Versatility starting at \$64 each.

Voice: 303.422.8088 Fax: 303.422.9800

www.sbc2000.com

Vesta Technology, Inc.

**SWITCHES — LEDs — MOTORS —  
SPEAKERS — POWER SUPPLIES —  
CONVERTERS — CHEMICALS — WIRE —  
OTHER ELECTRONIC PARTS — All types —  
All sizes — Commercial to Spec Grade**

Full Size Toggle Switch, 1/2" Dia., as low as	36¢
Mini Toggle Switch, 1/4" Dia., as low as	30¢
Sub-Mini Toggle Switch, 1/8" Dia., as low as	32¢
Rocker Switches, as low as	20¢
Slide Switches, as low as	20¢
Push Button Switch, 1/4" Dia., as low as	29¢
Surplus Small and Mini Motors, as low as	50¢
Mini Speakers, as low as	\$1.00
3mm LED — Red, Green, Yellow, as low as	15¢
5mm LED — Red, Green, Yellow, as low as	15¢

Let us quote on your specific LED needs

AC-DC Converters, 7 outputs, 1000 mA.....\$4.00

Chemicals, see catalog

WIRE: Hook-Up, Lead, Speaker & Telephone

**CALL OR FAX FOR QUOTES  
OR CATALOG**

### DEMARE ELECTRONICS

P.O. Box 7215, Algonquin, IL 60102  
Toll Free 877-655-6433  
Fax 847-854-4434

## Got Dial Tone?

**Telecom Hardware/Software Developers**  
STOP using your phone lines to test and demonstrate  
your telecom devices. Our affordable telephone line  
simulators offer authentic USA dial tone, busy signals  
and ringing. Supports high speed analog modems too!



**RING-IT! TELCO SIMULATOR**  
• Caller-ID  
• LED display  
• Audio Output Jack  
• Real 20Hz Ring  
• \$325 (\$199.95 kit avail)

### PARTY-LINE TELCO SIMULATOR

- Six Extensions
- Caller-ID
- Distinctive Ringing
- CPC Disconnect
- \$425 (\$199.95 kit avail)



### Digital Products

**COMPANY**

134 Windstar Circle

Folsom, CA 95630 USA

Tel: 916-985-7219

Fax: 916-985-8460

http://www.digitalproductsco.com

## PRINT to VIDEO!

Tiny BOB-II module superimposes up to  
308 characters on NTSC/PAL video or  
generates video automatically. Fast  
2.4-19.2kbps RS-232 serial interface.  
Simple to control; like a printer. Many  
powerful applications:

- Home Automation - MATV
- Video Inspection & Testing
- Surveillance - CCTV - ATV
- Remotely Piloted Vehicles
- Gaming - Racing - Sports
- Process/Experiment Monitor
- Robotics - Electronic Signs

BOB-II-NTSC only \$79.95



### DECADE ENGINEERING

5504 ValView Dr. SE, Turner, OR 97382

Tel: 503.743.3194 - Fax: 503.743.2095

Information & Ordering: www.decadenet.com

## GetToner.com

### Ink Jets - Toners - Fax Ribbons

Guaranteed Lowest Prices on  
Compatibles or We'll Match the  
Price and Give you 10% Additional  
Compatibles for:

- HP • Lexmark
- Canon • Brother
- Epson • Apple
- and MORE

FREE SHIPPING • NO MINIMUM

www.GetToner.com

1-800-933-8211

## Press-n-Peel Transfer Film

### PC Boards in Minutes

- 8.5" x 11" Shts.
- \* Or Photocopy
- \*\* Use standard household iron

1. LaserPrint\*
2. Press On\*\*
3. Peel Off
4. Etch



Use Standard Copper Clad Board  
20 Shts \$30/ 40 Shts \$50/ 100 Shts \$100  
Visa/MC/PO/CK/MO \$4 S&H/Foreign Add \$7

### Techniks Inc.

P.O. Box 463, Ringoes NJ 08551

ph. 908.788.8249 fax 908.788.8837

www.techniks.com

Visit Our E-Store On-Line!

## BATTERY — YUASA



Sealed Lead-Acid/Gel-Cell  
12V: 7AH \$19, 2.3/4AH \$16  
18AH \$39, 1.2AH \$13  
6V: 4AH \$9, 10AH \$13

Quantity Discounts Available  
Call for other models

### Aventrade


4518 Temple City Blvd., Temple City, CA 91780

Tel. 626-286-0118 Fax 626-287-9618

E-Mail: sales@aventrade.com

www.aventrade.com
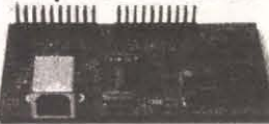
## New! ActiveWire™USB Simple USB Interface



- Internet Browser Script-able
- 24 MHz CPU core with USB
- Firmware downloadable via USB
- 16 bit parallel I/O
- Expandable add-on boards
- New firmware and scripts available from website

**\$59** plus shipping

ActiveWire, Inc.

www.activewireinc.com

ph(650) 493-8700 fx(650) 493-2200

## QUALITY KITS

### #1 Source for Electronic Kits

Great selection of Hi-Fi AUDIO Kits,  
PSUs, Transmitters, Oscilloscopes,  
PIC Programmers, and much more.

Toll Free Order Line:

**1-888-464-5487**

Secure On-Line Ordering

www.qkits.com

Call 613-544-6333 for free catalog

North American Kit Distributor

49 McMichael St., Kingston, ON

K7M 1M8, CANADA

## Convert RS-232 to RS-485 or TTL/CMOS for Only \$49.00

Communicate up to  
4,000 feet, at up to  
1 MEGA-BPS, full  
or half duplex, up to  
32 units on one serial  
link, with 31 jumper  
options for flexible  
configuration, LED  
indicators.



### COMMUNICATIONS CONVERTER

- FULL SCHEMATIC AND DOCUMENTATION
- FULL FAMILY OF MODULAR DESIGNS
- RS-485/RS-422 REMOTE I/O MODULE KITS
- NETWORK SOFTWARE AND SOURCE CODE
- AUTOMATIC OR RTS UNITS AVAILABLE
- RJ-11/12 CONNECTORS OR TERMINAL STRIP
- TURN YOUR PC INTO A DISTRIBUTED DATA ACQUISITION AND CONTROL SYSTEM

### R.E. SMITH

(513) 874-4796

4311 TYLERSVILLE RD. ■ HAMILTON, OHIO 45011

www.rs485.com

## Fast / Economical / Easy CIRCUIT BOARDS

As-Low-As **\$8000** Per Lot



- Next Day Delivery
- 2-Sided, plated thru
- Order over the Internet

For Complete Details and  
Instructions Log on:

www.pcbexpress.com



13626 South Freeman Rd., Mulino, OR 97042  
(503) 829-9108 Fax (503) 829-5482

## ESP CONNECTOR FOR HIGH-TECH GARMENTS

Electrical  
Contacts for  
Clothing

ESP:  
Electrical  
Snap Patch  
Connector easily  
sews into clothing

Audio applications, sensors,  
display panels or keypads

Molded cable assembly with  
3.5mm phono plug snaps  
into ESP

Gold plated for reliability

3" x 1.5" patch

EVALUATION KIT AVAILABLE  
www.autotime.com 503-452-1455


## GLOBALTECH DISTRIBUTORS

The Ultimate Electronic Saving Store

Call Today! --- 1-(800)582-5116

	25ps.	100ps.	500ps.
PIC12C508	1.30	1.20	1.15
PIC16C54	1.40	1.35	1.30
PIC16C56	1.65	1.50	1.45
PIC16C621	2.00	1.95	1.85
PIC16C622	2.25	2.15	1.95
68HC705C8A	5.50	5.00	4.85
ATF89C52	4.00	3.50	3.15
82S131	1.50	1.30	1.15
Gall16V8b	1.00	.95	.75
4mhz Res.	.45	.40	.32
20mhz Crystal	.50	.45	.40
CATV Remote	4.25	3.75	3.25
Universal Remote Controls	-----	4.50	

Order@globaltechdistributors.com

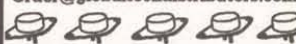

BEST MICROPROCESSOR STOCK DISTRIBUTOR WORLD WIDE.

## SURVEILLANCE

### UHF TRANSMITTERS

- ROOM Battery & Mains • TELEPHONE
- RECEIVERS • TELEPHONE RECORDER
- VEHICLE TRACKING SYSTEM

## DISPLAYS ON WEB SITE PRICE SURVEILLANCE

P.O. BOX 6856, TALLAGH,  
DUBLIN 24, IRELAND

Tel: +353-1-451-7653

Fax: +353-1-451-7706

E-Mail: crystal@pricesurveillance.com

www.PRICESURVEILLANCE.com



## PCB EXPRESS, INC.

### \*PROTOTYPE TO PRODUCTION\*

S/SIDED: 5-days, 10 Pcs.	\$275.00
D/SIDED: 5-days, 5 Pcs.	\$300.00
D/SIDED: 5-days, 10 Pcs.	\$350.00
4-LAYERS: 5-days, 5 Pcs.	\$750.00
4-LAYERS: 7-days, 10 Pcs.	\$850.00
6-LAYERS: 5-days, 5 Pcs.	\$950.00
6-LAYERS: 7-days, 10 Pcs.	\$1,175.00
(Up to 30 sq. inch each, includes Tooling)	

### \*SERVICES\* — UL Approved

SMOBC, LP1 mask & Legend  
Photoplotting, Electrical Testing  
Thru hole/SMT, Gold/Nickel Plating  
Routing and Scored Panel, Instant Quotes

PH: (888) 427-2920, Fax (847) 427-1949

E-Mail: cir1920@aol.com

**LOWEST COST & FAST DELIVERY**

## VIDEO PRODUCTS



CNL-100 \$49 BX-120-P \$59 SX-800 \$79

- 430 TV Lines Resolution
- 9-14 VDC Operation
- Infrared Sensitive
- SX-800 has Audio Output
- A-300 Camera Enclosure also available

### MATCO, INC.

Schaumburg, IL  
1-800-719-9605 • 1-847-619-0852 FAX  
E-Mail — info@mat-co.com  
Website — www.mat-co.com

## 10&14 Hour Telephone

### Recorders Starting at \$69



Times based on a 180 tape  
14 Hour \$89.95/S/H  
120 Tape included!

Automatically starts recording when the phone is picked up and stops when you hang up. Records both sides of the conversation!  
Printed catalog \$3 (free with order)

### Visit our Online Catalog

[www.mscelectronics.com](http://www.mscelectronics.com)

MSC Electronics  
PO BOX 461 Jessup, MD 20794  
(301) 497-1600  
FAX (301) 497-1925  
No Checks • US & Canada Only

## EPS

### EPROMS AS LOW AS 25¢

27C256	27C400	27C1024	87C51
27C512	27C4006	28F010	8751
27C32A	27C4006	28F020	8755
27C32	574000	28F040	MC68HC70
27C128	574200	8749H	5C8A
27C64	27C402	8748H	PIC16C56
2716	27C020	8741	PIC16C54
2708	27C210	8742	PIC16C62
27C512-90	27C010	8744	GAL16V8
			GAL22V10
			MEMORY
			D-RAMS
			SIMM

STATIC RAM PROCESSOR  
HM628128 8255  
62256 8254  
6264 80C31  
6116

• Many more parts in stock  
• All major brands  
• All guaranteed  
E-Mail: [eproms@aol.com](mailto:eproms@aol.com)

TEL: (818) 774-9444 • FAX: (818) 774-0822

**WE BUY EXCESS INVENTORY**



## FREE SAMPLE COPY! ANTIQUE RADIO CLASSIFIED

### Antique Radio's Leading Monthly Magazine

Articles — Classifieds — Ads for Parts & Services. Also: Ham Equip. — Books — Telegraph — 40's, 50's & 60's Radios — Early TV — Auction Reports & more...

1-Year: \$39.49 (\$57.95 by 1st Class)  
6-Month Trial — \$19.95. Foreign — Write.

A.R.C., P.O. Box 802-G23  
Carlisle, MA 01741

Call: 978-371-0512 — Fax: 978-371-7129  
Web: [www.antiqueradio.com](http://www.antiqueradio.com)

### SINGLE SIDED PCBs

**9¢**

\* 9¢ PER SQUIN, \$100 SET UP, SMOBC, ONE OUNCE COPPER, PC 75, 1/16", ONE SOLDER MASK AND ONE SILK SCREEN. PHOTO PLOT \$50.

### DOUBLE SIDED PCBs

**14¢**

\* 14¢ PER SQUIN, \$150 SET UP, PTH, ONE OUNCE COPPER, FR4 1/16", TWO SOLDER MASK AND ONE SILK SCREEN. PHOTO PLOT \$75.

### LOWEST PRICE IN THE INDUSTRY FOR PROTOTYPES DELIVERED IN 5 WORKING DAYS.

PLEASE VISIT OUR WEB SITE FOR MORE INFORMATION AND OTHER PRICE EXCEPTIONS [WWW.VANDVMACHY.COM](http://WWW.VANDVMACHY.COM)

\* THESE PRICES APPLY ONLY TO RECTANGULAR PCBs 3/4 WEEK DELIVERY

### V&V MACHY & EQUIP. INC.

V&V MACHY AND EQUIP. INC. (HOUSTON TX. OFFICE) PH. (281) 397 8101 FAX (281) 397 6220  
MARKETING TECH. S.A. (MEXICO PLANT) PH. 011 525 3613351, FAX 011 525 3615996

## PIC MICRO TOOLS

### PROGRAM PIC'S IN BASIC!

B2 compatible! Plus can be used within MPLAB IDE. Includes FREE Proto board! Pic n' Basic Pro Compiler \$129.00

ALLPIC Plus Programmer  
Program PIC - Scenix - Atmel  
Serial EEPROMs Only \$99.00

PIC & Scenix Prototyping Boards  
New design makes it easier to prototype PIC & Scenix micro than any other prototyping boards! Starting at \$9.95

New! Experimenter - Lab Board  
Several models available! Built in Graphics LCD, Servo, Button Matrix, EEPROM, Solderless Bread Boards. From Beginners to Professionals! PIC & Scenix! Kits Starting at \$49.95

VISA • MasterCard • American Express  
To Order Call 1-800-773-6698  
Send Money orders to: Worldwyde.Com, 33523 Eight Mile Rd #A3-261, Livonia, MI 48152  
Visit us online <http://www.worldwyde.com>

## ASSEMBLY & ENGINEERING

### Producible designs since 1970

Contract Engineering  
Embedded Microprocessors  
PCB Layout and Packaging Design  
Analog Including RF to 1 GHz  
Instrumentation  
A/D and D/A

Contract Assembly  
High-Speed Fujit Surface Mount  
Through hole  
Turn-key or Kit  
Run sizes one through thousands  
Test and burn-in available

Bilcocon Corp.  
800-736-5927  
425-353-2276  
[www.bilcocon.com](http://www.bilcocon.com)



Ph 650/367-8320  
Fx 650/365-5845  
VISA  
MC

3580 Haven Ave.  
Redwood City, CA 94063-4603

### STEREO MICROSCOPE

Model ST 251A  
10X and 30X  
4 in. Throat  
Top & Bottom light  
Dust cover  
Eyecups  
5 year warranty  
\$250.00



## CONTROL • MEASURE • INPUT


### MODEL 40—\$109

- RS-232 interface
- 28 lines digital I/O
- Eight analog inputs
- PWM output
- Three stepper ports


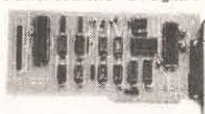
### MODEL 100—\$279

- 12-bit 100KHz A/D • Four analog outputs
- Three timer counters • 24 digital I/O



### PRAIRIE DIGITAL, INC.

920 SEVENTEENTH ST., INDUSTRIAL PARK  
PRAIRIE DU SAC, WI 53758  
TEL: (608) 643-8599 • FAX: (608) 643-6754

Specializing in  
hard-to-find, pre-owned, electronic  
parts, components and systems

- Monitors, 13"-21"
- Computer Systems
- Disk Drives
- CPU's
- PC Peripherals
- RF/Microwave
- Specialty Equipment
- Test Equipment
- Measurement Equipment
- Too many items to list

**Stock is continually changing.**  
Check our web site for current inventory and pricing.

[www.dmdsystems.com](http://www.dmdsystems.com)

DMD Systems Recovery, Inc.  
fax 602 365-8485 info@dmdsystems.com 602 305.8485

## CABLE CONVERTS

TV86/3	86/CH	TV86/3V/A
TRIVISON	550/3	\$37.95
VIEW MASTER	2600	
125 CHANNEL UNITS		
TRI 860/3	10 LOT	\$49.95
TRI 860/3V/A	10 LOT	\$59.95
V/MASTER	3800/3V/A	
FOSS WAREHOUSE DIS	289 SCHENCK ST	
N TONAWANDA NY	14120	
800-473-0506		
800-488-0525 FAX		
716-694-6400 716-693-4322 FAX		
E/M FOSS@BUFFNET.NET		
WEB PAGE: WWW.FOSSW.COM		
NO DISCRAMBERS ONLY CABLE CONVERTS		

## GPS Units from Communications Surplus

### Trimble SVEE Six-CM3

6 Chan Differential Module &  
Magnet Mt. Antenna \$49.95

Rockwell MicroTracker LP  
5 Chan NMEA Differential OEM  
Module \$59.95

Call 713-526-8000 Or  
1-877-878-8GPS Or Fax 713-522-8309  
Email @ [commsurplus@ev1.net](mailto:commsurplus@ev1.net)  
or [www.commsurplus.com](http://www.commsurplus.com)

## DEGREE ON A DISK!

### EM FORMULARY

500+ formulas, conversions, and tables. Electronics, science, math. Practical, educational, and easy to use. Internet Special \$19.95 + tax/shipping. Order online, more info and sample screen at our web site.

ELECTRO SCIENCE APPLICATIONS  
(562) 989-1190  
[www.esap.com](http://www.esap.com)

## SMARTCARD

DEVELOPMENT KIT  
INCLUDES: UNIVERSAL PROGRAMMER, POWER SUPPLY, DB9 CABLE  
DEVELOPMENT SOFTWARE, 4 BLANK BASIC SMARTCARDS.  
KIT \$200.00 + SHIPPING  
EXTRA CARDS \$20.00 EACH  
OR 8/\$100.00  
SOFTWARE INCLUDED.  
POSSIBLE APPLICATIONS INCLUDE:  
IDS, COMPUTER SECURITY, SECURE DATA, MEDICAL RECORDS, ETC.  
NOT FOR USE WITH DSS TV

Call TONY at  
WIZARD ENGINEERING  
1-419-385-3100



**Power Quality Inc.** 800-255-5545  
Fax: 520-344-8847

**Heavy Duty Surge Suppressor**  
Plug Strips, 6 outlet, circuit breaker,  
Case of 25 in individual boxes...\$50/case

**HP Power Supplies, HP6260B**  
current is 0-50A, .....\$100

**UPS, 250va to 3 kva, functional and**  
nonfunctional .....Please call

**Power Conditioners, Oneac, TLC,**  
Teal, Sola, various sizes .....Please call

**BMI, Dranetz, and RPM**  
Power Quality Monitors ..... Please call

[www.powerqualityinc.com](http://www.powerqualityinc.com)

**SURPLUS SALE**

**1,000,000 WALL TRANSFORMERS**




3VDC/100MA .... CX099 .... \$0.75  
6VDC/100MA .... CS039 .... \$1.45  
9VDC/100MA .... CR314 .... \$1.45  
12VDC/200MA .... CS033 .... \$0.99  
13.5VAC/400MA... CR574 .... \$1.29  
24VDC/500MA .... CR174 .... \$3.40

Min 1000/type -- Call for other types

**SURPLUS TRADERS**  
PO Box 276,  
Albany, VT 05440  
Tel: (01) 514-739-9328  
Fax: (01) 514-345-8303  
<http://www.73.com/w>

**FREE CATALOG!**

**NEW! SERIAL LED MODULE**



✓ Bright attractive highly visible display- super efficient  
✓ Compatible size, mounting with LCD 2x16 display  
✓ 4 digits (0.56" tall) plus decimal points  
✓ Customization available  
✓ Serial RS-232 and PC interface  
✓ 80mm wide x 36mm high (3.15" x 1.47")  
✓ Low power- less than an LCD display with backlight  
✓ Reasonably priced- \$29 in 100's \$43 each in singles  
✓ Order a few today for your next project

<http://www.trexon.com>  
email: [speff@trexon.com](mailto:speff@trexon.com)  
Trexon Inc. 905-271-4477 Fax: 905-271-9838

**MEMORY**

72-PIN SIMM

8x32 (32MB) EDO ..... \$82.50  
16x32 (64MB) EDO ..... \$132.00

SDRAM PC-100 DIM

4x64 (32MB) ..... \$39.00  
8x64 (64MB) ..... \$53.50  
16x64 (128MB) ..... \$126.00  
32x64 (256MB) ..... \$225.00

CACHE/VIDEO KITS UPGRADE

1MB Video for P.B. 486 ..... \$35.00  
1MB Video for P.B. Pentium ..... \$18.00  
128K Cache for P.B. 486 ..... \$18.00  
512K Cache for P.B. 486 ..... \$49.00  
256K Cache Module/Pentium ..... \$25.00

SPECIAL CONTROLLER

AT90S8515-4PC ..... \$7.00

We also stock EPROMs, CPU, UPGRADE KITS  
for other name brand computers and printers.

Visit our website for more details or order by  
calling directly to our toll free 1-800-586-4900

[www.lapazelectronics.com](http://www.lapazelectronics.com)

**La Paz Electronics International, Ltd.**  
PO Box 261095 San Diego, CA 92196  
Phone (858) 586-7610 Fax (858) 586-1482

## CUSTOM PLASTIC PARTS

• MODELS (WOOD AND RESIN), TO EVALUATE YOUR PARTS BEFORE YOU COMMIT TO MANUFACTURE A MOLD.  
• MOLD DESIGN AND BUILDING.



• PRODUCTION OF INJECTION MOLDED PARTS. NO ORDER TOO SMALL OR TOO BIG.  
• VERY COMPETITIVE ON HIGH LABOR PARTS.

We can also inject your parts on manual low pressure machines for very small runs or prototypes of parts up to 2 oz. At surprisingly low price.

USA Office: V&V Mach. And Equip. Inc.  
Tel. (281) 397-8101, Fax. (281) 397-6220.

Please send blue prints or samples to:  
Marketing Tech. S.A. Alamo 93, 4 Piso. Sta. Monica,  
Tlal. Edo. De Mexico 54040 Tel. 011 (525) 361-3351,  
Fax. 011 (525) 361-5996, ATTN: VICTOR M. MENDOZA.

PLEASE VISIT OUR WEBSITE  
[WWW.VANDVMACHY.COM](http://WWW.VANDVMACHY.COM)

**SECURETEK**

DIRECT FROM MANUFACTURER  
"WE WILL BEAT ANY COMPETITOR'S PRICE"

WORLD SMALLEST  
WIRELESS VIDEO CAMERA  
(BLACK & WHITE OR COLOR)  
TRANSMITS VIDEO UP TO 1000FT.

WE ALSO CARRY:  
• COVERT VIDEO CAMERAS  
• COUNTER-SURVEILLANCE PRODUCTS  
• CUSTOM MADE VIDEO SYSTEMS  
• IN HOUSE ENGINEERING DEPT.

DISTRIBUTOR PROGRAM AVAILABLE

CALL FOR CATALOG:  
**SECURETEK**  
7152 S.W. 47TH ST.  
MIAMI, FL 33155  
TEL. 305.667.4345  
FAX. 305.667.1744  
[www.securetek.net](http://www.securetek.net)

## Build Your Electronics Library At A Price You Can Afford!

Check out the Great Deals at the Nuts & Volts Bookstore!!

(See ad page 4.)

As a paid subscriber, you'll get 10% off the listed price!!

## Smart Cards in BASIC

**PROGRAM SMART CARDS IN BASIC!**  
Complete system! Program your own smart card applications in easy to use BASIC!  
Smart Card Tool Kit \$79.00



Security Systems, Time Cards, Emulation, Access Control for Home, Office, Auto, Computers, Robotics Programming, Interface with any application!

Tool Kit comes complete with:

- CyberMouse SmartCard Reader/Writer
- Developer Software Package
- Documentation on CD-ROM
- Technical manual in printed form
- 3 Blank Smart Cards Ready to Program

VISA • MasterCard • American Express  
To Order Call 1-800-773-6698  
Send Money orders to: Worldwyde.Com,  
33523 Eight Mile Rd #A3-261, Livonia, MI 48152  
Visit us online <http://www.worldwyde.com>

# FCC EXAMINATION CREDIT ...

The FCC Report & Order effective April 15, 2000, that revised and simplified the Amateur Radio license classes and examination requirements also grants Examination Credit to various licensees for examinations that they previously passed. This table summarizes the Examination Credit granted under the new FCC rules, and tells which additional Examinations must be passed in order to upgrade to a higher class of license. Please be sure to read definition of "Current" and "Expired" licenses in the notes included here.

Specific Group Amateurs (Current License Status)	Elements Needed to Pass for Upgrade				
	Receives Examination Credit for: Element 1	Upgrade to Technician	Upgrade to Technician w/ code credit Element 2	Upgrade to General Class Elements 2 & 3	Upgrade to Extra Class Elements 2, 3 & 4
Current <sup>1</sup> or expired <sup>2</sup> Novice Class operator					
Current FCC-issued Commercial Elements Radiotelegraph operator	Element 1		Element 2	Elements 2 & 3	Elements 2, 3 & 4
Current Technician Class operator licensed after 2/14/91	Element 2		Element 1	Elements 1 & 3	Elements 1, 3 & 4
Current Technician Class operator licensed between 3/22/87 and 2/14/91	Elements 1 & 2			Element 3	Elements 3 & 4
Expired Technician Class operator licensed after 2/14/91	Element 1		Element 2	Elements 2 & 3	Elements 2, 3 & 4
Current Technician-Plus operator licensed after 2/14/91	Elements 1 & 2			Element 3	Elements 3 & 4
Current Technician Class operator licensed on or before 3/21/87	Elements 1, 2 & 3			Now qualifies as a General Class operator	Element 4
Expired Technician Class operator licensed on or before 3/21/97	Elements 1 & 3			Element 2	Elements 2 & 4
Current General or Advanced Class operator	Elements 1, 2 & 3				Element 4
Expired Technician-Plus, General, Advanced, or Extra Class operator	No Credit	Element 2	Elements 1 & 2	Elements 1, 2 & 3	Elements 1, 2, 3 & 4

### NOTES:

1. A "Current" license is one that is not expired, or is within the FCC's two-year grace period for renewal.
2. An "Expired" license is one that is expired for two or more years and is beyond the FCC grace period for renewal.

An applicant must provide reasonable evidence that he/she was licensed as required to obtain the exam credit. This proof can be a copy of your old license, a photocopy of an old Callbook page, or any other evidence of your prior license status. The W5YI-VEC can assist applicants who wish to research old licensing information. There is a small charge for this service. Call 817-860-3800 if you need help.

Source: W5YI-VEC



# TECH FORUM

This is a READER TO READER Column. All questions AND answers will be provided by *Nuts & Volts* readers and are intended to promote the exchange of ideas and provide assistance for solving problems of a technical nature. All questions submitted are subject to editing and will be published on a space available basis if deemed suitable to the publisher. All answers are submitted by readers and **NO GUARANTEES WHATSOEVER** are made by the publisher. The implementation of any answer printed in this column may require varying degrees of technical experience and should only be attempted by qualified individuals. Always use common sense and good judgement!

## QUESTIONS

Send all material to **Nuts & Volts Magazine**, 430 Princeland Court, Corona, CA 92679, OR fax to (909) 371-3052, OR E-Mail to [forum@nutsvolts.com](mailto:forum@nutsvolts.com)

Is there a way to check components in small power supplier [electronic typewriters] without removing components? Seems like theory discussion doesn't cover troubleshooting.

**#8001** Richard Budrow  
Olympia, WA

Does anyone have a full service (POP3/SMTP) bios tweak for the Mail Station?

**#8002** John Williams  
Hayward, CA

In answer to #10011, Jan. '00 regarding a schematic/SW to allow the PC via its parallel port to connect to a GPIB device. The reply cited "plotgpi.zip" a shareware product.

I have looked many places in a lot of shareware sites (shareware.com, tucows.com, etc.), and have come up empty.

Can someone please come up with a more definite location for this software?

**#8003** John Hudak  
via Internet

I work with AVR microcontrollers which are being clocked with an external crystal or oscillator, typically at 4 MHz. I would like to be able to change the clock rate (slower) via an external circuit triggered either by an outside event or by the micro itself.

Ideally, the circuit to do this would be driven by a single clock source and send out as clean a pulse during switching as the source itself (i.e., no chopped pulses or shortened periods).

Dropping a few clocks during switching to keep things clean would not be problematic. I am remembering the turbo switches on PCs not so long ago, but I hope to find a simple (low-component count) solution.

There are several applications I have in mind for this, one of which is to enable testing of this fast micro with a PC-based logic analyzer.

**#8004** Kurt Stevens  
via Internet

I have an old DOS graphics program that uses printer control codes to control an NEC PC-8027 printer. This application was written for a DEC PDP-11 (RSX-11M), which runs

from DOS via a Strobe Data Osprey emulation board. The application was written by Minato (Japanese tester company), which has since been purchased by Ando. The printer is no longer supported by NEC and there's no new source code available for the program. Of course, it's a program that I still need to use. Is there a hardware or software means of translating the printer control codes from this printer to a more modern one? I thought of using an EPROM decoder or a TSR patch.

**#8005** Patrick McComas  
[pkm@cypress.com](mailto:pkm@cypress.com)

I have several 640 x 480 graphical LCD displays and I can't seem to find any controller ICs or chip sets to allow me to control them.

I'd like to be able to send serial data to it and have it displayed for an engine monitor.

I would rather use something that already exists rather than take all the time to design, build, and debug a one-of-a-kind controller.

**#8006** Norm Doty  
Hollywood, FL

I am desperately looking for a way to control a residential bath fan/light unit. It is now wired on one switch. I am seeking a way to control them independently while using the existing wiring which is two wires (only one load wire).

I have seen such a unit for paddle fans, but I can't locate one for exhaust fans. None of the major electrical manufacturers I contacted were any help.

**#8007** via Internet

Does anyone have the pinout for a miniature camera made by TVX International? The model is TVX04-IMAGER PCA. It looks like an 11-pin push-on type of connector. The unit was sold by Goldmine Electronics.

**#8008** Roy E. Kneale  
via Internet

LM3909 is an LED blinker chip, it is being discontinued. Jameco sells them for about \$5.00 a piece now. Does anyone know of any replacement LED blinker chip that sells for a reasonable price? RadioShack no longer carries LM3909. (I do not

have a computer.)

**#8009** Sumeth Kongsuwan  
Belvidere, IL

I would like to adapt an LP4081 Ricoh printer with a 50-pin connector — similar to Apple — to my PC with a 25-pin connector. Is there a way to do this?

Spec. info parallel (Centronics) and serial RS 232C adapter, comes installed in printer.

**#80010** Thomas Bristol

I recently acquired a surplus HP 7046B plotter that still works well. However, it only responds to analog voltage inputs. I would like to connect it to a PC printer port through a suitable interface device that is also compatible with HPGL software.

Does such a device exist or how would I go about building one?

**#80011** Bill Hawes  
Kirkland, WA

I have a problem with a small circuit in a Shop Light. It is made by Lifelite, model #8040. It has a small circuit after the transformer in the line to each light. I know the light is only \$7.00 to replace, but I would like to fix the one I have, although it may cost more to fix than to replace.

There is a semiconductor between the base (I think) of the TO92 transistor and a resistor on that little board. I would like to know what it is. Also, I'd like to know what type (NPN, PNP) the transistor is. It is marked "G102."

**#80012** Burton Daggett  
Shelton, WA

I am an older technician recently assigned to service EEPROM-based equipment. What is the best way to learn EEPROM repair technology? Do BASIC Stamps or PICs have any relevance to commercial equipment?

I prefer the non-math functional analysis approach to troubleshooting.

**#80013** Bob Kramer  
Aurora, IL

I have a Rustrak model 288 DC chart recorder that I would like to have measure a variety of DC input voltages (and, if possible, AC). I believe there were attachment kits

## ANSWER INFO

- Include the question number that appears directly below the question you are responding to.
- Payment of \$25.00 will be sent if your answer is printed. Be sure to include your mailing address if responding by E-Mail.
- In most cases, only one answer per question will be printed.
- Your name, city, state, and E-Mail address, (if submitted by E-Mail), will be printed in the magazine, unless you notify us otherwise with your submission.
- The question number and a short summary of the original question will be printed above the answer.
- Unanswered questions from a past issue may still be responded to.
- Comments regarding answers printed in this column may be printed in the Reader Feedback section if space allows.

## QUESTION INFO

### TO BE CONSIDERED FOR PUBLICATION

All questions should relate to one or more of the following:

- 1) Circuit Design
- 2) Electronic Theory
- 3) Problem Solving
- 4) Other Similar Topics

### INFORMATION/RESTRICTIONS

- No questions will be accepted that offer equipment for sale or equipment wanted to buy.
- Selected questions will be printed one time on a space available basis.
- Questions may be subject to editing.

### HELPFUL HINTS

- Be brief but include all pertinent information. If no one knows what you're asking, you won't get any response (and we probably won't print it either).
- Write legibly (or type). If we can't read it, we'll throw it away.
- Include your Name, Address and Phone Number. Only your name will be published with the question, but we may need to contact you.

for this purpose sold, but I've never been able to get a response from the manufacturer about them.

The power source for this is line voltage, but the input to the chart recorder marker must be DC. I have determined that a 1-1/2V battery in series with a 2200Ω resistor will give about a 60% deflection on the chart which was the pointer of the meter as a marker.

I already know I can use a variety of resistors or a variable pot to measure DC voltages, but I also would like



to be able to measure 105-125 VAC, if this is possible.

The only other things I know about this, is that the meter is rated 1.0 mA and the chart drive has an internal resistance of 80Ω. [Chart width for 0-100 is 2-1/4 inches.]

**#80014** Richard Flaws  
Oswego, IL

How can I access the Internet over my Motorola bagphone?

**#80015** Steve Lafontaine  
via Internet

I have an odd IBM power supply for an IBM 300GL socket 7 system. It has two connectors of AT design, plus two additional three-volt connectors of six pins each. It also has two three-pin mini connectors. The power supply has no on/off switch, so I assume it's of the same principle as an ATX supply where the power switch is through the motherboard. I need more of these supplies, so any information on them or how to convert an ATX to one would be greatly appreciated.

**#80016** Tyler Graff  
tgraff@mindspring.com

## ANSWERS

### ANSWER TO #7002 - JULY 2000

I have several Icom M80 marine VHF radios with a failed micro-processor. Icom says this chip is no longer available. It's a Motorola MC146805G2. I need a supplier for this chip or a substitute.

In response to Earl Walton's (and others) question regarding locating suppliers of chips, one website that provides a large database is FindChips.com @ <http://www.findchips.com/>

It is a very useful site that should be bookmarked for future use.

Barry Tuttleman  
Carson City, NV

### ANSWER TO #7008 - JULY 2000

I want to add an RS-485 network to the 68HC11. I am looking at SPI communication on the MCU and either a MAX483 or a SN75176A bus driver. What I need is a schematic of how to connect them and some sample software.

Get my book *Digital and Computer Projects* by Robert J. Davis, available on several Internet book sites. It has plans for a multi drop 68HC11F1 controller system that is used for a campus wide energy management system. It supports up to 16 devices, but with software modifications, many more could be added.

There is software listings in Basic for a controlling PC and Machine language for the 68HC11 controllers. It does not support bidi-

rectional communication over the same pair due to limitations of Basic on the PC. I understand this can be accomplished in hardware, however. I was amazed that no one seems to make a ready-made controller board for this application.

Bob Davis  
via Internet

### ANSWER TO #70011 - JULY 2000

I want to put strobe lights in the rear turn signals on my truck so that when I stop on the side of the road to aid someone, they will flash very brightly.

I want to build a circuit that will flash a strobe alternately in a back and forth motion.

It is a '98 Nissan Frontier with yellow turn/hazard lights.

I would like to drill a hole in the housing and install the strobes as secondary flashers so that the turn

and original lights still operate normally.

Galls, Inc., is a supplier for equipment for police, fire, and EMS departments. They sell the strobes that you are looking for. You can request a catalog at <http://www.galls.com/> or by calling 1-800-477-7766.

You may need to check with your local authorities regarding flashing lights on your vehicles, but since you are using only yellow colored strobes you should not have a problem.

Michael Weber  
Mifflinburg, PA

### ANSWER TO #7004 - JULY 2000

I have one of the old Atari calculators designed to be used without batteries. But under room light, it does not work very well. I would like to replace the cell with a battery, but I'm not sure where to start. The model is

the CC1200 folding calculator.

First, you must determine the output voltage of the solar cell. Carefully disassemble the calculator, measure the voltage across the solar cell when exposed to sunlight and note the polarity of the voltage.

Today's calculators operate off a single cell [1.5V]. This calculator being old may require two or more cells [3V or more]. Most likely you would need 3V.

You should be able to use a small button type 3V lithium battery with solder tabs, which you can buy at any RadioShack. Simply cut off the original solar cell, match the polarity and solder the wires to the new battery. The current draw from the battery is very low so it should not require an external on/off switch.


Haim Sandel  
Scottsdale, AZ

### ANSWERS TO #7007 - JULY 2000

I have a video transmitter that's operating on a 12 VDC at 300 mA wall adaptor, and a CCD camera, working on a 9V battery. I would like to operate both devices from a portable and compact [12 VDC] battery pack (the smaller, the better), for at least an hour.

Any suggestions and/or ideas on how to split the power supply for both devices, each having different power requirements?

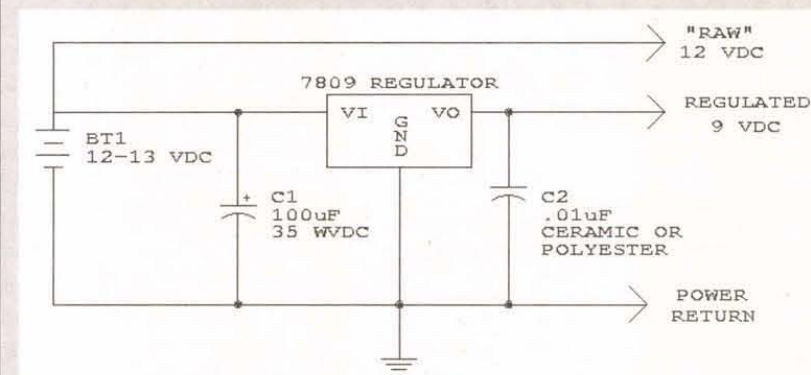**#1** Please refer to the attached schematic for a "power distribution system" that might suit your needs.



"Main" power is derived from "any old" gates-type sealed lead-acid 12V gelcell (or similar "high-capacity" 13V NiCad battery pack). Assuming the camera doesn't eat more than 1 amp, the 7809 three-terminal regulator shouldn't overheat. Nonetheless, make sure you attach the regulator to a suitable heatsink and insulate ALL wires/terminals to prevent unwanted short circuits.

It can be built on perfboard using "point-to-point" wiring — nothing is critical. However, make sure you have C2 (the .01uF bypass cap — DO NOT OMIT!) cap as close as possible to the regulator AND, depending on the length of cable from the regulator assembly, you may need another electrolytic paralleling C2.

Ken Simmons  
Auburn, WA

**#2** The easiest, least expensive, and perhaps the best way to solve your split power supply problem is with two linear voltage regulators.

Part number LM 7809 (NTE 1910) and LM 7812 (NTE 966) are two inexpensive voltage regulators that

recommend, but not require, two external capacitors to stabilize the ripple caused by regulation; and between the four capacitors and the two regulators, should come to a grand total of less than \$5.00, depending on where you shop.

At your low power requirements, the TO-220 package doesn't require a heatsink, but with a heatsink attached, they can handle loads as high as one amp each.

These regulators are simple to use and when viewing the chip like a book, and reading its numbers upright from left to right, the "power in" pin is at the left and the "power out" pin is at the right, with the center pin being ground.

On each chip it is recommended that you attach a .1 to 100 uFd to the input pin #1, and on the power out pin, you attach a capacitor with a value of .33 to 100 mFd (or multiples), and your circuit is complete.

The different values given here come from different schools of thought, but any capacitor within those values will suppress ripple. However, as I have found, you may need to experiment with your camera more so than your

transmitter in regards to these capacitors. A regulator circuit that works perfectly well on a monitor, a different camera, or other devices might show lines of ripple in some CMOS or other type CCD cameras.

If your transmitter requires more than one amp (value not mentioned), then there are bigger versions of the LM 7812 that will meet your needs such as the NTE 1912 @ 3 amps, or the NTE 933 @ 5 amps. And although these come in a different TO-5 package designed to deliver more current, they are still simple three-lead regulators.

Most of these chips when purchased over the counter from places like RadioShack and others, come with a setup diagram explaining all of your questions.

Other methods of split power supplies include switching regulators, buck/boost regulators and simple resistor voltage dividers, as well as a whole slew of other devices. But for the money, simplicity, and thermal shutdown that these regulators offer, you can't go wrong.

Chris  
Bieber, CA



## ANSWERS TO #7003 - JULY 2000

I am in the computer field and many times after moving a monitor, it has purple splotches on the screen. The built-in degausser just doesn't do the trick. I spoke with an "old timer" in the TV business and he said you can make a degausser:

Does anyone know how to do this as it appears to be a coil of lamp cord and a switch.

**#1** A simple manual degaussing device can be built from removing the degaussing coil from an old monitor and connecting it to a doorbell transformer. A 12- to 24-volt transformer is usually needed because degaussing coils are not designed to operate directly off 120 volts.

The coil can be found in an old monitor by looking for a coil wrapped in black tape near the front of the picture tube. Generally, it is as big as the outside circumference of the picture tube. In some cases, you need to remove the picture tube to get at the coil. It should have a two-

pin plug that plugs into the power supply of the monitor.

This coil can be used to degauss the monitor by waving it around the front of the monitor then slowly pulling it away before removing power. Do not leave it plugged in too long as the coil may get hot and the doorbell transformer may also overheat.

**Bob Davis**  
via Internet

**#2** Here is a "hot tip" from an old TV repairman. If you own a high-powered soldering gun (like the Weller 240 watt models) with a power transformer, you already own a pretty good degaussing tool. Turn the gun on while a foot or so away from the monitor. Then move the gun around the perimeter of the tube a few times and then slowly back off to a foot or so away from the monitor before turning it off. Remember, the tip on the gun is also a hot one.

**John Montalbano**  
via Internet

## ANSWERS TO #6004 - JUNE 2000

I am interested in scanning pixel values from my color webcam. I am theorizing that the webcam writes values to 'video' memory which are used to generate the picture on the screen. My missing link is the program to read this value while the camera is running in the 'background.'

Is this possible? Is my theorizing correct? What programming language is recommended? How do I run both camera and program at the same time?

**#1** Your assumption is correct that whatever is displayed on the screen is represented as a value in memory that can be queried. Any programming language from Assembly to Visual Basic could be used to write a program to acquire the values.

Here is the link to a program that will show you the RGB value of any color you point to on the screen. It sounds like just what you are asking for. It runs while any other program is running. [www.tucows.com/color95.html#apicker95](http://www.tucows.com/color95.html#apicker95)

**David Wolff**  
San Jose, CA

**#2** Possible: Yes. Theory: Close:

The program reads from the web-camera and places the data wherever.

In many Internet Web-Cam systems, single shots are stuffed in a file (Disk or REM-Disk) that the web server software reads to send to requesters. Your existing software

should be able to grab single frames to disk.

Language: C or Assembly. If you want full motion, then try to minimize use of OOP code.

How to run: You need the interface info to access the camera driver. Then you can put the data wherever you want.

**Jèrel D. Arbaugh**  
via Internet

## More On Telephone Busy Lights



Dear Nuts & Volts:

I read with much interest the "Reader Feedback" letters about Telephone Busy lights. While the suggestions are useful, I think I have a much simpler alternative that does not require any power source (i.e., batteries) other than the phone line itself.

Attached is the schematic of a commercial "Phone Line Blocker" that was given to me many years ago (I don't think such a device is currently available any more). Not only does it indicate when the line is in use (the LED), when attached to "auxiliary" phone devices that share one line, it will totally block those "auxiliary" phones when a "master" phone or modem is in use.

In other words, no more modem interruptions while indicating to the "other phones" that the line is currently in use. While "any old LED" can be used, one can certainly use a "blinking" or "high-brightness" LED if one desires.

There is one caveat to be aware of: the "master" telephone device (i.e., modem or "main" phone) **MUST NOT** have a blocker on its line! In other words, only the "auxiliary" devices can have the blocker installed. However, if the "master" device is not in use, the "auxiliary" device(s) can use the phone, one at a time (i.e., no "eavesdropping") as long as the "master" ("unprotected" device) is not taken off-hook. Here's a typical use:

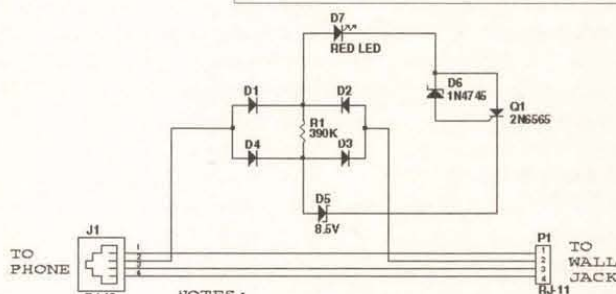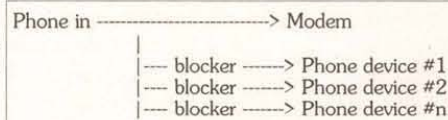

### NOTES:

- \* Q1 - 2N6565
- \* D1-D4: 1N4002
- \* D5 - 8.5V ZENER
- \* D6 - 1N4745
- \* D7 - "ANY OLD" RED LED
- \* WIRE CODING: 1 - BLACK
- 2 - GREEN
- 3 - RED
- 4 - YELLOW

**Ken Simmons**  
Auburn, WA

plug-ins  
test sets  
counters  
generators  
oscilloscopes  
power supplies  
spectrum analyzers  
& much more!

[www.levylatham.com](http://www.levylatham.com)

PRIVATE MARKETERS OF U.S. GOVERNMENT MILITARY SURPLUS ASSETS

Write in 57 on Reader Service Card.

**Honey, I shrunk the COMPUTER!**

PicStics are like BASIC Stamps® on steroids. They have more speed, more parallel I/O, more code and data space, and more neat features like a real-time clock, 12-bit ADC, and 12-bit DAC.

[www.micromint.com](http://www.micromint.com)

**Micromint, Inc.**

740 Florida Central Pkwy., Longwood, FL 32750

As low as \$29

Call for a catalog or visit our Web site today.

(800) 635-3355  
(407) 262-0066


BASIC Stamp is a registered trademark of Parallax, Inc.

Write in 58 on Reader Service Card.



# ADVERTISER INDEX

Abacom Technologies	44	M2L Electronics	88
ACP Superstore	70	Matco, Inc.	76-77
ActiveWire, Inc.	76	Matrix Multimedia	59
Advanced Transdata Corporation	38, 62	Meredith Instruments	88
All Electronics Corporation	58	Metric Equipment Sales, Inc.	46
Allison Technology Corporation	59	Metrologic	17
Alltronics	60	MFM Communications	76
Andromeda Research	49	microEngineering Labs	50
Antique Radio Classified	77	Micromint	81
Autotime Corp.	76	Miller Engineering	77
Aventrade	76	Motron	6
Baylin Publications	27	Mr. Noid	16
Bilcocon Corp.	77	MSC Electronics	77
Bitz Technology	91	MVS	61
BNC/Telux Div.	33	Netcom	19
C & S Sales, Inc.	69	Parallax, Inc.	Back Cover
C and H Sales Company	51	PCB Express, Inc.	77
Carl's Electronics	73	Picard Industries	6
Chicago Circuits Corporation	73	Pioneer Hill Software	46
Circuit Specialists, Inc.	94	Polaris Industries	29
Communications Surplus	77	Power Quality, Inc.	78
Corporate Systems Center	2, 95	Prairie Digital, Inc.	77
Cunard Associates	42	Price Surveillance	76
Decade Engineering	76	Privacy Electronics	34
Demar Electronics	76	Pulsar, Inc.	27
DesignNotes.com	61	Quality Kits	76
Digital Products Company	76	Ramsey Electronics, Inc.	41
Earth Computer Technologies	51	Ray's Robotic Racers	34
ECD	76	R.E. Smith	76
EDS	42	Resources Un-Ltd.	30
E.H. Yost & Co.	16	Roger's Systems Specialist	63
Electro Mavin	61	Saelig Company	8
Electro Science Applications	77	Sam's Electronics	61
Electronix Corp.	61	Scott Edwards Electronics, Inc.	74
EMAC, Inc.	56	Seabird Technical	77
ExpressPCB	70	Securetek	78
EPS	77	Shreve Systems	11
Fair Radio Sales Co.	53	Skycraft Parts & Surplus, Inc.	47
Foss Warehouse Distributors	77	Square 1 Electronics	56
Fusion Electronic Security	38	SuperCircuits	68
Gateway Electronics, Inc.	40	Surplus Traders	78
GetToner.com	76	Techniks, Inc.	76
Globaltech Distributors	76	Technological Arts	53
Graymark	55	Teklab, Inc.	72
Halted Specialties Co.	3	Test Equipment Connection	39
HobbyTron	44	Test Equipment Plus	45
Howard Electronic Instruments, Inc.	37	The End Connection	77
H.T. Orr Computer Supplies	71	The RF Connection	59
Information Unlimited	75	Timeless Products	92
Inkjet Southwest	36	Trexon, Inc.	78
Intronics, Inc.	47	Unicorn Electronics	74
Intuitive Circuits LLC	71	USI Corp.	42
J-Works, Inc.	59	V&V Mach. & Equipment, Inc.	77-78
Jam RF	32	Vesta Technology, Inc.	76
La Paz Electronics International	78	Viking Systems International	13
Lemos International Co., Inc.	7	Visitect, Inc.	39
Levy Latham	81	Weeder Technologies	72
Linear Systems	17	Western Test Systems	24-25
Lynxmotion, Inc.	32	Worldwyde	77-78

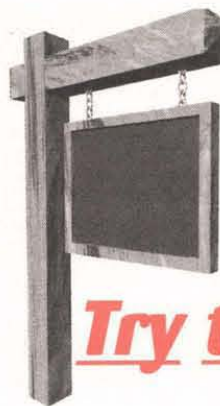

**Got  
something  
to sell?**

***Try the classifieds!!***

TYPE or PRINT your **ELECTRONICALLY RELATED** ad copy **CLEARLY** (not all caps) on a separate piece of paper. Spell out words when submitting handwritten copy. Calculate the number of words and multiply it by the appropriate rate (see RATE PER WORD section). Include any charges for bold and/or CAPPED words, any artwork costs that would be applicable, and/or costs for boxing your ad (explained below). Choose the appropriate classification for your ad(s) to appear in (see below). If no classification is indicated, it will be placed in Misc. Electronics or wherever we deem most suitable. **Enclose your name, address, phone number, and Nuts & Volts account number from your mailing label** (if available) for identification purposes. Include full payment — **CLASSIFIEDS RUN ON A PRE-PAID BASIS ONLY** — and mail your completed order to:  
**NUTS & VOLTS MAGAZINE, 430 Princeland Ct., Corona, CA 92879.**

## RATE PER WORD

The ad rate for current **PAID** subscribers is **60¢** per word. All others pay **\$1.20** per word. There is a **\$9.00** minimum charge per ad per insertion.

## WORDS IN BOLD AND/OR ALL CAPS

Words to be set in **bold** or **CAPS** are each **10¢** extra PER WORD. **BOLD CAPS** are **20¢** extra per word. The first two words of each ad are bold capped at no charge. Indicate bold words by underlining. Words normally written in caps (e.g., IBM) and accepted abbreviations such as VAC or MHz are NOT charged as all cap words. Use a two-letter abbreviation for states.

## PHOTOS, DRAWINGS, AND BOXES

A photo or drawing may be run at the top of your classified ad for an additional **\$10.00** (1" depth max.) for camera-ready art. No wording is allowed in this area. To **BOX** your ad, include an additional **\$50.00** for copy-only ads, or **\$75.00** for ads with art or photos.

## FAXING IN AD COPY

You may fax in ad copy or changes before the closing date (5:00pm on the **5th**) at 909-371-3052 using MasterCard or Visa. Include credit card expiration date, the name that appears on the card, a daytime phone number, and your Nuts & Volts account number. Ads without credit card information will not be listed as received until payment is received in full. **WE DO NOT CALL OR FAX BACK VERIFICATION OR QUOTES OF FAXED-IN ADS.** For verification of faxed-in ads, please call 909-371-8497.

## DEADLINE

Prepaid ads received by 5:00pm on the **closing date (5th of the month)** will appear in the following month's issue. Ads postmarked through the **5th**, but received after the closing date, will be placed in the next available issue. No cancellations or changes after the 5th. Cancellations and changes must be submitted in writing.

## IMPORTANT INFORMATION

All classified ads are running copy only. No special positioning, centering, dot leaders, extra space, etc. is allowed. All advertising in Nuts & Volts is limited to **electronically related items ONLY**. All ads are subject to approval by the publisher. We reserve the right to reject or edit any ad submitted. We do not take ad copy or changes over the phone. We do not bill for classified ads. Repeat ads or ads run in multiple classifications within the same issue are allowed. Paid subscribers may run ads at the 60¢ rate only through their subscription expiration date. **NO REFUNDS.** Credit only. No credit for typesetting errors will be issued unless you clearly print or type your ad copy.

*Choose a category for your ad from the classifications listed below.*

10. Ham Gear For Sale	120. Components
20. Ham Gear Wanted	125. Microcontrollers
30. CB/Scanners	130. Antique Electronics
40. Music & Accessories	135. Aviation Electronics
50. Computer Hardware	140. Publications
60. Computer Software	145. Robotics
70. Computer Equipment Wanted	150. Plans/Kits/Schematics
80. Test Equipment	155. Manuals/Schematics Wanted
85. Security	160. Misc. Electronics For Sale
90. Satellite Equipment	170. Misc. Electronics Wanted
95. Military Surplus Electronics	175. BBS & Online Services
100. Audio/Video/Lasers	180. Education
110. Cable TV	190. Business Opportunities
115. Telephone/Fax	200. Repairs/Service



# Product/Category INDEX

Find what  
you need  
**FAST**

## AMATEUR RADIO & TV

Alltronics	60
Communications Surplus	77
Decade Engineering	76
Gateway Electronics, Inc.	40
HobbyTron	44
Lemos International Co., Inc.	7
Motron	6
Ramsey Electronics, Inc.	41
The RF Connection	59

## ASSEMBLY SERVICES

Bilcocon Corp.	77
----------------	----

## BATTERIES/CHARGERS

Aventrade	76
Cunard Associates	42
E.H. Yost & Co.	16
Globaltech Distributors	76
Mr. NiCd	16
Power Quality, Inc.	78

## BUSINESS OPPORTUNITIES

## BUYING ELECTRONIC SURPLUS

C and H Sales Company	51
Earth Computer Technologies	51
Metric Equipment Sales, Inc.	46
Roger's Systems Specialist	63
Skycraft Parts & Surplus, Inc.	47

## CABLE TV

Foss Warehouse Distributors	77
Sam's Electronics	61
Timeless Products	92
Worldwyde	77-78

## CB/SCANNERS

USI Corp.	42
-----------	----

## CCD CAMERAS/VIDEO

Circuit Specialists, Inc.	94
Decade Engineering	76
Fusion Electronic Security	38
Matco, Inc.	76-77
MSC Electronics	77
Polaris Industries	29
Ramsey Electronics, Inc.	41
Resources Un-Ltd.	30
Seabird Technical	77
Securetek	78
SuperCircuits	68
USI Corp.	42

## CIRCUIT BOARDS

Chicago Circuits Corporations	73
Cunard Associates	42
ECD	76
ExpressPCB	20
PCB Express, Inc.	77
Pulsar, Inc.	27
V&V Mach. & Equipment, Inc.	77-78

## COMPONENTS

Chicago Circuits Corporation	73
Communications Surplus	77
ECD	76
La Paz Electronics International	78

Linear Systems	17
Pulsar, Inc.	27
Skycraft Parts & Surplus, Inc.	47
Unicorn Electronics	74
Visitect, Inc.	39

## COMPUTER

### Hardware

ActiveWire, Inc.	76
Allison Technology Corp.	59
Corporate Systems Center	2, 95
Earth Computer Technologies	51
Electro Mavin	61
Halted Specialties Co.	3
La Paz Electronics International	78
Roger's Systems Specialist	63
Shreve Systems	11
Techniks, Inc.	77
The End Connection	77

### Software

Electro Science Applications	77
Electronix Corp.	61
Globaltech Distributors	76
Matrix Multimedia	59
Pioneer Hill Software	46

### Microcontrollers / I/O Boards

Autotime Corp.	76
EMAC, Inc.	56
Intuitive Circuits LLC	71
La Paz Electronics International	78
Micromint	81
MVS	61
Parallax, Inc.	Back Cover
Prairie Digital, Inc.	77
Ray's Robotic Racers	34
R.E. Smith	76
Scott Edwards Electronics, Inc.	74
Square 1 Electronics	56
Technological Arts	53
Trexon, Inc.	78
Vesta Technology, Inc.	76
Worldwyde	77-78

### Printers/Printer Supplies

GetToner.com	76
H.T. Orr Computer Supplies	71
Inkjet Southwest	36

## DESIGN/ENGINEERING SERVICES

Chicago Circuits Corporation	73
DesignNotes.com	61
Electro Science Applications	77
ExpressPCB	70
Prairie Digital, Inc.	77
Pulsar, Inc.	27
V&V Mach. & Equipment, Inc.	77-78

## EDUCATION

EMAC, Inc.	56
HobbyTron	44
Matrix Multimedia	59

## EVENTS/SHOWS

ACP Superstore	70
----------------	----

## KITS

Alltronics	60
C & S Sales, Inc.	69
Digital Products Company	76
Earth Computer Technologies	51
EMAC, Inc.	56
Gateway Electronics, Inc.	40
HobbyTron	44
Information Unlimited	75
Inkjet Southwest	36

Miller Engineering	77
Quality Kits	76
Ramsey Electronics, Inc.	41
Scott Edwards Electronics, Inc.	74
USI Corp.	42
Weeder Technologies	72
Worldwyde	77-78

## LASERS

Information Unlimited	75
Meredith Instruments	88
Metrologic	17
Resources Un-Ltd.	30
Unicorn Electronics	74

## MISC./SURPLUS

All Electronics Corporation	58
C and H Sales Company	51
Communications Surplus	77
Demar Electronics	76
EPS	77
Fair Radio Sales Co.	53
GetToner.com	76
Halted Specialties Co.	3
Jam RF	32
Levy Latham	81
Linear Systems	17
PCB Express, Inc.	77
Picard Industries	6
Power Quality, Inc.	78
Resources Un-Ltd.	30
Shreve Systems	11
Skycraft Parts & Surplus, Inc.	47
Surplus Traders	78
Unicorn Electronics	74
Viking Systems International	13
Visitect, Inc.	39
Weeder Technologies	72

## PROGRAMMERS

Advanced Transdata Corporation	38, 62
Andromeda Research	49
Intronics, Inc.	47
M2L Electronics	88
microEngineering Labs	50
Worldwyde	77-78

## PUBLICATIONS

Antique Radio Classified	77
Netcom	19
Square 1 Electronics	56

## RF TRANSMITTERS/ RECEIVERS

Abacom Technologies	44
Matco, Inc.	76-77
Securetek	78

## ROBOTICS

Lemos International Co., Inc.	7
Lynxmotion, Inc.	32
SuperCircuits	68

## SATELLITE

Baylin Publications	27
Worldwyde	77-78

## SECURITY

Bitz Technology	91
Decade Engineering	76

Fusion Electronic Security	38
Information Unlimited	75
Lemos International Co., Inc.	7
Matco, Inc.	76-77
Motron	6
MSC Electronics	77
Polaris Industries	29
Price Surveillance	76
Privacy Electronics	34
Securetek	78
SuperCircuits	68
Visitect, Inc.	39

## SOLAR EQUIPMENT

## STEPPER MOTORS

Alltronics	60
------------	----

## TELEPHONE

BNC/Telux Div.	33
Carl's Electronics	73
Digital Products Company	76
Globaltech Distributors	76
MFM Communications	76
Privacy Electronics	34
Weeder Technologies	72

## TEST EQUIPMENT

Allison Technology Corp.	59
BNC/Telux Div.	33
C & S Sales, Inc.	69
C and H Sales Company	51
Circuit Specialists, Inc.	94
DesignNotes.com	61
Digital Products Company	76
EDS	42
Intronics, Inc.	47
J-Works, Inc.	59
Levy Latham	81
Metric Equipment Sales, Inc.	46
Pioneer Hill Software	46
Power Quality, Inc.	78
Prairie Digital, Inc.	77
Price Surveillance	76
Saelig Company	8
Seabird Technical	77
Teklab, Inc.	72
Test Equipment Connection	39
Test Equipment Plus	45
Western Test Systems	24-25
Worldwyde	77-78

## TOOLS

Advanced Transdata Corporation	38, 62
C & S Sales, Inc.	69
Graymark	55
Howard Electronic Instruments, Inc.	37
The RF Connection	59

## WIRE/CABLE & CONNECTORS

Roger's Systems Specialist	63
The RF Connection	59



# Build a Party Strobe Light



Unlike most strobe units used at parties, the Party Strobe is sound-sensitive using a built-in microphone. The strobe flashes with the beat of the music! Designed by David McDonald and powered by the AC line, it uses no batteries, and can be built from a \$24.90 kit or from scratch.

In the '70s, '80s, and still in the '90s, discotheques ("discos") were extremely popular. Loud, pounding music with flashing vari-colored lights and rotating mirrored balls reflecting over crowded, jiggling dancers was the norm.

The flashing vari-colored lighting was created by stroboscopic ("strobe") lights with colored lenses. The sophistication of some of these devices is described in an advertisement for a commercial "Dazzling Strobe Bar." It reads: "Pump up the volume and turn down the lights."

Let the alternating color flashes of this dramatic strobe bar get the dance floor in groove with the tunes. It has seven different lighting effects, a full-function remote, and a built-in microphone that makes the lights strobe with the beat of the music."

These days many disco parties are held in the home and are less elaborate. The single "Party Strobe Light" described here, together with a rotating mirrored ball and some loud music, should be all that's needed for a home disco party.

A complete kit of parts, including an etched, drilled, and silkscreened printed circuit board, is available for \$24.90. Some of the more difficult-to-find parts and the printed circuit board are offered separately if you have some of the common parts.

## Circuit Description — Power Supply

The schematic of the Party Strobe Light is shown in Figure 1. The circuit may be considered as having three main parts working together: Power Supply, Audio Amplifier, and Xenon Strobe. When P1 is plugged into 110 VAC and switch S1 is closed, power is supplied separately to the amplifier and Xenon sections.

The incoming AC line power is directed to the amplifier section through diode D3. This only allows the pulsating positive cycles of the line power to be fil-

tered (smoothed) by a pi-filter consisting of electrolytic capacitor C4, resistor R4, and electrolytic capacitor C5.

The filtered DC voltage at C4 is about 165 volts. The values of R4 and R6 create a voltage divider, so the filtered DC voltage at C5 — which powers the amplifier circuit — is about 10 volts.

Power to the Xenon strobe portion of the circuit is divided into two parts. A high voltage of about 320 volts is provided through a "voltage doubler" circuit. Looking at Figure 1, when the positive half of the 110 VAC cycle (about 160 volts peak) appears at the lower contact of the AC plug, current flows through switch S1 and diode D1, charging electrolytic capacitor C1 over a short period of time to 160 volts. Diode D2 is non-conductive during this time since both the top and bottom of electrolytic capacitor C2 are at positive voltage.

During the other half of the cycle, D2 conducts and C2 becomes charged with the AC peak voltage plus the volt-

age in C1, for a total of about 320 volts (depending on the actual AC voltage).

Resistor R1 is used to limit the surge current during the initial cycle, since C1 and C2 look like a short-circuited load. Also, during rapid flash sequences when sound is detected, resistor R1 is used to limit the actual charging of C1 to 125 volts and C2 to 250 volts — the rated Xenon flash tube voltage — since C1 and C2 don't have time to fully charge between flashes.

Also, positive half-cycles pass through R1 and current limiting resistor R2 to the anode of silicon-controlled rectifier Q1 in the trigger circuit, as we'll see later.

In summary, with relatively few parts, the 110 VAC is converted into about 10 VDC to supply the amplifier circuit, into about 250 VDC to supply the Xenon flash tube, and voltage to power the trigger circuit.


## Circuit Description — Audio Amplifier

Looking at the lower portion of the Figure 1 schematic, the audio amplifier consists of electret microphone E1 and two sections of U1, an LM324 quad op-amp integrated circuit, together with the associated resistors, capacitors, and potentiometer. Only sections A and B of U1 are used; sections C and D are intentionally grounded to prevent oscillation or interference.

Resistor R14 provides a path and the biasing voltage required for E1. Sound waves received at E1 generate small AC voltages that add and subtract from the bias voltage, and are carried through capacitor C10 to the (+) non-inverting input, pin 3, of U1-A.

Resistors R12 and R13 form a voltage divider, creating a five-volt bias voltage (one-half the supply voltage) to U1-A so that U1-A may then amplify both

Figure 1: Party Strobe Light Schematic

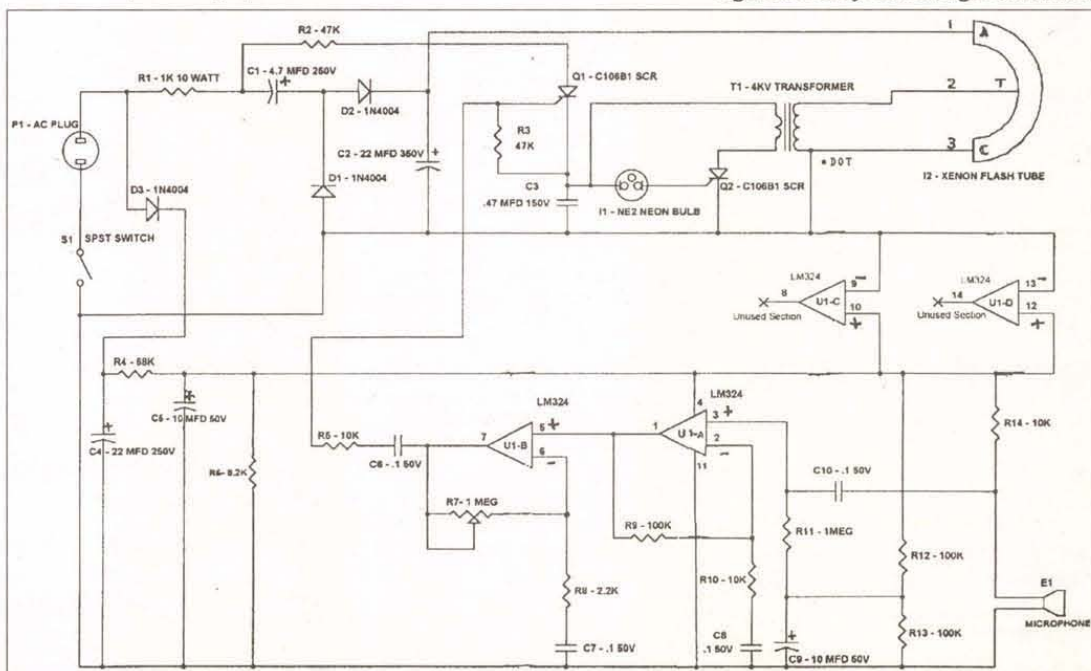



## Parts List

Note: The relatively hard-to-find parts marked with an asterisk (\*) are available from Hobbytron (see SOURCE below).

- \* C1 - 4.7uF 250-volt axial electrolytic capacitor
- \* C2 - 22uF 350-volt axial electrolytic capacitor
- \* C3 - 0.47uF 200-volt axial capacitor
- \* C4 - 22uF 250-volt axial electrolytic capacitor
- (Note: See SOURCE for Capacitor Set of C1-C4)
- C5, C9 - 10uF 50-volt radial electrolytic capacitor
- C6, C7, C8, C10 - 0.1uF 50-volt disc capacitor
- D1, D2, D3 - 1N4004 silicon power diode
- \* E1 - Electret microphone (GK09002 \$1.20)
- \* I1 - NE2 neon bulb (GK10004 \$0.35)
- \* I2 - 5-watt xenon flash tube (GK10001 \$3.85)
- \* P1 - AC line cord with plug (GK12001 \$1.25)
- \* Q1, Q2 - SCR C106B1 (GK13001 \$1.00 each)
- \* R1 - 1K 10-watt resistor (GK48001 \$0.79)
- R2, R3 - 47K 1/2-watt resistor
- R4 - 68K 1/2-watt resistor
- R5, R10, R14 - 10K 1/2-watt resistor
- R6 - 8.2K 1/2-watt resistor
- \* R7 - 1 megohm 1/2-watt potentiometer (GK33010 \$1.25)
- R8 - 2.2K 1/2-watt resistor
- R9, R12, R13 - 100K 1/2-watt resistor
- R11 - 1 megohm 1/2-watt resistor
- \* S1 - SPST slide switch (GK25001 \$0.65)
- \* T1 - 4,000 volt trigger transformer (GK23010 \$1.50)
- \* U1 - LM324 quad op amp integrated circuit (GK14002 \$0.90)
- \* Circuit Board - GK#7785 \$8.95
- \* Capacitor Set = C1, C2, C3, C4 (GK39000 \$6.95)

**SOURCE:**

A complete kit or parts (Kit #9985 for \$24.90), or the parts identified with an asterisk (\*) above, can be ordered from HobbyTron, Inc., 1185 South 1480 West, Orem, UT 84058. 1-888-606-TRON (8766), Fax 1-800-470-1606 or local number 801-221-9822, Fax 801-221-9280. Shipping and handling UPS Ground in the USA is \$6.95 per order. Sales tax for Utah residents is 6.25 percent. The E-mail address is [qarvq@tsnet.com](mailto:qarvq@tsnet.com), and the website is [HobbyTron.com](http://HobbyTron.com).


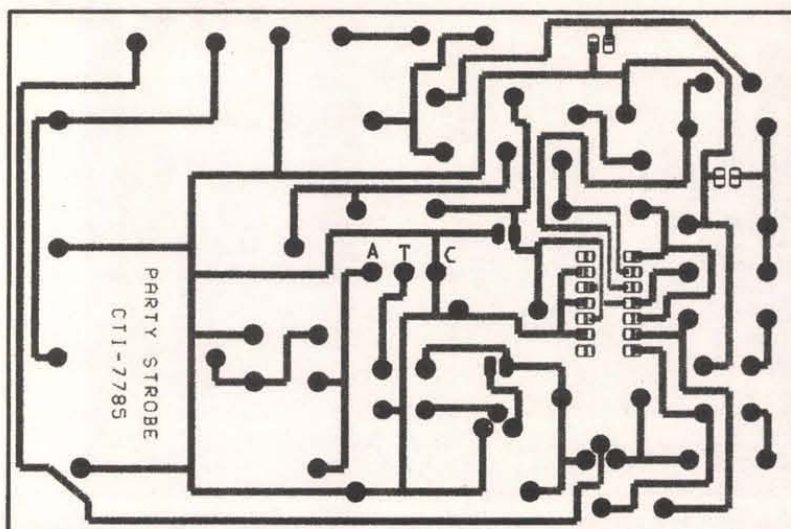


Figure 2: Party Strobe Light Printed Circuit Traces

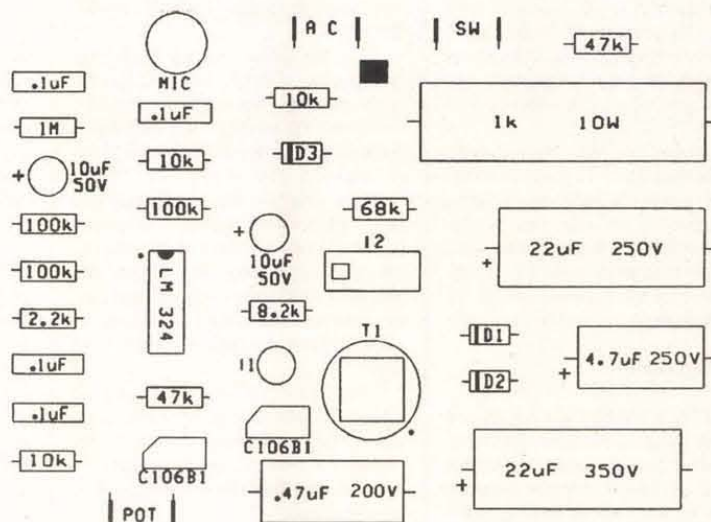

**Figure 3: Party Strobe Light Parts Layout**

positive-going and negative-going signals. Electrolytic capacitor C9 filters this voltage further to eliminate any 60-cycle or line interference. Resistor R11 delivers the bias voltage to U1-A, and is of a high enough value so as to prevent the microphone signal from being shunted to ground through C9.

The voltage gain of U1-A is controlled by resistors R9 and R10. The formula is: Voltage Gain =  $1+(R9/R10) = 1+(100K/10K) = 11$ . Capacitor C8 bypasses unwanted noise.

The output of U1-A at pin 1 goes directly to the (+) non-inverting input, pin 5, of U1-B. The gain of U1-B is controlled by the values of potentiometer R7 and resistor R8, with capacitor C7 bypassing unwanted noise.

However, since R7 is variable — from 0 to 1 megohm — and the voltage gain equals  $1+(R7/R8)$ , the voltage gain can vary from 1 to over 450. The total gain of the amplifier (U1-A times U1-B), therefore, varies from 11 to 4,950 (11 times 450).

The output of U1-B at pin 7 is sent through capacitor C6 and resistor R5 to the gate of Q1. More on that soon.


### Circuit Description — Xenon Strobe

In order for xenon tube 12 to flash — igniting the gas in the tube to emit a white light — it requires at least 200 volts DC between the anode (pin 1) and cathode (pin 3), as well as a "trigger" voltage (pin 2) of approximately 4,000 volts DC.

When P1 is plugged into 110 VAC and S1 is closed, the voltage doubler circuit described earlier causes as much as about 320 volts DC to build up between the positive anode and the grounded cathode of I2.

But how do we create 4,000 volts DC for the trigger? Look again at Figure 1, and locate Q1, the silicon controlled rectifier (SCR). The symbol represents three terminals. The top of the arrow is the anode, the line at the point of the arrow is the cathode, and the line at an angle at the cathode is the gate.

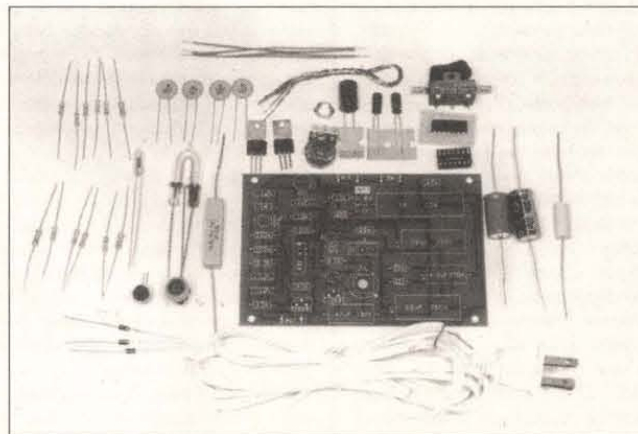The SCR differs from a regular silicon rectifier in that it will not conduct (anode to cathode) until the gate current (gate to cathode, with positive voltage on the gate) reaches a critical value. Then the SCR conducts in the forward direction and the gate current no longer



**A complete kit, including the printed circuit board and some hard-to-find parts, is available for \$24.90**


has any control — as long as sufficient current flows through the rectifier due to positive voltage on the anode.

As earlier in the discussion of the audio amplifier, when sound is picked up by the microphone and amplified sufficiently, the output of U1-B, through C6 and R5, appears at the gate of Q1. When positive voltage from R2 appears

at the anode of Q1 (during the positive half-cycle from the AC line 60 times a second), gate current turns on Q1, and capacitor C3 does some charging during each cycle. This builds voltage at one terminal of the neon bulb I1 and the primary coil of trigger transformer T1.

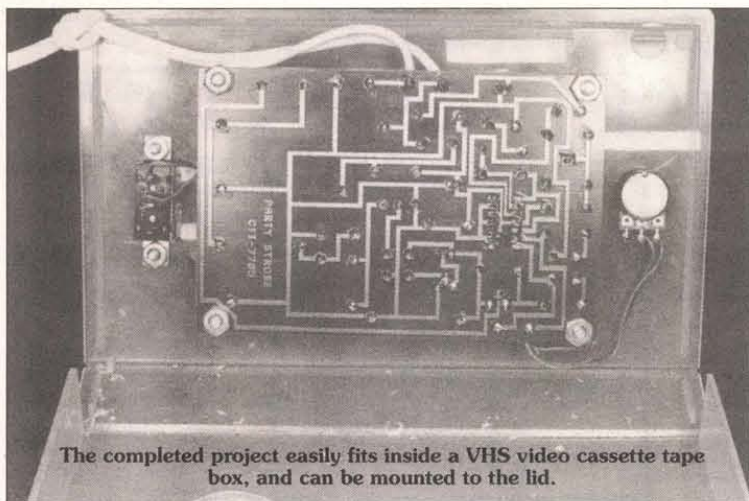When the charge on C3 is over about 65 volts, neon bulb I1 fires, caus-





The completed project easily fits inside a VHS video cassette tape box, and can be mounted to the lid.

ing a positive voltage pulse to reach the gate of SCR Q2. With positive voltage on the anode of Q2 from C3 through the primary of T1, Q2 conducts. This grounds the primary of trigger transformer T1, creating a pulse spike across the primary. Resistor R3 prevents any "misfires" from the highly sensitive SCR gate.

By induction, this voltage spike across the primary of T1 causes a 4,000 volt spike across the secondary winding of T1, triggering the xenon gas tube to conduct, emitting a bright, white flash. This flash continues until C2 is discharged. Once the flash has ended, C2 begins charging again for the next flash.

## Construction

The Party Strobe Light has quite a few parts, many of which are difficult to find. Unless you are good at locating odd parts, or have a very well-equipped junk-box of parts, it is recommended you build the Party Strobe from the complete kit. This includes all the parts and a printed circuit board that is etched, drilled, and silkscreened with the location of all parts.

If you choose to build using some of your own parts, a complete parts list is shown, with some of the hard-to-find parts and the printed circuit board available directly from the kit source. Note that some of the electrolytic capacitors have a high working voltage and are difficult to locate in these days of mostly low-voltage circuits.

Figure 2 shows the single-sided printed circuit board, and Figure 3 is the parts layout. When assembling this project, make sure all polarity-sensitive parts are properly oriented when installed. The polarity-sensitive parts here are the microphone, integrated circuit, electrolytic capacitors, diodes, SCRs, xenon tube, and the trigger transformer.

The microphone should have some indication of the ground lead by looking at the back. The integrated circuit has a notch or indent near pin 1. Electrolytic capacitors normally have the negative lead identified; the other lead is the positive lead. Diodes have a stripe or colored band on the cathode end (the straight line on the circuit symbol).

The specified C106B1 SCR has

three leads. Holding the SCR with the metal tab at the top and the beveled edge facing you, the leads at the bottom are, from left to right, cathode, anode, and gate.

For the xenon tube, the black burn on the glass is the cathode, C (pin 3). When mounting the trigger transformer, make sure the terminal identified with a colored dot or stripe is connected to the cathode of the xenon tube.

The resistors, disc capacitors, and neon bulb have no polarity. The potentiometer, looking from the front with the terminals at the top, should have the jumpered wire between the left and center terminals for sound sensitivity to increase when the shaft is turned clockwise.

As always, be very careful that all soldered joints are good (shiny, not grainy) and that there are no solder "bridges" across circuit traces or between pins that are not supposed to be connected.


Also, be certain that all resistors and capacitors are properly placed. Capacitor values are marked with numbers, but small resistors use a color code. If you are not familiar with the color code, see Figure 4. Putting the wrong resistor value in a circuit by misreading the standard color code can wreak havoc with circuit operation.

## Testing

Note that this circuit is powered by 110 VAC, and that some very high voltages are generated. Avoid touching any circuit lead or solder joint, and be sure the soldered side of the circuit board does not come in contact with any metal parts on your workbench!

Before testing the completed circuit, rotate potentiometer R7 fully counter-clockwise, which should be minimum sensitivity. Now, plug the line cord into 110 VAC, turn on the power switch — and nothing should happen! If you see smoke, immediately unplug the power!

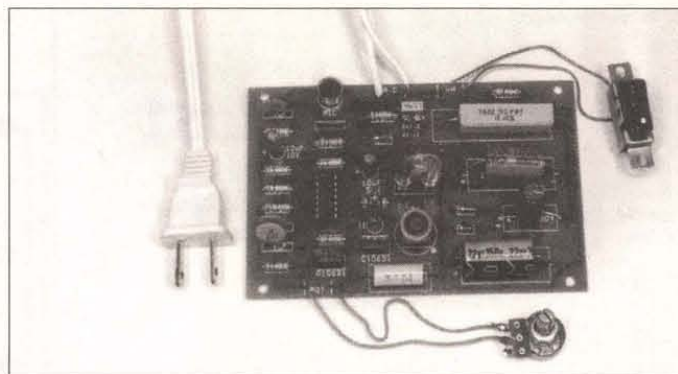Assuming everything seems okay, start talking to the microphone as you rotate the potentiometer shaft slowly clockwise. The xenon tube should start flashing in response to your voice, becoming more sensitive as you rotate the potentiometer shaft more clock-



Except for the line cord, a switch, and a potentiometer, all other parts are mounted on the printed circuit board.

wise. At the maximum sensitivity setting, the xenon tube will flash with a hand clap from over 50 feet away!

## Troubleshooting

The most common reasons for failure of a circuit to work properly are bad soldering and misplaced or misoriented parts, as discussed earlier. Another possible problem could be hairline cracks or shorts on the printed circuit board if you made it yourself. Any part not properly soldered will be slightly loose if you try to move it.

If the xenon tube does not flash, it could have been put in backwards, or its relatively heavy leads might not be soldered properly to the board. Also, xenon tube leads are sometimes covered with a varnish-like substance which should be sanded off before soldering.

If the trigger transformer is misoriented or defective, the xenon will not flash. The DC primary resistance of T1 is about 0.5 ohms, and the secondary about 60 ohms. Also, if SCR Q2 is open or shorted, or U1 is defective, the xenon will not flash.

Suppose the neon I1 flashes, but the xenon does not. Check the voltage across the anode and cathode of the xenon; it should be about 325 volts. If capacitor C2 heats up and pops, either diode D2 is shorted or C2 is installed backwards. For reference, depending on the input AC voltage, here are some typical DC voltage readings you should expect if the strobe is not flashing:

- C1; approximately 165 volts DC
- C2; approximately 325 volts DC
- C3; approximately 60 volts DC
- C4; approximately 165 volts DC
- C5; approximately 10 volts DC

Note that the voltage readings of C1, C2, and C3 should vary up and down if those portions of the circuitry are working properly.

## Packaging

We don't like having circuits with high voltage exposed to curious or misplaced fingers, so we packaged the Party Strobe Light as shown in the photos. The housing is a standard — though translucent — VHS video box.

Four long screws were used through the existing corner holes of the

kit-furnished printed circuit board to hold it to the lid of the box.

Before mounting the board, you'll need to drill holes for the screws, as well as a hole above where the microphone will be. You'll also need a slotted hole for the xenon tube to project up through the box lid. Holes will be needed to mount the switch and the potentiometer, and a notch in the side of the box for the line cord.

RESISTOR COLOR CODE				
BAND	COLOR	1st DIGIT	2nd DIGIT	MULTIPLIER
BLACK	0	0	0	1
BROWN	1	1	1	10
RED	2	2	2	100
ORANGE	3	3	3	1,000 (K)
YELLOW	4	4	4	10,000
GREEN	5	5	5	100,000
BLUE	6	6	6	1,000,000 (M)
VIOLET	7	7	7	10,000,000
GRAY	8	8	8	100,000,000
WHITE	9	9	9	1,000,000,000

Figure 4: Resistor Color Codes

## Using the Party Strobe Light

The intended use for the Party Strobe Light is to react to a musical or drum beat. Turn it on in the sound environment, set the sensitivity to minimum, and then increase the sensitivity until the strobe picks up the beat.

Of course, if there is a lot of background noise, the Party Strobe will "hear" that as well, so set the sensitivity for the optimum lighting effect. Add a rotating mirrored ball and you can have a simple home disco of your own.

You can also use the Party Strobe as a sensing device to flash whenever a desired sound is heard. For example, placed near a ringing telephone, with the sensitivity set low enough to ignore ambient noise, the Party Strobe will flash when the phone is ringing — a real need for the those with limited hearing.

Also, it can detect an attempted burglary when placed near a door or window so that it will flash if the door or window is rattled with attempted entry. Knowing that they have been detected will discourage all but the most determined burglars!

You may discover other uses for this versatile device. **NV**



**S**it down at just about any technician's workbench, and you will find a power supply of some sort. I bought mine from RadioShack when I was about 10 years old. It has an on-off switch, a knob to select the voltage, an analog meter to display the voltage and current, and a switch to select what the meter measures; either voltage or current. I doubt that I can count the number of times I've tried to adjust the output for an exact 5.0 volts using the analog meter. In retrospect, I probably never hit 5.0 volts exactly due to the inaccuracy of the analog meter.

Over the years, I've come close to retiring the old power supply in favor of a newer one with digital readouts and multiple outputs, but I didn't because the new supply wouldn't give enough of an advantage over what I already had ... especially considering the cost.

I finally decided that in order to justify the expense, the new supply had to provide a significant increase in capability over what I already had. This meant computer control and programmability. The few power supplies I've seen on the market that have a PC interface (serial port, GPIB/HPIB) are a little out of my comfort zone price wise.

When I embarked on this project, I decided that the goal for the end product would be a supply with specs similar to those of my old RadioShack unit. The output would go from 0-20 volts with a maximum output current of just over one amp. In addition, the supply would be able to accurately measure its own output voltage and current and report it back to the host PC. Then, since I was going to this much trouble, I decided to add several other features like a two-channel voltmeter, an SPDT relay, an optically isolated digital input and some expandability. (We'll cover these features later in detail.)

## Switching Regulator

For this power supply, I decided to use a switching regulator (LT1176) and avoid the large heatsinks that are normally found on the medium-to-high power linear voltage regulators. The power that must be dissipated by a linear regulator and heatsink can be calculated by subtracting the regulator's output voltage from its input voltage and multiplying that voltage drop by the current into the load.


For low output voltages, this dissipated (or wasted) power can be rather high. For instance, if the voltage into the regulator is 22 volts, the output is two volts and the load is drawing one amp of current, then the total power dissipated in the regulator is  $22V - 2V / 1A$  or 20 watts of power lost in the form of heat in the regulator.

A switching regulator controls its output voltage by varying the duty cycle of a squarewave that is used to open and close a transistor switch. When the switch is open, no energy is used by the regulator or load. When the switch is closed, a very small amount of energy is lost in the switch itself, and the vast majority is passed through to charge the external capacitor. The regulator itself dissipates much less energy and,

# IOMKit and Bridge Software



by Don L. Powrie

PCB — Fully Assembled

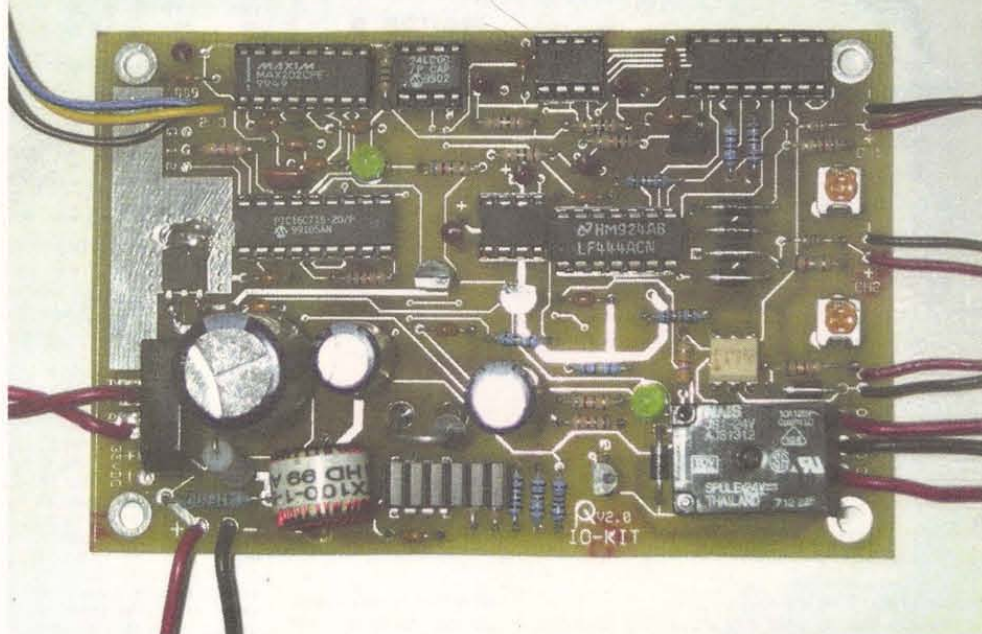



as a result, is much more efficient than a linear regulator. The efficiency of both regulators can be calculated with power out / power in x 100%. (It is worthy to note that the efficiency of linear regulators can be as low as 10%, while switching regulators are typically 70% efficient or higher!)

For this power supply design, the duty cycle of the main power switch located in the LT1176 (U8) is varied until the desired voltage is reached at the summing node connected to pin 4 (Figure 1). When the switch closes, current flows through the inductor (L) creating a magnetic field of energy stored in the form of magnetic flux. This current also charges capacitor (C). When the switch opens, the magnetic flux will collapse with an opposite polarity. Diode (D) then becomes forward biased, and passes the collapsing energy from the inductor to ground. The charge on the capacitor appears at the output and is also divided down by resistors (R1) and (R2), which serve as feedback to the Pulse Width

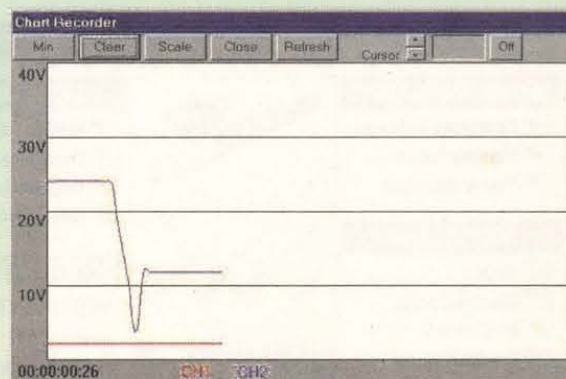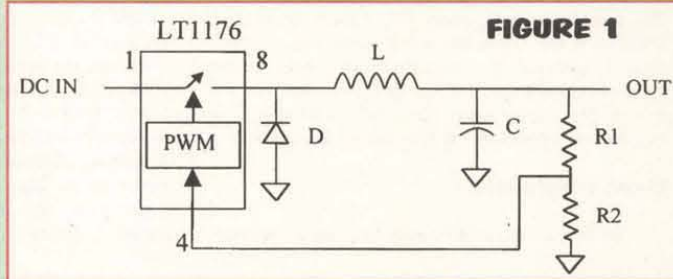

Bridge101.EXE's chart recorder dialog



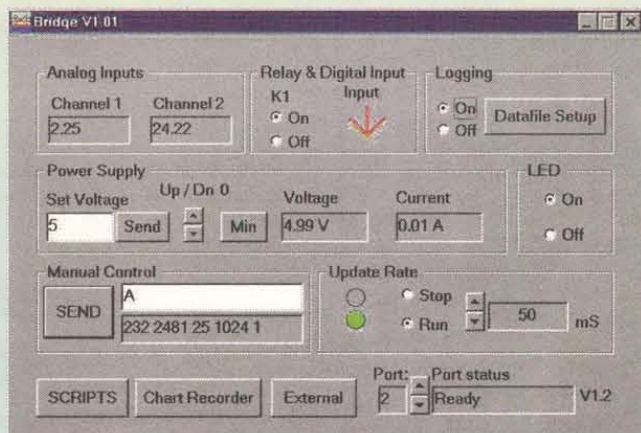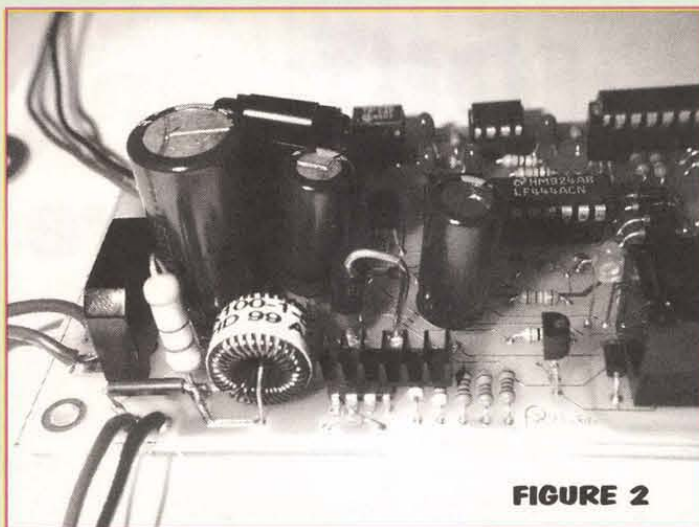

### Bridge101.EXE main program window

Modulator to close the loop.

By now you are probably wondering, why do I need the inductor and diode? Why can't there just be the switch and capacitor? The inductor limits the inrush current when the switch is closed. Without it the capacitor would look like a direct short to ground. In reality, there are losses in this type of regulator, and it can get quite hot, but the losses are much lower than non-switching type regulators, especially at low output voltages.

## Heat Dissipation

While you wouldn't expect to see a heatsink

attached to an eight-pin dip package, I am including one in the IOKit listed at the end of this document. It is very small (Figure 2) and can be attached with a single drop of Super Glue® or any thermally-conductive adhesive. There are other tricks that can help pull the heat away from the

		Part #	Reference Designator	
1	16MHz resonator	X908-ND	CR1	1
2	Microcontroller	PIC16C715-20/P	U6	1
3	Neg 5V Inverter	ILC7662 PDIP	U9	1
4	A/D	ADS7841P	U4	1
5	DAC	DAC7611P	U7	1
6	SW Regulator	LT1176CN8	U8	1
7	EEPROM	24LC00/P	U11	1
8	op amp	LF444ACN	U3	1
9	optoisolator	4N25	U10	1
10	12V Regulator	MC78M12CDT	U2	1
11	5V Regulator	NJM78L05A	U1	1
12	24V Regulator	NJM78L24A	U12	1
13	RS232 chip	MAX202CPE	U5	1
14	Inductor	Coiltronics CTX100-1.52 or Pulse Engineering PE-92102	L1	1
15	transistor	2N3904	Q1	1
16	diode	1N4001	D3,4,5, 6,8,9	6
17	Schottky Diode	1N5822	D7	1
18	bridge 4A	RS403LMS-ND	BR1	1
19	LED - Green 12V	160-1130-ND	D1,11	2
20	5V Reference	LM4040AIZ-5.0	D2	1
21	DB-9 Conn	A2043-ND	P1	1
22	Power Transformer	Hammond 166L24 (HM547-ND) or MagneTek VPS24-1800 MCI Transformer 4-47-5-024 (dual pri)	T1	1
23	relay	24V, 13mA coil, SPDT	International Use K1	1
24	socket 8 pin			3
25	socket 16 pin			2
26	socket 18 pin			1
27	socket 14 pin			1
28	CAP 2200/50	P5187-ND	C1	1
29	CAP Tant 10/10	P2026-ND	C4,5,7, 12,14, 25	6
30	CAP CER .1/50	1210PHCT-ND	C2,3,6, 8,9	13
31	*****	*****	C10,11,13,15, 16,22,23,24	
32	CAP ELE 470/50	P5185-ND	C18,19	2
33	CAP CER .01/50	1206PHCT-ND	C17	1
34	.1Ohm/2W resistor	12FR100-ND	R19	1
35	RES 1.87K 1/4W 1%	1.87KXBK-ND	R13	1
36	RES 3.16K 1/4W 1%	3.16KXBK-ND	R12	1
37	RES 10.0K 1/4W 1%	10.0KXBK-ND	R14	1
38	RES 113K 1/4W 1%	113KXBK-ND	R20,22	2
39	RES 2.94K 1/4W 1%	2.94KXBK-ND	R18,21	2
40	RES 9.76K 1/4W 1%	9.76KXBK-ND	R25	1
41	RES 2.87K 1/4W 1%	2.87KXBK-ND	R26	1
42	RES 10K 1/4W 5%	10KQBK-ND	R2,5,15,30	4
43	RES 47K 1/4W 5%	47KQBK-ND	R3, 31	2
44	RES 1K 1/4W 5%	1KQBK-ND	R4	1
45	RES 2.7K 1/4W 5%	2.7KQBK-ND	R16	1
46	RES 620 1/4W 5%	620QBK-ND	R34,35	2
47	POT 500K single turn	D4AA55-ND	R23,24	2
48	RES 10M 1/8W 5%	10MEBK-ND	R6,8	2
49	RES 1.2M 1/4W 5%	1.2MQBK-ND	R7,9	2
50	RES 10 1/4W 5%	10QBK-ND	R27,28, 32	3
51	RES 120 1/4W 5%	120QBK-ND	R33	1
52	RES 430 2W 5%	430W-2-ND	R17	1
53	Heatsink	HS227-ND	IC	1
			HEATSINK	1

Note: The following items are available from Protoqual. Click on [www.protoqual.com](http://www.protoqual.com) for details. Orders only 1-888-291-2111. Double-sided, printed-circuit board with plated-through holes, \$19.95; Preprogrammed U6, \$19.95; Complete kit of all electrical components, PCB, microprocessor and power transformer, \$149.95. Shipping and handling extra. CA residents must add appropriate sales tax.

## LASERS & ACCESSORIES

## HELIUM NEON LASERS

- ☒ Complete Systems
- ☒ Plasma Tubes
- ☒ Power Supplies

## ACCESSORIES

- ☒ Optics
- ☒ Electro-Optics
- ☒ IR Viewers
- ☒ Books & More

MEREDITH— INSTRUMENTS

## DIODE LASERS

- ☒ **Visible / IR**
- ☒ **Complete Modules**
- ☒ **Collimating Optics**
- ☒ **Drive Circuits**

## FREE CATALOG

**WEB SITE:**  
**www.**  
**mi-lasers.com**

**Phone: 623-934-9387 • Fax: 623-934-9482**

**EZ-EP DEVICE PROGRAMMER - \$169.95**

Check Web!! -- [www.m2l.com](http://www.m2l.com)

**Fast** - Programs 27C010 in 23 seconds

**Portable** - Connects to PC Parallel Port

**Versatile** - Programs 2716-080 plus EE and flash (28, 29) to 32 pins

**Inexpensive** - Best for less than \$200

**Inexpensive** - Best for less than \$200

- Correct implementation of manufacturer specified algorithms for fast, reliable programming.
- Easy to use menu based software has binary editor, read, verify, copy, etc. Free updates via bbs or web.
- Full over current detection on all device power supplies protects against bad chips and reverse insertion.
- Broad support for additional devices using adapters listed below.


### Available Adapters

EP-PI-C6 (C5Sx61,62x71,84)	\$49.95
EP-PI-C64 (16C82-5.72-4)	\$39.95
EP-PI-C12 (12C50x)	\$39.95
EP-PI-C17 (17C4x)	\$49.95
EP-51 (87S1,C51)	\$39.95
EP-11E (88HC11 E/A)	\$59.95
EP-11D (88HC711D3)	\$39.95
EP-16 (16BH EPROMS)	\$49.95
EP-Z8 (288602,3,4,6,7,8)	\$39.95
EP-SEE3 (93x24,25,18x5)	\$39.95
EP-750 (87CT50,1,2)	\$59.95
EP-PEEL (IC722V10,85x)	\$59.95
EP-1051 (89C1051,2051)	\$39.95
EP-PLCC (PLCC EPROMS)	\$49.95
EP-SOIC (SOIC EPROMS)	\$49.95
EP-TSOP (TSOP EPROMS)	\$59.95

Many Other Adapters Available

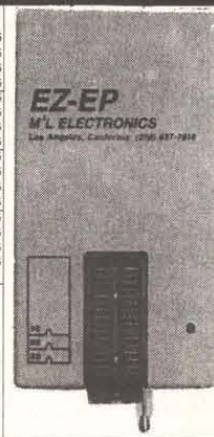**M<sup>2</sup>L Electronics**

**970/259-0555**  
**Fax: 970/259-0777**  
**250 CR 218**  
**Durango, CO 81301**  
**CO orders please add 7%**  
**sales tax.**  
**<http://www.m2l.com>**






The last step is to add a fan blowing directly on U8 and the PCB. While these heat-sinking measures are not mandatory, they can help keep the output voltage from sagging in situations where one amp of current is required.


To drive the regulator, I used a Burr Brown DAC7611 digital-to-analog converter. This DAC is a voltage output type, and generates from zero to 4.096 volts. This voltage is then buffered through a unity gain op amp that drives the summing node of the LT1176.

**FIGURE 3 — Power transformer, ground, fuse, and power switch**

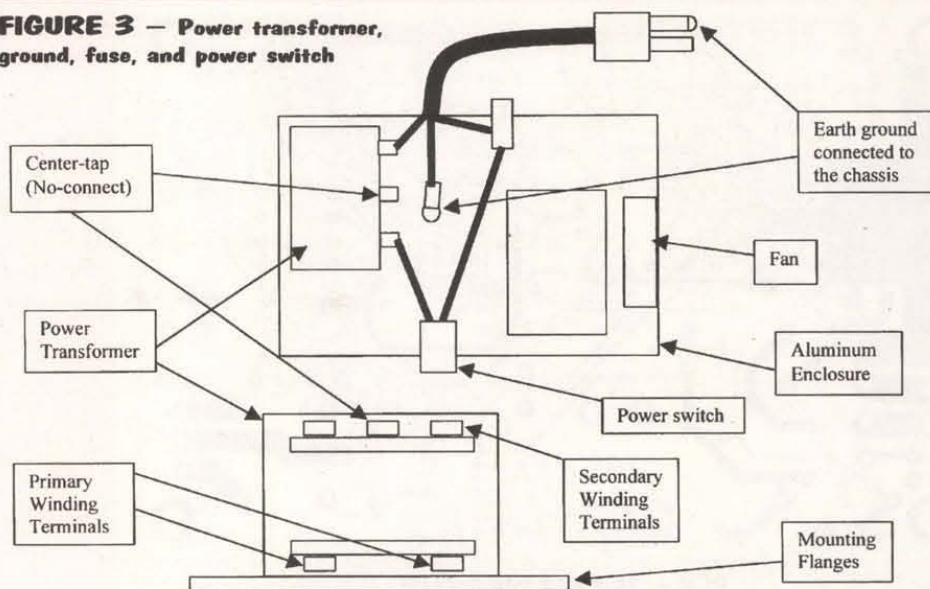

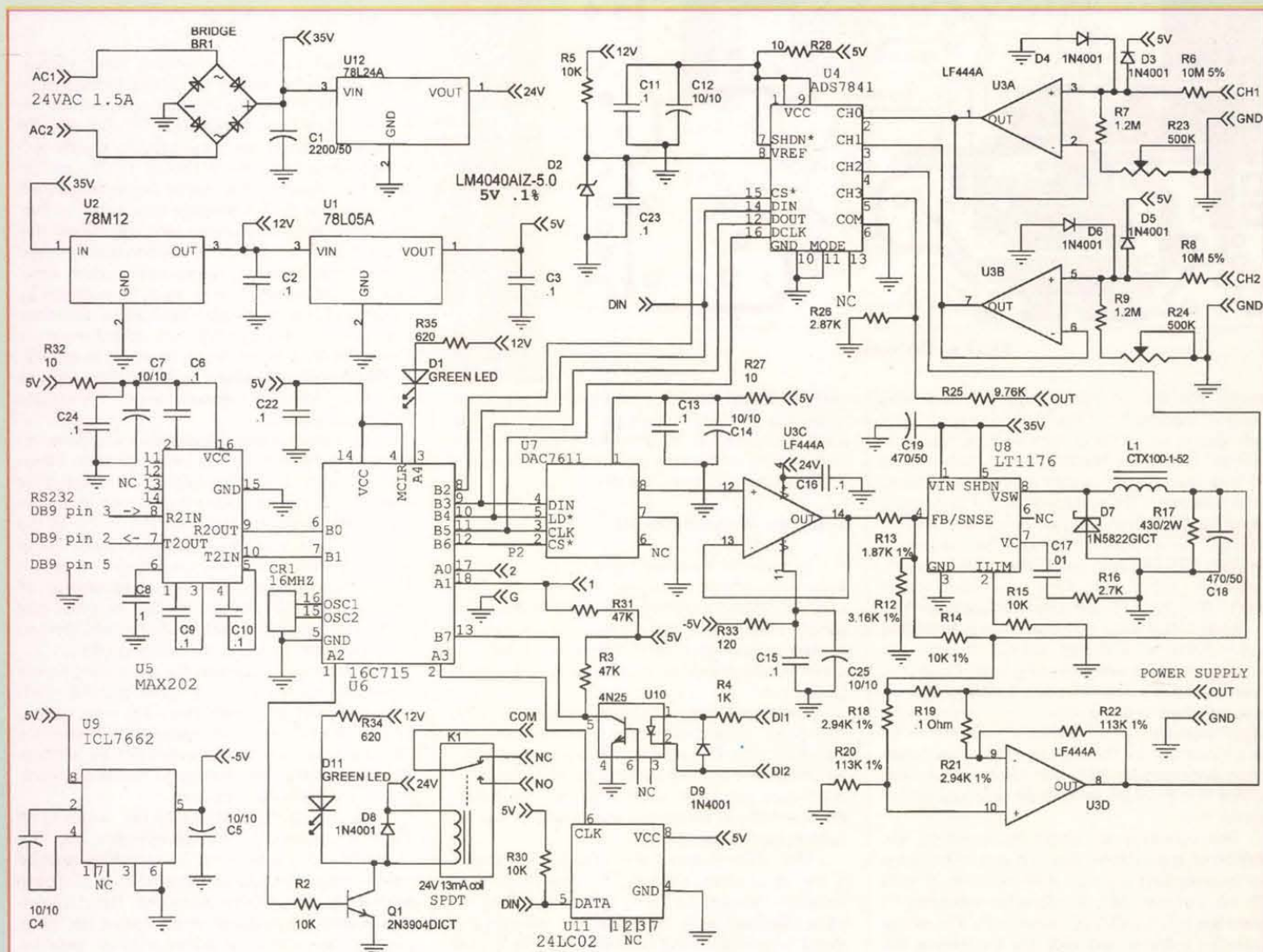
## Program Control


controller, but since there is no direct correlation between DAC output voltage and regulator output voltage, the power supply cannot be directly set to an exact voltage. Instead, the microcontroller must work with the DAC and A/D converter to search for the desired voltage. This is accomplished by moving the DAC in small steps





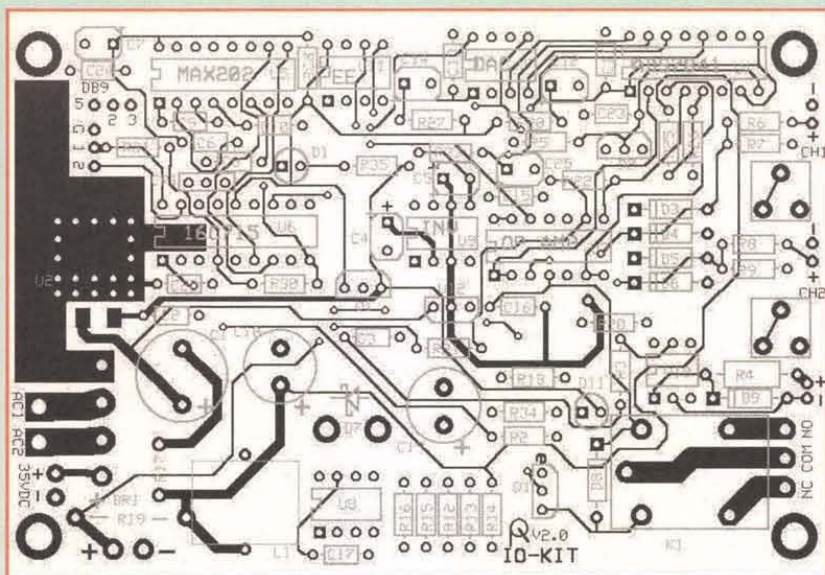

PCB – Top and Silkscreen

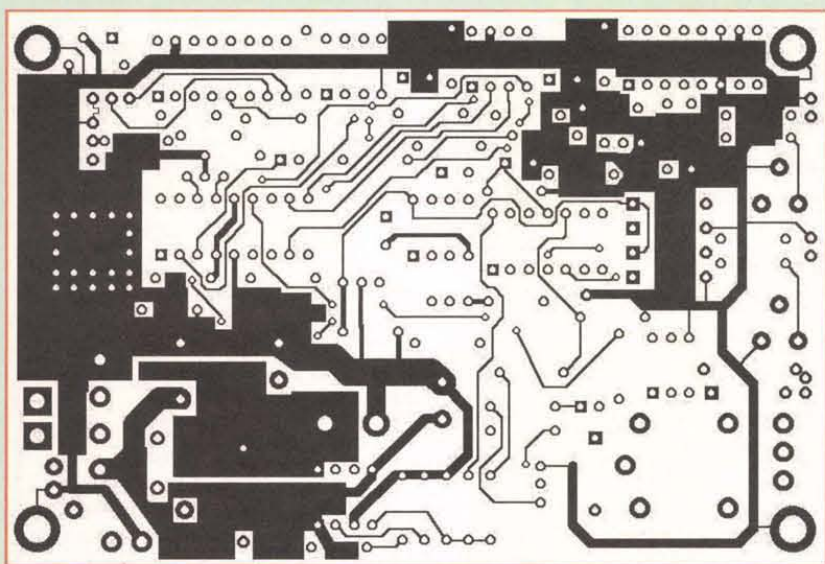

PCB – Bottom

towards the desired power supply voltage and taking a reading from the A/D converter after each step to see if the desired voltage has been reached. Thankfully, the DAC and A/D converter are very fast, so the overall process only takes about a second. The resolution of the regulator's output is about 5mV, so just about any voltage between .1 and 20 volts can be achieved. Resistors R25 and R26 divide the power supply's maximum output down to a maximum of five volts so that the A/D converter can measure it.

While this design works well when searching from a lower to a higher voltage, it does not always perform as well searching from a higher to a lower voltage when there is a light load (or no load) attached to the output. This is because the output capacitor (C18) wants to hold on to its charge and not let the voltage drop. This condition is improved by R17, the 430-ohm, two-watt resistor that provides an ever-present load to the supply.

This condition is further improved by the addition of any external load. (It should be noted that in searching from 20 volts down to .5 volts with no external load, it might be necessary to repeat the SET VOLTAGE command.) The microcontroller software will only try to achieve the desired setpoint for so long before timing out. If

given sufficient load, the search routine performs quite well, and any voltage from about 100 millivolts to 20 volts can be achieved in about one second, as long as the load does not draw more than the regulator's current limit of one amp.

### Current Measurement

In order to measure the amount of current being drawn from the power supply, a very low-ohmage resistor is placed in series with the power supply output, and the voltage drop across the resistor is measured by the A/D converter. The current can then be calculated using simple Ohm's Law.

The circuit uses a 100-milliohm resistor (R19) and an op amp configured as a difference amp with R18, R20, R21, and R22 to measure the voltage drop. The op amp selected for this circuit is a little more expensive than most, but the added expense will pay for itself in this and two other circuits to be discussed later.

One of the features of the LF444A op amp is a low input offset voltage. The manufacturer — National Semiconductor — guarantees that the input offset will be no more than five millivolts and that it is typically about two millivolts. The low offset voltage spec is important because the circuit

must multiply the voltage dropped across R19 by 38.4 (113K / 2.94K ohms) to fully use the 0-5 volt input voltage range of the A/D converter. Any offset error present at the input of the op amp will be multiplied right along with the voltage we are trying to measure. While the LF444A op amp works well for this circuit, I should mention that there are other op amps available with much lower input offset voltage specs. Of course, as the spec for the offset voltage goes down, the price for the part goes up ... way up!

To calculate the gain needed by the difference amp, I began with the assumption that the maximum amount of current that will ever be drawn from the switching regulator is 1.3 amps. This is acceptable since the LT1176 is limited to a maximum current of just over one amp by R15. The voltage dropped across a .1-ohm resistor with 1.3 amps running through it is 130 millivolts (.1 ohms x 1.3 amps), so the difference amp needs a voltage gain of 38.4615 to fully utilize the 0-5 volt range of the A/D converter. R18, R20, R21, and R22 were selected for a gain of 38.43 which is pretty darn close. These resistor values only come in 1% tolerances unless you want to take an ohmmeter and hand-select your parts.

### A/D and Analog Inputs

Both analog input channels have an input range of from 0-40 volts with 10-millivolt resolution. A 12-bit A/D can resolve 4,096 (2<sup>12</sup>) steps between zero and five volts.

$$40 / 4096 = 9.76 \text{ mV}$$

In order to have an analog input voltage range of 0-40 volts, the incoming voltage must first be divided down to the 0-5V range which the A/D converter can handle. R6, R7, R8, and R9 divide the voltage down and provide a sufficiently high input impedance (about 11 Mohms) to keep from loading the circuit being measured. However, the A/D converter has about a five-megaohm input impedance, and the overall system accuracy would most likely be compromised by the resistor divider. To maintain system accuracy, the incoming voltage must be buffered by an op amp. This is another area where the more expensive op amps justify their added expense. The LF444A has an input impedance of 10<sup>12</sup> ohms (tera-ohms), which is sufficiently high to keep from affecting the accuracy of the resistor voltage divider.

The circuit being measured must have an output impedance of 10K ohms or less, otherwise an error due to loading could result. This error happens because the impedance of the circuit being measured is added in parallel to the input impedance of the measuring device. Keep in mind that any time you are trying to measure the voltage dropped across a resistance of greater than 10K ohms with this or most any other voltmeter, you will probably not get an accurate reading due to this loading effect.

Overvoltage protection for the analog inputs is provided by diodes D3, D4, D5, and D6 which pass any voltage greater than 5.6 volts or less than -.6 volts to the power supply. Potentiometers R23 and R24 provide calibration for the voltage dividers to keep from having to locate the hard-to-find 1%, 10M-ohm resistors.

The last device that affects the accuracy of the A/D converter is voltage reference D2. The LM4040AIM3 is a five-volt, .1% precision voltage reference that the A/D converter uses to compare against the voltage to be measured. The .1% tolerance makes this device more expensive, but this is another case where the added expense pays for itself in overall system accuracy. The spec sheet



for this device states that a bypass cap isn't necessary, but I found that the A/D converter ran a little quieter (one LSB) with the .1  $\mu$ F cap.

The overall accuracy of the analog inputs is affected by the source impedance of the circuit being measured, the input offset of the op amp, the noise in the A/D converter's power supply, the A/D converter itself, and the precision voltage reference. In my tests, I found the total system error to be less than 1%, and that was mostly due to system noise.

## Power Source for the Power Supply

The power transformer selected for this system must satisfy several criteria. It must (1) provide sufficient current for the switching voltage regulator; (2) have a high enough output voltage so that the 24-volt regulator doesn't drop out under heavy power supply loads or low line voltage; and (3) not have so high an output voltage that it overdrives either of the linear voltage regulators. A 24-volt, 1.5-amp transformer will work best in this application. The voltages needed for this design are +5V, -5V, +12V, and +24V.

Standard linear voltage regulators work well for all of these voltages except the -5V. The ICL7662 was used for generating the -5V since the only external components it requires are two tantalum capacitors. It only provides about 10mA without starting to sag, but that should be sufficient since the -5V is only needed for the op amp's negative rail. This is another area where a more expensive op amp justifies its cost. The LF444A only requires 200 microamps per amplifier, as compared to some op amps that require five milliamps or more per amplifier. This 800 microamps combined with the op amp's output current is less than five milliamps, so the ICL7662 works just fine.

## Noise in the Power Supply

Controlling power supply noise in any circuit can be a challenge. If you are trying to minimize the LSB dither (noise) of an A/D converter, then power supply noise can be your worst nightmare. A/D converters need a very quiet power source. If you can't get the noise down to an acceptable level, the converter's LSBs will dance with wild abandon.

Bypass caps and other noise reduction techniques can be used to both attenuate noise on the power bus that could affect the performance of an integrated circuit and keep noise that is generated by an integrated circuit from getting on the bus. Some devices can get by with just a .1 $\mu$ F bypass cap, while others need a little more isolation from the power bus. The A/D and DAC both need more isolation from bus noise, while the serial interface chip needs to be isolated from the bus so that the noise it generates in the process of creating  $\pm 10$  volts from +5 volts doesn't get onto the bus. For this circuit, adding a 10-ohm resistor in series with the +5-volt bus just before the bypass caps is sufficient for reducing noise to an acceptable level.

## SPDT Relay, OPTOISOLATOR, LED, and EEPROM

Since there were leftover port pins on the microcontroller after the switching regulator design was complete, I added a few gadgets that I thought might come in handy. The relay is of the single-pole/double-throw persuasion, and is driven by a simple NPN transistor. Make sure to select a relay that draws less than 50mA from the 24-volt regulator.


The digital input uses an optoisolator that pulls its output low when sufficient current is

applied to the input to make its internal emitter diode start to conduct. The optoisolator will report a "high" input condition with any positive input voltage above two volts. The 1K resistor (R4), which limits the current through the emitter diode, is a 1/4-watt device which sets the upper limit on the applied voltage to about 12 volts assuming 50% power derating on the wattage of the resistor and continuous operation.


There are two LEDs in this design: one that goes on and off with the closing and opening of the relay; and the other which is connected to the open drain output (port pin A4) of the microcontroller. The LED connected to the microcontroller is turned on about 500 milliseconds

after power up and can be turned on and off via software.

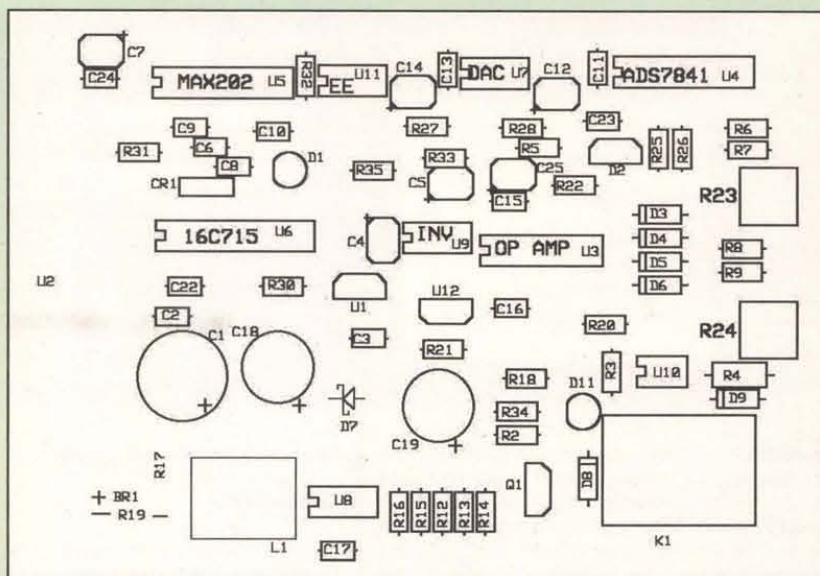The EEPROM is a 2K bit device configured as 256 eight-bit bytes. This non-volatile device can be used to store setup parameters, program/script



PCB - Silkscreen

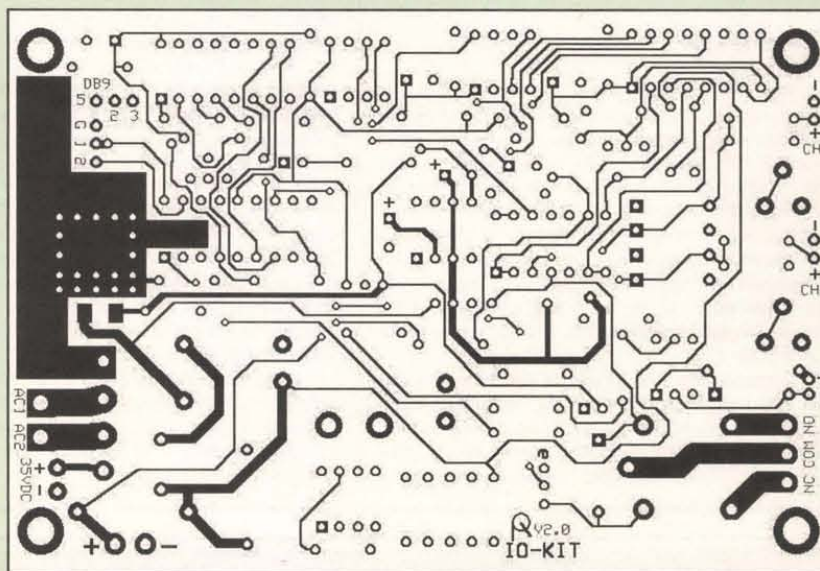

PCB - Top



SURVEILLANCE


Room Transmitters . . . . from **\$30.00**  
 Telephone Transmitters . from **\$29.00**  
 UHF Pen Transmitters . . . . **\$299.00**  
 Crystal-Controlled  
 Transmitters . . . . . from **\$75.00**  
 UHF Telephone Transmitter  
 & Receiver & Recorder . . **\$299.00**

Catalogues **\$5.00**

**And much more - too much to list here!**

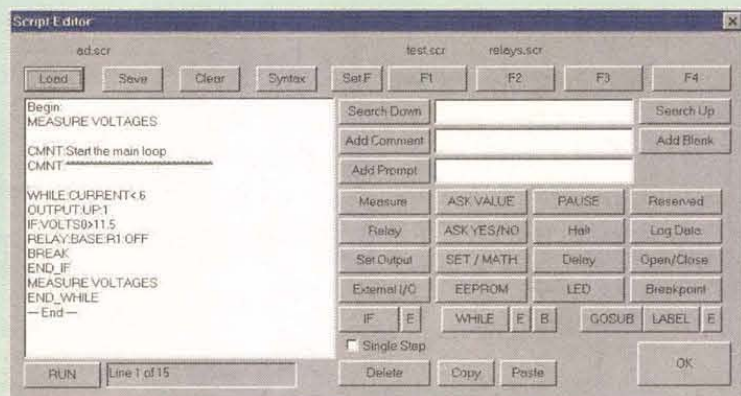**E-Mail: [BitzTechnology@Compuserve.com](mailto:BitzTechnology@Compuserve.com)**





constants, or anything else that can be stored eight bits at a time. Of course, integers larger than eight bits and floating point numbers can be stored in the EEPROM by breaking them down into eight-bit pieces first. Remember to wait for 10mS between successive writes to the EEPROM. The spec for the write speed varies from manufacturer to manufacturer but waiting 10mS between writes generally works well.

### External I/O

With the remaining two microcontroller port pins, I decided to implement a port that could communicate with external devices. I labeled the ports 1 and 2, but they are really transmit and receive lines. I decided on 1 and 2 so that external boards labeled in the same way could be easily connected without the ambiguity of having to determine whether to connect transmit to receive or transmit to transmit. A complete description of the communications protocol is included with the IOKit and is also available from my website ([www.protoqual.com](http://www.protoqual.com)).

Currently, the only products available that use this external I/O port are a relay board with eight individually controllable relays and an eight-channel, optically-isolated digital input board (not CMOS or TTL compatible). Information on both

kits is also available on my website.

### Software

The serial protocol implemented in the microcontroller is rather unsophisticated in that it doesn't require checksums and doesn't have a long list of error codes that can be returned to the host PC if something goes wrong. In fact, if the microcontroller receives a command that it doesn't understand, it simply responds with "WHAT?"

Two software programs are available for downloading for free from the website as well. The first is BRDG\_DOS.EXE, which is a DOS based program that will issue commands to the microcontroller at a fixed baud rate of 19,200 baud and print the microcontroller's raw data response to the screen. This program is intended to be a development tool for those wishing to write their own Windows/DOS software for communicating with the microcontroller. The second program (Bridge101.EXE) is a full implementation of all features and functions of IOKit, and will run under Windows 95, 98, or NT.

Its features include a chart recorder window for graphically monitoring the voltages of both analog channels 1 and 2, the ability to set the voltage and monitor the current of the switching voltage regulator, and a point-and-click interface for control of

the relay and LED indicator. Last, but certainly not least, Bridge101.EXE has a fully functional scripting language interpreter. With it, you can build long lists of commands using WHILE loops and IF statements that let you set up a mini automated test system in your home workshop.

### Construction

**NOTE: Do not attempt to connect the power transformer to 120VAC unless you are experienced with both high voltage and the wiring of high-voltage components.** Make sure your work area is free of static electricity. Some of the integrated circuits in this design can be easily weakened or damaged by a static discharge that is too small to be felt by your hand.

Start by placing all of the resistors, capacitors, ICL7662, and 78xxx series linear regulators on the board first. Apply power to the board, and verify that all of the voltage regulators are issuing the correct voltage. Then remove power from the board and install the 16MHz ceramic resonator, MAX202, and microcontroller chips. Connect the board to the host PC via the three-wire interface, and then apply power. Test for correct communication by running BRDG\_DOS.EXE with the following command: BRDG\_DOS 1 P where "1" is the serial port number that the IOKit is connected to and "P" is the command for "Ping." The IOKit should return with "IOKit V1.xx." If it does not, check all solder connections, and verify that all resistors are the correct value and in their correct location on the board. Once the microcontroller is running, place the rest of the components on the board, re-apply power, and you're ready to roll.

### Additional Parts

Mounting the IOKit PCB within an enclosure will require additional parts (ref. Figure 3). The enclosure selected should be made of aluminum or some other metal so that it can be electrically connected to earth ground (usually the green wire in a three-conductor power cord). The enclosure should have a fan mounted adjacent to the circuit board so that air will flow across the switching regulator circuitry. Stand-offs will be needed to mount the PCB so that it doesn't short out against the enclosure. Mount the power transformer in a corner for better structural support with its power connections pointing towards the middle of the enclosure.

Miscellaneous wiring terminals can be mounted to the enclosure and connected to the PCB. Make certain that you add a power switch and a fuse in series with the power cord and primary winding of the power transformer. A 500mA, 250-volt fuse will work just fine.

The only calibration that can be performed is to set the voltage divider potentiometers R23 and R24. Apply voltage to analog input channel 1 and monitor the voltage at the PCB terminals with a digital voltmeter. If available, use 39 volts DC for the calibration voltage. If not, use as high a voltage as you can get (less than 40 volts). Adjust R23 for the correct voltage reported by Bridge101.EXE and repeat this procedure for channel 2. **NV**

## TIMELESS PRODUCTS

The Best Prices and Service • In Business over 15 years!

Phone 218-346-6660 Fax 218-346-6664

### CABLE TV CONVERTERS

WILL NOT DECODE

New! "TP 125 V"  
128 Channel Converter with Volume

Special Prices for  
TP1550PC

Call for Details

Panasonic still available!

• REFURBISHED CONVERTERS ALSO AVAILABLE •

• QUALITY REPAIR DEPARTMENT FOR ALL YOUR  
TUNER REPAIRS •

• REMOTES AVAILABLE FOR MOST CABLE BOXES •

DEALERS ONLY • GREAT QUANTITY PRICES • NO DECODER SALES



# New Product News



## SURETESTER L™

The SureTester L™ is a hand-held battery-powered test instrument. It is easily carried and can be connected to a powered down motor in seconds. The motor's condition is determined

by flipping a switch and reading the resulting delta number on the backlit display. A chart on the front of the tester equates the delta number to the motor's status. Within seconds you will know the condition of the motor.

No more guessing with a megohmmeter. You can even test through your starter and wiring.

The SureTester L will test: single or three-phase AC motors and AC servos fractional to 250 HP, 50 or 60 Hz, and 100 to 500VAC.

The SureTester L comes complete with: batteries, case, test leads, and two-year limited warranty.

For more information, contact:

**LEMON-PLADD, INC.**  
**5300 MERCHANT CIR. UNIT 2**  
**DEPT. NV**  
**PLACERVILLE, CA 95667**  
**530-344-9192 FAX: 530-344-9193**  
**EMAIL: sales@lemonpladd.com**  
**WEB: www.lemonpladd.com**



## EIGHT-CHANNEL DTMF (TOUCH-TONE) CONTROL BOARD

Uddle Systems presents the DTMF-1. This board listens to any audio source such as telephone line, two-way radio, scanner or satellite receiver. Each of the eight outputs can be programmed for latched (on/off) or momentary (0.25-32 second pulse) operation.

Each output provides up to 500 mA of current sink. The DTMF-1 will drive relays directly for control of high current loads.

Ideal for commercial and amateur repeater control, dial-up telephone control (requires an answering machine), and call screening.

The DTMF-1 features two-level command security, programmable one-to-five digit user, and programming passwords, individual channel lockouts, programmable command acknowledge channel, valid tone LED, and mute output. Other features include: on-board lithium battery retains programming in the event of a power failure; easy connection to any system via mini screw terminal connections; and requires 6-30 volts DC.

See the website for more information and application hints. The cost is \$59.95 plus \$5.00 shipping by Priority Mail. Visa/MC/Discover accepted.

For more information, contact:

**UDDLE SYSTEMS**  
**825 SHERMAN AVE., DEPT. NV**  
**ACKLEY, IA 50601**  
**VOICE/FAX: 1-877-733-4351**  
**WEB: http://www.uddle.com**



## THE PEDALER™

The Pedaler™ is great for those who want a fun and motivating way to increase their daily exercise. It discourages excess TV watching, video game, and computer use while at the same time increases physical activity. It's perfect for children, as well as adults.

Studies have shown that moderate daily exercise can reduce obesity and lower cholesterol while improving ones cardiovascular health. People involved in rehabilitation and physical training will find the Pedaler useful as both an arm and leg ergometer for upper and lower body training, improving muscle strength, and stamina.

The new and unique Pedaler exercise system will get you moving and help keep you healthy as we move into the 21st century!

For more information, contact:

**D SQUARED TECHNOLOGIES, INC.**  
**71 BIRCHWOOD PARK DR., DEPT. NV**  
**JERICHO, NY 11753-2238**  
**516-939-0646 FAX: 516-932-7319**  
**EMAIL: info@d2tech.net**  
**WEB: www.tvpedaler.com**

**Showcase your New Products here!**

**Send all press releases or information/photos to:**

**Nuts & Volts Magazine**  
**New Product News**

**430 Princeland Court,**  
**Corona, CA 92879**

**or E-Mail to**

**newproducts@nutsvolts.com**

## INTERNET-BASED TEMPERATURE/RELATIVE HUMIDITY DATALOGGER

Pinnacle Technology, Inc., introduces the ezLogger/TRH, the first Internet-based temperature and relative humidity datalogger. The ezLogger/TRH offers worldwide access from any computer with an Internet connection and the proper password.

The ezLogger/TRH provides real-time monitoring of environmental conditions, and web-based downloading of collected data, ending the need for labor intensive manual downloading.

Room conditions are monitored at 2-30 minute intervals. Easy to read text and graphic displays show daily or long-term trends in room conditions.

Previously logged data can be downloaded in spreadsheet compatible format via email or directly from any web browser.

Temperature and humidity alarm limits, email alarm destinations, sampling rate, unit identification, and network settings can

be easily changed through a telnet or serial connection.

The ezLogger/TRH is compatible with any web browser. No additional software is required.

Immediate alarms will be emailed whenever temperature or relative humidity limits are exceeded or standing water is detected (optional water sensor).

The ezLogger was designed specifically for library and museum conservation professions, but is also applicable for computer rooms, warehouses, hospitals, and industrial applications, wherever accurate, reliable monitoring of temperature and humidity is required.

For more information, contact:

**PINNACLE TECHNOLOGY, INC.**  
**619 E. 8TH ST., STE. D**  
**DEPT. NV**  
**LAWRENCE, KS 66044**  
**785-832-8866 FAX: 785-749-9214**  
**EMAIL: info@pinnacle.net**  
**WEB: www.pinnacle.net**



**High Performance Auto Ranging DMM**

New to our DMM line-up and possibly (probably) the best DMM value anywhere! Includes: Analog Bar Graph! Auto-Ranging! Data Hold! Temperature Probe! Frequency Test! Continuity Test! AND MORE!

**Features:**  
**Data Hold:** Freezes reading for easy checking  
**Auto Ranging:** For easy precise range settings  
**Range Hold Control:** allows for manual selection of your test range  
**3-1/4 Digit LCD Display:** Reads up to 3260.  
**Easy to read display.**

**Function Dial:** Easy to use to select measurement type or turn unit off.  
**4 Jack Plug-ins:** Safety design with different capacities for different functions.

**Diode, Continuity Check Push-Buttons:** For toggling between diode check and continuity check.  
**Low Battery Indicator:** Advises you when it's time to change battery.  
**Extra Long 44" Test Leads:** Helps get to hard to reach places.

**Screw-On Alligator Clips:** Convert one or both probe tips to alligator clips.  
**Fuse-Protected Circuitry:**  
**Built-In Stand:** Makes one hand operation easier.  
**Shock Absorbing Rubber Carrying Case:** with convenient probe storage clips and hanging tab.  
**Helps protect the DMM from damage if accidentally dropped.**

Measures:  
 DC Volts: up to 1000V  
 AC Volts: up to 750V  
 ANPS: up to 20 Amps (AC & DC)  
 Resistance: up to 30M ohm  
 Continuity Check: with audible signal (signal sounds if resistance is less than 20 ohms. Display reads actual resistance).  
 Frequency: (1KHz to 300KHz) displays both digital and bar graph reading.  
 Transistor hfe Test: Display shows approximate hfe value based on test condition of 10uA base current and Vce of approx. 3V.  
 Temperature Test: Measures from 0° to 1832° F (probe supplied).  
 Diode Test: Tests if diodes are shorted or open.

Accuracy:  
 Vdc:  $\pm 1.0\%$  reading  $\pm 5$  digits  
 Vac:  $\pm 1.5\%$  reading  $\pm 8$  digits  
 Adc:  $\pm 1.2\%$  reading  $\pm 5$  digits  
 Aac:  $\pm 1.5\%$  reading  $\pm 5$  digits  
 Resistance:  $\pm 1.0\%$  reading  $\pm 5$  digits  
 Frequency:  $\pm 1.0\%$  reading  $\pm 6$  digits  
 Temperature:  $\pm 1.0\%$  reading  $\pm 6$  digits

Input Impedance: 10Mohm (Vdc/Vac); over 100Mohm on 300 mVdc range

Requires two AAA batteries sold separately.



#CS19903

**2GHz RF Field Strength Analyzer**

**ONLY \$1589**

• Frequency Range: 100KHz to 2,000MHz  
 • Narrow Band FM (NFM)  
 • Wide Band FM (WFM)  
 • AM and Single Side Band (SSB) Modulated Signals May Be Measured  
 • PLL Tuning System for Precise Frequency Measurement and Tuning  
 • LED Backlight LCD (192x192 dots)  
 • Built-In Frequency Counter  
 • Hand-Held and Battery Operated  
 • All Functions are Menu Selected  
 • RS232C for PC Interface and Printer

#3201

See the web site for details

**Removable Hard Drive Rack**

For IDE/Ultra DMA Hard Drives

We Sold Over 14,000 in 1998!

**ONLY \$14.95** any qty.

This product can be used with any 3-1/2" IDE hard drive up to 1" high. It includes an electronic keylock for safe removal and insertion. Made of ABS 707 fireproof plastic. Use this product to protect sensitive hard drive data, take your hard drive between work and home or even set up different users with their own hard drives that they physically insert every time they use a PC. Other models available from C.S.I. include RH100 series and RH200 series, which are interchangeable within the same interface design (IDE or SCSI). Other Models are Available. See [www.web-tronics.com](http://www.web-tronics.com) under "hard drive and accessories" for more details and pictures.



RH-10C-IDE

**Removable Hard Drive Rack with Auto Door And Cooling Fan**

**ONLY \$18.95** any qty.

• Auto door on the outer frame  
 • ABS material of outer frame, High efficiency cooling fan  
 • Worldwide patent pulling function handle  
 • CE Approved  
 • Coating iron bottom cover  
 • For IDE interface  
 • For 1" high 3.5" HDD  
 • Not compatible with our RH10 & RH20 series. Compatible with our RH17-IDE model.



#MR-27

Details at [www.web-tronics.com](http://www.web-tronics.com)

**Auto-Temp Solder Station with Ceramic Element**

**ONLY \$39**

• With Ceramic Heating Element for More Accurate Temp Adjustment  
 • 3 Conductor Grounded Power Cord  
 • 250°C-480°C (470°F-900°F)  
 • Fast Heating Feature



SR-976

Extra Tip Options Available. See Web!

For More Info See [www.web-tronics.com](http://www.web-tronics.com)

**www.web-tronics.com**  
 Don't forget the dash  
**Circuit Specialists, Inc.**

• Easy to Navigate  
 • Includes a Search Engine That Really Works  
 • New Items Added Constantly

In Business Since 1971

**CCD B&W Board Cameras**

• ASIC CCD Area Image Sensor  
 • Extremely Low Power Consumption  
 • 0.5 Lux Min Illumination  
 • Built-In Electronic Auto Iris for Auto Light Compensation

Detailed Specs on the Web


VM1030PA-B 30mmx30mmx25mm, Pinhole lens, 12V \$39.00 any qty.

VM1030A 30mmx30mmx26mm, Standard lens, 12V \$39.00 any qty.

VM1035A 42mmx42mmx26mm, Standard lens, 12V with back light compensation \$49.00 any qty.

VMCB21 44mmx38.5mmx28mm, with 6 infra-red LEDs, 12V \$49.00 any qty.

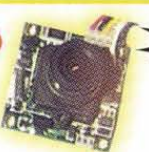VM1036A 32mmx32mmx25mm, Standard lens, 12V, reverse mirror image feature \$49.00 any qty.



**LOWER PRICES**

**Bullet CCD Cameras**

B&amp;W and Color

• Smart Rugged Metal Housing  
 • Extremely Low Power Consumption  
 • 12 Volt  
 • CCD Area Image Sensor for Long Camera Life  
 • Built-In Electronic Auto Iris for Auto Light Compensation  
 • No Blooming, No Burning  
 • 0.1 Min Lux Illumination (B&W) (1 Lux Min Lux Illumination (color))

VMBLT1020 B&W, 21mm(D)x55mm(L) \$49.00 any qty.

VMBLT1020W B&W Weatherproof, 21mm(D)x58.5mm(L) \$79.00 any qty.

VMBLTJC19BW COLOR! Weatherproof, 17mm(D)x88mm(L) \$139.00 any qty.



**LOWER PRICES**

**COLOR CCD Mini Board Cameras**

• Low Power Consumption  
 • 1 Lux Illumination  
 • Built-In Electronic Auto Iris for Auto Light Compensation  
 • Internal Synchronization  
 • 12Volts  
 • 400 TV Lines

VM3010PA 33mmx33mmx18mm, Pinhole lens \$99.00 any qty.

VM3011-A 45mmx40mmx24mm, Standard lens, single board \$89.00 any qty.

VM3010-A 33mmx33mmx32mm, Standard lens \$99.00 any qty.



**PRICE REDUCTION**

**new! 3-1/2 Digit JUMBO Digital Panel Meters Check these LOW PRICES!**

• 21mm Figure Height  
 • 5 Volt Common Ground or 9V Independent Power Supply Versions Available  
 • Voltage Divider Resistors included and max. Measured Range Selectable by Soldering a Selection Joint  
 • Easy Bezel Snap-In Design (84mm x 41mm rectangular hole typical)  
 • "0" Reading for "0" Voltage Input  
 • High Quality SMD Production Method  
 • Dual Slope Integration A-D Converter System  $\pm 0.5\%$  Accuracy

PM-1028A LCD 9V Independent Power Supply Version 1/\$12.95 10/\$10.89 100/\$7.99 250/\$6.25

PM-1028B LCD 5V Common Ground Power Supply Version 1/\$13.95 10/\$11.84 100/\$8.89 250/\$7.15

PM-1029A LED 9V Independent Power Supply Version 1/\$14.95 10/\$12.50 100/\$9.95 250/\$7.89

PM-1029B LED 5V Common Ground Power Supply Version 1/\$15.95 10/\$13.40 100/\$10.79 250/\$8.65

**NOW IN STOCK!**

**AS LOW AS \$6.25**

**Our Most Sophisticated DMM We Sold Over 700 Last Year!**

with RS-232 Interface & Software, 3-3/4 Digit, 4000 Count, Auto-Ranging with Analog Bargraph

• True RMS Mode  
 • 10MHz Frequency Counter  
 • Time Mode with Alarm, Clock, and Stop Watch  
 • Dual Display  
 • 10 Location Memory  
 • Min, Max, Avg and Relative Mode  
 • Decibel Measurement  
 • Cap and Ind. Measurement  
 • Temperature Mode (C/F)  
 • K Type Temperature Probe Included  
 • Pulse Signal for Logic & Audible Test  
 • Continuity/Diode Test  
 • Logic Test  
 • Auto Power OFF/Keep ON Mode  
 • Fused 20A Input with Warning Beeper  
 • Back Light  
 • Data Hold/Run Mode  
 • Safety Design UL1244 & VDE-0411  
 • Protective Holster  
 • Silicon Test Leads



**NOW ONLY \$129**  
 Reg. \$169

More Details on our Web Site

PROTEK 506

**3000 Series Digital R/O Bench Power Supplies**

♦ Low Cost Single Output ♦ 3 Amps

High stability digital read-out bench power supplies featuring constant voltage and current outputs. Short-circuit protection and current limiting protection is provided. Highly accurate LED accuracy and stable line regulation make the 3000 series the perfect choice for lab and educational use.

Line Regulation:  $2 \times 10^{-4} + 1\text{mA}$   
 LED Accuracy: Voltage:  $\pm 1\% + 2$  digits  
 Current:  $\pm 1.5\% + 2$  digits  
 Wave Line Noise:  $\pm 1\text{mVrms}$   
 Dimensions: 291mm x 158mm x 136mm



CSI3003: 0-30V/0-3amp  
 Digital R/O Bench PS,  
 1x10<sup>-4</sup> 5mV Load Regulation  
 \$99.00 5/\$89.00

**AS LOW AS \$89**

**new! O'Scope Offer**

30MHz! ONLY \$299! ONLY \$299  
 Take Advantage of this low price!

• Dual Channel  
 • Dual Trace  
 • Vert Trigger  
 • 1 Year C.S.I. Warranty!



#OSC-1030

Manufactured for CSI by a leading O.E.M. manufacturer. See our website for detailed specifications!

**new! Hot Air SMD Rework Station**

WOW! ONLY \$489  
 Similar Systems Cost 100s More!

**ONLY \$489**

#SR-979



For technicians, service/repair depots and assembly rework. We also stock a selection of nozzles for QFP, SOP & PLCC devices (see our website for selection details). Hot Air temperature variable from 100°C to 400°C (212°F to 754°F) power consumption: 275W max. Auto cooling feature cools system after shut off to extend service life of heating elements and handle. One year limited warranty from C.S.I. Comes with QFP Nozzle (0.68" x 0.68")

**new! 2.4 GHz A/V Sender/Receiver System**

• Wireless FM transmission of video (color or B/W) and sound (stereo or mono) up to 150 meters (line of sight)  
 • Directional Antenna Design optimizes performance  
 • Use with remote cameras or any input (satellite TV, cable etc.) where wireless transmission is desired.  
 • View on a TV set.  
 • Performance through walls varies depending on construction methods etc.  
 • Each set includes a plug-in power supply for the transmitter & receiver.  
 • 7 segment LED displays channel (1-4) on receiver & transmitter.



CSIHT2400 Includes One Transmitter & One Receiver with Power Supplies \$139.00 \$109.00  
 CSIHT2400TX Extra Transmitter/Each Receiver will Monitor up to 4 Transmitters \$89.00

See more detailed specifications at [www.web-tronics.com](http://www.web-tronics.com) in the CCD camera section.





# CLONE, TEST OR REPAIR ANY HARD DRIVE

"THE MOST COMPLETE HARD DRIVE WORKSTATION WE'VE SEEN!" BOB ROSENBLUM, DIGITAL VIDEO, INC.

## DRIVE SERVICE STATION

Copy entire hard drives with ease. Drive duplicators are essential tools for dealers and system builders. Don't spend hours installing and formatting drives. Do it instantly with the Pro. Set up any SCSI or IDE drive with your original software. Connect blank drives to the Pro and press start. You'll copy entire drives faster and more accurately than is possible on any PC. With our combination IDE and SCSI model, you can even copy data between different interfaces. All models include both 2.5" and 3.5" interface adapters. The Pro also supports SCA and Wide SCSI drives.

Choose the Pro, and you'll also have an entire factory drive test and repair system for under \$1000. The Pro gives

**BUY MANUFACTURER DIRECT: \$995**  
**408 330-5525**

you the ability to copy, reformat, repair, translate, and test any hard drive. Use the Pro to put any hard drive through its paces. A full factory final test and performance analysis is performed. Complete test and repair reports are sent to any standard printer.

The Pro will also reassign and eliminate drive defects. Here's how it works: First, a precise media analysis system scans the disk for errors. Defects are mapped out, and effectively "erased." The error correcting system then "trains" the drive to permanently avoid defective areas. Data is stored only on the safe

areas of the disk. Capacity is reduced by an insignificant amount, and the drive works flawlessly once again. Get the technology used by major repair shops and data recovery centers. The Pro repairs all disk defects caused by normal wear. Drives with mechanical damage may not be repairable.







**CORPORATE SYSTEMS CENTER**  
3310 WOODWARD AVE., SANTA CLARA, CA 95054  
[WWW.DRIVEDUPLICATORS.COM](http://WWW.DRIVEDUPLICATORS.COM)

Call today for high volume multi-drive copiers and CD Duplicators  
Sold and intended for backup purposes only. Copyright laws must be observed.


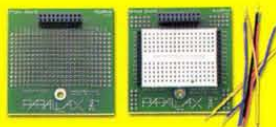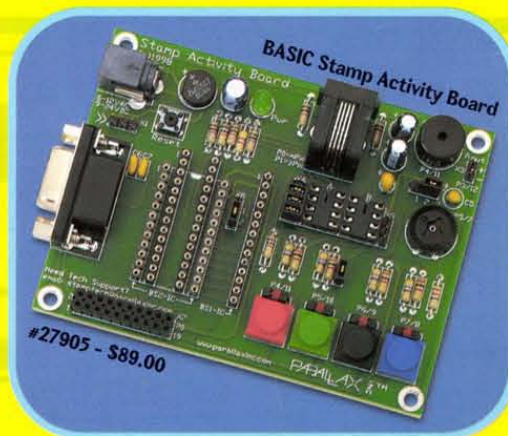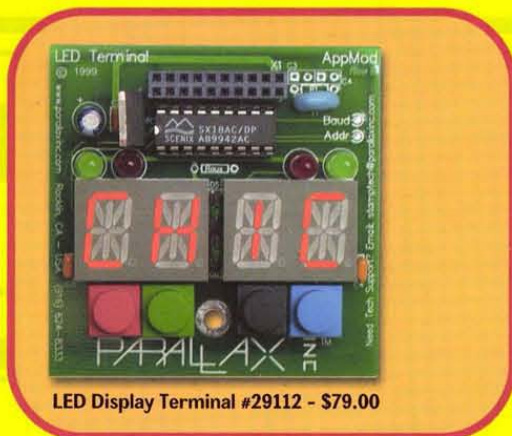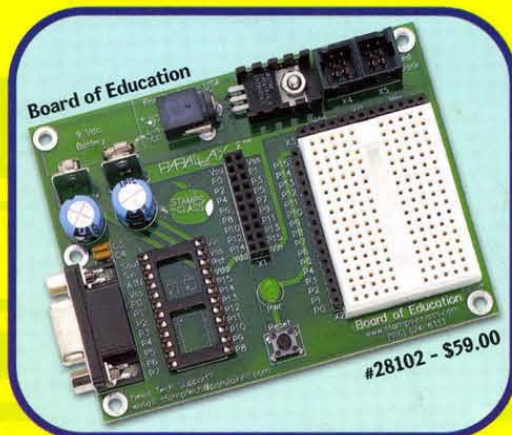
# APPMOD SQUAD

plug-in modules for your BASIC Stamp boards



Now you can record 60 seconds of sound with your BASIC Stamp using our new Sound Module. It's a mini-sound studio

complete with on-board microphone, audio amplifier, and speaker, (line-in and line-out jacks too). How about displaying and scrolling alphanumeric characters using our LED Display Terminal? These handy modules that work right out of the box without complex wiring! Each provides a serial interface with standard baud rates between 2400 and 38.4 Kbaud. All AppMods plug into Parallax BASIC Stamp boards.

BASIC Stamp and the Parallax logo are registered trademarks of Parallax, Inc.

For example, sound may be recorded using serial commands or the pushbuttons. This is the PBASIC code to play the code back under control of your BASIC Stamp:

```
serout 4,188+$8000,[ "!SM0P",75]
'play sound at address 75 (4800 bps)
```

Order Online or call toll-free 888.512.1024 (U.S.) Mon-Friday 7 a.m. - 5 p.m. PST. (international dial direct 916.624.8333)

[www.parallaxinc.com](http://www.parallaxinc.com)

**PARALLAX** 

Write in 194 on Reader Service Card.

**NUTS & VOLTS MAGAZINE**  
430 PRINCELAND COURT  
CORONA, CA 92879-1300

